

electronics today

ISSN. 0142-7229


INTERNATIONAL

MAY 1981 65p

REMOTE CONTROL YOUR HOME!

Everything from heaters to dimmers at a distance

Over
100
pages

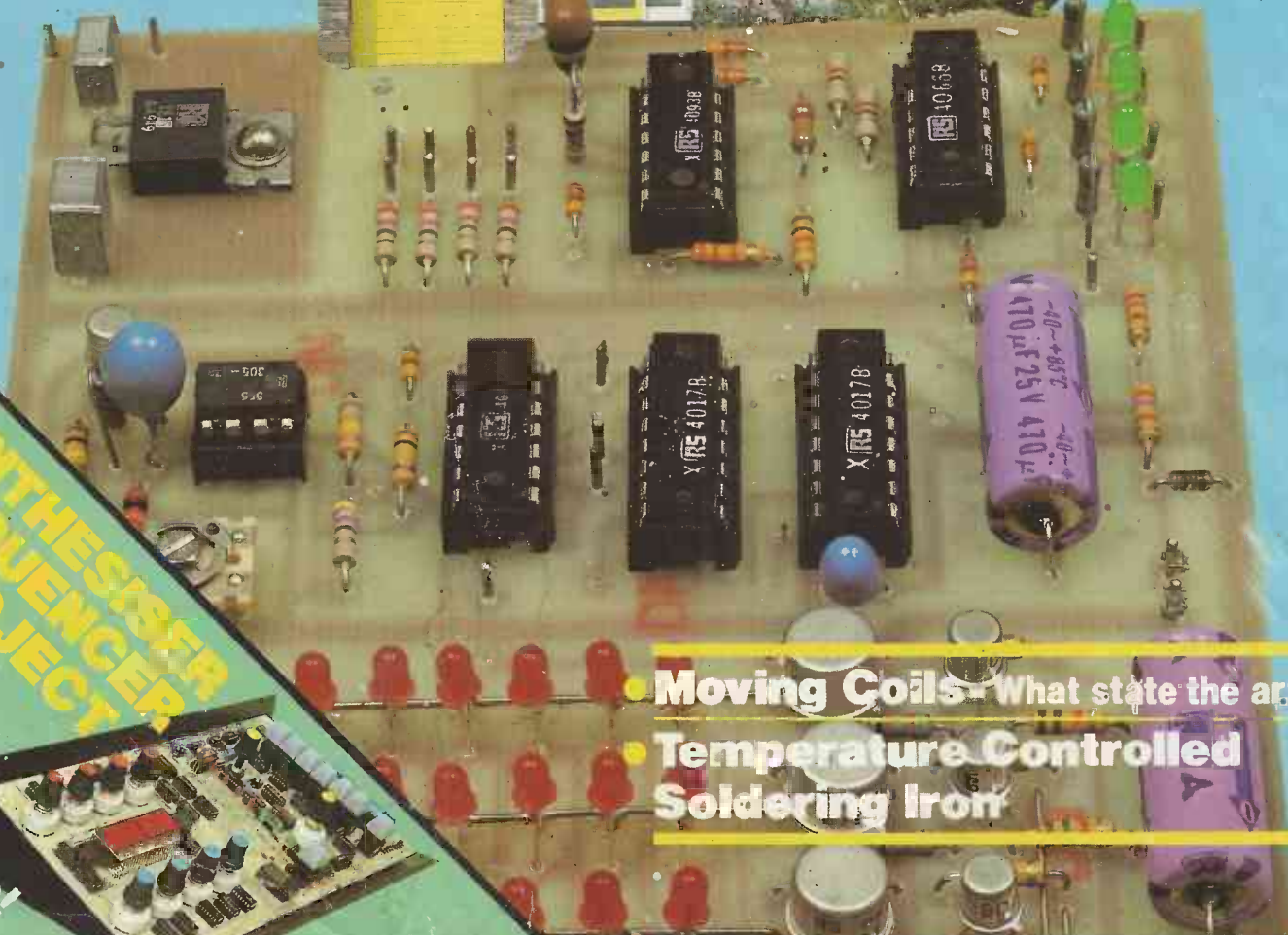

**SYNTHESIZER
SEQUENCER
PROJECT**
Over
1000
note
storage!

- Moving Coils - what state the art?
- Temperature Controlled Soldering Iron

MICROPROCESSORS... AUDIO...

TRANSCENDENT POLYSYNTH

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready built equipment costing thousands of pounds. Designed by synthesizer expert Tim Orr and being featured in this issue of Electronics Today International, this latest addition to the famous Transcendent family is a 4 octave (transposable over 7½ octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes. Whereas conventional synthesizers handle only one at a time.

The basic instrument is supplied with 1 voice and up to 3 more may be plugged in. A further 4 voices may be added by connecting to an expander unit, the metalwork and woodwork of which is designed for side by side matching with the main instrument. Each voice is a

complete synthesizer in itself with 2 VCOs, 2 ADSRs, a VCA and a VCF (requiring only control voltages and a power supply, the voice boards are also suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to ensure consistency between the voices.

Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plugs and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

EXPANDABLE POLYPHONIC SYNTHESIZER



COMPLETE KIT

ONLY

£320 + VAT

(Single voice)

Plug in extra
Voices — Kit price £52 + VAT
(£48 + VAT if ordered with kit)

Cabinet size 31.1" x 19.6" x 7.6" rear 3.4" front

Kit also available as separate packs

Item	Price	Pack	Price	Pack	Price
ADSR IC CEM 3310	£4.00	POLY 1	£9.50	POLY 14	£6.80
VCO IC CEM 3340	£6.00	POLY 2	£8.20	POLY 15	£4.80
0.1% 25 ppm M.F. Res	£0.50	POLY 3	£32.25	POLY 16	£8.20
0.5% 25 ppm M.F. Res	£0.25	POLY 4	£12.00	POLY 17	£16.30
30 ppm multilayer ceramic cap	£0.50	POLY 5	£17.25	POLY 18	£27.50
ICs and details of all packs in our		POLY 6	£10.50	POLY 19	£6.30
FREE CATALOGUE		POLY 7	£31.30	POLY 20	£3.90
		POLY 8	£18.90	POLY 21	£13.00
		POLY 9	£14.10	POLY 22	£8.45
		POLY 10	£13.10	POLY 23	£25.60
		POLY 11	£18.80	POLY 24	£25.80
		POLY 12	£9.30		
		POLY 13	£11.80		
				Total cost for individually purchased packs for single voice instrument	£355.15
				Complete kit for 4 voice expander including connectors	£295.00
				All prices VAT exclusive.	

POWERTRAN

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!
POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until June 30th, 1981, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and postal documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m. - 12 noon, 1-4.30p.m. Monday-Thursday.

MANY MORE KITS ON PAGE 8



electronics today

MAY 1981 VOL 10 NO 5

FEATURES

DIGEST	9	And now the good news...
DESIGNER'S NOTEBOOK	17	Switch to IC switches
KIT REVIEW	30	Cheap amplifier
SONIC HOLOGRAPHY	45	Surround yourself with sound
ASTROLOGUE	61	Crossword competition results
MICROBASICS	72	Six-five (oh-two) Special
SPOT DESIGNS	77	Spotted all over the place
AUDIOPHILE	84	Hi-fi hardware
TECH TIPS	94	Your very own circuits

PROJECTS

SOLDERING IRON	24	Superb switched-mode design
1024 COMPOSER	36	Synth sequencer
IR REMOTE CONTROL	51	Keep your distance
DIGITAL CLOCK	65	Horological hugeness
TOUCH DIMMER	79	Remote control too
POWER SWITCH	90	Yet another IR add-on
FOIL PATTERNS	100	Project PCBs

INFORMATION


NEXT MONTH'S ETI	15	Our coming attractions
EXHIBITION	49	Down your way
BOOKS	59	Read the fine print
NEXT MONTH'S CT	74	Computing Today — tomorrow
SUBSCRIPTIONS	105	Don't take chances
ETIPRINTS	109	PCBs — with ease



Compose yourselves p.36



Sounds amazing p.45

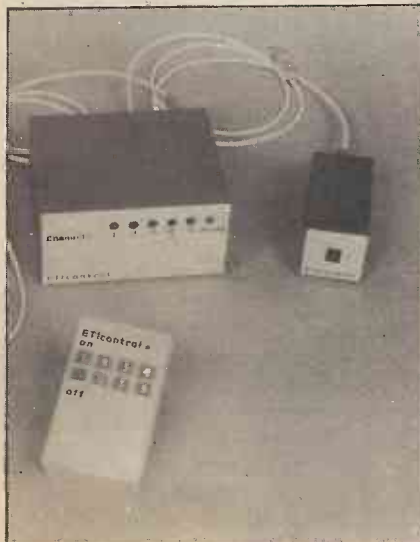

Remotely interesting p.51

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.

Ron Harris B.Sc. Editor
 Peter Green Assistant Editor
 Tina Boylan Editorial Assistant
 Paul Wilson-Patterson Group Art Editor
 Paul Edwards Drawing Office Manager
 Ray Marston Project Editor
 Steven Rowe Advertisement Manager
 Sally Holley Advertisement Representative
 T.J. Connell Managing Director

OVERSEAS EDITORS and their EDITORS
 AUSTRALIA — Roger Harrison
 CANADA — Halvor Moorshead
 GERMANY — Udo Wittig
 HOLLAND — Anton Kriegsman




Member of the Audit Bureau of Circulation



PUBLISHED BY Modmags Ltd., 145 Charing Cross Road, London WC2H 0EE
 DISTRIBUTED BY Argus Press Sales & Distribution Ltd., 12-18 Paul Street, London EC2A 4JS (British Isles)
 PRINTED BY QB Limited, Colchester
 COVERS PRINTED BY Alabaster Passmore

Electronics Today is normally published on the first Friday in the month preceding cover date. © MODMAGS LTD 1981. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. Subscription Rates: UK £11 including postage. Airmail and other rates upon application to ETI Subscriptions Service, Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE.

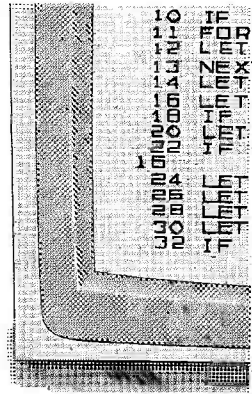New! Sinclair ZX81 Personal Computer. Kit: £49.⁹⁵ complete



Reach advanced computer comprehension in a few absorbing hours

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. At £99.95, the ZX80 offered a specification unchallenged at the price.

Over 50,000 were sold, and the ZX80 won virtually universal praise from computer professionals.

Now the Sinclair lead is increased: for just £69.95, the new Sinclair ZX81 offers even more advanced computer facilities at an even lower price. And the ZX81 kit means an even bigger saving. At £49.95 it costs almost 40% less than the ZX80 kit!

Lower price: higher capability

With the ZX81, it's just as simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8KBASICROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, or to select a program off a cassette through the keyboard.

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

Proven micro-processor, new 8KBASIC ROM, RAM – and unique new master chip.


Built:
£69.⁹⁵
complete



Kit or built – it's up to you!


The picture shows dramatically how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

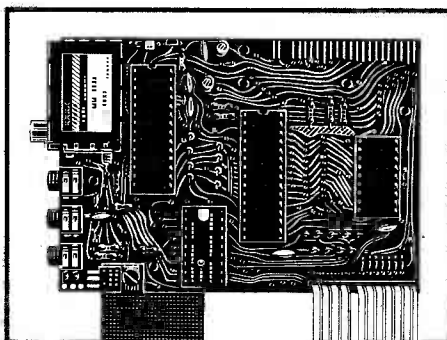
Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



New Sinclair teach-yourself BASIC manual

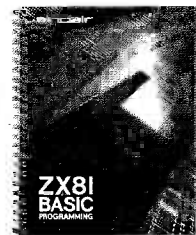Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs. You need no prior knowledge – children from 12 upwards soon become familiar with computer operation.



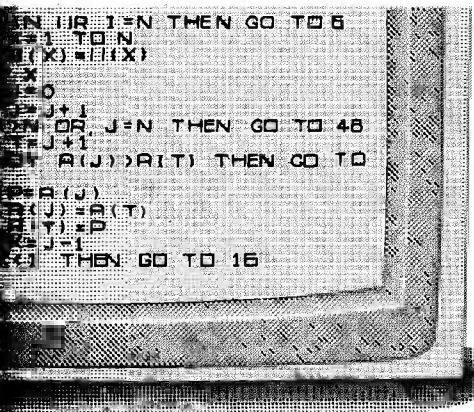

If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 - including the ability to drive the Sinclair ZX Printer.

Coming soon - the ZX Printer.


Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumeric across 32 columns, and highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50 - watch this space!



16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

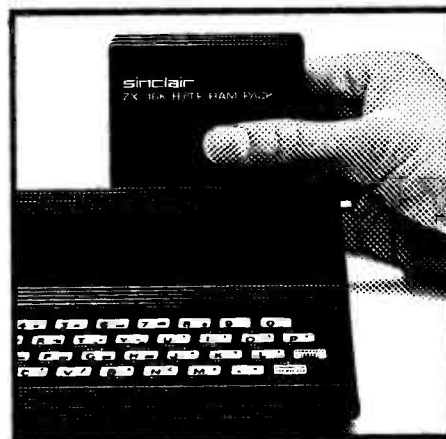Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.



How to order your ZX81

BY PHONE - Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay by cheque, postal order, Access or Barclaycard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	8K BASICROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

TOTAL £ _____

Please tick if you require a VAT receipt

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ _____

*Please charge to my Access/Barclaycard account no. _____

*Please delete/complete as applicable. Please print.

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST - no stamp needed. ET105

New, improved specification

- Z80A micro-processor - new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function - useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer (not available yet - but coming soon!)
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip - unique, custom-built chip replacing 18 ZX80 chips.

sinclair ZX81

Sinclair Research Ltd,
6 Kings Parade, Cambridge, Cambs.,
CB2 1SN. Tel: 0276 66104.
Reg. no: 214 4630 00

DIGEST

Visionary Idea

That world-famous character Uncle Clive Sinclair has struck again. This time Sinclair Research Ltd has developed a new flat-screen pocket-size television which should be available by the middle of next year. Its announcement follows a five year development project costing £1 million and partly backed by the National Research and Development Council. The investment for manufacturing what will initially be a pocket black-and-white TV with FM radio will be around the £5 million mark, supported by industry grants from the Scottish Economic Planning Department who will provide £1.5 million plus a regional development grant of £1.1 million, making 22% of the total capital employed. (Perhaps Sinclair's catch-phrase should be 'your wish will be granted?') Sinclair's contribution will be funded from profits derived from its equally well-known personal computer business. Sinclair have managed to achieve a number of interesting breakthroughs with their flat screen TV, not least perfect-

ting a new method of vacuum-forming glassware, a volume reduction of 2½ times over a conventional CRT, and a power requirement reduction five times better than previously achieved. Impressive huh? Manufacture of the tube has been sub-contracted to Timex who will produce it in Dundee and expect to employ an extra 1,000 people by 1985.

The cathode ray tube measures approximately 4 x 2 x ¾ inches and is assembled from two sheets of glass, a flat front plate and a vacuum-formed backing plate. The phosphor screen is coated on the interior of the backing plate and is viewed through the front face from the same side that the electrons strike. As a result, the brightness is more than double that of a conventional CRT with the same beam energy. The electron gun is set to one side of the screen with its axis parallel to the screen. Two sets of electrostatic deflection plates in the gun assembly provide horizontal and vertical scanning and a third set between the phosphor screen and front face bends the electron beam



towards the screen. The tube assembly lends itself to low-cost mass production and has significantly fewer components than a conventional CRT. There will be many applications for this new tube; doubtless to say Sinclair will consider linking it to his personal computer, and the basic tube can be

modified for projection TV systems. A full colour three-tube system is being carefully considered with the electronics and optics able to fit into a shoe-box-sized unit projecting onto a wall-mounted screen. The initial TV/radio unit should retail for about £50. We ask ourselves 'is there anything this man can't do?'

Mini-Movies

Matsushita Electric of Japan have come up with a new mini colour video camera which contains the tape recorder as well. They think that it's such a good design that it should be made a world standard for miniature video. It uses metal


evaporated magnetic tapes which are actually slightly smaller than standard audio cassettes. The camera/recorder is almost as small as a conventional hand-held video camera; 229 mm (D) x 118 mm (H) x 67 mm (W) and weighs only 2.1 kg including batteries. The tape speed is 14.3 mm/S which is the slowest among systems of this kind. Matsushita achieved the compactness of this device thanks to the development of the 'Cosvicon' ½ inch colour image pick-up tube coupled with extensive use of LSI in the circuitry. For further details on this camera contact: National Panasonic UK Ltd, 300-318 Bath Road, Slough, Berkshire, SL1 6JB.



Kitting Out

TK Electronics, who specialise in electronic mini-kits for hobbyists, have extended their range to include some remote control kits. These include the MK6 Simple Infra-Red Transmitter (as featured in Kit Review last month), the MK7 Infra-Red Receiver, the MK8 Coded Infra-Red Transmitter and the MK12 16-channel Receiver. The MK6 and MK7 consist of a small hand-held, battery operated transmitter and a small mains powered receiver with a triac output capable of switching mains loads of up to 500 W. The MK8

can transmit up to 32 different commands depending on the keyboard used. The MK12 is a mains-powered unit with 16 CMOS outputs (0 to 15 V) which may be interfaced with logic, or used to drive relays or triacs for power switching. By changing the value of one resistor in the MK8 kit and adjusting the present on the MK12, simultaneous operation to two or more receivers in the same area can be achieved. Prices are: MK6 — £4.20, MK7 — £9.00, MK8 — £5.90, MK12 — £11.95 plus 40p postage and 15% VAT. TK Electronics, 11 Boston Road, London W7 3SJ.

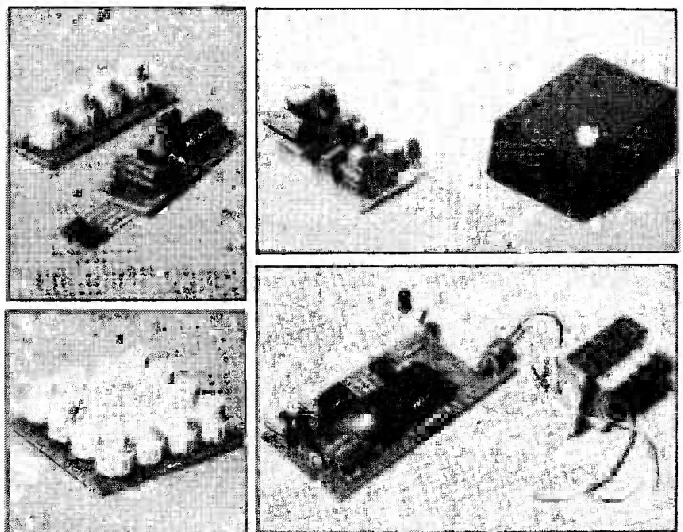


TRANSCENDENT 2000

COMPLETE KIT ONLY £168.50 + VAT!

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd) and featured as a construction article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal trim) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price! Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

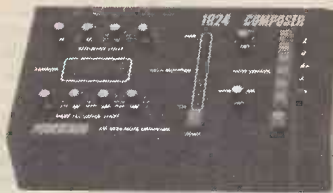

SINGLE BOARD SYNTHESIZER



Cabinet size 24.6" x 15.7" x 4.8" (rear), 3.4" (Front).

1024 COMPOSER

THIS MONTH'S FRONT COVER FEATURE!
COMPLETE KIT ONLY £89.50 + VAT!

ETI VOCODER

COMPLETE KIT ONLY
£195 + VAT!

KIT INCLUDES FREE FOOT CONTROL
AND TEST OSCILLATOR



Panel size 19.0" x 5.25". Depth 12.2".

Featured as a construction article in **Electronics Today International** this design enables a vocoder of great versatility and high intelligibility to be built for an amazingly low price. 14 channels are used to achieve its high intelligibility, each channel having its own level control. There are two input amplifiers, one for speech either from microphone or a high level source e.g. mixer or cassette deck and one for external excitation (the substitution signal) from either high or low level sources. Each amplifier has its own level control and a rather special type of tone control giving varying degrees of bass boost with treble cut or treble boost with bass cut. The level of the speech and excitation signals are monitored by LED PPM meters with 10 lights — 7 green and 3 red which indicate the level at 3dB steps. There are three internal sources of excitation — a noise generator and two pulse generators of variable frequency and pulse width. Any of the internal sources and the external source can be mixed together. There is a voiced/unvoiced detector which substitutes noise for the excitation signal at the points in speech where the vocal chord derived sounds of the speaker are substituted for by the unvoiced sounds of sibilants, etc. There is a slow rate control which smooths out the changes in spectral balance and amplitude enabling a change of the speech into singing or chanting and other special effects. A foot switch is provided to permit a complete freeze in spectral balance and amplitude whenever required. An LED on this indicates when the freeze is in operation.

An output mixer allows mixing of the speech, external excitation and vocoder output. The majority of the components fit into the large analysis/synthesis board with the rest on 8 much smaller boards with the controls and sockets mounted on them for ease of construction. Connectors are used for the small amount of wiring between the boards. The kit includes fully finished metalwork, professional quality components (all resistors 2% metal oxide) nuts, bolts, etc. — even a 13A plug!

TRANSCENDENT DPX

MULTI-VOICE SYNTHESIZER

Another superb design by
synthesizer expert Tim Orr
published in
Electronics Today International

COMPLETE KIT
ONLY
£299 + VAT!



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound—fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrator comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.



The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

POWERTRAN



MANY MORE KITS ON PAGE 107. MORE KITS AND ORDERING
INFORMATION ON INSIDE FRONT COVER


All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.

PCB FOIL PATTERNS

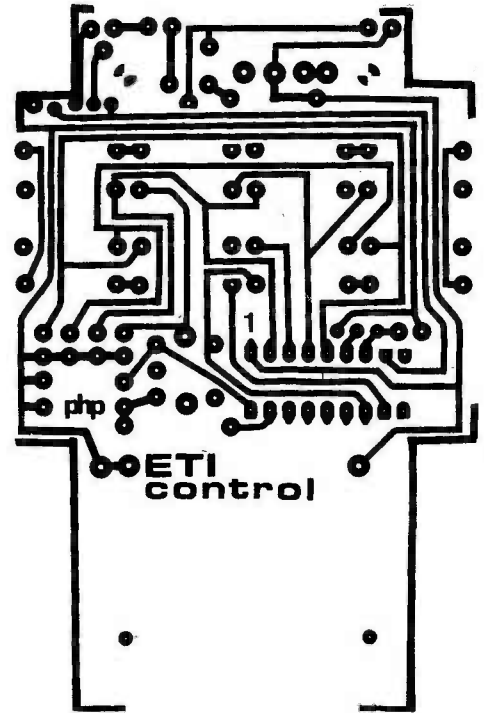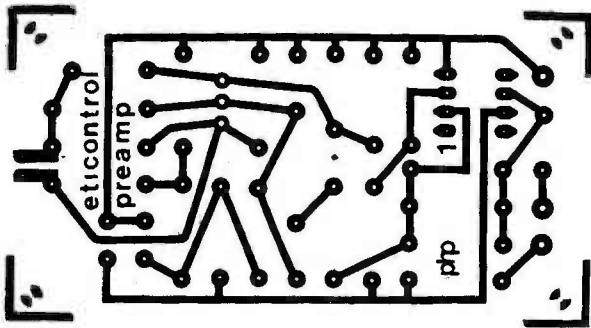

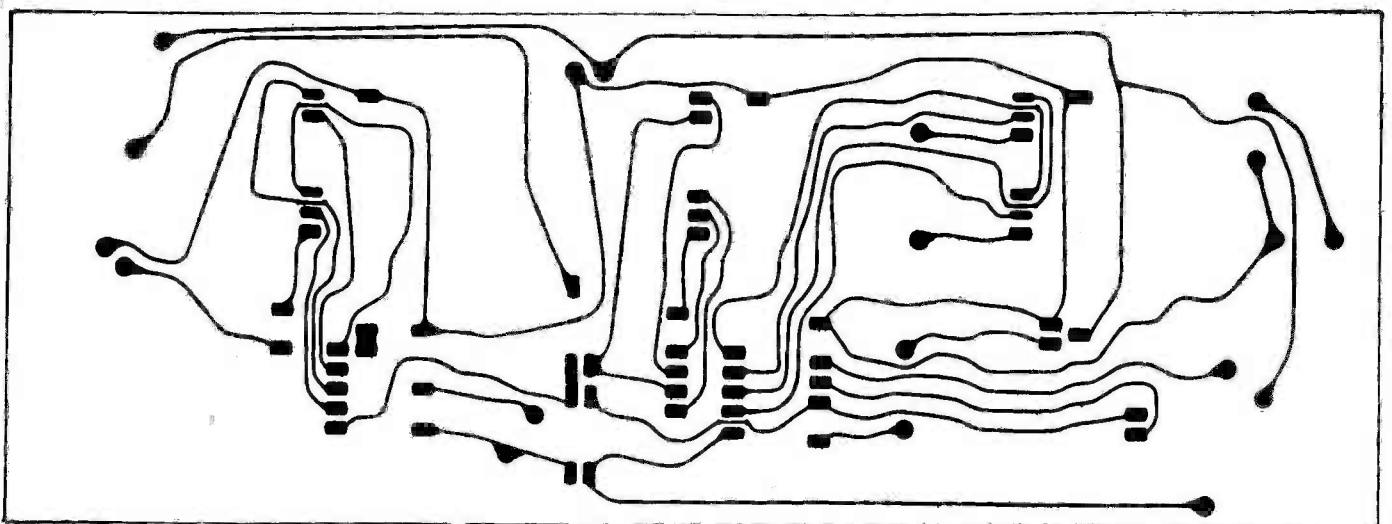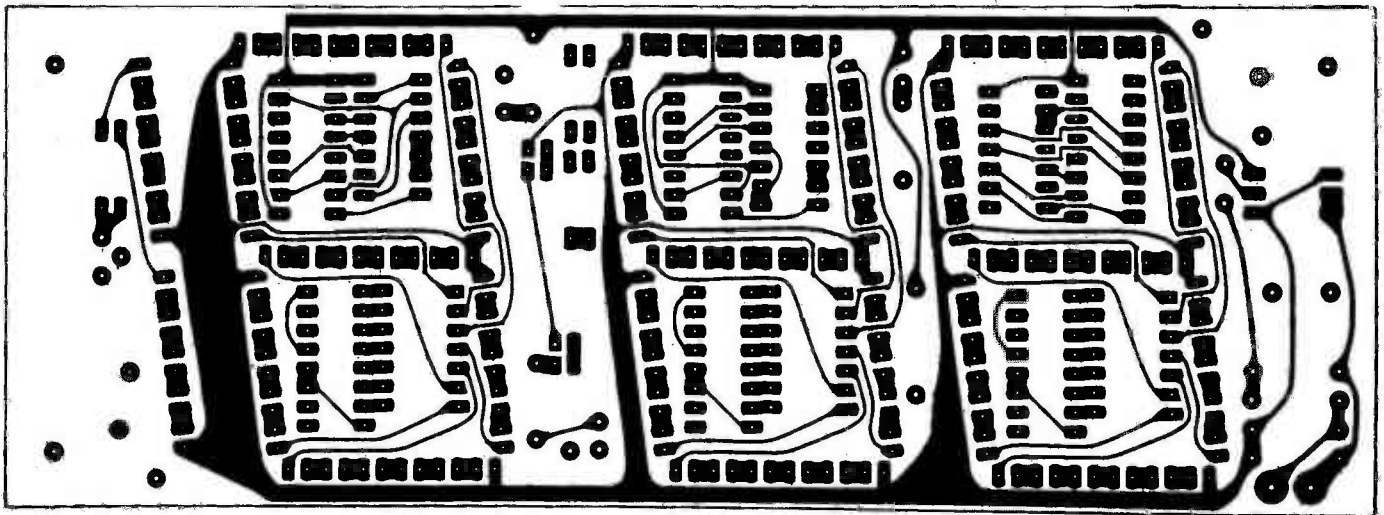Above: The Remote Control preamp board.
Right: Remote Control transmitter board.
Below: The two sides of the Digital Clock PCB.





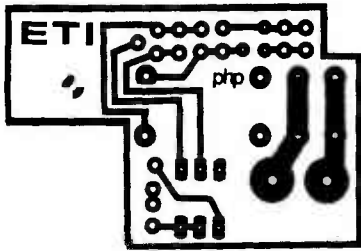


Above: Power switch foil pattern.

The foil patterns for the 1024 Composer are too large to fit into the magazine. You can obtain them by sending us a large SAE. Commercial firms should note that Powertran hold the copyright on the board.

Below: The Remote Control decoder board.

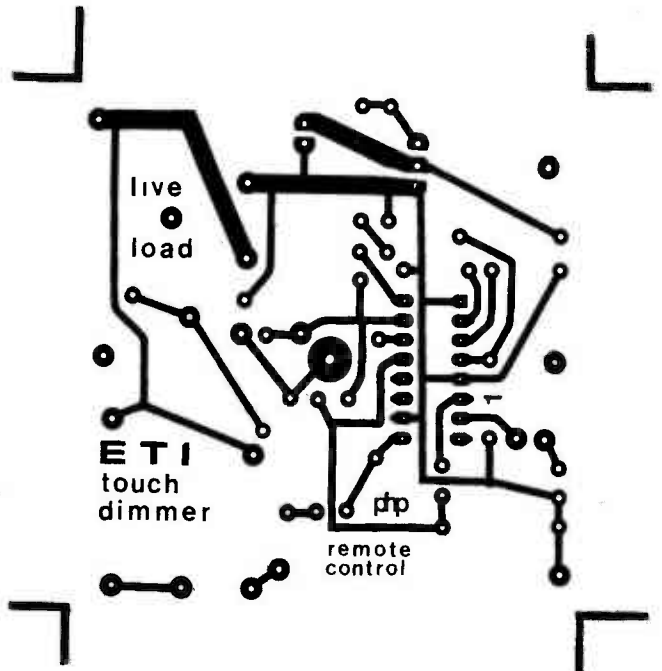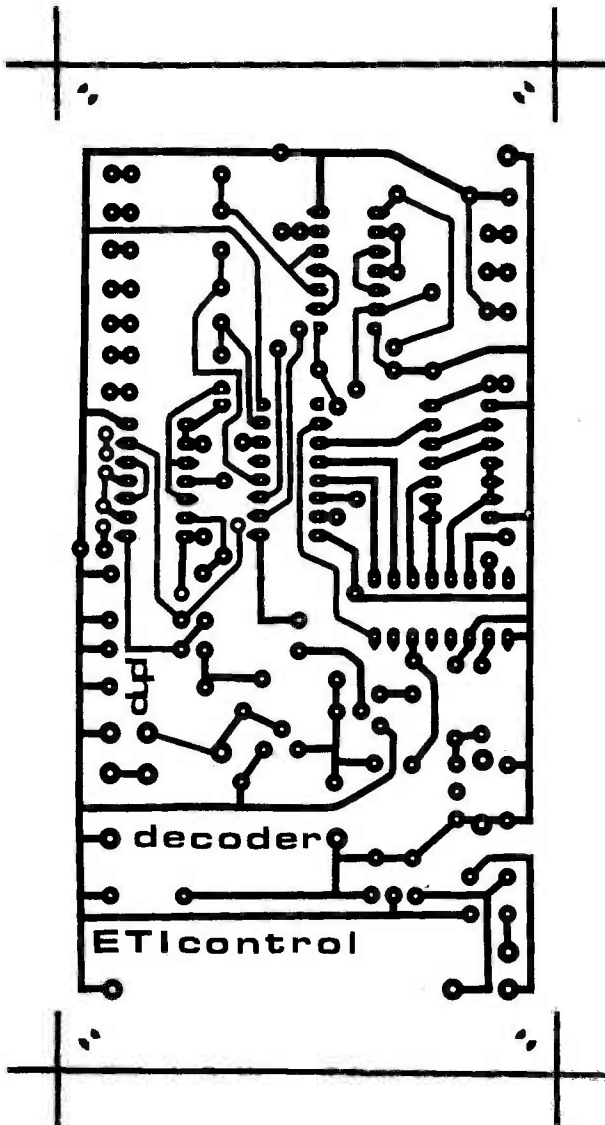

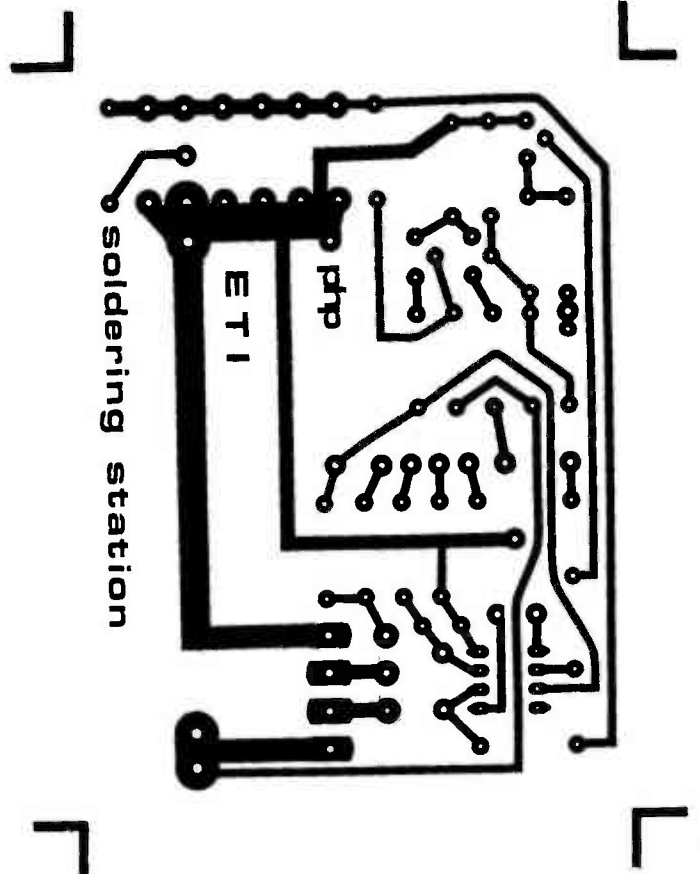Above: Touch dimmer PCB.
Below: Foil pattern for the Microstation.



TV SOUND TUNER ETI SEP 80 PROJECT

All parts available / send for list
ALSO

**No. 1 for Teletext Kits
TV Spare Parts and Components**

Callers welcome at Shop Premises

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD
TELEPHONE: 01-794 8751

Near West Hampstead Jubilee & British Rail Stations

CHESS COMPUTERS TV GAMES HAND-HELD GAMES

EGS

A DIVISION OF CIRCOLEC
SPECIAL SPRING OFFERS!

ELECTRONIC GAMES SHOP

TV GAMES

Atari VCS.....	£98
Philips V7000.....	£99
Mattel.....	£199
Database.....	£54
Cartridges.....	P.O.A.

ALL
PRICES
INC.
VAT

CHESS COMPUTERS

Challenger 7'.....	£78
Sensory '8'.....	£113
Voice Sensory.....	£243
Chess Champion.....	£25
Backgammon Challenger.....	£54

HAND HELD GAMES

Galaxy Invader 1000.....	£22.95
Earth Invader.....	£24.95
Jet Fighter.....	£21.95
Vermin (Mole Bashing!).....	£17.95
Fire.....	£17.95

Free Mains Adaptor
While Stocks Last!
New!

MANY OTHERS AVAILABLE

RING 01-767 1233 FOR DETAILS!

★ P&P on Games Free ★ Please add £1 for Cartridges ★
Make cheques payable to Circolec

FREEPOST (NO POSTAGE REQD.) LONDON SW17 8BR



TELEPHONE CREDIT ORDERS WELCOME



**WORTH
UP TO
£30**

FREE QUARTZ WATCH OFFER on all Thandar test equipment

If you are interested in purchasing a hand-held digital multimeter, a bench digital multimeter, a hand held frequency meter, bench frequency meter, a pulse generator, a function generator, a fully portable brief-case size oscilloscope, a 2" video monitor or even an eprom programmer and obtain a **quality QUARTZ watch free of charge** then why not take advantage of our special offer.

For purchases of between £39 and £99 we will send free of charge a gold-plated Digital LCD, ultra-slim, five-function watch. For purchases of £100 and over we will send a gold-plated, ultra-slim, analogue watch, as per photograph. Both these watches have leather straps. This watch offer is subject to availability and in any event we will send alternative watches with a retail value of £12 and £30 respectively. **YOUR WATCH MAY BE SENT SEPARATELY TO ANY ADDRESS WITHIN THE UK IF REQUIRED.**

Hand-held digital multimeters
PDM 35 L.E.D. hand held DMM £39.68
TM 354 L.C.D. hand held DMM £45.94
TM 352 L.C.D. hand held DMM £57.44

Bench frequency meters
TF 040 bench frequency meter £126.50
TF 200 bench frequency meter £166.75

Bench digital multimeters
DM 235 L.E.C. digital multimeter £60.38
DM 350 L.E.D. digital multimeter £83.38
TM 353 L.C.D. digital multimeter £96.60

Pulse Generator
TG 105 pulse generator £97.95

Hand-held frequency meter
PFM 200 frequency meter £57.27

Bench Function Generator
TG 100 function generator £90.85

Fully Portable Oscilloscope
SC 110 Oscilloscope £159.85

2" Video Monitor
MON 1A 2" Video monitor £109.25

Eprom Programmer
PKW 5000 Eprom Programmer £918.85

All prices include V.A.T. Official orders welcome. Mail order only, or callers at our warehouse by prior appointment. Barclaycard/Access welcome. Cheque/P.O.s, etc., with order. Large s.a.e. for complete Thandar list. All items POST FREE.


B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex, SS9 5TY
Tel: Southend 527572

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL
PRICES
INCLUDE
VAT

BECKER
Hi-Fi Speakers

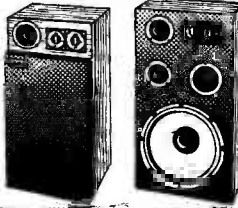


All models multi-speaker systems

With controls, attractive woodgrain finish.
RMS ratings for 8 ohm.

12.60 12" 4 speaker system 60 watts
26 1/2" x 14 1/2" x 11" £115.95 pair

15.90 15" 5 speaker system 90 watts 28"
x 17 1/2" x 11 1/2" £135.95 pair
(UK c/p £12.00 pair)

ON DEMONSTRATION TO CALLERS

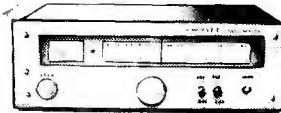


SCOTT T516 STEREO FM/AM TUNER

HIGH QUALITY STEREO FM/AM
TUNER BY SCOTT OF USA.

Overall size 5" x 14 1/2" x 12". Brand new and fully
guaranteed at a special low price.
(C/P £1.55)

£38.95

On demonstration for callers.

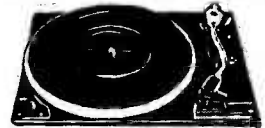


JVC BELT DRIVE TURNTABLE

JVC TURNTABLE WITH FREE AUDIO
TECHNICA AT100 STEREO CARTRIDGE.

- ★ S shaped tone arm
- ★ Belt drive
- ★ 12" Platter ★ Calibrated counter-balance weight
- ★ Anti-static device

Size 12 1/2" x 15 1/2"
(C/P £1.55)

£29.95

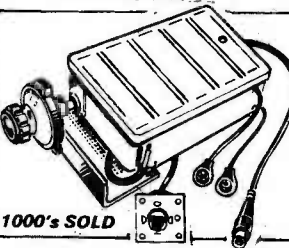

1000's SOLD

TV SOUND FROM YOUR HI-FI

High quality TV sound converter plugs into serial
socket of your FM tuner. 9 volt battery operated
(Battery not supplied). Nothing to look at ... but just
listen!

- ★ Filtered slow-motion drive

(UK Post etc. 65p)

On Demonstration for callers.

£11.50



SEAS SPEAKER KITS



Professional sound hi-fi speaker kits with high
sensitivity (80-92dB). Extended frequency response
[223-50-20kHz, 253-35-25kHz]. Designed and
made in Scandinavia to the highest quality. All
supplied with complete cabinet plans, tweeters/
crossovers/leads etc. ★ On Demonstration to
callers.

- ★ HI-FI 223. 30/45 watt 3 speaker 8" system £43.50 pair
- ★ HI-FI 253. 60/100 watt 3 speaker 8" system £34.50 each
- ★ HI-FI 403. 60/100 watt 3 speaker 10" system £44.50 each
- ★ HI-FI 603. 90/150 watt 3 speaker 12" system £84.50 each

(UK C/P £7.50)

COMPLETE RANGE OF SEAS
CHASSIS SPEAKERS ETC
ALWAYS IN STOCK
ALSO STOCKISTS FOR
AUDAX, GOODMANS, KEF, PEERLESS ETC.

PIEZO TWEETERS



Clean sound, very low distortion tweeters. No
crossover required. Suitable up to 100 watts - more
in series.

- 1 Mid-range horn for disco/pa/groups £8.95
- 2 Tweeter horn for hi-fi/disco/pa £5.50
- 3 Popular hi-fi and disco £4.40
- 4 Flat type hi-fi £3.50

On Demonstration to callers.
C/P 50p (up to 4 Home)

STEREO ACCESSORIES

- ★ GE1305 Hi-Fi Frequency Equaliser £62.95
- ★ APN 200 Peak programme meter (twin scale) £30.95
- ★ MS3219 Twin Scale audio output meter £12.95
- ★ MC350 Tape echo chamber £59.95

FREE CATALOGUE

Large range of
speakers/stereophones/microphones/mixers/PA
equipment etc - and much more!
Plus huge range of test equipment.

ALL PRICES INCLUDE VAT

SEND LARGE 20p SAE

PRICES CORRECT AT 1.3.81

AUDIO ELECTRONICS

Cubgate
Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND.
TELEPHONE 01-724 3564 OPEN 9-6 Mon-Sat


ALSO AT HENRY'S RADIO,
404/406 EDGWARE ROAD, LONDON W2 1ED

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
OR CALL IN AND SEE FOR YOURSELF



ELECTRONIC IGNITION SAVES PETROL

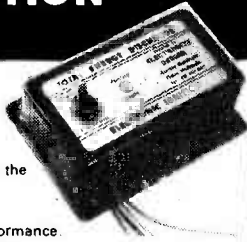More and more new cars use electronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.



TOTAL ENERGY DISCHARGE gives all the advantages of the best capacitive discharge ignitions:

- ★ **Peak Performance**—higher output voltage.
- ★ **Improved Economy**—consistent high ignition performance.
- ★ **Better Starting**—full spark power even with low battery.
- ★ **Accurate Timing**—prevents contact wear without 'contactless' errors.
- ★ **Smooth Performance**—immune to contact bounce effects.

PLUS

- ★ **SUPER HIGH POWER SPARK**—3½ times the energy of ordinary C.D. systems
- ★ **OPTIMUM SPARK DURATION**—to get the very best performance and economy with today's lean carburettor settings.
- ★ **DESIGNED IN RELIABILITY**—with the 'ultimate insurance' of a changeover switch to revert instantly to standard ignition.

TECHNICAL DETAILS

HIGH EFFICIENCY INVERTER. A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4 volts.

SUPERB DISCHARGE CIRCUIT. A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the H.T. system.

SOPHISTICATED TRIGGER CIRCUIT. This circuit removes all unwanted signals caused by contact volt drop, contact shuffie, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

IN MONEY-SAVING KIT FORM at £14.85

Also MOTORCYCLE TWIN OUTPUT KIT at £22.94

Inc. V.A.T. and P. & P.

All you need is a small soldering iron and a few basic tools — everything else is supplied with easy-to-follow instructions.

FITS ALL 6/12-volt NEGATIVE EARTH VEHICLES

ELECTRONIZE DESIGN

2 Hillside Road, Four Oaks
Sutton Coldfield, West Midlands, B74 4DQ
Phone 021-308 5877

DISCO LIGHTING KITS!!!

First class constructional projects. c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 3 channel sound-to-light.
£9.90 300 w/channel 1v — 100w input

LK3 2kW slider dimmer
£8.90 suitable for clubs/pubs.
A professional unit c/w
FACE PLATE

LK2 3 channel 3kW
£17.90 zero voltage firing
200mV — 100 watts input.

LK4 4 channel 4kW
£16.50 audio — forward/reverse
auto — two speed ranges.

ALL KITS C/W
circuit, comprehensive
instructions & full
parts guarantee



Carriage on above 70p

Suitable case for
LK 1/2/4 **£3.50**
100w spots ES or BC
£1.50.
Coloured pigmy lamps
65p.
8m rope lights
£49

UNREPEATABLE HI-FI BARGAIN


3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

- ★ 6" linen surround bass unit
- ★ 5" mid-range unit
- ★ 3" tweeter
- ★ 3 way crossover, fixing screws & baffle
- ★ 20 watts handling capability.
- ★ 20 watts handling capability.

Full instructions provided
Must be heard to be believed!!

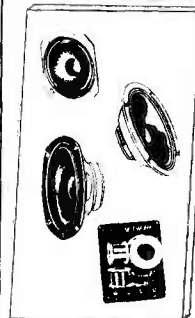£10.50 or 2 kits for **£20** Carr. £1 per kit



SAXON ENTERTAINMENTS (ETI)

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.


(01) 684 8007

Order by phone — Access/Barclaycard/C.O.D.
Open Mon. — Sat. 9am — 5pm.

Some day all
power amps will
be made this way

THE POWERFET AMPLIFIER

See next month's issue for
our component bargains
or send SAE for lists

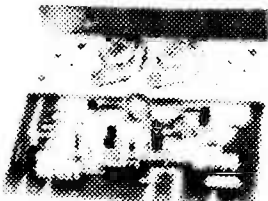

PFA 80
(100W plus into 8Ω)

Elegant Simplicity

Advances in high technology should make life simpler. A cluttered power amplifier board may well perform superbly, but its busy elaboration is an indication that its design is pushing the limit of its component technology.

There are now many first-class bipolar power amps on the market. All of them are complex and consequently expensive. Any additional improvements in the areas where they are weak (e.g. H.F. distortion) can only be obtained with yet further complexity and cost.

Only a new technology can provide the sort of "quantum jump" in component performance necessary to reduce the clutter on the board, reduce the cost and make the highest fit once more affordable.

Powerfets

So far 29 semiconductor manufacturers have invested in this new technology. Clearly powerfets are something special.

Their enormous power gains eliminate conventional drive circuitry in power amps, permitting delightfully simple designs. Their freedom from secondary breakdown and their tendency to shutdown when thermally overstressed, result in inherently stable and destruction proof output stages, not needing protection circuitry. And perhaps best of all, their lack of charge storage make them fast and responsive, producing amplifiers of wide bandwidth and low distortion even at high frequencies.

Power supplies available. VAT inclusive prices. P&P 40p or 75p with PFA or transformers

IT GROWS!



PFA80/120

The PFA is perhaps the perfect realisation of the classic powerfet amp design. The superb P.C.B. allows the use of either one or two pairs of output devices, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads.)

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

Specification	PFA80	PFA120
Bandwidth	10Hz—	100KHz± 1dB
Output power	X22	X22
RMS into 8Ω	80W (Vs ± 50V)	120W (Vs ± 55V)
T.H.D.	≤ 0.008%	≤ 0.005%
from 1w to rated output at all audio frequencies		
SNR	120dB	120dB
Slew Rate	20V/μs	20V/μs
Gain	X22	X22
Rin	30K	30K
Vs max.	+ 70V	+ 70V
Cost		
(built)	£15.95	£22.85
(kit)	£13.95	£20.85

PFA 120

(150W plus into 8Ω, 300W into 4Ω)

Pre-amp PAN 20

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain/attenuator control (volume control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag. PUs, and space on the board is available for different equalisations.

Specification
B.W. 20Hz-30KHz ± 1dB
THD 0.003%

SNR 85dB (ref. 5mV RIAA)
105dB (ref. 100mV flat) ± 20V
Vs Output 1V (clips at +20dB)

Cost (built board less controls) **£4.75**, 2 needed for stereo

Power Amp PAN 1397

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation, providing high powers from low supply voltages.

Specification
Output power RMS 20W into 8Ω at ± 22V
20W into 4Ω at ± 19V
THD 0.02% at 1KHz, 1W to 12W
SNR 90dB
Input 100mV into 50K

Cost (Built) **£5.80**

FROM THE POWERFET SPECIALISTS **J. W. RIMMER**

Mail order only to —
Technical enquiries **148 QUARRY STREET, LIVERPOOL L25 6HQ. Tel: 051 428 2651**
367 Green Lanes, London N4 1DY
01-800 6667

ELECTRO SUPPLIES

TRANSISTORS

BC107	10p	BF194	12p	2N3055	45p
BC108	10p	BF195	12p	2N3583	60p
BC109	8p	BF197	14p	2N3702	10p
BC125B	10p	BF245	30p	2N3705	10p
BC149	10p	BF256A	40p	2N3710	10p
BC154	12p	BF324	30p	2N4061	15p
BC159	9p	BF469	65p	2N4123	10p
BC171	10p	BF495	20p	2N4125	12p
BC237	12p	BF595	30p		
BC337	15p	BFR40	25p		
BC547	10p	BFY90	50p		
BD238	40p	BUW81A	200p		
BD239	40p	MJE340AT	50p		
BD371A	30p	MPF131	25p		
BDX94	65p	MPF132	25p		
BDY92	120p	MPU131	25p		

LINEAR ICs

CA3012	45p	SAJ110A		TDA1170	75p
CA3080	50p	SAS580	100p	TDA1190	200p
LM324	60p	SAS590	100p	TDA2524	150p
LM741	15p	TAA320	40p	TDA2541	150p
LM1458	40p	TBA120S	60p	TDA2560	150p
LM3900	60p	TBA651	100p	TDA2581	175p
MC1307	75p	TBA661B	125p		
MC1310	100p	TBA800	70p	SPECIAL OFFER	
MC1349	90p	TBA810S	80p	AY-5-3507 DVM	
MC1350	90p	TBA920	150p	CHIP (with data)	
MC1558	100p	TCA270S	90p	£2.75 (limited quantity)	
NE535T	50p	TDA0470			
NE555	22p	TDA1010	150p		

LOW PROFILE IC SOCKETS

14 pin - 12	100 (150 £10)
16 pin - 10	100 (130 £10)
22 pin - 7	100 (100 £10)
24 pin - 6	100 (70 £10)
40 pin - 3	100 (40 £10)

For larger quantities please phone for prices

35-amp 50-volt Stud Diodes, c/w mounting kit **4 £1**

Semi-conductor Packs. Diodes/Transistors/SCRs/ICs. over 100 items (no rejects) **£1.50 each, two for £2**

SPECIAL OFFERS

LM1101N (DOLBY B I/C)	£2.50
TDA2020 (20 watt amp)	£2.50
MM57105 (PAL colour TV game I/C)	£2.00
MM53100N (TV clock timer)	£2.00
AY-5-1013 (UART)	£2.00

Prices include VAT, please add 50p P&P

MAIL ORDER DEPT.
(Callers please phone first)
BOWNESS MILL
SHAWCLOUGH RD
WATERFOOT
ROSSENDALE, LANCS
TEL: ROSSENDALE 5556

RETAIL SHOP
(Open 6 days)
6A TODD ST
MANCHESTER
(next to Victoria Stn.)
TEL: 061-834 1185

CALCULATORS

All equipment new boxed and fully guaranteed
Price includes V.A.T., Post and Packing

PRICES

ANY CASIO, SHARP OR TEXAS CALCULATOR SENT FOR £1 LESS THAN ANY OTHER ADVERTISED PRICE IN THIS MAGAZINE (subject to stock)

CASIO PROGRAMMABLES	
FX 180P programmable FX 100	£18.95
FX 2700 P, new model, 38 steps	£21.95
FX 3500 P, new model, 38 steps	£49.95
FX 501 P, 51 function, 11 memory, 128 steps	£89.95
FX 502 P, 51 function, 22 memory, 256 steps	£19.95
FA 1 CASSETTE INTERFACE transfers progs to tape	£65.95
FX 501 P with FA 1	£85.95
FX 502 P with FA 1	£85.95
CASIO SCIENTIFICS	
FX 58, 38 function, 8 digits	£18.95
FX 330, 38 function, 8 digits	£18.95
FX 510, 50 function, 10 digits	£18.95
FX 3200, 43 function, 10 digits	£20.95
FX 6100, 39 function, 8 digits plus time/alarm	£18.95
FX 7100, 39 function, 8 digits plus time/alarm	£23.95
FX 8100, 48 function, 8 digits plus time/alarm	£13.95
FX 81, low cost, 30 function, 8 digits	£15.95
FX 100, low cost, 44 function, 10 digits	£15.95
CASIO	
BO 1100, biorhythms/clock	£12.95
MG 770, SPACE INVADERS, card size	£10.95
MG 880, SPACE INVADERS, full size	£13.95
LC 80, HIGH-QUALITY CARD CALCULATOR	£13.95
SHARP	
POCKET COMPUTER 1211 with interface	£108.95
EL 5101 PROGRAMMABLE 16 digit	£41.95
EL 5100 PROGRAMMABLE 24 digit	£51.95
TEXAS INSTRUMENTS	
*TI 51-11 PROGRAMMABLE 32 step	£28.95
*TI 57 PROGRAMME 50 step	£27.95
*TI 58 PROGRAMMABLE 480 step	£83.95
*TI 58C as above with constant memory and programme	£78.95
*TI 59 Programmable 360 step	£178.95
PC 100C printer for TI 58/58C/59	£173.95
*TI PROGRAMMER	£31.95
BATTERY PACKS for all models; * includes mains adaptor/charger	£8.95

LITTLE PROFESSOR	TEXAS ELECTRONIC LEARNING AIDS	LETTER LOGIC	£21.95
DATAMAN	£11.95	SPEAK & SPELL	£39.95
	£18.95		
TELEPHONES			
CORDLESS PRO FF 3000, up to 600 feet range			£139.95
CORDLESS PHONE 4001, up to 500 feet range			£108.95
FLIP PHONE 788 with memory radial, easy to connect as extension			£28.95
ANSWERING MACHINE CALLSAVER twin tape			£143.95

FULL RANGE OF CASIO, SHARP AND TEXAS CALCULATORS AVAILABLE
SEND P.O., CHEQUE, ACCESS NUMBER OR ADD 75P FOR C.O.D. (up to £100)
CALCULATOR SALES & SERVICE
FREEPOST, REDDITCH, WORCS, B97 4BR

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 20p PER PACK UP TO FOUR PACKS
FIVE OR MORE POST FREE
BUY SIX PACKS AND GET A SEVENTH PACK FREE!

MN1. 300 ¼-watt Resistors pre-formed for P&C Mtg.	MN23. 116 asstd. screws, nuts, washers, self-tappers etc.
MN2. 200 ¼ & ½-watt Resistors	MN24. 100 asstd. small springs.
MN3. 100 1 & 2-watt Resistors.	MN25. 50 asstd. pop rivets.
MN4. 50 Wirewound Resistors.	MN26. 50 asstd. insulated crimps.
MN5. 100 metal oxide Resistors: 1%, 2% and 5%.	MN27. 200 items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.
MN6. 12 asstd. potentiometers.	MN28. 20 asstd. fuses, 1¼" 20mm etc.
MN7. 25 asstd. skeleton pre-set Resistors.	MN29. 75mts equipment, wire, asstd. colours and sizes.
MN8. 50 asstd. Electrolytic Capacitors.	MN30. 3 x 2m length, 3 core, mains cable.
MN9. 100 asstd. Ceramic Capacitors. Pile, disc, tub and monolithic etc.	MN31. 12 asstd. trimmer capacitors, compression film. Air-spaced etc.
MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.	MN32. 15 30pF Beehive trimmers.
MN11. 20 asstd. Silver Mica Capacitors	MN33. 20 coil formers, ceramic, plastic, reed relay etc.
MN12. 8 Tantalum Bead Capacitors (useful values).	MN34. 25 min. glass reed switch.
MN13. 20 asstd. Transistors. BC, 2N Series + Power etc.	MN35. 10 asstd. switches, toggle, slide, micro etc.
MN14. 40 1N4148 Diodes.	MN36. 10 ex equipment panel lamps (no rubbish).
MN15. 5 Light Sensitive Devices.	MN37. 10 asstd. audio connectors. Din phono etc.
MN16. 20 min. wire-ended Neons.	MN38. 1 PCB with triac control IC data inc.
MN17. 2 12-volt Relays. Ex nearly new equip.	MN39. 1 oscillator PCB loads of components. (no data).
MN18. 3 Encapsulated Reed Relays. 9 12v. coil, d-pole and t-pole.	MN40. 50 Polystyrene capacitors.
MN19. 2 24-volt Relays. Ex nearly new equip.	MN42. 10 BC107 Transistors.
MN20. 1 240-110 to 12-volt, 100ma Transformer.	MN43. 10 BC108 Transistors.
MN21. 1 240-110 to 24-volt 100ma Transformer.	MN44. 10 Screwfix S.P.C.O. min. slide switches.
MN22. 8 .2" Led s with clips. 4 red, 2 yellow, 2 green.	MN58. 2xCA723 Voltage Regulator

CHORDGATE LTD.

75 FARINGDON ROAD, SWINDON, WILTS

TEL: SWINDON (0793) 33877

RETAIL SHOP AT ABOVE ADDRESS

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

SUBSCRIPTIONS

This year we present a new twelve-part, non-fiction series — ETI 1981. available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £11.00 we'll send you twelve issues of ETI.

To claim your years' supply of ETI, send your PO or cheque direct to :

ETI Subscriptions,
Modmags Ltd,
145 Charing Cross Road,
London WC2H 0EE



MICRO TIMES

19 Mill St. Bideford, North Devon. EX39 2JR
Telephone Bideford (023 72) 79798

★★ SUPER SAVERS ★★		
MEMORIES		EPROMS
Z114L 450ns..... £1.85	4116 200ns..... £1.85	2708 450ns..... £3.00
Buy 10 for £18★	4116 150ns..... £3.65	2716 450ns..... £4.60
Z114L 300ns..... £2.00	CMOS RAM 5101 £3.45	2732 Intel type £12.00
Buy 10 for £19.50★		

<p>★ SUPER SAVER PRICE ★</p> <p>The TC 5514P from Toshiba</p> <p>£4.75</p>	<p>6809 SINGLE-BOARD COMPUTER</p> <p>IEEE S-100 Standard Bareboard £48★★</p> <p>Uses 6809, 6850, 6821</p> <p>Buy set of 3, £21★</p> <p>ADSMON. (2716) £24</p> <p>Board plus all parts. Kit form £160★ plus 15% V.A.T. Plus £1 P. & P.</p>	<p>DATA S.A.E.</p> <p>AY-3-8910 G1 SOUND COMPUTER CHIP and music generator</p> <p>★ £7.25 ★</p> <p>SPECIAL</p>
--	---	--

JUST ARRIVED FROM VERO®
S100 Prototyping Boards.

Microboard Pattern 06-2175L.....	£16.40★
Square Pad Universal Pattern 06-2338F.....	£16.40★
Prototyping Board for your APPLE/ITT 2020.....	£8.37★

LM1871 ENCODER/TRANSMITTER
LM 1872 RECEIVER/DECODER

£4.50 each; pair for £8★

SUPER SAVER

FLOPPY DISC CONTROLLERS

FD1771.....	£23.95
FD 1791-2.....	£35.00
WD 1691D.....	£14.50
WD 2143-09.....	£5.00

★ SPECIAL ★ Complete Pkg. £53.00
Includes FD1791-2 + WD1691D + WD2143-09

INDIVIDUAL DATA AVAILABLE
50p per copy
Large S.A.E. please

COMBO CHIPS
Intended for Z80 usage.

Z80 Combo Chip (MK3886) 2½ meg.....	£25.00
Z80A Combo Chip (MK3886N-4), 4 meg.....	£29.95

DATA AVAILABLE ON SOUND CHIP
SN76477, 25p

ALSO:
LM 1871..... 25p
LM 1872..... 25p

Please send S.A.E.

L.P. DOUBLE FACE WIPE DIL SOCKETS BY VERO

40 pin.....	39p
28 pin.....	29p
24 pin.....	25p
22 pin.....	24p
18 pin.....	20p
16 pin.....	18p
14 pin.....	16p
8 pin.....	12p

LINEAR ICs

NE 555.....	18p
NE 556.....	50p
RC 4136.....	80p
LM 301AN.....	26p
LM 311P.....	48p
LM 324N.....	43p
LM 339N.....	43p
LM 380.....	65p
LM 3900N.....	48p
LM 3915.....	£2.10
SN76477N.....	£1.70
LM 741.....	18p
TLO 74CN.....	£1.25
1488.....	75p
1489.....	75p
8T26.....	£1.50
8T28.....	£1.70
8T95.....	£1.70

★ SPECIAL ★

LM 3914.....	£2.10★
LM 13600.....	£1.20★

LEDs

TIL 209.....	10p
TIL 212.....	16p
TIL 220.....	72p
TIL 224.....	18p

CPUs

6502.....	£6.00
6504.....	£7.25
6802.....	£9.00
6809.....	£15.95
8080A.....	£4.15
8085A.....	£6.80
Z80.....	£5.80
Z80A.....	£7.00

VOLTAGE REGULATORS

78L05.....	29p
78L12.....	29p
79M12.....	64p
79M05.....	64p
723.....	32p

THYRISTORS

C106D.....28p★

SOLDERLESS BREADBOARD
New from Vero the VEROBLOC. A prototyping method of building and testing circuits, designed to dovetail together to form a cont. 2-54 pitch; any size of IC can be accommodated. 29 rows of contact sockets enables mounting of 3 15-lead devices contiguously 3 Blocs can be interlocked and mounted on single Euro-card 100 x 160mm.
SPECIAL £3.55 each★

SUPPORT DEVICES

6520.....	£3.25
6522.....	£6.00
6532.....	£8.15
6810.....	£3.25
6821.....	£3.20
6845.....	£16.00
6850.....	£2.85
6852.....	£3.45
8212.....	£1.95
8216.....	£1.95
8228.....	£4.25
8255.....	£4.40
Z80 CTC.....	£5.70
Z80 PIO.....	£5.70
Z80A CTC.....	£8.85
Z80A PIO.....	£6.85
Z80 DMA.....	£19.50
Z80A DMA.....	£24.25
Z80 S10/0.....	£27.50
Z80 S10/1.....	£32.50
Z80 S10/1.....	£32.00
Z80 S10/2.....	£27.50
Z80A S10/2.....	£32.50

EUROPEAN ORDERS ACCEPTED
Add 15% P. & P. on total order
V.A.T. not applicable

MAIL ORDER
Access/Barclaycard
Welcome
Please add 50p P. & P.
Plus 15% V.A.T. to all orders

It is our policy to offer you brand-new, full-spec. devices. Prices subject to change without notice.



It's easy to complain about advertisements.

Every week, millions of advertisements appear in the press, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice and are legal, decent, honest and truthful.

But if you find one that, in your opinion, is wrong in some way, please write to us at the address below.

We'd like you to help us keep advertising up to standard.



The Advertising Standards Authority. If an advertisement is wrong, we're here to put it right.

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

MAIL ORDER ONLY				TRIACS				TRANSISTORS				DIODES																															
DELTA TECH & CO.				4021/2 95p				74194 70p				1N41A 60p																															
62 NAYLOR ROAD, LONDON, N20 0HN				4023 22p				74195 68p				TIP42A 60p																															
Tel: 01-445 8224				4024B 55p				74196 95p				TIP2955 70p																															
Prices include VAT. Add 35p P&P				4025 20p				74197 45p				TIP3055 30p																															
Minimum Access order £3				DIAC 24p				74198 120p				ZTX107/8 12p																															
SWITCHES				VOLTAGE REGULATORS				74199 80p				ZTX109 12p																															
DIL 3WAY 55p 7WAY 80p				LM3909N 75p				AC126/7 22p				ZTX300/1 14p																															
TOGGLE 3A/250V DPDT 35p				LM3909N 75p				AC128 20p				ZTX302/3 18p																															
ROTARY 2A/250V DPST 35p				MC1496P 80p				AC153 25p				ZTX304 23p																															
CERAMIC CAP (50V)				NE531 120p				AC176 22p				ZTX500/1 15p																															
33 pF to 4700 pF				NE555 26p				AC187/B 22p				ZTX504 24p																															
POLYSTYRENE CAP (50V)				NE556 45p				AC187/C 22p				ZTX507 20p																															
10 pF to 1000 pF				NE566 140p				AD149 40p				2N698 20p																															
POLYESTER CAP (100V)				SN76115N 80p				AD161/2 28p				2N706 14p																															
1 nF to 68 nF 6p; 100 nF 7p; 150 nF 8p;				SN76023N 150p				AF114 30p				2N914 20p																															
220 nF 9p; 330 nF 10p; 470 nF 11p; 680 nF 7p; 1uF 7p; 1.5 uF 7p; 2.2 uF 20p;				TBA641B 200p				AF124 35p				2N918 25p																															
3.3uF 15p; 4.7uF 15p; 15p				TBA800 75p				AF125/6 35p				2N1302/3 35p																															
ELECTROLYTIC CAP (uF/V)				TBA810S 110p				AF127 35p				2N1304 35p																															
1/25 to 47/25 6p; 68/25 7p; 100/35;				ZN414 90p				BC107/8 10p				2N1306 30p																															
150/25 8p; 160/25 5p; 200/12 6p;				ZN1034E 220p				BC109 10p				2N1308 30p																															
250/12 7p; 220/25 10p; 470/25, 500/30				DIODES				BC140 20p				2N1613 25p																															
12p; 470/40 mini 15p; 640/16 8p;				OA47 8p				BC142/3 30p				2N1711 13p																															
1000/10 10p; 1000/40 30p; 1500/25/40				OA91 7p				BC147/8 10p				2N1893 25p																															
35p; 2200/6.3 12p				OA200 5p				BC149 10p				2N2217 18p																															
ZENER DIODES (400mW)				OA202 6p				BC157/8 12p				2N2222A 23p																															
2V7 to 33V 8p				1N916 4p				BC159 12p				2N2369 17p																															
VEROBOARDS (.1" copper)				1N916 4p				BC167 14p				2N2484 25p																															
2.5" x 5"				1N4148 4p				BC171 10p				2N2484 25p																															
3.75" x 5"				1N4001/2 4p				BC173 8p				2N2484 25p																															
RESISTORS (5% E12)				1N4003 5p				BC177/8 16p				2N2484 25p																															
10 Ohms to 10Mohms				1N4004/5 6p				BC182 10p				2N2904/5 21p																															
PRESETS (.15W HORIZONTAL)				1N4006/7 8p				BC182L 8p				2N2906/7 21p																															
100 Ohms to 2 Mohms				1N5400 11p				BC184 10p				2N2926G 10p																															
POTENTIOMETERS (1/4W)				1N5401 12p				BC186 25p				2N3053 20p																															
Linear & Log Scales				1N5402 13p				BC187 15p				2N3054 30p																															
4K7 to 2M2				1N5404 14p				BC207/9 13p				2N3055 45p																															
LINEAR CIRCUITS				BRIDGE RECTIFIERS				BC212L 8p				2N3442 140p																															
709-8 28p				WO2M 18p				BC213L 8p				2N3702 10p																															
710-14 35p				WO6M 20p				BC214L 10p				2N3711 11p																															
741-8 22p				1A/50V 20p				BC238 18p				2N3772 70p																															
747-14 50p				1A/200V 23p				BC238L 18p				2N3773 250p																															
748-8 35p				1A/400V 28p				BC261B 23p				2N3819 21p																															
CA301B 70p				1A/600V 29p				BC301/3 32p				2N3820 40p																															
CA3028A 85p				2A/50V 30p				BC328 17p				2N3823 70p																															
CA3046 50p				2A/100V 32p				BC461 40p				2N3866 65p																															
CA3054N 40p				3A/100V 60p				BC477 35p				2N3903/4 15p																															
CA3080 78p				3A/600V 75p				BC478 20p				2N3906 15p																															
CA3090AQ 200p				TRISTORS				BC479 23p				2N4037 45p																															
CA3130E 95p				4A/300V 20p				BC547/8 12p				2N4058 10p																															
CA3140E 48p				4A/400V 40p				BC549 12p				2N4059 10p																															
				12A/100V 30p				BC557/8 14p				2N4060 10p																															
				8A/400V 75p				BC559 14p				2N4061 10p																															
												2N4548 40p																															
												2N4549 40p																															
												2N6027 30p																															
												3N128 50p																															
MINIMUM 25 PIECES EACH				4001B 15p				4016A 25p				7473 16p				1N4005 4.5p				ZD5V6 5p				BFY50 15p				CA3090AQ 70p				160 uF/25V 4p				W06 19p							
				4007A 13p				4017A 40p				7490 23p				1N4007 6p				ZD9V1 5p				TIP31A 22p				SN76115N 50p				640 uF/16V 4p				S01 23p							
				4011B 15p				7420 13p				1N5404 10p				BF244C 14p																											


CHROMATHEQUE 5000

5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT

ONLY

£49.50 + VAT!

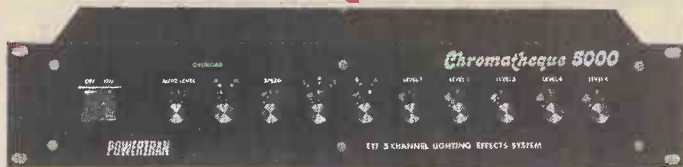

Panel size 19.0" x 3.5".

Depth 7.3"

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!


MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

COMPLETE KIT
ONLY

£49.90 + VAT!

MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!

Panel size 19" x 3.5". Depth 7.3"

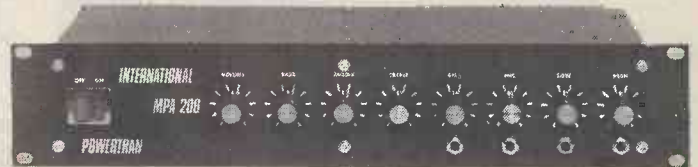

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

SP2-200 2-CHANNEL 100W AMPLIFIER



Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT

ONLY

£64.90 + VAT!


NEW!

The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new design uses two of these amplifier section powered by separate power supplies fed from a common toroidal transformer. Input sensitivity is 775mV. Even simultaneously driven, each channel delivers over 100W rms into 8 ohms. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc — complete down to the last nut and bolt!

POWERTRAN

SYNTHESIZER KITS ON PAGE 10. MORE KITS AND ORDERING INFORMATION ON INSIDE FRONT COVER.

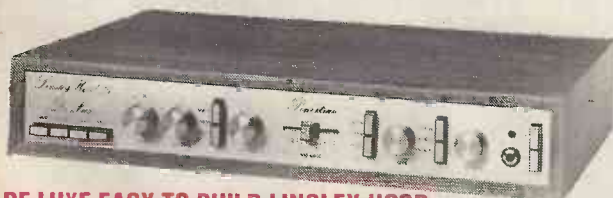
All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £85.00 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.

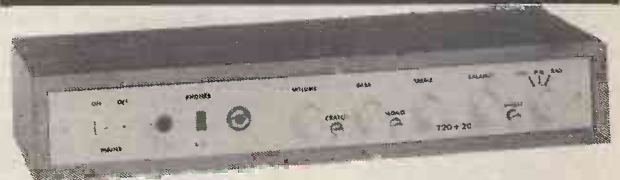Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!



T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for £38.40+VAT.

MATCHING TUNERS — See our FREE CATALOGUE!

BLACK HOLE CHORALIZER

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 +VAT (single delay line system)

De Luxe version (dual delay line system) also available for £59.80 +VAT

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



Lights-on Reminder

If you are apt to forget to switch on the car lights at the onset of darkness, this indicator lamp should prove useful. It switches on when the ambient light level drops below a preset threshold value, unless the sidelights have been switched on already. If the lamp does come on, it is automatically cancelled when the sidelights are turned on.


The circuit utilizes a CMOS 4025 IC, which is a triple three-input NOR gate. In this circuit the three inputs of each gate are connected together so that each gate actually operates as a simple inverter. IC1a and IC1b are wired in series and R2 and R3 provide positive feedback, giving a sort of Schmitt trigger action. IC1c is connected as an inverter/buffer stage at the output of the trigger circuit, and this drives indicator lamp LED1 by way of current limiting resistor R4. If the input voltage to the trigger circuit is more than about half the supply voltage

LED1 will be switched off, but it will be turned on if the input voltage falls below about half the supply potential.

The input of the trigger is fed from a potential divider circuit which consists of LDR1 and PR1. When the light level becomes inadequate, the resistance of LDR1 increases and gives an input voltage to the trigger circuit sufficiently low to cause LED1 to switch on. The point at which this occurs can be adjusted by PR1.

D1's anode connects to the junction of the side lights and the switch that controls them. Assuming the vehicle is of the usual negative earth variety, D1 will be reverse biased when the lights are switched off and will not affect the circuit. When the lights are switched on it is forward biased and the input of the trigger circuit is taken to almost the full positive supply voltage. This ensures that LED1 is switched off and the photocell is rendered ineffective.

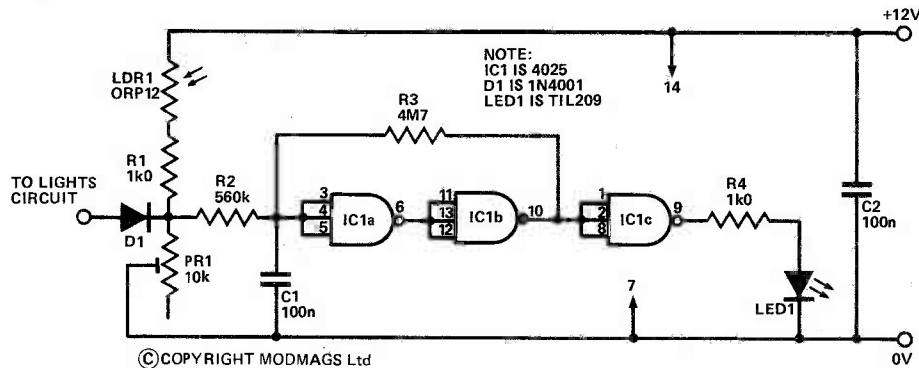The circuit can only be used with positive earth systems if D1 and the connection to the sidelights are omitted, and LED1 will not then be muted by switching on the sidelights.



Power Controller

This is a conventional diac-triac mains power controller which can handle loads of up to about 300 W or so (higher loads of up to about 1000 W can be controlled if the triac is fitted with a suitably substantial heatsink).


Circuits of this type operate by switching full power to the load for only part of each half cycle. For example, half power is obtained by switching power through the load for only the second half of each half cycle. Since the switching device (which is triac SCR2 in this circuit) is either switched fully on or off it dissipates little power, and good efficiency is obtained.

Full power is obtained with RV1 at minimum resistance, as the voltage on C1 is then virtually equal to the mains voltage. Thus the voltage on C1 reaches the trigger potential of diac SCR1 early in each mains half cycle, causing SCR1 to fire and switch on the triac for the major part of each half cycle. The triac switches itself off at the end of each half cycle when the current flowing through it falls to zero, so that it is ready to start afresh at the beginning of each new half cycle.

As RV1 is adjusted for increased resistance, the voltage on C1 lags further behind the mains voltage so the triac is not triggered until later in each half cycle, giving reduced output power. The triac will fail to trigger at all with RV1 set towards maximum resistance, giving zero output power.

Due to its fast switching time the circuit inevitably generates strong radio frequency signals, and L1, C2 and R2 are included to largely suppress these signals and prevent the unit from radiating RFI. Make sure that L1 has a sufficiently high current rating for the load in use.

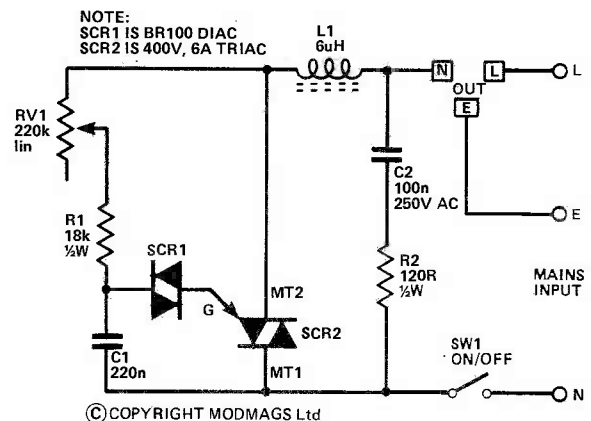In the interest of safety the unit should either be housed in an earthed metal case, or a plastic case should be used (with any exposed metalwork being earthed). RV1 should be a type having a plastic spindle and it should be fitted with a plastic control knob. Do not touch any of the wiring while the unit is plugged into the mains supply.



ETIPRINTS

ETIPRINTS offer you the easy way to produce high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

PARTS LIST

040A	ETI 80 VCO/VCLFO	Feb 80	Speed Control	
040B	ETI 80 PSU Tuning Fork Hi-Lo Filter Coin Toss	Feb 80	DTM Switching Board	
041A	Audiophile Driver Amp VCA Signal Tracer Heater Controller Main Board Electromyogram	Mar 80	RIAA Preamp	
041B	ETI 80 VCM Heater Controller Sensor	Mar 80	047C	ETI 80 Envelope Shaper TV Sound Survival
046A	ETI 80 Dual VCA 100 W Power Amplifier	Aug 80	048A	Sustain/Fuzz Box Flash Trigger FM Radio Control Receiver: (Top side) (Bottom side) FM Radio Control Transmitter
046B	Capacitance Meter US Alarm BGM 100 W Amplifier Logic Tester 100 W Power Amp	Aug 80	048B	Vocoder Slew Rate Control Vocoder Output Amp Vocoder Input Amp Vocoder PSU Vocoder LED PPM Display
047A	Digital Test Meter	Sep 80	048C	Cassette Interface ETI 80 Monitor Amp
047B	Vocoder Internal Excitation	Sep 80	049	AF Generator Multi-Option Board Space Invasion PSU

BUYLINES

Sheets for Sep 79, Dec 79, Jan 80 and April - July 80 are temporarily out of stock. Earlier ETIPRINT sheets are available.

Send a cheque for PO (payable to ETI) for £1.20 per sheet with details of the project for which you require an ETIPRINT, and the month and year of publication to:

ETIPRINTS,
ETI,
145 Charing Cross Road,
London WC2H 0EE.

HOW IT WORKS

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ETIPRINTS



Sticky Solution

From Devcon come two types of epoxy adhesives in handy 9 oz bottle twin packs. A really useful aid for DIY and modelling, there is a choice of '5 Minute' or 'Slow Cure' adhesives. The five minutes type, as its name suggests, cures in 4 to 7 minutes and provides superfast bonding even with thin films and at low temperatures. It is clear, non-shrinking and has good chemical resistance, though is not suitable for long term immersion in water. The 'Slow Cure' epoxy is a tough adhesive setting in about 30 minutes, has a long working life and can be drilled, sanded or machined. For more information, Devcon is a division of ITW Ltd at Station Road, Theale, Reading, Berks, RG7 4AB.

Testing, testing...

If you're still using neon screwdrivers and moving coil voltmeters, get with it and take a look at the two new additions to the Steinel range of voltage testers. The Mono Check is a single pole phase tester with great improvements over the conventional electrician's screwdriver. The internal resistance of the instrument is 10M and the current through the human body is reduced to a fraction of that required by neon testers. Under extreme conditions of insulation (for example, you're standing on a wooden ladder on an insulated floor) the tester will maintain as bright an indication as if it were directly earthed. The test range is 80-250 V AC relative to earth and the Mono Check remains safe at overloads six times this range. There is a function test switch located in the handle to confirm correct operation. The recommended retail price of the Mono Check is £3.80 plus VAT.

The Steinel range of two-pole voltage testers have a unique design; each instrument consists of two probe tips connected by a lead, with a solid state readout (LEDs or neons in the existing testers) built into one of the probes. This makes the testers inexpensive, reliable and practically unbreakable. The instruments are

NEWS NEWS NEWS NEWS NEWS NEWS

Home, Home on the...

The Design Council is currently exhibiting a range of products representing in all its glory the microelectronics revolution which now affects all our lives. The exhibition shows some 40 British-made microelectronics products which are available now or will be in the near future. These products are meant to

make life easier — improving efficiency or simply for amusement. The exhibition is divided into different areas of the home, for example the kitchen includes the 'Sensamatic' tumble dryer and the Satchwell Suvic 'HC1201' central heating controller. The playroom section is filled with electronics games and kits, like Rowtron's Home Entertainment Centre which is a microcomputer-based television games system. In the living-room there is a highly


sophisticated Chess Computer. In the sports and hobbies categories there is Paterson's digital thermometer and time signal for developing photographs, a car computer from Smith's Industries and at the 'front door' is a Yale Diplomat burglar alarm system. There are plenty more things to see at the Microelectronics Come Home exhibition which will be at the Scottish Design Centre from 30th March to 30th May.

DIY Sound

A new company called DIY Hi-Fi has just launched 'Cecilia', a pair of low cost DIY loudspeakers. They are of the bookshelf variety utilising the Pioneer TS 107 drive unit which was originally developed for in-car hi-fi systems. The speakers will cost around £35 to build and one of the contributing factors to this low cost is that there are no electrical components, such as crossovers etc, except for the drive units themselves which incorporate a strontium magnet and a compact dual cone giving a full extended frequency of 50-20,000 Hz! The finished speakers are extremely efficient, producing 91.5 db at 1 W/metre, power handling is 20 W maximum with a nominal impedance of 4 R which can be converted to 8 or 16 R. The finished size is 17" x 9" x 8½" deep. DIY Hi-Fi reckon you can easily build them in a weekend and they provide complete step-by-step, easy-to-follow instruction guides and full size blueprint plans for just £2.50 including postage and packing. DIY Hi-Fi, York House, Swan Street, West Malling, Kent.

Lights Out

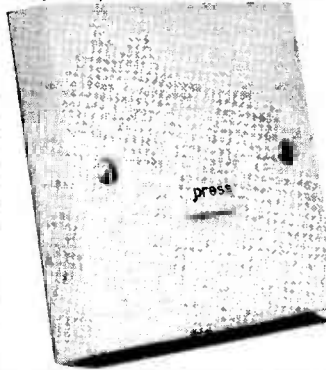MK Electric have recently brought out a new logic time delay switch. It is an ideal way to provide lighting economically in buildings where stairways, landings and corridors only need intermittent lighting. At the heart of the device is an oscillator with a variable pulse frequency. When the built-in




counter has recorded a set number of pulses, the switch is turned off. For a short delay period, the oscillator frequency is increased, resulting in a shorter counting period. The delay adjustment screw is on the back of the switch which is set during installation for a time delay of between two and 15 minutes. It cannot be altered once set. The triac is protected by a fuse located at the front of the switch, but this can be locked to prevent unauthorised removal. The Logic Time Delay Switch can be installed for one-way, two-way or multi-way operation, with the delay switch as the master unit and standard logic press switches or architrave switches as extension units. There is also an override facility provided, useful when maintenance work or routine cleaning is carried out. A built-in neon indicator glows through the face-plate for easy location. The switch has a 400 W rating, for tungsten lighting only. For further details contact MK Electric Ltd, Shrubbery Road, Edmonton, London N9 0PB.

Is It A Bird? Is It A Plane?

Not entirely unexpected after the Sony Stowaway's runaway success (along with the offerings of its many competitors), comes the first of a new breed of 'music on the move' ideas. It is a miniature stereo cassette/radio from Panasonic — the RX 2700. It is a pocket-sized unit which includes a compact FM/AM radio and cassette recorder producing 550 mW power output. It has a built-in speaker as well as stereo

headphones and is able to record from its own radio in either stereo or mono, or can record in mono from its built-in microphone — useful for dictation. Among its other features are LED indicators, two-step tone control, one-touch recording, auto-stop, pause control and variable sound monitor. For the mere sum of £133.50 you too can have this versatile little device along with a carrying case and hip/shoulder strap. It is available now from Panasonic dealers. This is not likely to be the last of the miniature stereo devices we are likely to see,

so keep watching these pages!

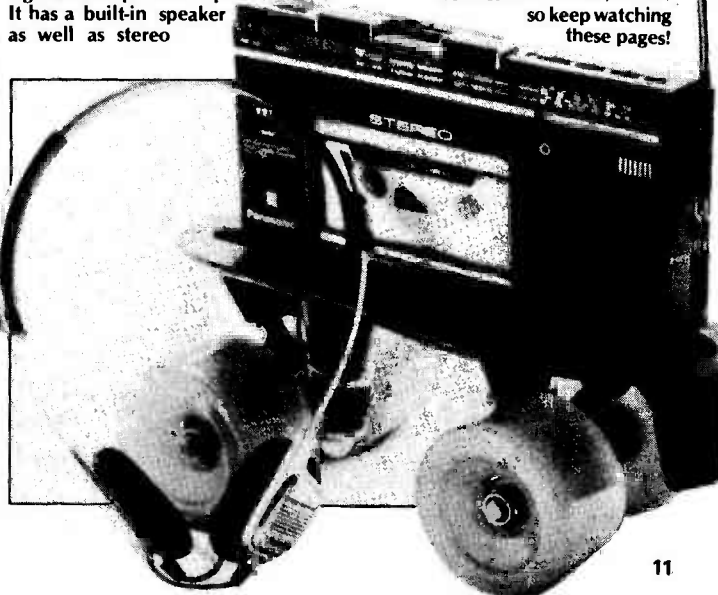

CLASSIFIEDS

ETI RATES

1-3 Insertions £7.00 per scc
 4-11 Insertions £6.50 per scc
 12+ Insertions £6.00 per scc
 24p per word (min 15 words)
 Box No. £1.50

Closing date 1st Friday in month preceding publication.

HE RATES

1-3 Insertions £5.00 per scc
 4-11 Insertions £4.50 per scc
 12+ Insertions £4.00 per scc
 18p per word (min 15 words)
 Box No. £1.50

Closing date 2nd Friday in month preceding publication.

Classified Advertisements must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No

- 100 ALARM TRIGGER MODULE. 100% Solid State. Battery operation. Pos. & Neg. Rings. N/C for 4 wire contacts. N/O for Mats, etc. One Amp Switching Capacity. Only **£9.95**
- 210 Quality White Flush fitting 4-wire **MAGNETIC REED CONTACT** + matching magnet **£1.10**
- 220 Surface 4-wire **MAGNETIC REED CONTACT** **£1.50**
- 240 **PRESSURE MAT**. Standard size 4-wire 30"x15" **£2.20**
- 250 **PRESSURE MAT**. Stair size 4-wire 7"x6 1/2" **£1.73**
- 388 **NEW PASSIVE MULTI-BEAM**. Infra-red Detector. 8 metre range **£85.00**
- 390 **SIX INCH UNDER DOME BELL** **£9.95**
- 390 **BEST QUALITY BELL HOUSING**. PVC coated metal, not to be confused with the cheaper decoy covers. Fully signwritten with our Centurion insignia **£9.50**
- 400 **DECOY P.V.C. BELL COVER** **£6.60**
- NEW TWO-TONE U.S.A. POLICE SOUNDERS**, complete with weatherproof horn **£14.50**
- SOUNDER PCB Module**, only **£4.95**
- WEATHERPROOF** Loudspeaker, 8 ohm horn, only **£9.55**

Note: All equipment operates on 12 Volts DC.

Terms: Add 15% VAT to Prices + 60p Postage & Packing.



No Minimum Order.
 Access telephone orders welcome on: **0484-35527** or send S.A.E. for Full List to:
CENTURION ALARMS & ELECTRONIC SALES, Dept. ET1, 285 Wakefield Road, Huddersfield, W. Yorks HD6 9BE.

MK 14 KITS. Keyboard £11.80. 1/2in display £12.80. 4K memory board, fitted 1K £19.82. Ditto fitted 4K £39.47. 16 bit LED board £10.41. Mother board £8.53. Cassette interface £7.52. 5v, 1.5A power supply, less transformer £7.55. Super VDU interface £35.60. New monitor £14.95. VDU monitor PROM (5v) £14.95. PICO-2 Basic PROM (5v) £14.95. Also connectors, printer, Z80 conversion, etc. Second-hand Mk 14 £37. Postage 80p. Plus 15% VAT. Catalogue 90p postage 25p. Full price list send SAE. Redditch Electronics, 21 Ferney Hill Avenue, Redditch, Worcestershire B97 4RU. Tel: (0527) 61240 evenings.

PRE-WAR ONWARD VALVES, wireless (S.W.s included). S.A.E. 100 transistors £5. Bargains list 15p. — Sole Electronics, ET1, 37 Stanley Street, Ormskirk, Lancs.

WANTED

Test equipment, valves, tubes and scrap electronics.

Reasonable prices paid. Distance no object (UK mainland only).

FRG General Supplies
 Unit 3, Longhill Industrial Estate
 March, Cambridgeshire
 PT15 8NQ

Tel: March (03542) 56614
 or 01-404 5011
 Telex: 24224 Quote Ref. 3165

CIRCUIT DESIGN, Prototype construction: Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write **A. J. ATTWOOD**, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 6336.

CITIZEN BAND RADIO and accessories. — Phone 0527 43169 or s.a.e. with enquiries to P.O. Box 13, Redditch B98 8NS.

100 IN4148 £1, 150 Resistors £1, 100 Capacitors £1. P&P 25p. S.A.E. lists. Dept. T, D.B. Products, P.O. Box 8, York YO1 1FT.

ZX80, ATOM, MK 14 wanted. Tel. Redditch Electronics (0527) 61240 evenings.

CB SPARES

Japanese original transistors and integrated circuits.

Largest selection in Britain at very low prices.

Write or phone for free list.

McLaughlin Electronics
 44 Carlisle Road
 Londonderry
 N. Ireland BT48 6JW

Tel: (0504) 65002

SPEED — VERSATILITY — ECONOMY



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers, to carry out work on: — *P.C.B. REPAIRS *ANALOGUE BREADBOARDING *SIMPLE LOGIC WIRING *COMPLEX INTERCONNECTING OF MICROS AND MEMORIES.

EURO INTROKIT £16.70. PROJECT KIT £8.18. MINIKIT (A) £7. PENCIL WITH LOADED USE BOBBIN £2.81 WITH T.C.W. BOBBIN £2.76. STRIPS: GLUE FIX 20/PKT. 6" LONG £3.20. HIGH DENSITY GLUEFIX 20/PKT. 6" LONG £3.20. PRESS FIX 20/PKT. £3.20. SINGLE HIGH DENSITY D-SIDED EUROCARD £5.18. SINGLE SIDED £3.80. DOUBLE HIGH DENSITY D-SIDED EUROCARD £8.60. PROJECT CARD £2.50. BOBBINS. BLUE 4/PKT. £2.12. GREEN 4/PKT. £2.12. GOLD 4/PKT. £2.12. PINK 4/PKT. £2.12. 1 OF EACH COLOUR £2.20. TINNED COPPER 2/PKT. £0.96. ADHESIVE £0.41. SOLDERING IRON 420° C £5.52. REPLACEMENT WELLER TIPS — PTA48 430 C £1.40. PTA49 480 C £1.40.


Please add 40p for P&P + VAT to all orders

FOR FURTHER INFORMATION ON ROADRUNNER PRODUCTS SEND

LARGE S.A.E. TO:

T. J. BRINE ASSOCIATES
 FREEPOST, Haslemere, Surrey GU27 3BL

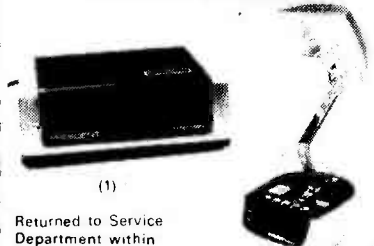BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period

1. With alarm repeat. S.R.S.P. of £17.00. Offered at **£3.95**, inc. VAT, or 3 for **£9.95**, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00. Offered at **£7.95** inc. VAT each, or 3 for **£19.95** inc. VAT.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

U.K. only
 Discounts available on large bulk purchase.

PRESCOTT CLOCK & WATCH CO. LTD.
 PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

T. & J. ELECTRONICS COMPONENTS — Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

BURGLAR ALARM Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

TELEPHONE ANSWERING MACHINES, Super Phones, Radio Phones, etc. Ring C.W.A.S. 0274 682674.

PARAPHYSICS JOURNAL. Russian / Czech translations. Autogenics (self-training) improves vitality. Psychotronic Generators, UFOs, contacting extraterrestrials, Kirlianography, telekinesis, levitation, gravity lasers. S.A.E. 4x9": Paralab, Downton, Wilts.

TELEPHONE ANSWERING MACHINE. Build your own for under £10 plus any cassette recorder. Send £3 for circuit and plans. S. D. Cross, 24 Thorney Road, Streetly, Sutton Coldfield, West Midlands.

MEMORY MADNESS

4116-200ns £2.13, 16K E15.92, 32K E29.92, 48K E41.76, 64K E50.56
 2114-300ns 1-24 E2, 24-100 E1.96
 2708 1-4 E3.65, 5-9 E3.50
 2716 1-2 E4.22, 3-9 E4, 10-24 E3.76
MICROPROCESSORS 8080, 6800, 280 & peripherals.
 Data & application info available. SAE for parts & price lists.
 Prices inc. VAT P/P only 20p per order

TIES DEVELOPMENTS & SERVICES
 57 Westmead, Woking, Surrey GU21 3BS
 Tel: Woking (04882) 20435

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories.

Selected range of popular components Full range of HE printed circuit boards normally ex-stock. same day despatch at competitive prices.
P.C. Boards to individual designs Resist-coated epoxy glass laminate for the diy man with full processing instructions (no unusual chemicals required)

Full range of etch resist transfers and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MADONS ROAD
STRATFORD-ON-AVON
WARWICKS, Td. 4878

ZX80 'LIVE ACTION' SOFTWARE. Top quality games at unbeatable prices: BREAKOUT (1K) £4; SPACE INTRUDERS (2K) £4. Also MOVIES (2K plus), 7x8 character pictures displayed in rapid rotation giving animation effect £3 — No hardware modification whatsoever. Written in machine code without loss of T.V. synchronisation. SOUNDS INCREDIBLE? — YES, but it's true. Reviews say the ZX80 can't be used for continuous live action ARCADE type games — WELL IT CAN — WE'VE DONE IT — SEEING IS BELIEVING — Send cheques or P.O.'s for program listing (or S.A.E. for list of all software) to: MACRONICS (K. Macdonald), 26 Spiers Close, Knowle, Solihull, B93 9ES.

COPPER CLAD BOARD DOUBLE-SIDED FIBRE GLASS: — 1,000 sq inches of assorted sizes £6, 800 sq inches of assorted sizes £5, 600 sq inches of assorted sizes £4 and 400 sq inches of assorted sizes £3. Will cut to size if required, maximum size 12in x 12in. Postage free. Also complete P.C.B. service. H.C.R. (Chelmsford), 1 Bankside, off New Street, Chelmsford.

TRS-80 or ZX80. 4 games on cassette. TRS-80, £3.50; ZX80, £3. S.A.E. Details/ list. — Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

WANTED. Electronic components and test equipment. Good prices given. Q Services, 29 Lawford Crescent, Yatley (0252) 871048, Camberley, Surrey.

BUILDING AUDIO EQUIPMENT?

You need the ATEK catalogue. Lists 100s of components/accessories. 100w modules; £9.95. 120w Mos-Fet modules; £14.95. Also POWERTEK speakers, 50w from £10.95, heatsinks, connectors, knobs, switches, wire, hardware, cabinet materials, etc., PLUS LOTS MORE. Catalogue 70p post free, includes discount offers. Mail order only. ATEK (ETI 1), 8 Parsons Close, Church Crookham, Aldershot, Hants GU13 0HL. Tel: 02514 22303.

SUPERBOARD II

STILL the best value in Home Computers Just compare the features:

- ★ 8K floating point BASIC in ROM
- ★ Full ASC11 keyboard
- ★ Standard cassette/TV interface
- ★ RS232 printer interface
- ★ 4K user RAM
- ★ Expandable to 32K & dual mini floppy.

AVAILABLE NOW from:
C.T.S.
31/33 Church Street
Littleborough
Lancs.

Please ring or write for latest prices
Tel: Littleborough (0706) 74342 any time

PLEASE SEND FOR OUR MAIL ORDER CATALOGUE

CROPTON ELECTRONICS LIMITED
35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD · Tel: 01-891 1923

VIDEO MUSIC



The amazing Videograph, as featured recently in Electronics Today International, links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically-minded, a square-wave signal generator is built-in, permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

DIY KIT ONLY £33.95
Case & Controls £15.95
or READY BUILT £69.95

All prices include VAT and postage

WILLIAM STUART SYSTEMS Ltd

Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD
Telephone, Brentwood (0277) 810244

2114s - 200ns — Brand-new batch for disposal, £2.25 each inclusive. Please add 60p P&P. R. Downs, 12a Ashgrove Road, Ashford, Middlesex.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

SHARP MZ-80K

and PC1211 Computers at **LOWEST PRICES!!**
With lots of **FREE PROGRAMS**
KING PIN COMPUTERS
PO Box 40, Stevenage, Herts.
SGA ZNF
Tel. Stev. (0438) 59677, up to 9 p.m.

SN76477 sound generator plus data	160p
XR2206 tone decoder plus data	270p
MM57160 STAC timer	500p
ZN425E 0 to A converter	380p
NE555 timer	18p
2708 450ns EPROM	300p
TBA800 5W audio amplifier	70p
NE567 tone decoder	100p
LM13600 dual transconductance amp.	120p
LM387 low noise preamp plus data	130p
LM386 power amplifier	80p
LM377 dual 2w. amplifier	150p
LF351 operational amplifier	40p
LF353 dual LF351	80p
TOA1022 delay line	500p
7805 or 7812 TO220 regulator	50p
7905 or 7912 TO220 regulator	60p
Metal film 1/4w. 1% resistors 51Ω to 300K. E24 series	4p
Siemens polyester capacitors 0.01, 0.022, 0.047, 0.1	9p
Pack 50 each 6BA nuts, washers, 1/2" screws	50p
Pack 50 each 4BA nuts, washers, 1/2" screws	70p
Connecting cable single strand, 1 metre of eight different colours, total 8 metres	30p
As above but 5 metres each colour, total 40m	140p
Light duty stranded 10/0.1mm, 8 colours	4p metre
Extra flex 55/0.1, red or black	12p metre
Twin cable, speaker type	10p metre
Single screened cable	18p metre
Twin individually screened	20p metre
Min. 3-core mains cable, 2.5A	22p metre

All prices exclude V.A.T. Please add 40p carriage. All brand new components.

J. NELSON 203 HIGH STREET LONDON, S.E.13

REAL TIME CONTROL

ARE DISPOSING OF EXCESS STOCK AS FOLLOWS:

TTL 74LS			ICs				
74LS00	12	74LS125	40	74LS390	100	IM6402(uart)	300
74LS02	12	74LS138	60	74LS393	100	Mostek 34073	500
74LS03	12	74LS139	60			Mostek 3890(280)	500
74LS04	12	74LS146	70			Mostek 4927	150
74LS05	14	74LS153	130	TTL 74		N8X01(CRC)	600
74LS08	18	74LS157	50			82S126(ROM)	160
74LS10	16	74LS161	60	7400	10	2101AL4(RAM)	180
74LS20	16	74LS164	70	7442	50		
74LS27	24	74LS173	80	7447	60	TRANSISTORS	
74LS37	24	74LS174	80	74259	180	T1P 30A	40
74LS38	28	74LS175	80			T1P 120	70
74LS42	60	74LS195	100			T1P 122	70
74LS47	60	74LS221	100			2N3906	14
74LS74	28	74LS260	40				
74LS75	34	74LS367	50			IC SOCKETS	
74LS92	70	74LS368	80	74S112	80	14 PIN	10
74LS112	36	74LS373	120	74S189	140	16 PIN	11
				74S387	150		

POWER SUPPLIES
Coutant 12 volt/9amp
Over. volt prot for above
Coutant 5 volt/1.2amp

7000
1000
4000

D' CONNECTORS
Plugs
Sockets
Cover

15 way
110
160
140

MEKTRON BUS STRIP
822-3-10-7
822-4-10-7

75
80

TERMS OF BUSINESS: CASH/CHEQUE/PO WITH ORDER. ADD 40p POST & PACKING. ADD 15% VAT. CHEQUES PAYABLE TO REAL TIME CONTROL LTD.

REAL TIME CONTROL LTD
KEBBELL HOUSE
CARPENDERS PARK
WATFORD, HERTS. Tel: 01-428 0088

C.B.S.

If you are in Business and considering an application of a Minicomputer or Microprocessor based System and are a little confused why not attend one of our courses.

- A. Microcomputer Application — BUSINESS
- B. Microcomputer Application — ENGINEERING AND CONTROL
- C. Programming in BASIC — INTRODUCTION
- D. Programming in BASIC — ADVANCED

We are an independent consultative organisation specialising in business and engineering application, prepared to recommend systems when required and provide full software and programming support.

*Courses are available for individual or group instruction, and may be arranged to suit your specific applications.

For full details and dates available write or phone:

CLEVELAND BUSINESS SERVICES

Cleveland House
Routh, Near Beverley
North Humberside. HU17 9SR
Tel: Leven 0401-43139

A superb value stereo power amplified offer for Easter: ● Stabilised psu; 2N 3055 output ● Stereo 60 watt rms; ● IC preamp, case includes controls volume, selector, etc., din output/inputs for magnetic pick-up/microphone (3 mv) + tuner + tape/aux. 26 transistors — 2 ic screened Douglas transformer, 240 V AC mains lead.

New-tested-data £19.95 (inclusive). Kliffco Electronics, 1 Regent Road, Ilkley, W. Yorkshire LS29 9EA.

BARGAIN OFFER

Massive clearout of electronic components. Ideal for home constructors, experimenters and beginners

2lb Box£2.00 plus £1.50 P&P
10lb Box£10.00 plus £2.50 P&P
Prices include VAT. Money back if not satisfied on goods returned within 14 days.

Send your order to:

HARRISON BROS
PO Box 55
Westcliff-on-Sea
Essex S50 7LQ



C
A
M
E
R
A

C
O
M
P
L
E
T
E

£126.50 + P&P £3.45
(inc VAT)
Total £129.95

BEST OFFER EVER
Camera Kit, Lens,
Vidicon & Modulator

CROFTON

Tel: 01-891 1923 For full details

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (ET24)
11 Percy Avenue, Ashford, Middx. TW15 2PB

COLOUR MODULATOR

- R G B inputs, PAL/UFH output
- Unlimited colour combinations
- TTL etc interface details supplied
- 1000's already in use!



KIT: only £12 Built & Tested: only £18

— please add VAT at 15% to all prices
— Barclay/Access orders accepted by telephone

WILLIAM STUART SYSTEMS Ltd

Dower House, Bitterley Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

TIME WRONG?

MSF CLOCK IS ALWAYS CORRECT — never gains or loses. SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, can expand to Years, Months and Milliseconds, also parallel BCD output for computer, etc, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, ABSOLUTE TIME. £54.80.

V.L.F. EXPLORE 10-150KHz, Receiver £13.70.

60KHz RUGBY RECEIVER, as in MSF Clock, serial data output, built-in antenna, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage, etc., money back assurance, so GET yours NOW.

CAMBRIDGE KITS

45 (TS) Old School Lane, Milton, Cambridge

MAIL ORDER PROTECTION SCHEME

If you order goods from mail order advertisers in this magazine and pay by post in advance of delivery, this publication *Electronics Today International* will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication *Electronics Today International* explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for any one advertiser so affected and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures has not been complied with, at the discretion of this publication *Electronics Today International*, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc. received as a result of answering such advertisements). Classified advertisements are excluded.

COMPUTER SALE: — Ex-computer memory boards. 16K x 8. Uses 4K dynamic RAMs. Superb boards easily interfaced to your Micro. Circuit diagrams and Nascom interface plans included. Now only £15. Same board, slightly modified with 16K Bytes of 16K dynamic RAMs — £30 or 32K Bytes — £42. Carriage/insurance all orders £1. S.A.E. for details. Payment with order to: J. Wright, 27 Broomhill Drive, Glasgow G11 7AB.

ZX80 £75. Mk 14 £37. **ATOM £115** occasionally available second-hand. Tel: Redditch Electronics (0527) 61240 evenings.

EDUCATION

Inner London Education Authority
LONDON COLLEGE OF FURNITURE
41-71 COMMERCIAL ROAD
LONDON E1 1LA

Department of Musical Instrument Technology

COURSES IN ELECTRONICS FOR THE MUSIC INDUSTRY

Tec Diploma in Musical Instrument Studies
(2-year full time specializing in electronics)

TEC HIGHER DIPLOMA IN MUSICAL INSTRUMENT TECHNOLOGY
(2-year full time specializing in electronics)

The electronics options of these TEC courses allow the student to specialize in music industry application. Suitable students would be interested in both music and electronics and wish to combine them within this course. Application forms and further details are obtainable from the Senior Administrative Officer at the College.

2708 EPROM PROGRAMMING
 ★ from Hex listing 50p + 1/2p per byte
 ★ from Master 2708 85p each
 ★ for erasing 50p each
 ★ for printout in Hex 50p each
 ★ for supplying 2708 £4.50 each
 Prices include postage, etc.
 M. Willard, Unit 5, Block 1, Woolwich
 Dockyard Ind. Est., London SE18

ADAM HALL
 Cabinet & Flightcase Fittings, fretcloths, coverings
 handles, castors etc. Jacks & sockets. Cannons
 Bulgins, reverb trays, Emular compression drivers, AKG
 mixS, Celestion speakers, ASS glasshire horns
 Send 30p postal order for illustrated catalogue to
ADAM HALL (E T SUPPLIES)
 Unit 8, Charlton Court
 Grainger Road, Southend-on-Sea
 Essex SS2 5BZ

CIRCOLEC
**THE COMPLETE ELECTRONIC
 MANUFACTURING SERVICE**
 We can undertake all electronic manufacturing
 activities including circuit design and
 artwork preparation, component purchas-
 ing, prototypes, production runs (any quan-
 tity), Q.C. activities including mod consul-
 tancy work, test/repair activities.
 Quality work delivered on time at a reason-
 able price is our aim.
 Ring for details of our Free assembly offer!
 Tel: 01-767 1233 or write to:
Freepost (no postage required) SW17 8BR
 and Diner's Club welcome



£1 BARGAIN PACKS
 All packs £1 each; any 12 for £10. Post 25p. All top grade new
 components - no rubbish.
 PC17 20 PBC108
 PC19 50 02 discs
 PC19 25 50V neons
 PC20 60 0R47 34WR's
 PC21 7 4001B
 PC22 7 4011B
 PC23 3 4013AF
 PC24 3 4017A
 PC25 8 4025A
 PC26 2 4029A
 PC27 2 4511B
 PC28 12 8DIL skts
 PC29 11 14DIL skts
 PC30 10 16DIL skts
 PC31 10 7400
 PC32 7 74C00
 Send SAE for 8 page list/enquiries. Mail only PC ELECTRON-
 ICS 1, Thornhill, Romsey Road, Whitparish, Salisbury SP5
 2SD

**GUITAR/PA
 MUSIC AMPLIFIERS**
 100 watt superb treble/bass overdrive, 12 months guarantee.
 Unbeatable at £49; 60 watt £42; 200 watt £68; 100 watt twin
 channel sep. treble/bass per channel £82; 60 watt £52; 200
 watt £78; 100 watt four channel sep. treble/bass per channel
 £75; 200 watt £98; slaves 100 watt £34; 200 watt £58; fuzz
 boxes, great sound £12; bass fuzz £12.90; overdriver fuzz with
 treble and bass boosters £22; 100 watt combo superb sound
 overdrive, sturdy construction, castors, unbeatable £38; twin
 channel £110; bass combo £112; speakers 15in. 100 watt £38;
 12in. 100 watt £24; 60 watt £18; microphone Shure Unidyn B
 £25; 3-Channel sound/light £28.
 Send cheque or P.O. to:
WILLIAMSON AMPLIFICATION
 62 Thorncliffe Avenue, Duffield, Cheshire
 Tel: 061-308 2064

THE SCIENTIFIC WIRE COMPANY
 PO Box 30, London E.4.

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE
 14 to 30 6.50 3.75 2.20 1.40

TINNED COPPER WIRE,
 14 to 30 3.85 2.36 1.34 0.90

Prices include P&P and VAT
 Orders under £2 please add 20p.
 SAE for List of Copper and Resistance
 Wires. Dealer enquiries welcome

IMPROVE YOUR CIRCUITS
LM334Z 3-LEAD CURRENT SOURCE
 1uA to 10 mA set by resistor, 1 to 30 volt drop. Use
 for Linear ramps, Dynamic loads, High gain Low
 voltage amplifiers, Linear temperature sensing,
 95p Data, circuits 40p.
ZN404
 Precision 2.45 Volt Bandgap Reference for Cal-
 ibrators, Power Supplies, DVMs, DACs, Signal
 Clamps. 80p Data, circuits 20p. Mail Order Only.
 VAT included. Postage 30p. PO/cheque to:
Silicon Cellar
 17 Gurney Court Rd
 St Albans
 Herts

If it's a case of making your project
 look good, then use one of ours.
 Simply send a S.A.E. for
 Details and prices.

**TRADE ENQUIRIES
 INVITED.**

H. M. ELECTRONICS
 271a/275a Fulwood Road.
 -Broomhill
 Sheffield S10 3BD

POCKET COMPUTERS
SHARP AT LAST - THE PRINTER FOR PC1211
 CE-122 Printer/Cassette interface £79.45
 PC1211 with CE-122 printer £172.00
 PC1211 with CE-121 cassette interface £105.95
 PC-1211 only £92.15
FREE PAPERMATE PEN WITH ALL ORDERS
 All prices include (15% VAT) and UK Delivery
ELKAN ELECTRONICS
 28 Bury New Road
 Prestwich, Manchester M25 8LD

BREAKER, BREAK
 Build your own CB rig (27 mhz transceiver), full
 circuit diagram and parts list. All components avail-
 able in UK. Send large S.a.e. and £2.95 to P. Sher-
 wood, 84 Aylestone Walk, Manchester M10 9NU.
 I'm Down and On the Side.

**ADVERT
 INDEX**

Aitek Instruments	92
Ambit International	22 & 23
Audio Electronics	16 & 102
Audio Video Services	75
Aura Sounds	69
Baydis	29
Bi-Pak Semiconductors	92
BK Electronics	33 & 102
B.N.R.S.	50
Boss Industrial	34
Butterworths	47 & 87
Calculator Sales & Service	104
Cambridge Learning	64
CCAT	21
Chiffmead	44
Chordgate Ltd	104
Chromasonics	82 & 83
Chromatronics	58
Circolec	102
Clef Products	78
Comp. Comp. Comp	114 & 115
Crimson Elektrik	81
Crofton Electronics	58
Delta Tech & Co	106
Display Electronics	48 & 78
Doram Electronics	60
E.D.A.	34
Electronize Design	103
Electro Supplies	104
Electrovalue	28
Greenbank	70
Greenweld	50
G.S.C.	57
Happy Memories	98
Henry's Radio	23, 58 & 78
ILP Electronics	27, 42 & 43
Imp Electronics	21
LB Electronics	98
L&B Electronics	92
Linsac	28
Macro Marketing	75
Manor Supplies	102
Maplin	116
Marshalls	8
Micro Circuits	76
Micro Times	105
Midwich Computers	28
Mitrad	63
NIC Models	22
Parndon Electronics	58
T. Powell	75
Powertran	2, 10 & 107
Prentice-Hall	75
Rapid Electronics	58
J. W. Rimmer	103
R.T.V.C.	93
Safgan Electronics	22
Saxon Entertainments	103
Science of Cambridge	4 & 5
Silica Shop	35
Swanley Electronics	50
Tangerine	88 & 89
Technomatic	12
Teleradio	98
Tempus	97
Timedata	98
TK Electronics	99
Transam	14
Vero	83
Watford Electronics	6 & 7
Wilmslow Audio	23

ELECTRIFY YOUR SALES! • CLASSIFIED ADVERTISEMENT

1	2	3
4	5	6
7	8	9
10	11	12
13	14	15

Advertise nationally in Electronics Today International/Hobby
 Electronics. Simply print your advertisement in the coupon
 here (left), indicating which magazine you require.
 Or telephone for more information.

Name

Address

.....

Tel. No. (Day)

Send, together with your cheque to:
Jenny Naraine, ETI/HE,
145 Charing Cross Rd., London WC2H 0EE.
Tel: 01-437 1002 Ext. 50.

Please place my advert in: **Electronics Today International**
 (Delete as applicable) **Hobby Electronics**

JUST COMPARE OUR CASH AND CARRY PRICES!

NEW REDUCED PRICES

8K **£399**
 16K **£499** } VAT
 32K **£599**
 RRP £795 for 32K




The PEDIGREE PETS Very popular for home & business use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard. All with green screen
 Cassette Deck **£55** extra Full range of software available
 Interface PET IEEE — Centronics Parallel
 Decoded **£77.00** + VAT

EXTENDED WARRANTY BY COMPUTARE
 We give a full one year's warranty on all our products.

SPECIAL SCOOP GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only **£299** + VAT

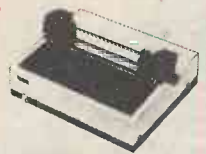

Interface Cards for Apple, Pet, TRS80, Nascom and Komputik — **£49** + VAT

Full Pet Graphics including cables. Ready to go. **EX-STOCK.**

NASCOM 2 DISC DRIVES

Add a powerful, double density, mini floppy disc to your Nascom system.
 ● Disc Controller Card (includes Nasbus 6 S100 interface)
 ● Will control 4 Drives.
 ● CPM operating system.
 ● Extended Disc Basic Compiler.
 ● Power supply included



One Disc System — **£499** + VAT
 Additional Disc Unit — **£299** + VAT

NASCOM 2 GAMES TAPE


featuring Space Invaders and Android Nim, Re-numbering program and other goodies!
£7.50 + VAT

NEC SPINWRITER

only **£1490** + VAT



NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel, giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds. 55 characters per second bidirectional printing — with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.

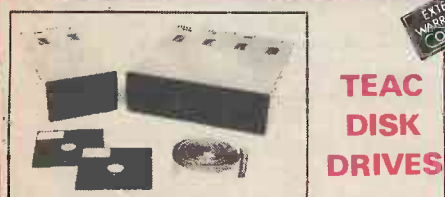


TEAC DISK DRIVES

- TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.
- The FD-50A can be used in double density recording mode.
- The FD-50A is Shugart SA400 interface compatible.
- Directly compatible with Tandy TRS80 expansion interface.
- Also interfaces with Video Genie, SWTP, Heathkit, North Star Horizon, Superbrain, Nascom, etc, etc.
- Address selection for Daisy chaining up to 4 Disks.
- Disks plus power supply housed in an attractive grey case.

Single Disk Drive **£225** + VAT Double Disk Drive **£389** + VAT

COMP POCKET COMPUTER GREATEST BREAKTHROUGH YET

£79.90 + VAT

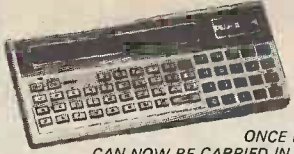

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

- Programs in BASIC ● "QWERTY" Alphabetic Keyboard ● 1.9K Random Access Memory ● Long Battery Life.

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24-character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

FANTASTIC FOR FILE HANDLING ACULAB FLOPPY TAPE

The tape that behaves like a disc, for TRS-80 LEVEL 2.

only **£169** + VAT



The Aculab Floppy Tape for the TRS-80 and Video Genie is a highly reliable digital storage system that provides many of the advantages of floppy disks at less cost. Automatic debounce routine for the Level 2 keyboard. Connects directly to TRS-80 Level 2 Keyboard. Operating and file handling software in ROM. 8 commands add 12 powerful functions to Level 2 BASIC.

THE VIDEO GENIE SYSTEM

Ideal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.

EG3000 Series



WITH **£279** + VAT
 ● 16K user RAM plus extended 12K Microsoft BASIC in ROM ● Fully TRS-80 Level II software compatible ● Huge range of software already available ● Self contained, PSU, UHF modulator, and cassette ● Simply plugs into video monitor or UHF TV ● Full expansion to disks and printer ● Absolutely complete — just fit into mains plug.
 The Video Genie is a complete computer system, requiring only connection to a domestic 625 line TV set to be fully operational; or if required a video monitor can be connected to provide the best quality display. 51 key typewriter style keyboard, which features a 10 key rollover. Supplied with the following accessories:- ● BASIC demonstration tape; ● Video lead; ● Second cassette lead; ● Users manual; ● BASIC manual; ● Beginners programming manual. Write useful programs in the BASIC computer language yourself.

EPROM 2716 **£12.50** + VAT

only **£325** + VAT



TRS80 LEVEL 2 16K

Fully converted to UK T V Standard. Comes complete with easy to follow manuals UK Power Supply Cassette Leads Sample tapes Special box to enable you to plug into your own TV Recommended for first time buyers Just plug in and go Full Range of Software Available
 Interface to Centronics Parallel for TRS80 **£75.00** + VAT

only **£295** + VAT

TRS80 EXPANSION INTERFACE

Expand your TRS80 by 32K 32K Memory on board Centronics parallel port Disk controller card Real time clock Requires Level II Basic Interface for 2 cassette decks complete with power supply

YOU NEED NEVER MISS AN IMPORTANT CALL AGAIN TWO CORDLESS TELEPHONE SYSTEMS — DIRECT FROM USA



THE ALCOM

only **£147** + VAT

Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling — Bleeps when call arriving — Nicad rechargeable batteries. Charger in base unit.



LOW COST TELEPHONE ANSWERING MACHINE

only **£99.95** + VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

COMMERCIAL EXPANDABLE • COMPLETE TRS 80 • MODEL II

+ NOW IN — TRS80 MODEL 111

64K 1-Disk Model II

£1995.00 + VAT

RRP £2250.00




EXTENDED WARRANTY BY COMPUTARE

This new unit from the world's most successful micro company is now available immediately with software. The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another 1/2 million extra characters including the disc operating system. More disc expansion is now available. The Model II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic. A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation. Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can operate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

CP/M2	£95.00	M BASIC	£155.00
CIS COBOL	£400.00	FORTRAN	£220.00
C BASIC	£75.00	WORDSTAR	£255.00

COMP PRO MIXER

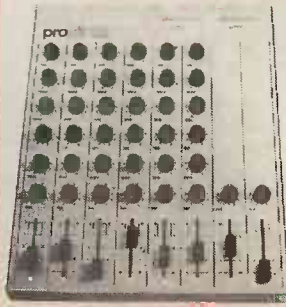

Professional audio mixer that you can build yourself and save over £100.

Only **£99.90**

plus VAT for complete kit. Plus **FREE** power supply valued at **£25.00**

FULL RANGE OF ACCESSIT AUDIO ADD-ONS

NOBODY CAN GET NEAR OUR PRICES EXCEPT OUR CUSTOMERS

RRP £540 only **£395** + VAT
ANADEX DP8000

Super Quality — Low cost printer. Tractor Feed with full 96 ASCII character set. Accepts RS232C at baud rates between 100 and 9600 and Parallel Bit data. Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, CompuKit etc.

THE NEW ANADEX DP9500 and DP9501 A PROFESSIONAL PRINTER

● Bi-directional printing
 ● Up to 220 chars/line with 4 print densities
 ● 500 char buffer
 ● RS232C and Centronics Parallel interface built in
 ● Full software control of matrix needles allowing graphics capability
 ● 200 chars/sec ● Adjustable width tractor feed.

DP9500 — ONLY **£795** + VAT
 DP9501 — ONLY **£845** + VAT

THE ATARI VIDEO COMPUTER GAMES SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!
 Most Cartridges only **£13.90** + VAT
 Prices may vary with special editions: Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle, Codebreaker*, Miniature Golf.

Extra Paddle Controllers — **£14.90** + VAT
 *Keyboard Controllers — **£16.90** + VAT

SPACE INVADERS NOW IN STOCK £25

NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ET1. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.

MINI KIT — PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. **£14.90** + VAT
OR PCB £2.90 MAIN LSI £8.50 Both plus VAT

WE ARE NOW STOCKING THE APPLE II AT REDUCED PRICES

16K **£599**
 32K **£649**
 48K **£659** + VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too, because of built-in features like:
 ● BASIC — The Language that Makes Programming Fun.
 ● High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays. ● Sound Capability that Brings Programs to Life. ● Hand Controls for Games and Other Human-Input Applications. ● Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM, for Big-System Performance in a Small Package. ● Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.



EUROPE'S FASTEST SELLING ONE BOARD COMPUTER
COMPUKIT UK101

★ 6502 based system — best value for money on the market. ★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for CompuKit expansion **£8.50** + VAT

Build, Understand and Program your own Computer for only a small outlay. **KIT ONLY £179** + VAT **NO EXTRAS NEEDED**

Available ready assembled, tested & ready to go **£229** + VAT

NEW MONITOR FOR COMPUKIT UK101
 ● In 2K Eprom 2716 ● Allows screen editing ● Saves data on tape ● Flashing cursor ● Text scrolls down **£22.00** + VAT
Special Bonus SAVE £22. New Super Monitor inc. in each kit or sold separately for **£22** + VAT.

FOR THE COMPUKIT		Game Packs		Super Space Invaders (8K)	
Assembler/Editor	£14.90	1. Four Games	£5.00	Space Invaders	£5.00
Screen Editor Tape	£1.90	2. Four Games	£5.00	Chequers	£3.00
		3. Three Games 8K only	£5.00	Real Time Clock	£3.00
All Prices exclusive VAT				Case for CompuKit	£29.50

HITACHI PROFESSIONAL MONITORS

9" — ~~£129~~ **£99.95**
 12" — ~~£199~~ **£149**

● **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability. ● **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved in picture center. ● **Stable picture** Even played back pictures of VTR can be displayed without jittering. ● **Looping video input** Video input can be looped through by built-in termination switch. ● **External sync operation** (available as option for U and C types) ● **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

ENGLISH COLOUR TV/ AMERICAN NTSC COLOUR MONITOR

Suitable for Apple, Atari and Texas 99/4 **£295** + VAT

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes	10 for £4.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Discs 5 1/4" Hard and Soft Sector	£3.50
Floppy Disc Library Case 5 1/4"	£3.50
Verocases for Nascom 1 & 2 etc.	£24.90
Keyboard Cases	£9.90

MEMORY UPGRADES

16K (8 x 4116) **£17.90** + VAT
 4K CompuKit (8 x 2114) **£17.90** + VAT

SPECIAL OFFER

We will part exchange your Sinclair ZX80 for any of our products.

Refurbished ZX80's—fully guaranteed **£69.90** + VAT
 (Supply dependant upon stocks).

We have one of the largest collections of Computer Books under one roof, along with racks of software for the PET and TRS80. **Come and see for yourself.**

NOW OPEN

OUR NEW SHOWROOM & SALES CENTRE AT
 311 Edgware Road,
 London W2.
 Telephone: 01-441 2922

APPLE DISC II

Disc with Controller **£349** + VAT
 Additional Drives **£299** + VAT

● Powerful Disk Operating Software Supports up to 6 drives ● Name Access to Files for Ease of Use ● BASIC Program Chaining to Link Software Together ● Random or Sequential File Access to Simplify Programming ● Dynamic Disk Space Allocation for Efficient Storage ● Individual File Write-Protection Eliminates Accidental File Alterations ● Loads an 8K Byte Binary Image in 6.5 sec. (1.2 sec. in Pascal) ● Storage Capacity of 116 Kilobytes (143K Bytes with Pascal) on Standard 5 1/4" Diskettes ● Powered Directly From the APPLE (Up to 6 Drives) for Convenience and High Reliability ● Packaged in Heavy-Duty, Colour-Coordinated Steel Cabinet

A SELECTION OF APPLE INTERFACES ARE NOW AVAILABLE AT OUR NEW SHOWROOM.

COMP SHOP

"Europe's Largest Discount Personal Computer Stores"

Delivery is added at cost. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

MAIL ORDER AND SHOP:
 14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station — Moorgate Line).
 Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G
OPEN (BARNET) — 10am - 7pm — Monday to Saturday

NEW WEST END SHOWROOM:
 311 Edgware Road, London W2.
OPEN (LONDON) — 10am - 6pm — Monday to Saturday

★ **IRELAND:** 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933
 ★ **COMP SHOP USA,** 1348 East Edinger, Santa Ana, California, Zip Code 92705. Telephone: 0101 714 5472526



COMP COMPUTER COMPONENTS
 (Part of the Compshop Ltd. Group)


Make it for a Song!



The New **Maplin Matinée**

Amazing Value
For Only **£299.95** + £99.50 for cabinet if required.

Easy to build. Latest technology — means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard. Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money. Full construction details in Electronics & Music Maker magazine.

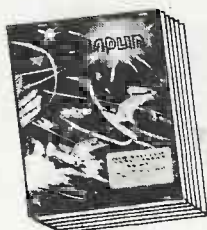

The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't afford to be without.



Post this coupon now for your copy of our 1981 catalogue price £1.

Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons. I enclose £1.25.

Name

Address

ET1581


MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554155 Sales (0702) 552911

Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
Both shops closed Mondays.

Catalogue now on sale in all branches of WHSMITH  Price £1.00

Socket to me!

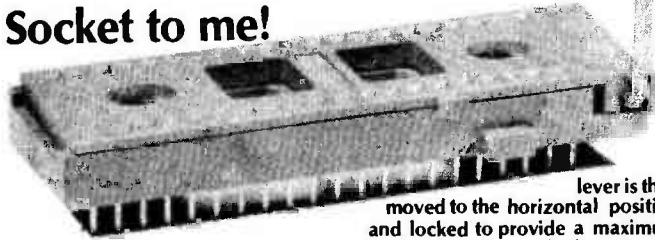

A range of Lever Actuated Zero Insertion Force sockets has been recently launched by Winslow International. The design is space saving — giving a height above the PCB of only 0.283 inches. When the lever is lifted to the upright position the socket will accept the IC without any force being applied to it. The

lever is then moved to the horizontal position and locked to provide a maximum contact resistance of 20 milliohms at 10 mA. The socket is manufactured from Glass Reinforced PBT Resin and contact plating is 75 microinches of gold over hard nickel. It is available in 24, 28, 40 and 64 contact versions. More details are available from Winslow Component Systems Ltd, 71 Tunnel Road, Tunbridge Wells, Kent TN1 2BX.

A Case In Point

Lascar Electronics are offering a FREE custom moulded handheld instrument case worth over £1 to any enthusiast building their LCD meter kit, which they claim to be the first of a new generation of DPMs. The meter gives a battery life of at least 10 times that of existing types. LCD watch manufacturing techniques have been used to reduce the depth to a minimum. The 0.6 inch digits can be read to a distance of 10 m. The unit also incorporates a digital hold facility, auto-zero, auto-polarity, programmable decimal points and a


200 mV full scale deflection. Display backlighting is a customer option. The meter is supplied with brackets for front or rear panel mounting. The custom moulded case accepts the DPM, a PP3 battery and allows space for the customer's own PCB (the data sheet on the meter includes 10 small easy-to-build handheld instruments). The total cost of the meter is £19.95 plus 50p postage and packing and £3.06 VAT. The offer of the free case is valid until the end of December this year. For further information contact Lascar Electronics at Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH.

Phone Around

Now that British Telecom has taken over the communications network for the Post Office, some ex-



citing new innovations are taking place, not the least of which is the yellow telephone box idea. Enough of the controversy though, let's get on with the real story. British Telecom has placed an order worth £10 million for the Herald electronic business telephone system. With this new system Britain can no longer be accused of being inefficient and old-fashioned in its approach to telecommunication by comparison with other countries. Herald is the most advanced small business system in the world. Based on a micro-processor and purpose designed large-scale integrated circuits, the Herald offers a unique range of programmable facilities. It can be arranged to function as a multi-line exchange, as a key system, as an automatic call distribution system or as a satellite to a large PABX. It is easy to install and maintain and is low-cost. The terminal is available in either standard or de-luxe models with a compact Central Control designed to blend into the office environment. Unfortunately the company hasn't mentioned whether the standard colour is British Telecom yellow! Buzby, you've got a lot to answer for!

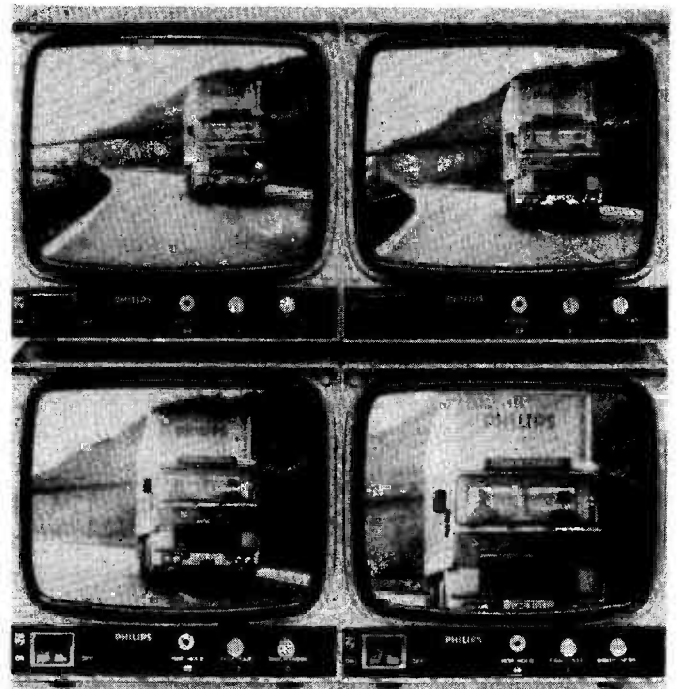

Dial-a-Picture

Still pictures can now be sent over any distance for the cost of a single phone call with the Philips Slowscan system. The system is ideal for cheap remote observations of buildings, industrial processes and motorways where it is not feasible to install high quality video circuits for real-time pictures. The application for this system is already in evidence on the M4 motorway. A CCTV camera is located at the Chepstow interchange, viewing the approach road. Still pictures, updated every 8.5 S, are displayed on monitors situated 17 miles away in the Police

Control Centre at Cwmbran, providing the Police with information on motorway conditions. The system has the facility for selecting up to four pre-set camera positions, and should the operator require closer examination of an incident, he can switch the Slowscan transmission system from a low definition/high speed scan of 8.5 S to a high definition/low speed scan of 17 to 35 S. The system comes from Pye Business Communications, Cromwell Road, Cambridge, CB1 3HE. This division of Philips will be re-named the Communication and Control Division of Philips Business Systems after 1st April this year.

Swimming Around?

The Casio W-100 series of watches are able to function up to a depth of 100 m and feature a 12-digit display. The integrated LCD shows full information simultaneously — hours, minutes, seconds, AM/PM (or 24 hour clock), day, month and date. Even when operating the secondary functions such as countdown alarm and stopwatch the W-100 still displays the current hour and minutes in an offset position. It is also capable of a daily alarm and half-hourly time signal. The Casio W series is a range that offers a choice of bracelet or case styles. The W-100 itself has a resin case and strap and costs £22.95. The W-150C features a stainless steel case with black resin strap at £27.95. Top of the range is the W-150 with full stainless steel case and strap at £32.50. (All these are recommended retail prices and this type of product is usually sold at lower prices.) Fur-

ther information from: Casio Electronics Co. Ltd, 28 Scrutton Street, London EC2A 4TY.



electronics today

INTERNATIONAL

NEXT MONTH

THE WAA-PHASE



Well what would you call a unit that offers a waa-waa sound and a unique phase-type sound? Our design also features a built-in mixer; you can add both these effects to the original guitar note to get exactly the sound you require.

LED JEWELLERY

Fancy a flash on your next visit to the disco? Feel like fighting back when the DJ starts up his little coloured lights? Frightened of getting lost in the gloom? Amaze your friends with ETI's LED jewellery — available in a range of sizes to suit your chest.

CARVER MAGNETIC FIELD AMP

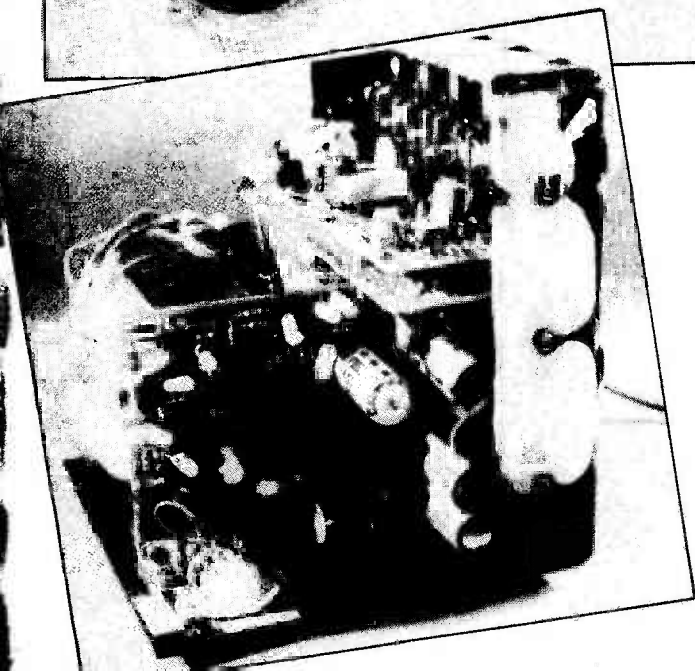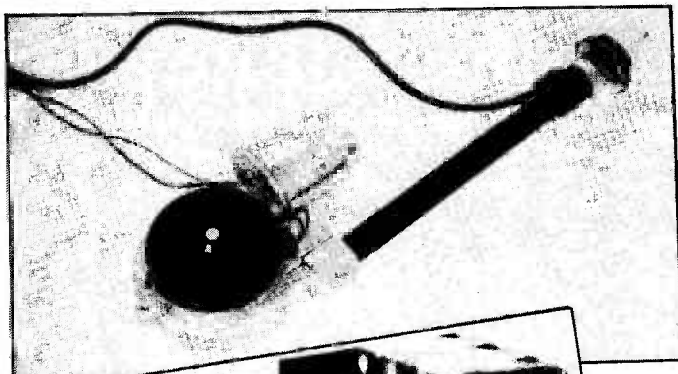An ETI exclusive! Despite what our friends across the Atlantic would call a 'low profile situation', we've been able to obtain details of Bob Carver's latest brainchild, the M-400 magnetic field amplifier. Would you believe a 7 inch cube that can push 200 W into an 8 ohm load? Neither did we until we read this article by Stan Curtis.



VOLTAGE CONTROLLED AUDIO

Continuing our current theme of remote-controlling everything (almost), we look at a range of Mullard ICs, intended for use in hi-fi systems, that allow DC control of just about all the functions you can think of. In this article Keith Brindley examines two members of the family; applications circuits and suitable PCBs are included so you can try them out for yourself.

TECH TIPS SPECIAL

Always one of our most popular features, Tech Tips gets the star treatment this month with extra pages of our readers' circuits. Essential for experimenters.

ANTENNA EXTENDER

It's pouring with rain; you jump into your car and turn on the radio to cheer yourself up. Nothing — you've forgotten to put up the aerial. Leap back out of the car, get soaked, and resolve to fit a motorised antenna driven by the ETI Antenna Extender. The aerial extends when you turn on the radio, retracts when you switch off, and has lots of built-in safeguards. Sheer luxury.

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.



LOOK OUT FOR THE
JUNE ISSUE ON SALE
MAY 1st

- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- CALL IN AND SEE FOR YOURSELF



AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL - MAIL ORDER EXPORT INDUSTRIAL
- OPEN SIX DAYS A WEEK

ALL PRICES INCLUDE VAT

SCOPES

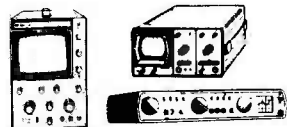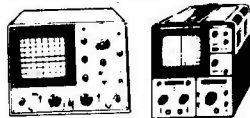A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace. Mains and Battery/Mains Portables. Many on demonstration.



HAMEG ● TRIO ● LEADER ● SINCLAIR ● HITACHI

SINGLE TRACE

- (UK c/p etc £2.50)
Hm 307-3 10mHZ, 5mV, 6 x 7 cm display plus component test **£158.78**
£109.25
CO1303D 5mHZ, 10mHZ, 7 x 7cm display **£158.95**
SC110 10mHZ battery portable, 10mV 3.2 x 2.6cm display (Optional case **£8.85**, Nicads **£8.83**, Mains unit **£4**) **£195.00**
+LBO512A 10mHZ 10mV, 5" display **£190.50**
C81559A 10mHZ 10mV, 5" display **£241.50**
+V151 15mHZ 1mV 5" display

OPTIONAL PROBES (ALL MODELS)

- XI** £6.50, **X10** £8.50, **X100** £12.95, **X1-X10** £10.95

SAFEG DUAL TRACE

- 10 MHz **£104.35**
 12 MHz **£201.25**
 15 MHz **£216.20**

HAMEG ● TRIO ● SINCLAIR ● LEADER ● HITACHI


DUAL TRACE

- (UK c/p etc £3.50)
C81552A 10mHZ, 10mV 5" display **£267.00**
C81575 5mHZ 1mV 5" display **£284.00**
Hm 312-2 20mHZ, 5mV 8 x 10cm display **£263.00**
C81566A 20mHZ, 5mV, 5" display **£339.00**
+LBO 3085 70mHZ, 2mV, 5 x 6.3cm display. Battery/mains. Portable built-in Nicads **£482.00**
HM412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay **£399.50**
C81577A 35mHZ, 2mV, 5" display **£478.00**
C81530 30mHZ, 2mV, 5" display plus sweep delay and delay line - new model **£669.00**
Hm512-2 50mHZ, 5mV, 10 x 8cm display. Delay Sweep **£667.00**
+LBO514 10mHZ, 1mV, (5mV) 5" display **£204.00**
+V152 15mHZ, 1mV, 5" display **£286.00**
+V302 30mHZ, 1mV, 5" display **£447.35**
+V550 50mHZ, 1mV, 10 x 8cm Delay sweep + 3 channel display **£799.25**

*PRICE INCLUDES FREE PROBE(S)

GENERATORS RF

(UK c/p £1.75)

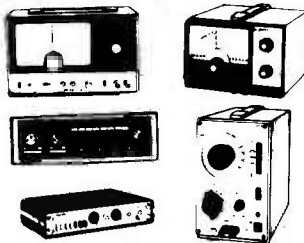

TRIO ● LEADER ● CSC
SINCLAIR ● LEVELL

- SG402** 100 KHZ-30mHZ with AM modulation **£68.00**
LS916 100KHZ-100mHZ (300mHZ on Harmonics) **£63.25**
SG2030 250KHZ-100mHZ low cost range **£46.95**
ARF 300 18HZ-200mHZ low cost range audio and RF **£76.95**

PULSE

- 2001** 1HZ-100KHZ (function) **£89.70**
TG105 5HZ-5mHZ **£92.50**
4001 0.5HZ-5mHZ **£109.25**
TT100 (function 10KHZ) **£90.85**

AUDIO

- (All sine/square)
AG202A 20HZ- 200KHZ **£69.00**
LAG26 20HZ- 200KHZ **£73.60**
AG203 10HZ- 1mHZ sine/sq **£126.75**
LAG120A 10HZ- 1mHZ **£146.00**

LOGIC PROBES/MONITORS

Logic probes indicating high/low, etc., states that scopes can miss. All circuit powered for all ICs.

- LP3** 50 mHZ logic probe **£55.95**
LP1 10 mHZ logic probe **£35.50**
LP2 1/2 mHZ logic probe **£19.95**
LM1 Logic monitor **£33.00**
LP1 50 Mhz logic probe with case **£51.00**
 Also in stock range of Protoboard kits and breadboards.

'PRO' MULTIMETERS

- M1200** 100K/Volt 30 ranges plus AC/DC 15 amp **£67.00**
K1400 20K/Volt 23 range large scale **£79.95**
M1500 20K/Volt 42 range plus AC/DC 10 amp **£53.50**
 (UK c/p £1.20)
K200 3B range FET 10m ohm input 20HZ to 30mHZ multimeter **£95.00**
 (UK c/p £1.50)

SWR/FS AND POWER METERS




Range in stock covering up to 150mHZ and up to 1K watt power PL259 sockets. Also 250 UHZ Grid Dipmeter.
SWR50 SWR/FS 3-150mHZ **£9.50**
SWR50 SWR/Power meter, 3/-150mHZ 0-1000 watts **£13.95**
110 SWR/Power 1/-144mHZ 0/10/100 watts **£11.50**
171 As 110 Twin meter plus F/S £14.50
 Plus large range of BNC/PL259/etc leads / plugs / adaptors / connectors always in stock.
175 SWR/Power/FS 1/-144mHZ 5-50 watt **£16.60**
KDMM Grid Dip 1/-250mHZ **£36.50**

DIGITAL MULTIMETERS

KAISE ● SINCLAIR ● LASCAR ● THURLBY

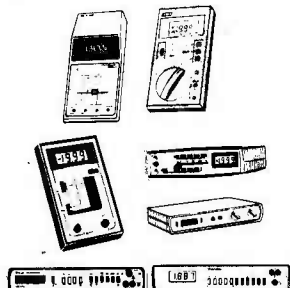A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors some with optional Nicads. All supplied with batteries and leads.



BENCH PORTABLES


- (UK c/p £1)
DM235 3 1/2 Digit LED 21 ranges, 0.5% AC/DC 2A **£60.38**
DM350 3 1/2 Digit LED 34 ranges AC/DC 10A **£87.38**
TM353 3 1/2 Digit LCD AC/DC 2 amp **£96.60**
TM351 3 1/2 Digit LCD AC/DC 10 amp **£113.85**
LM100 3 1/2 Digit LCD AC/DC 2 amp **£86.50**
DM450 4 1/2 Digit LED 34 ranges AC/DC 10 amp **£113.85**
 (DM series options. Carry case **£8.86** Nicads **£8.63** Mains adaptor **£4**)

HAND HELD

- (UK post etc 85p)
TM352 3 1/2 Digit LCD plus 10 ADC and Hfe checker **£54.95**
TM354 3 1/2 Digit LCD 2A AC/DC **£45.94**
ME502 3 1/2 Digit LED plus 10A DC and Hfe checker **£43.95**
LM2001 3 1/2 Digit LCD 2 amp AC/DC 0.1 % **£51.70**
6200 3 1/2 Digit LCD 0.2A AC/DC. Auto range **£45.95**
6220 As 6200 plus 10A AC/DC **£55.95**
6100 As 6200 plus Cont. test/range hold **£69.95**
6110 As 6100 plus 10A AC/DC **£85.95**
GL35C 3 1/2 Digit LCD 1A AC/DC with case **£37.50**

MULTIMETERS

(UK post etc 75p)

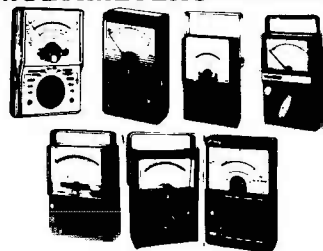

- KRT101** 1K/Volt 10 range pocket **£4.60**
ATM1/LT1 1K/Volt 12 range pocket **£5.98**
NH55 2K/Volt 10 range pocket **£6.50**
ATI 2K/Volt 12 range pocket de luxe **£7.75**
NH56 20K/Volt 22 range pocket **£11.95**
YN360TR 20K/Volt 19 range pocket plus hfe test **£13.50**
AT1020 20K/Volt 19 range de luxe plus hfe test **£8.95**
7081 50K/Volt 36 range plus 10 amp DC **£20.80**
TR303TR 20K/Volt + 12A DC + Hfe test **£16.95**
AT20 20K/Volt 21 range de luxe plus 10A DC and 5KV DC **£21.95**
AT205 50K/Volt 21 range de luxe plus 10A DC **£24.95**
7080 20K/Volt 26 range large scale, 10A DC plus 5KV AC/DC **£26.95**
AT2050 50K/Volt 18 range de luxe plus hfe test **£28.50**
AT210 100K/Volt 21 range de luxe 12A AC/DC **£29.95**
360TR 100K/Volt 23 range plus hfe cv/ker and AC/DC 10 amps **£34.95**

FREQUENCY COUNTERS

Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.

HAND HELD

- (UK post etc 85p)
PFM200 20HZ to 200mHZ 8 Digit LED **£52.27**
MAX50 100HZ to 50mHZ 6 Digit LED **£61.00**
MAX550 30KHZ to 550mHZ 6 Digit LED **£106.00**

BENCH PORTABLES

- (UK c/p £1)
MAX100 8 digit LED 5HZ to 100mHZ **£89.00**
TF200 8 Digit LCD 10HZ to 200mHZ **£166.75**
7010A 9 Digit LED 10HZ to 600mHZ **£169.00**
200SPC 6 Digit 100mHZ LED built into 0.002HZ to 5.5mHZ Pulse Generator **£437.00**
TF600 600mHZ Pre-Scaler for TF200 **£43.13**
TF040 8 Digit LCD 60mHZ **£126.50**

CSC ● SINCLAIR ● SPC ● OPTO ELECTRONICS

SOLDERLESS BREADBOARD AND KITS

- EXP350** **£3.45**. **EXP650** **£3.95**.
EXP300 **£5.95**. **EXP600** **£6.50**.
P86 **£9.95**. **PB100** **£12.95**.
PB101 **£17.95**.
 (UK c/p EXPs 30p. Kits 55p)

MINI DRILLS AND KITS

- (9-12 Volt 1/8" chucks)
 Small Drill plus 3 collets **£7.25**
 Medium Drill plus 3 collets **£10.50**
 Small Drill plus 20 tools **£14.95**
 Medium Drill plus 20 tools **£17.95**
 Mains Drill **£13.95**
 Mains Drill plus 20 tools **£21.50**

CHOOSE FROM UK'S LARGEST SELECTION



FREE CATALOGUE!

Send large SAE (17 1/2p UK) Schools, Companies, etc. free on request.

AUDIO ELECTRONICS Cubegate Limited OPEN SIX DAYS A WEEK
 301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564
 ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2 1ED

DESIGNER'S NOTEBOOK

The CMOS family contains many useful ICs, and in this month's extended Notebook, Ray Marston takes an in-depth look at the 4066B quad bilateral switch.

The 4066B CMOS IC is described in the manufacturer's literature as a 'quad bilateral switch', a pretty fair description since the device contains four independent electronic switches, each capable of passing signals in either direction and being controlled (turned on or off) by a single high-impedance terminal. The switches have a very high off impedance, an on impedance of about 90 R, and can be used to switch both analogue and digital signals. The ICs typically cost a mere 50 pence each, not bad for four independent SPST switches.

Basic 4066B Circuits

Figure 1 shows the outline and pin notations of the 4066B quad bilateral switch, which can be used with any supply voltage in the range 3 to 18 V. Note that, since the switches are of the bilateral type, either switch terminal can be used as the input or output.

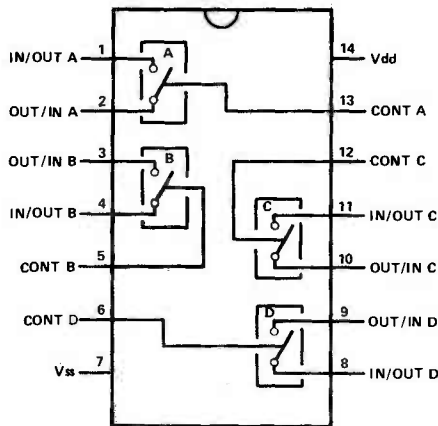


Fig. 1 Outline and pin notations of the 4066B quad bilateral switch.

Figure 2a shows the basic way of using the bilateral switch; the switch can be turned off (open circuit) by taking the control terminal to V_{SS} or turned on by taking the control terminal to V_{DD} . In digital switching applications (Fig. 2b) the IC can be used with a single-ended supply, with V_{SS} at 0 V and V_{DD} at the desired positive supply. In analogue switching applications (Fig. 2c), a split power supply (either true or effective) must be used, with the positive rail to V_{DD} and the negative to V_{SS} ; in this case, of course, the maximum supply limits are restricted to ± 9 V. Typically, the bilateral switch introduces less than 0.5% of signal distortion when used in the analogue mode.

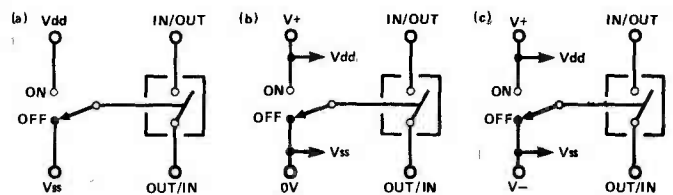


Fig. 2 (a) The basic bilateral switch is turned off by taking the control terminal to V_{SS} and turned on by taking the control to V_{DD} . (b) In digital switching applications, V_{DD} is $V+$ and V_{SS} is 0 V. (c) In analogue switching applications where a split power supply is used, V_{DD} must go to $V+$ and V_{SS} to $V-$.

Certain simple precautions must be observed when using the 4066B. First, the switch signals must in no circumstances be allowed to rise above the V_{DD} voltage or fall below the V_{SS} voltage. Each unused switch in the 4066B package must be disabled (see Fig. 3) either by taking its control terminal to V_{DD} or V_{SS} (as most convenient), or by taking all three terminals to V_{SS} .

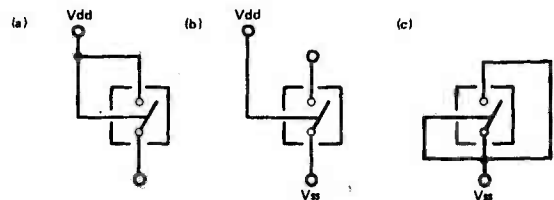


Fig. 3 Unused bilateral switches must be disabled, either by taking the control terminal to V_{DD} and one of the switch terminals to V_{DD} (a) or V_{SS} (b), or by taking all three terminals to V_{SS} .

Figure 4 shows how the 4066B can be used to implement the four basic switching functions of SPST, SPDT, DPST and DPDT. Figure 4a shows the SPST connections, which we have already discussed. The SPDT function is implemented by wiring an inverter stage (a 4001 or 4011, etc) between the IC1a and IC1b control terminals as shown. The DPST switch (Fig. 4c) is simply two SPST switches sharing a common control terminal, and the DPDT switch (Fig. 4d) is two SPDT switches sharing a common inverter stage in the control line.

Note that the basic switching functions of Fig. 4 can be expanded or combined in any desired way by simply adding extra switches/4066B-packages, as appropriate. Thus, a 10-pole double-throw switch can, for example, be made by using five of the Fig. 4d circuits and joining their control inputs together. →

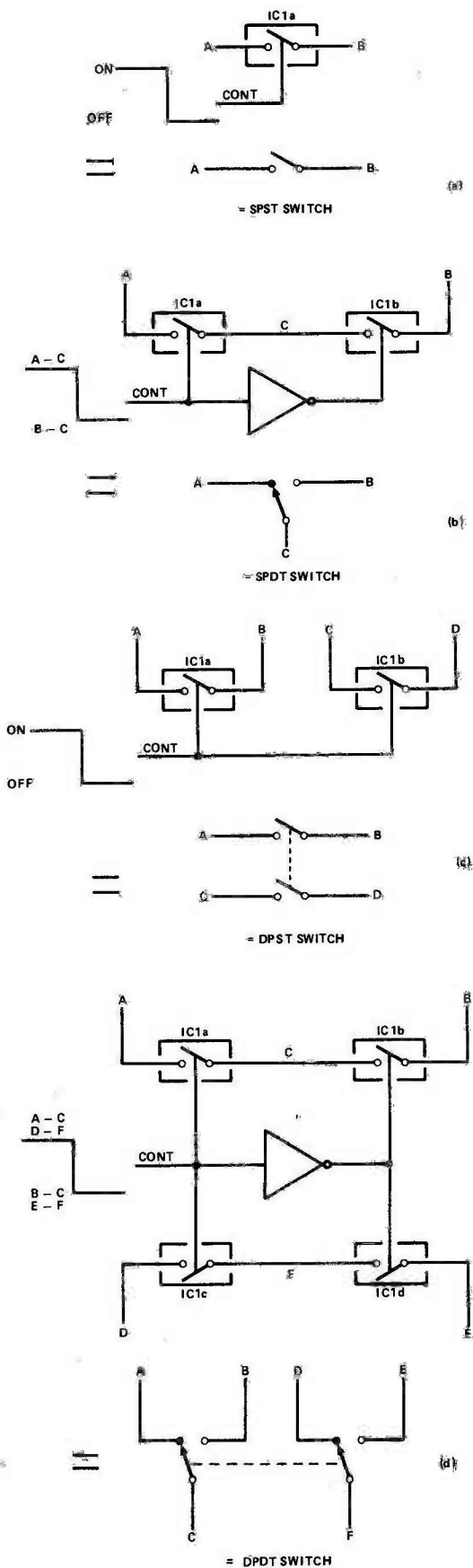


Fig. 4 Using the 4066B to implement the four basic switching functions.

Six Latching Circuits

Figure 5 shows how a 4066B switch can be used as a simple but very useful press-button activated latch; the LED is merely used to indicate the state of the latch and can be replaced with a short circuit if preferred. Circuit operation is easily understood.

Suppose initially that the latch is off (switch open). In this case the output, and hence the control bias applied via R2, will be zero, so the switch will maintain its off state. If PB1 is now momentarily closed the control voltage will go high and turn the switch on, thus driving the output high and maintaining the control drive high (switch on) once PB1 is released. This new state will be maintained until PB2 is closed, at which point the switch will latch into the off state again. R1 is used in the circuit to ensure that a supply short will not occur if both buttons are pressed at the same time; with R1 in the position shown, the switch will turn off if both buttons are pressed at once; if R1 is moved to the low side of PB2, the switch will turn on if both buttons are pressed at once.

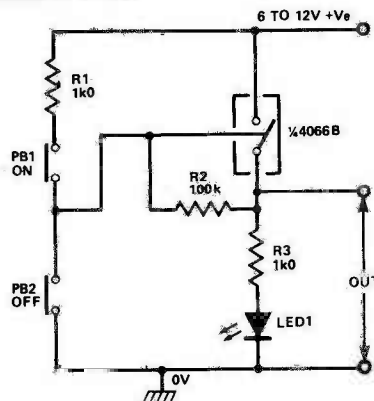


Fig. 5 Push-button latch using the 4066B.

The Fig. 5 circuit has a couple of interesting characteristics. First, the control bias resistor can be given any desired value up to practical limits. Figure 6, for example, shows how the value can be increased to 10M to make a latching touch switch that can be activated by placing a finger across the upper or lower set of touch contacts. R1 and C1 are used to suppress hum signals and ensure positive switching.

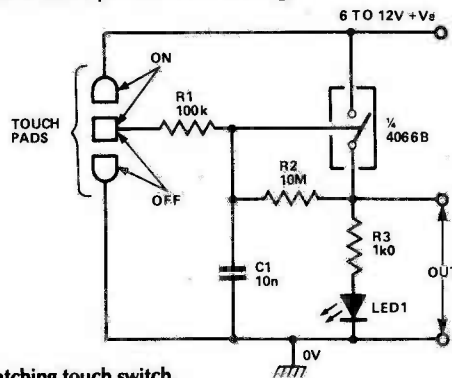


Fig. 6 A latching touch switch.

Another useful feature is that, since the on resistance of the switch is only 90 Ω or so, the voltage loss across the switch can be quite low (90 mV at 1 mA); in practice, the on current should be limited to 10 mA maximum. Figure 7 shows how this low-loss effect can be exploited to make a push-button power switch that can be used to connect or disconnect the power supply to a piece of electronic equipment (amplifier, test gear, etc).

When the switch is off, Q1 is cut off and the circuit consumes a typical standby current of less than 1 μA. When the

switch is on, Q1 acts as a voltage follower with its base tied to the positive line via IC1a, so the output voltage is high. The actual voltage drop between the output and the supply is equal to the IC1a drop plus the base-emitter drop of Q1 and typically ranges from 600 to 800 mV. The available output current depends on the gain and current rating of Q1, but currents of a few hundred milliamps are readily available from a single transistor.

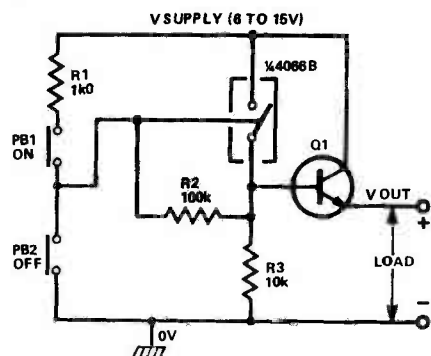


Fig. 7 This push-button-activated power switch can be used to replace a conventional slide or toggle switch.

A slightly more efficient version of the push-button power switch is shown in Fig. 8. In this case the load is wired between the collector of Q1 and the positive supply rail. The voltage drop in this circuit is determined only by the saturation characteristics of Q1 and may typically be in the range 200 to 600 mV.

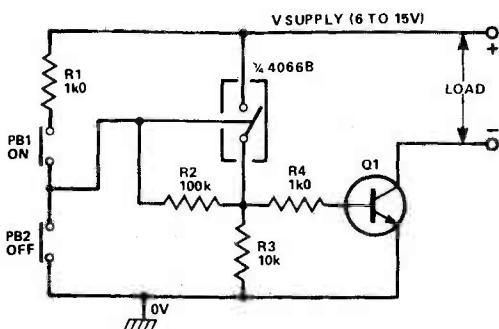


Fig. 8 An alternative version of the push-button power switch.

Figure 9 shows how the above circuit can be modified for use as a 'close-to-activate' burglar, panic or fire alarm, in which Q1 output feeds directly to a heavy duty 'alarm' relay which, in turn, actuates an external bell or siren. Any number of normally-open sensors/switches can be wired in parallel in the 'PB' positions. The circuit consumes only a microamp or so when in the 'ready' or off mode.

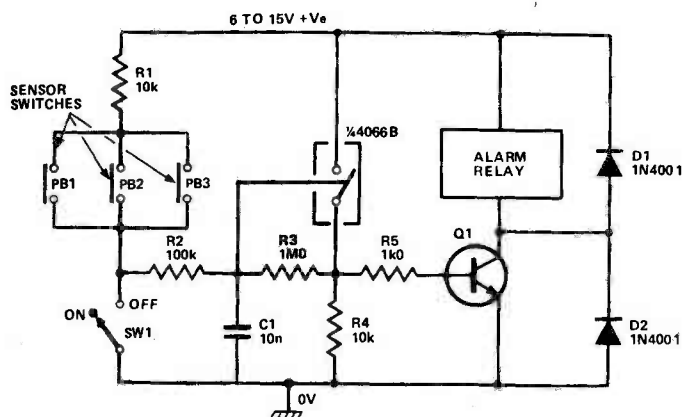


Fig. 9 A close-to-activate burglar/panic/fire alarm.

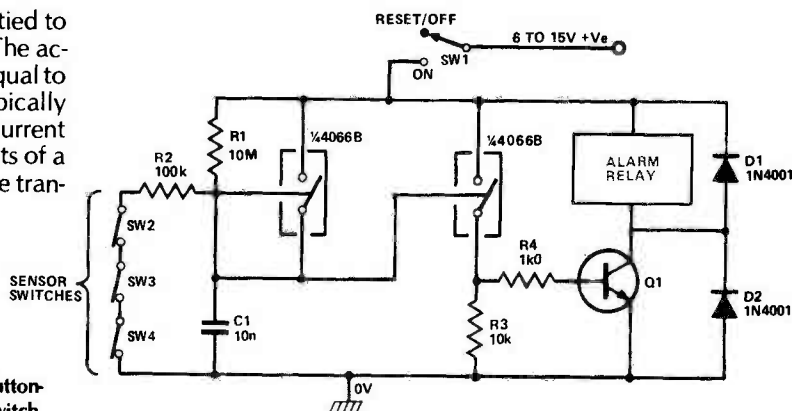


Fig. 10 A break-to-activate burglar alarm.

Finally, Fig. 10 shows how a pair of 4066B switches can be used to make a break-to-activate burglar alarm in which any number of normally-closed sensor switches can be wired in series and which typically consumes a standby current of only 1 uA or so. Here, if any of the switches open, the control terminals of IC1a and IC1b are pulled high by R1 and cause both switches to close; IC1a then shorts out R1, ensuring that the switches will not turn off again when the sensor switches close. Simultaneously IC1b activates the alarm relay via Q1. Note that, once this alarm circuit has been activated, it can only be turned off again by resetting the sensor switches and momentarily breaking the supply connections via SW1.

Digital Control

The 4066B can be used to digitally control or vary resistance, capacitance, impedance, amplifier gain or oscillator frequency in any desired number of discrete steps. Figure 11 shows how the four switches of a single 4066B can be used to vary the effective value of a resistance in 16 digitally-controlled steps of 10k each. In practice, of course, the step magnitudes can be given any desired value (determined by the value of the smallest resistor) so long as the four resistors are kept in the ratio 1-2-4-8.


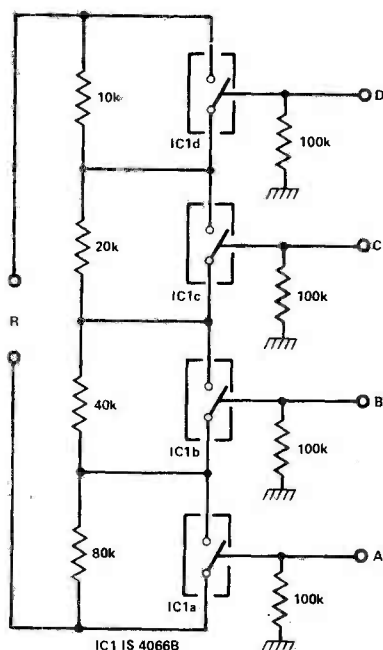


Fig. 11 This circuit gives 16-step digital control of resistance. R can be varied from zero to 150k in steps of 10k.

A	B	C	D	R
0	0	0	0	150k
0	0	0	1	140k
0	0	1	0	130k
0	0	1	1	120k
0	1	0	0	110k
0	1	0	1	100k
0	1	1	0	90k
0	1	1	1	80k
1	0	0	0	70k
1	0	0	1	60k
1	0	1	0	50k
1	0	1	1	40k
1	1	0	0	30k
1	1	0	1	20k
1	1	1	0	10k
1	1	1	1	0

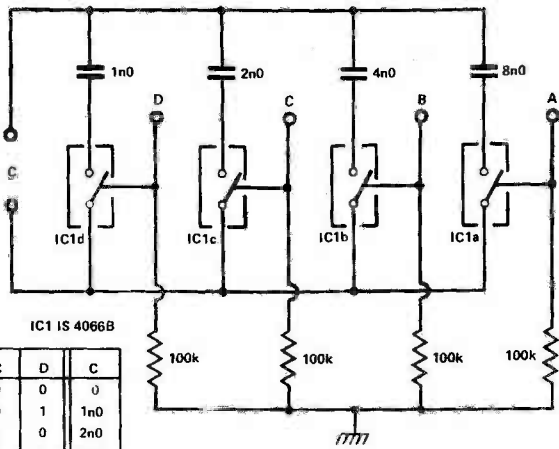

A	B	C	D	C
0	0	0	0	0
0	0	0	1	1n0
0	0	1	0	2n0
0	0	1	1	3n0
0	1	0	0	4n0
0	1	0	1	5n0
0	1	1	0	6n0
0	1	1	1	7n0
1	0	0	0	8n0
1	0	0	1	9n0
1	0	1	0	10n
1	0	1	1	11n
1	1	0	0	12n
1	1	0	1	13n
1	1	1	0	14n
1	1	1	1	15n

Fig. 12 A similar circuit to that of Fig. 11 gives 16-step digital control of capacitance. C can be varied from zero to 15n in steps of 1n0.

Figure 12 shows how four switches can be used to make a digitally-controlled capacitor that can be varied in sixteen steps of 1n0 each.

Note that in the Fig. 11 and 12 circuits the resistor/capacitor values can be controlled by operating the 4066B switches manually, or automatically using simple logic networks, microprocessors, up/down counters, and so on.

The circuits of Figs. 11 and 12 can be combined in a variety of ways to make digitally-controlled impedance and filter networks. Figure 13, for example, shows three different ways of using the circuits to make a digitally-controlled first-order low pass filter.


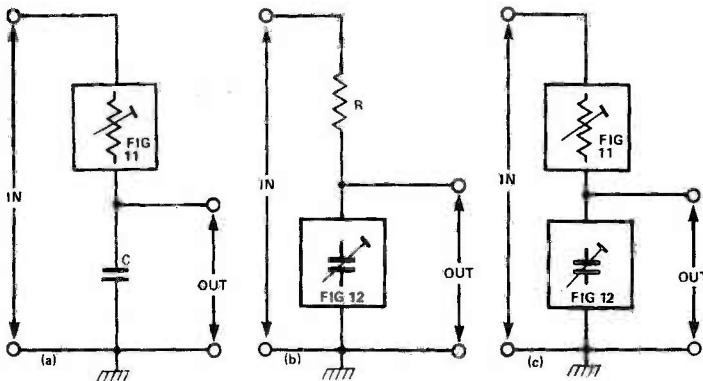
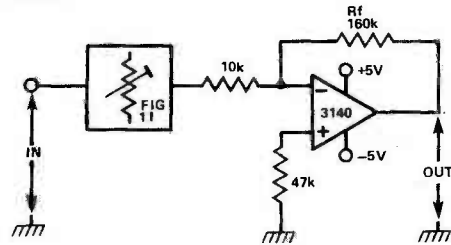


Fig. 13 Three ways of using the circuits of Fig. 11 and Fig. 12 to make a digitally-controlled first-order low pass filter.

Digital control of amplifier gain can be obtained by hooking the 'resistance' circuit of Fig. 11 into the feedback or input path of a standard op-amp inverting circuit, as shown in Figs. 14 and 15. The gain of such a circuit is equal to R_f/R_{IN} , where R_f is the feedback resistance and R_{IN} is the input resistance. Thus, in the Fig. 14 circuit, where the controlled resistance is in the feedback loop, the gain can be varied from zero to unity in 16 discrete steps of 'one fifteenth' each, ie giving a sequence of 0, 1/15, 2/15, 3/15, ..., 14/15, 15/15.

Fig. 14 Digital control of gain using the Fig. 11 circuit. The gain can be varied between zero and unity in 16 steps.

Fig. 15 This application of the Fig. 11 circuit gives digital control of gain between unity and x 16 in 16 steps.

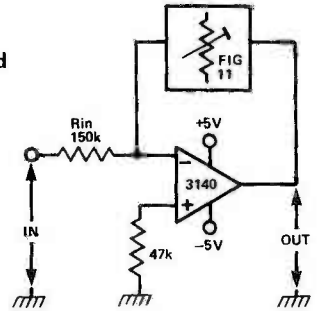

In the Fig. 15 circuit, where the controlled resistance is in the input path, the gain can be varied from unity to x 16 in 16 steps, giving a gain sequence of 1, 2, 3, 4, 5, 6, ... Note that in both of these circuits, the op-amp uses a split power supply so the 4066B control voltage must switch between the negative and positive supply rails.

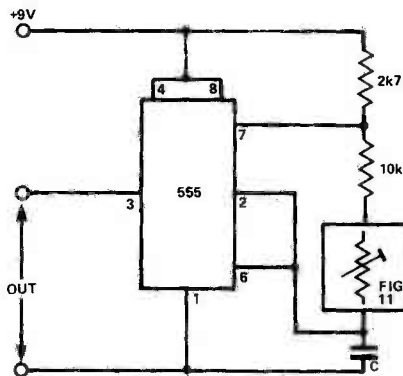


Fig. 16 Digital control of the frequency of a 555 astable. The frequency can be varied in 16 steps.

Figure 16 shows how the Fig. 11 circuit can be used to digitally control the frequency of an oscillator in 16 discrete steps. In this example the circuit is that of a 555 astable, but the general control principle can be applied equally well to many other types of oscillator circuit.

Figure 17 shows how a trio of 4066B switches can be used to implement digital control of the decade range selection of 555 astable. Here, only one of the switches must be turned on at any time. Naturally, the circuits of Figs. 16 and 17 can be combined to form a wide-range oscillator that can be digitally controlled by a computer, for example.

Synthesized Multi-Gang Pots

The synthesizing principle is quite simple and is illustrated in Fig. 18, which shows the circuit of a synthesized four-gang 10k - 100k rheostat for use at signal frequencies up to about 15 kHz.

Here, the 555 is used to generate a 50 kHz (nominal) rectangular waveform whose mark/space ratio can be varied from 11:1 to 1:11 by RV1, and this waveform is used to control the switching of the 4066B stages. All of the 4066B switches are fed with the same control waveform, and each switch is wired in series with a range resistor (RA, RB, etc), to form one gang of the 'rheostat' between the pairs of terminals, as shown.

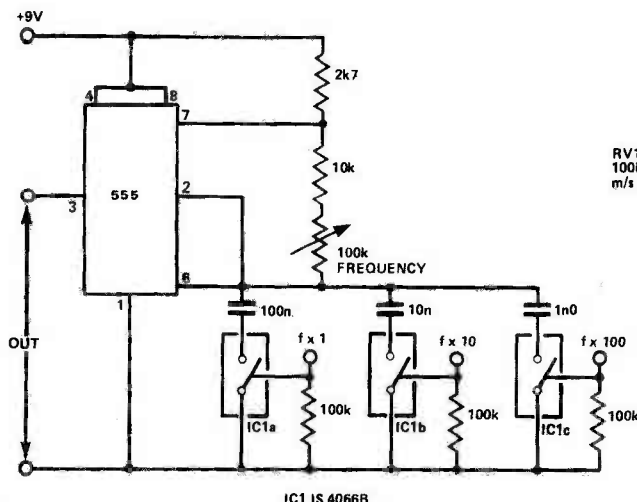


Fig. 17 Digital control of decade range switching of a 555 astable.

Remembering that the switching rate of this circuit is very fast (50 kHz) relative to the rheostat's maximum signal frequency (15 kHz), it can be seen that the mean or effective value of the 'rheostat' resistance can be varied with mark/space ratio control RV1. Thus, if IC2a is closed for 90% and open for 10% of each duty cycle (mark/space ratio of 9:1), the apparent (mean) value of the resistance will be 10% greater than RA, ie 10k. If the duty cycle is reduced to 50%, the apparent RA value will double, to 18k2. If the duty cycle is further decreased, so that IC2a is closed for only 10% of each duty cycle (mark/space ratio 1:9), the apparent value of RA will increase by a decade, to 91k. Thus, the apparent resistance of each 'gang' of the 'rheostat' can be

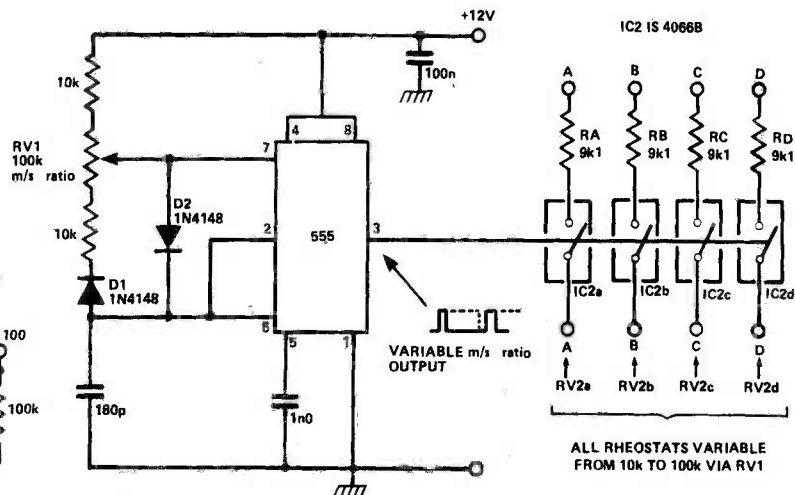


Fig. 18 Synthesized precision four-gang rheostat.

varied by RV1.

There are some important points to note about the Fig. 18 circuit. First, the circuit can be given any desired number of 'gangs' by simply adding an appropriate number of switch stages and range resistors. Since all switches are controlled by the same mark/space ratio waveform, perfect tracking is automatically assured. Individual gangs can be given different ranges, without affecting the tracking, by giving them different range resistor values. The sweep range and the law of the rheostat can be changed by changing the characteristics of the mark/space ratio generator.

ETI

CCAT

CAMBRIDGESHIRE COLLEGE
OF ARTS AND TECHNOLOGY

Courses in Electronics

BSc IN ELECTRONIC ENGINEERING

A four year part-time degree course for mature students. Of particular interest to those engaged in Digital, Telecommunications or Control Systems. Entry qualification required is an HNC or equivalent in Electrical and Electronic Engineering or Applied Physics. This CNAA degree is considered by the Council of Engineering Institutions as meeting their C.Eng. academic requirements.

CEI PART II

One year full-time or two years part-time course in preparation for the CEI Part II examination which is the present academic qualification for Chartered Engineers. Subjects offered include Electronics, Communication, Control and Computer Engineering. Entrants should have passed CEI Part I or have been exempted; holders of HNC and endorsements or HND are so qualified.

Further details and application forms are available from the Information Office, Room H267, Cambridgeshire College of Arts and Technology, Cambridge, CB1 2AJ. Telephone (0223) 63271.

SoundLink

Wireless
Loudspeaker
Extension
Kit

With a SoundLink Kit you can listen to your HiFi in the bedroom, garage, study; anywhere you have a mains socket! No long, trailing wires any more!

The Kit consists of two assembled and tested printed circuit boards: simply wire the input board to your existing audio system - the music signal is then picked up by the output board via a mains socket elsewhere in the house, giving up to 10W of FM quality sound to drive the loudspeaker of your choice.

Frequency Response: 30-12000 Hz
Noise: -57dB
Input sensitivity: 100 mV adjustable (50kohm)
Output power: 10W into 8ohm
Power requirements: 12-0-12VAC at 6VA (Input board)
at 20VA (Output board)

£45.50

The two boards contain all the electronics needed, all you need is two mini transformers, wire, controls and connectors to suit your own equipment. Full instructions supplied, including details of suitable enclosures; the output board may be built into a loudspeaker cabinet to make a portable plug-in SoundLink.

To: IMP Electronics, 34 Caraway Road, Fulbourn, Cambridge CB1 5DU. Telephone (0223) 881105

Please send me SoundLink Kit(s) at £45.50 each.

I enclose cheque/postal order for

Please tell me more about SoundLink.

NAME

ADDRESS

POSTCODE

Professional ASCII Keyboards



ONLY £29.95
ADD + VAT
POST £1.50
SCOOP

The 'APPLE' Computer Keyboard

- 52 KEY 7 BIT ASCII CODED
- POSITIVE STROBE. +5V - 12V
- FULL ASCII CHARACTERS
- PARALLEL OUTPUT WITH STROBE
- POWER LIGHT ON CONTROL
- NATIONAL mm 5740 CHIP. TTL OUTPUT
- SUPERBLY MADE. SIZE 12x5.5x1.5ins
- BLACK KEYS WITH WHITE LEDGENS
- ESCAPE. SHIFT. RETURN & RESET KEYS

Complete with CIRCUIT & DATA

Ideal for use with TANGERINE TRITON

Ex-Stock from HENRY'S TUSCAN APPLE & most computers

This is definitely the **BEST BUY**
Supplied **Brand NEW** in manufacturers original jacking (ANTI-STATIC)
Just post remittance total £35.95 (incl. VAT & Post)



HENRY'S



Computer Kit Division
404 Edgware Road, London, W2, England
01-402 8822



Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS - CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD - DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMAN'S - HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS - KEF - LOWTHER - MCKENZIE - MISSION - MONITOR AUDIO - MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS - RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNY - VIDEOTONE - WHARFEDALE.

WILMSLOW AUDIO

35/39 CHURCH STREET
WILMSLOW, CHESHIRE SK9 1AS


Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 SWIFT OF WILMSLOW)
5 SWAN STREET, WILMSLOW, CHESHIRE SK9 1HF)
FOR HI-FI AND COMPLETE SPEAKERS



Chokes, block filters, ceramic filters, resonators, HTs, oscillator coils, audio filter blocks etc.

LOW PASS FILTERS

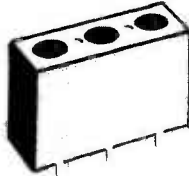Now from 10kHz to 20MHz
TOKO's recently expanded LPF series covers from the audio spectrum through to 20MHz in a series of LPFs for mpX, video, radio etc.




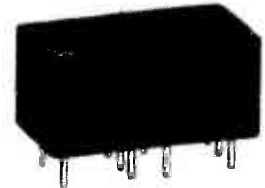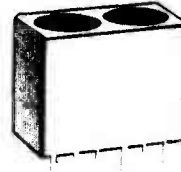The LPFs are based on 7&10mm formats with up to 4 LC tuned elements per block. Many stock types available.




HELICAL FILTERS 2 & 3 elements available for VHF and UHF:

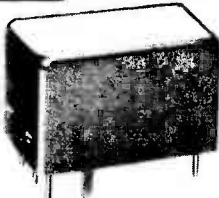Featuring low insertion losses, -80dB at the +/- 21.4MHz points. Ask for details.




CERAMIC RESONATORS & PIEZO SOUNDERS

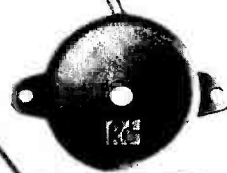Audio buzzers now down to 1kHz - low cost 400-600kHz crystal replacements for MPUs, RCs etc. Low cost - wide range.



VIDEO FRAME STORES

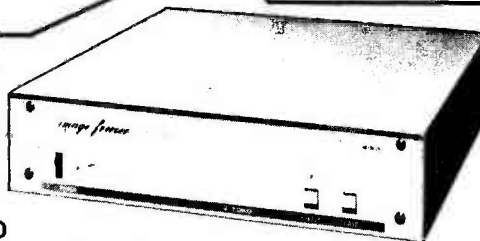- ★ 525/625 operation
- ★ 512 pixels/line
- ★ Local or remote control
- ★ Top/bottom & L/R reverse
- ★ Models available with digitized I/O



Video frame stores are a new addition to TOKO's memory product range. They permit easy analysis of low dose X-Ray pictures, digital processing of picture information (including the VFM10D with 8" disk drive) with much better resolution than available from VTR

AMBIT international TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
200 North Service Road, Brentwood, Essex

TEMPERATURE-CONTROLLED SOLDERING IRON

Sorry, no more excuses for dry joints or solder blobs on your projects. Our all-electronic soldering station has all the advantages of the best professional equipment, without the price. Design and development by Plamen Pazov.

It is something of an anachronism that in this day of high technology, we should still use solder to join the pieces of our electronic puzzles. And it isn't due to lack of choice: conductive polymers, force-fit, ultrasonics, wire-wrapping, clamp mass or unit terminators and even microweld have all been tried and are very useful in some specialised areas. But the fact remains that soldering is one of the most reliable and versatile ways of making an electrical and mechanical joint with a minimum of cost and time.

The ETI Microstation has been designed to make the process even more reliable and versatile. Its main purpose is melting the solder and locally heating the parts to be joined. It must do so:

- Whatever the thermal mass of these parts;
- In a very short time (before the heat has diffused into and damaged the electronic component or lifted the PCB track — a good rule of thumb is less than 3 S)
- Without overheating the solder (the flux burns and an oxide layer is formed, making it extremely difficult to wet the component).

The key words here are 'thermal mass' and electronic components vary wildly in this respect. Because of this, one usually ends up with three or even four irons in the tool box.

Thermomechanically-controlled irons (magnetic Curie point or thermocouple-switched) can be an improvement, but they are not adjustable and the switching of the heating element creates current spikes that can be very nasty to MOS and other sensitive devices. In addition, they are usually bulky and slow-reacting.

Electronically-controlled soldering stations with adjustable temperature are an improvement; the trouble with many of them is the relatively low maximum output power. The trouble with *all* of them is the price! Practically all electronic stations use a special heating element incorporating a temperature sensor. Unfortunately, this increases the



maintenance costs as well.

As a last criticism, on practically all models the tip is invariably too far from the handle and does not allow a precise work control.

The Microstation is based on a very low voltage heating element-bit initially introduced on portable, battery-powered irons. It has a very low thermal mass and no thermal resistance between element and bit, allowing a very fast-reacting temperature regulation. In addition, the low voltage operation makes it completely harmless to sensitive integrated circuits.

The temperature sensing is performed by measuring the resistance of the heating element itself (by including it in a Wheatstone bridge configuration) and therefore does not require any complicated thermal sensors.

The low working voltage of the element (2V5) implies a high current consumption at maximum power (12 to 15 A). The only type of power supply that can effectively handle and control such currents is the switched mode step-down converter. This circuit accepts a high, unregulated voltage and generates a high current-low voltage output that can be easily controlled. The principle is to store packets of energy in an inductor and then discharge them into the load at a different voltage. The current tends to be constant, so the ratio of the times taken to store and release the energy are the same as the ratio between input and output voltage.

As the power-controlling transistors are either switched on or off, the theoretical efficiency of the circuit is 100%. In practice, the finite switching times mean that some power is dissipated, and the heatsink can become quite hot.

One of the most crucial parts of a switched mode supply is the storage inductance and many tomes have been written

Fig.1 Circuit diagram. Components above the dotted line are mounted either on the heatsink, case or in the actual soldering iron.

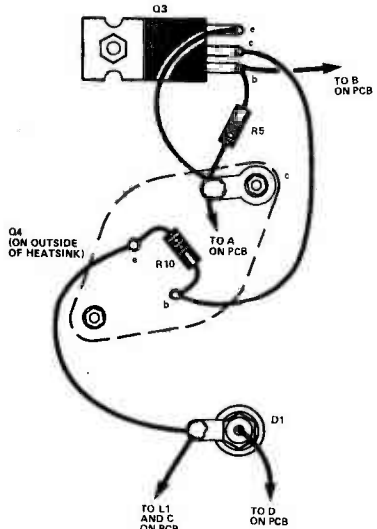
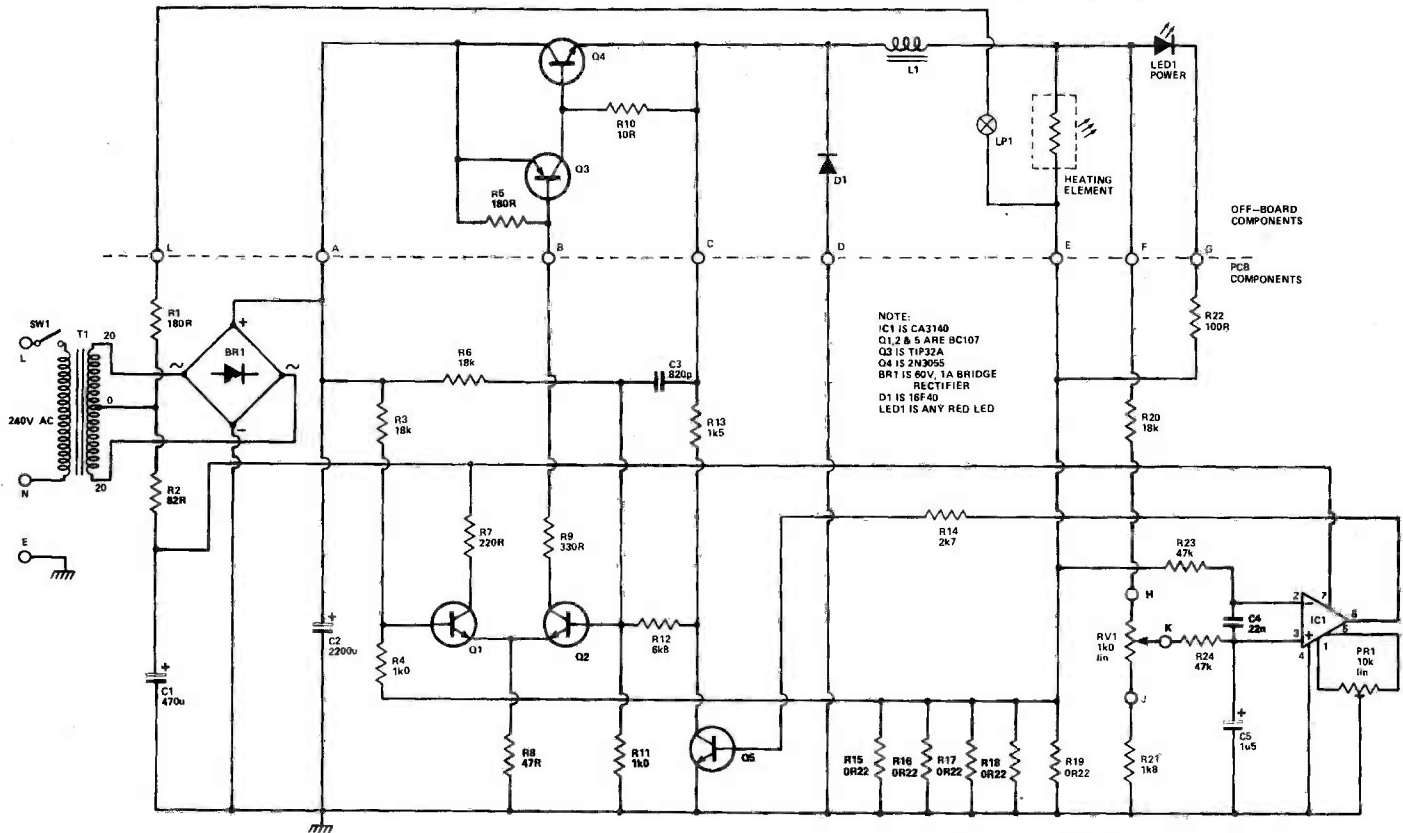


Fig.2 This drawing shows the off-board components as they should be mounted on the heatsink (seen from the inside of the case). The photograph on the last page may also help with construction.

about the pros and cons of different materials, magnetic polarisation and loss distribution. The basic problem is that core loss and size are proportional to the energy packet, but minimising them means increasing the switching frequency, and therefore the power semiconductor loss. This loss occurs during the transition period between the on and off states and is directly proportional to switching frequency. In practice, the core choice was mainly dictated by availability to the hobby market and many a beautiful formula had to stay in its book.

As mentioned earlier, no thermal sensor as such is used. The temperature is sensed by measuring the resistance of the heating element itself which is slightly temperature-sensitive. (It

HOW IT WORKS

The circuit can be split into three main sections; power supply, main converter and temperature-sensing circuitry.

The supply rail for the main converter is standard, with the transformer output being full-wave rectified by BR1 and smoothed by C2. The op amp supply relies on the fact that the centre tap of the transformer is always at mid-voltage, $V_{cc}/2$, whatever the polarity of the incoming AC; it only needs to be filtered by R2/C1.

The circuitry of the main converter can be considered to be equivalent to an op amp, with the differential pair Q1, Q2 functioning as the inverting and non-inverting inputs respectively, and Q3, Q4 being the output stage. The circuit will oscillate at a high frequency, as follows. Assume Q4 is turning on, so that Q4 emitter is now at the supply voltage — this increase in voltage is coupled to the base of Q2 by C3 and R12-R13. C3 is included to improve the high frequency response. Q2 now conducts more heavily, tending to turn on Q3 (and hence Q4) still further and this regenerative action means that Q4 turns hard on. D1 will not conduct as it is reverse biased.

Current does not flow in the load immediately because of inductor L1; instead the current increases exponentially towards V_{cc}/R_{LOAD} . As the current flows through R15-19 it generates a voltage which is coupled to Q1 base via R4. As the load current increases, it reaches a point where the voltage on Q1 base exceeds that on Q2 base, and Q4 now begins to turn off. L1 again opposes this voltage change and lowers the voltage at Q4 emitter, a regenerative action that turns Q4 hard off. L1 forces Q4's emitter so low that D1 conducts and allows current to continue to flow through the load. The energy stored in the coil is discharged into the load and so the current through the heating element and R15-19 is decreasing. Thus the voltage on Q1 base eventually falls below that on Q2 base, turning Q4 on and starting the whole cycle again.

During each cycle, when Q4 conducts, the power output is $V_{cc} \times I_{LOAD}$ but the power in the load is only $V_{LOAD} \times I_{LOAD}$. The difference is stored in L1 and delivered to the load when Q4 is blocked. The mean current output of Q4 is therefore much lower than the effective continuous load current.

Temperature control is achieved by using the Wheatstone bridge built around IC1. The heating element and R15-19 form one arm of the bridge, R20, RV1 and R21 form the other. The reference voltage from RV1 is compared with that across the inputs of IC1. The output of the op amp controls the oscillator feedback voltage by means of Q5.

varies between 0.155 and 0.22 R at 100°C and 400°C respectively.)

In practice, we don't even need to measure the temperature itself. By including the heating element into a Wheatstone bridge configuration, its resistance is continuously compared to the fixed resistors. Any change from the preset balance condition appears as an error signal that can be directly used to control the power input and therefore correct the temperature. The resulting temperature regulation is effective between 50°C and 500°C (as we discovered by melting a couple of heating elements during our trials), but for practical purposes, the temperature range was limited to 200°C-450°C, with a very good linearity.

Construction

The main point to remember throughout the construction of this project is the fact that the output currents can be very high indeed — more than 15 A peak. All current-bearing conductors (and that includes the output leads, the internal connections and the coil) must accept such currents without overheating. A 0.75 mm square cross-section wire seemed adequate. A well-ventilated enclosure is also recommended, a few holes in the bottom and the back can do wonders.

All power semiconductors (Q3, Q4 and D1) should be mounted on a 2.1°C/W heatsink (100 mm or 125 mm wide extrusion — see pictures). Make sure that each one is insulated with mica washers and thermal compound. The power semiconductors should be protected from electrical contact with the outside world by some form of cover on the heatsink and the whole thing mounted in a case that would not curl up at the sight of molten solder.

Coil L1 is made by winding 50 turns of 1 mm square enamelled copper wire onto a toroidal core. A bit of masking tape keeps things tidy, as you can see from the photograph.

The soldering iron itself is made from a small piece of double-sided PCB, press-fitted into a piece of aluminium tubing (100 mm by 14 mm). Screw connections from an ordinary terminal block are soldered at the right spacing onto the PCB. Although it can be replaced by some insulating material, note that the aluminium uniformly dissipates the heat coming from the element and allows a very comfortable grip at a small distance from the tip. A small magnet mounted on the side of the tubing is one of the quickest and most practical stands. The size of tubing even allows for mounting a small lamp inside the handle: very useful for precision work.



The PCB before interwiring.



The element and light bulb are mounted on a piece of double-sided PCB.

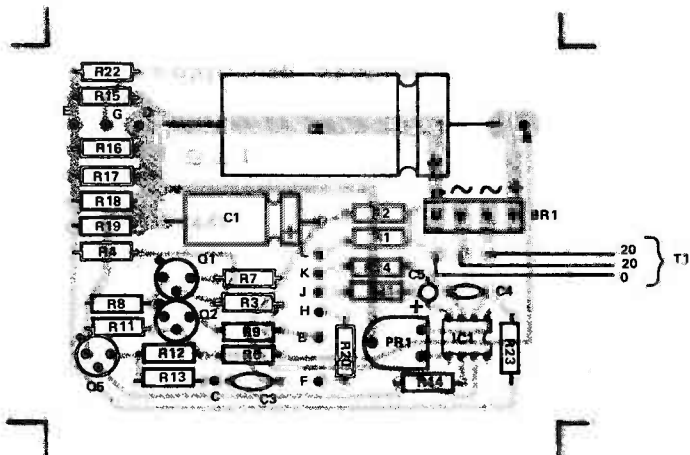


Fig.3 Component overlay for the PCB.

PARTS LIST

Resistors (all 1/4 W, 5% except where stated)

R1	180R, 1 W
R2	82R
R3,6,20	18k
R4,11	1k0
R5	180R
R7	220R
R8	47R
R9	330R
R10	10R
R12	6k8
R13	1k5
R14	2k7
R15-19	0R22, 2W5 wirewound
R21	1k8
R22	100R
R23,24	47k

Potentiometers

RV1	1k0 linear
PR1	10k miniature horizontal preset

Capacitors

C1	470u 25 V axial electrolytic
C2	2200u 63 V axial electrolytic
C3	820p polystyrene
C4	22n ceramic
C5	1u5 35 V tantalum

Semiconductors

IC1	CA3140
Q1,2,5	BC107
Q3	TIP32A
Q4	2N3055
BR1	60 V, 1 A bridge rectifier (in-line type)
D1	16F40
LED1	any red LED

Miscellaneous

LP1	6 V, 60 mA bulb
SW1	mains switch
Transformer	(20-0-20), toroidal core (see Buylines), heatsink (see text), case ref. BA1016, aluminium tube, magnet, sponge.

PROJECT : Soldering Iron

Setting Up


Once all connections are made, the converter section should function immediately — the setting-up procedure only applies to the thermal stabilisation circuitry. The op amp IC1 must be a true zero detector and for that, we must remove any offset voltage. To do so, short-circuit the two inputs (pins 2 and 3) and adjust PR1 until the output starts flickering on and off. Remove the short circuit and the Microstation is now ready for use.

BUYLINES

One of the objectives that we set ourselves at the start of this project was to keep things simple. Although a whole new breed of components specially designed for switched mode supplies is slowly appearing, these are still very difficult to obtain from hobby suppliers. Most of the semiconductors we used are widely available types; D1 can be obtained from Electrovalue.

The toroidal core used for L1 can be obtained from Electro-Tech Components Ltd, 317 Edgware Road, London W2 — the order code is TMC3.

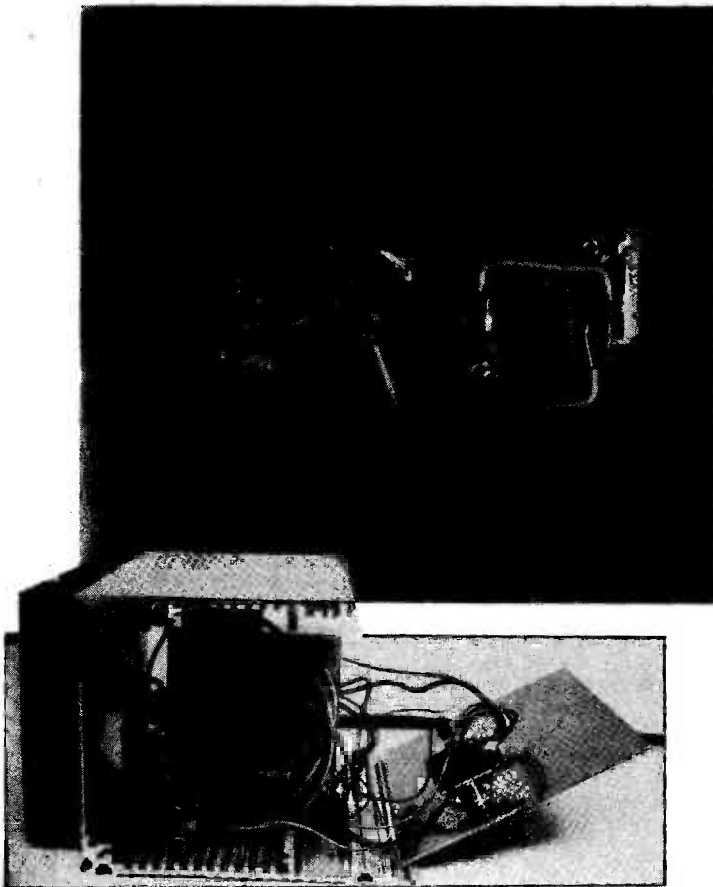The case used for the prototype is a new model from West Hyde and the heating elements can be supplied by most distributors who sell cordless rechargeable irons, eg Marshall's, Electrovalue.



Top: This photograph shows the mounting details of the heatsink components. All these components must be completely insulated from the heatsink by mica washers.

Bottom: Internal view of the case after the interwiring has been completed. The PCB slides into the channels provided.

ETI

Toroidal

TRANSFORMERS

IN A RANGE OF
76
TYPES

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
30VA 70mm dia. x 30mm Weight 0.45 Kg (+£1.20 p.p. + 0.89 VAT)	6+6	2.50	160VA 110mm dia. x 40mm Weight 1.8 Kg (+£1.80 p.p. + £1.60 VAT)	12+12	6.66
1X010	6+6	2.50	5X012	12+12	6.66
1X011	9+9	1.66	5X013	15+15	5.33
1X012	12+12	1.25	5X014	18+18	4.44
1X013	15+15	1.00	5X015	22+22	3.63
1X014	18+18	0.83	5X016	25+25	3.20
1X015	22+22	0.68	5X017	30+30	2.86
1X016	25+25	0.50	5X018	35+35	2.28
1X017	30+30	0.50	5X028	110	1.45
50VA 80mm dia. x 35mm Weight 0.9 Kg (+£1.30 p.p. + 0.97 VAT)	6+6	4.16	5X029	220	0.72
2X010	6+6	4.16	5X030	240	0.66
2X011	9+9	2.77	225VA 110mm dia. x 45mm Weight 2.2 Kg (+£1.90 p.p. + £1.87 VAT)	18+18	6.25
2X012	12+12	2.08	6X014	18+18	6.25
2X013	15+15	1.66	6X015	22+22	5.11
2X014	18+18	1.38	6X016	25+25	4.50
2X015	22+22	1.13	6X017	30+30	3.75
2X016	25+25	1.00	6X018	35+35	3.21
2X017	30+30	0.83	6X028	40+40	2.81
2X028	110	0.45	6X028	110	2.04
2X029	220	0.22	6X029	220	1.02
2X030	240	0.20	6X030	240	0.93
80VA 90mm dia. x 30mm Weight 1 Kg (+£1.50 p.p. + £1.09 VAT)	6+6	6.64	300VA 110mm dia. x 50mm Weight 2.6 Kg (+£2.00 p.p. + £2.14 VAT)	25+25	6.00
3X010	6+6	6.64	7X016	25+25	6.00
3X011	9+9	4.44	7X017	30+30	5.00
3X012	12+12	3.33	7X018	35+35	4.28
3X013	15+15	2.66	7X026	40+40	3.75
3X014	18+18	2.22	7X025	45+45	3.33
3X015	22+22	1.81	7X028	110	2.72
3X016	25+25	1.60	7X029	220	1.36
3X017	30+30	1.33	7X030	240	1.25
3X028	110	0.72	500VA 140mm dia. x 60mm Weight 4 Kg (£2.10 p.p. + £2.77 VAT)	30+30	8.33
3X029	220	0.36	8X017	30+30	8.33
3X030	240	0.33	8X018	35+35	7.14
120VA 90mm dia. x 40mm Weight 1.2 Kg (+£1.60 p.p. + £1.25 VAT)	6+6	10.00	8X026	40+40	6.25
4X010	6+6	10.00	8X025	45+45	5.55
4X011	9+9	6.66	8X033	50+50	5.00
4X012	12+12	5.00	8X028	110	4.54
4X013	15+15	4.00	8X029	220	2.27
4X014	18+18	3.33	8X030	240	2.08
4X015	22+22	2.72			
4X016	25+25	2.40			
4X017	30+30	2.00			
4X028	110	1.09			
4X029	220	0.54			
4X030	240	0.50			

• I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

* CUSTOMER DESIGN ENQUIRIES INVITED.
QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility. (U.K. only).

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.

I.L.P. TRANSFORMERS
A division of I.L.P. ELECTRONICS LTD.
FREEPOST T4 GRAHAM BELL HOUSE ROPER CLOSE
CANTERBURY CT2 7EP
Phone (0227) 54778 Technical (0227) 64723 Telex 965 780

MICROPROCESSORS, MEMORIES, TTL

MICROPROCESSORS

Z80 CPU	6.84
Z80 CTC	4.75
Z80 PIO	4.75
Z80 SIO-0	20.11
Z80 SIO-1	20.11
Z80 SIO-2	20.11
Z80 DART	13.44
Z80 DMA	17.62
Z80A CPU	8.23
Z80A CTC	5.78
Z80A PIO	5.78
Z80A SIO-0	24.17
Z80A SIO-1	24.17
Z80A SIO-2	24.17
Z80A DART	16.13
Z80A DMA	21.02
6800	3.82
6802	5.74
6809	18.94
6810	1.43
6821	1.93
6840	5.87
6850	1.95

MOS MEMORIES

2708 1kx8	
450ns	2.00
2716 2kx8	
450ns	3.85
2114 1kx4	
200ns	2.15
4027 4kx1	
200ns	1.80
4116 16kx1	
150ns	2.00
4116 16kx1	
200ns	1.85

8-BIT CONVERTERS

ZN425E(A/D)	3.50
ZN427E(A/D)	6.28
ZN426E(D/A)	3.00
ZN428E(D/A)	4.78
ZN429E(D/A)	2.10
Data Converter Handbook	1.00

TTL

74LS 00	0.20
74LS 01	0.21
74LS 02	0.20
74LS 03	0.20

TTL

74LS 04	0.21
74LS 05	0.21
74LS 08	0.20
74LS 09	0.21
74LS 10	0.20
74LS 11	0.21
74LS 12	0.21
74LS 13	0.41
74LS 14	0.71
74LS 15	0.21
74LS 20	0.20
74LS 21	0.21
74LS 22	0.21
74LS 26	0.27
74LS 27	0.21
74LS 28	0.25
74LS 30	0.20
74LS 32	0.20
74LS 33	0.25
74LS 37	0.25
74LS 38	0.25
74LS 40	0.20
74LS 42	0.56
74LS 47	0.58
74LS 49	0.86
74LS 51	0.20
74LS 54	0.21
74LS 55	0.21
74LS 73	0.30
74LS 74	0.27
74LS 75	0.42
74LS 76	0.30
74LS 83	0.76
74LS 86	0.26
74LS 90	0.52
74LS 91	1.13
74LS 92	0.56
74LS 93	0.55
74LS 95	0.68
74LS109	0.36
74LS112	0.36
74LS113	0.36
74LS114	0.36
74LS122	0.63
74LS123	0.81
74LS124	1.49
74LS125	0.41
74LS126	0.41
74LS132	0.71
74LS136	0.41
74LS138	0.56
74LS139	0.56

TTL

74LS145	1.06
74LS151	0.49
74LS153	0.49
74LS155	0.70
74LS156	0.70
74LS157	0.50
74LS158	0.56
74LS160	0.61
74LS161	0.61
74LS162	0.61
74LS163	0.61
74LS164	0.71
74LS174	1.06
74LS175	0.84
74LS181	2.10
74LS190	0.85
74LS191	0.85
74LS192	0.97
74LS193	0.97
74LS194	0.58
74LS195	0.58
74LS196	0.96
74LS197	0.96
74LS221	0.90
74LS240	1.41
74LS242	1.19
74LS243	1.19
74LS244	1.18
74LS245	1.69
74LS247	0.57
74LS248	1.05
74LS249	1.05
74LS251	0.64
74LS253	0.64
74LS258	0.56
74LS259	1.61
74LS273	1.37
74LS279	0.51
74LS283	0.63
74LS293	0.73
74LS366	0.54
74LS367	0.54
74LS368	0.54
74LS373	1.11
74LS374	0.70
74LS375	0.70
74LS377	1.37
74LS378	1.03
74LS379	0.78
74LS386	0.41
74LS390	0.96
74LS393	0.85



68
LARGE
PAGES

The larger
Catalogue
that means

FREE POSTAGE
IN U.K.

ADDITIONAL
DISCOUNTS

KEEN PRICES

GUARANTEED
SATISFACTION

GOOD STOCKS

We pay postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

ELECTROVALUE

FREE
FOR THE
ASKING

ELECTROVALUE LTD. (Dept. HE4) 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Telephone: (STD 0784) (London 87) 33603. Telex: 264475

KNOW YOUR ZX80

With LINSAC products for the Sinclair ZX80



THE ZX80 COMPANION
(Second Edition)

NOW ONLY
£7.95

Moulder, Logan and Trotter

ISBN 0 907211 00 3. Price £7.95 incl. UK postage.

This bestselling manual on the Sinclair ZX80 covers ZX80 BASIC, hardware and programs and has a detailed explanation of the ZX80 Monitor, routines and entry points. A routine for generating moving displays is also included.

Ch.1 - Operating the ZX80.
Ch.2 - Theory of Computers
Ch.3 - ZX80 BASIC
Ch.4 - The ZX80 Monitor
Ch.5 - Construction and Hardware
Ch.6 - ZX80 Programs
App.1 - Comparison of Z80 Opcodes and ZX80 Characters.
App.2 - The 8K ROM.

For a cassette of ten programs from the Companion add £4.95.

The ZX80 Monitor. A complete assembly language listing of the ZX80's 4K Monitor, with annotation is - Price £5.95 incl. UK postage

Cassette Software

All LINSAC program packs are on single C12 cassettes with printed run instructions. All run on 1K ZX80's unless otherwise stated. Price £7.95 per pack incl. UK postage.

GAMES PACK 1	- Three Towers, Number Guessing, Mastermind, Sketcher, Hurtle, Nim, Symbol Simon
GAMES PACK 2	- Nine Lives, The Maze Game, Plain Sailing, OXO, Chinese Puzzle, Tower of Hanoi, Battleships
GAMES PACK 3	- (2K+) - Fruit Machine, Four in a line, Zombes
EDUCATION PACK 1	- Maths Drill, Dot Recognition, Musical Notes, Spelling Quiz, Day Finder.
EDUCATION PACK 2	- Graph Plotter, Prime Factors, Number Bases, Bar Charts, Statistics.
EDUCATION PACK 3	- (2K+) - CAL Quiz Package with three sample data sets
UTILITY PACK 1	- Memory Display, Hex Code Monitor, Renumber, Memory Search

LINSAC

68 Barker Road, Linthorpe,
Middlesbrough, Co. Cleveland TS5 5ES

All devices brand new, full spec. and fully guaranteed. Please add 15% VAT (and 50p post and packing on orders under £10). All orders despatched by return of post. E.&O.E.

MIDWICH

Computer Co. Ltd., Hewitt House
Northgate Street, Bury St. Edmunds
Suffolk IP33 1HQ
Tel: (0284) 701321 Telex: 817682

Home-built amplifiers are very popular and this month Kit Review takes a look at one of the cheapest.



The subject of Kit Review this month is the RTVC IC 10+10 amplifier, which at £14.95 must be the cheapest stereo amplifier you can buy. The finished amp features 10 W RMS output per channel, three inputs (MIC, PU and AUX) and bass and treble tone controls. The volume of each channel is varied by independent slider pots on the front panel; the tape output level has similar controls. Push-buttons are provided for mute, mono and a 'disco' function, which converts the power amps to mono operation and the preamplifier to a two-channel mixer (so that two mono record decks, for example, may be faded in and out independently). A pre-punched chassis is included in the kit, with a black vinyl finish cover.

Starting Out

As with any kit, the first thing to do is check that all the parts are present (they were) and read the instructions thoroughly. This caused my confidence in RTVC to flag slightly, as, despite their assurances, there are several errors. The colour code for a 1R0 resistor is brown-black-gold, not brown-black; 6k8 is blue-grey-red, not blue-grey-blue; and D2 is shown the wrong way round on the circuit diagram.

It is also disconcerting to discover that three holes in the chassis have to be redrilled because they're in the wrong place, and the power amp PCB has to be drilled. I would have thought that, on the whole, a kit like this is more likely to be bought by the beginner or less experienced constructor who is unlikely to own a PCB drill. I don't recommend using a domestic drill; I tried it with the first PCB I made myself and ended up with two halves. Slapped wrists, RTVC.

As well as a PCB drill, you might find a solder sucker handy as well. Two components on the preamp (a Mullard module) have to be removed and replaced with different values. Take care when you do this as the PCB tracks are thin and can lift off.

Power Amp

Once the board had been drilled, the construction of the power amp presented no problems, except that the diodes are marked on the overlay with a '+'; I would have preferred to see


'anode' or 'cathode' which is less ambiguous. The overlay is a photographic one and fairly clear. Lengths of wire should now be soldered for all connections (except the inputs) as these solder directly to the foil side of the board, which is inaccessible once the board has been mounted. A good point about this kit is that power ICs are used which make construction a great deal easier than if power transistors were used.

Preamp And Controls


I found this part of the kit very tedious and fiddly. Being basically lazy I hate interwiring, and there's a lot of it in this kit. The best method is to fit the lower switch bank and the slider pots to the front panel first — interconnect them and solder generous lengths of wire where appropriate for connections elsewhere in the chassis. Note that some of the links between pins on the switches can be made on the underside as the pins go right through; otherwise things get a bit cramped. Then mount the top switch bank and the DIN input sockets on the rear panel and complete that part of the wiring. Finally, solder lengths of wire to all the rotary pot pins (including the two cross-connections) before mounting them on the front panel. Once they're in place you can complete all the connections to the preamp and fit cable ties to keep things neat. Wirestrippers are essential to prevent damage to your fingers and/or sanity.

Rearguard Action

Before bolting the power amp to the chassis, the signal earth lead from the front panel switches should be cut to length and soldered to the copper panel side of the board. The board is held in place by the ICs which should *not* be insulated from the chassis — this acts both as a heatsink and the negative supply connection. The input connections from the switch bank can now be soldered directly to the leads of the input resistors. Fit-

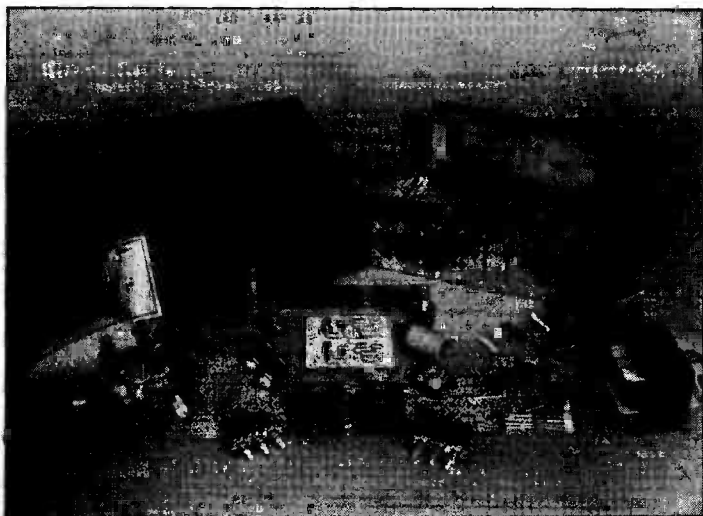

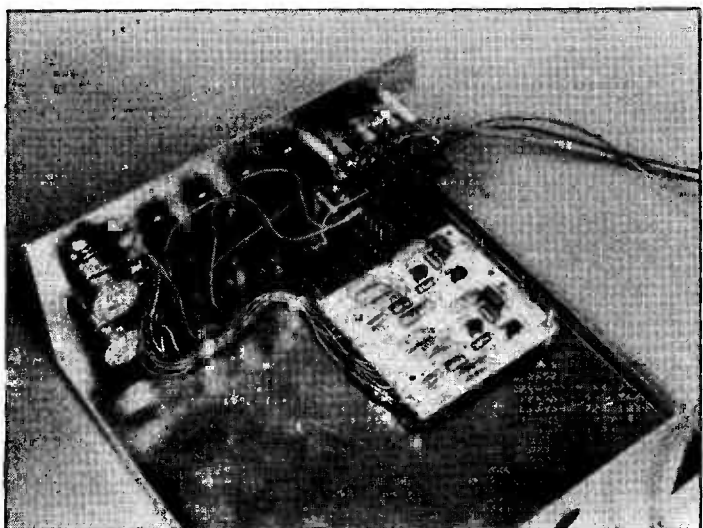This is what you get in the kit. What you *don't* get includes connecting wire, mains lead and a mains switch. The preamplifier is supplied as a ready-built module.




Halfway home and the worst is over. As you can see, the amount of interwiring required is extensive. The section shown corresponds to the instructions below.

ting the remaining rear panel sockets proved a trial of strength, as the retaining rings are very stiff! The photograph showing the output connections is a bit indistinct and reference to the main circuit diagram for clarification revealed another mistake — the pins on the headphone socket are incorrectly numbered. I finally solved the problem by assuming the wiring was symmetrical.


Finishing Off

The final bits to fit are the fuseholder, rectifier, transformer and mains switch — you have to provide the latter yourself as RTVC describe it as optional. I would have thought it was essential. After making the power supply connections and completing the case construction the amp is ready to go. The instructions do not say anywhere that the mains earth lead should be bolted to the chassis — this is a serious omission considering the large amount of bare metal on the chassis.

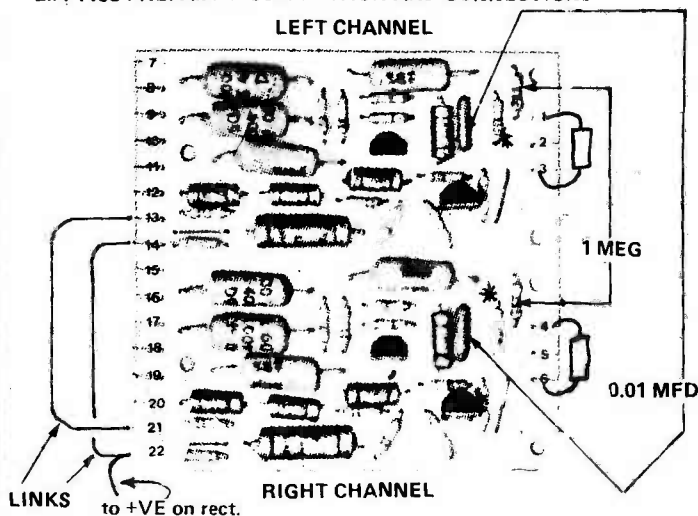
L.P. 1183 PRE. AMP MODIFICATION AND CONNECTIONS



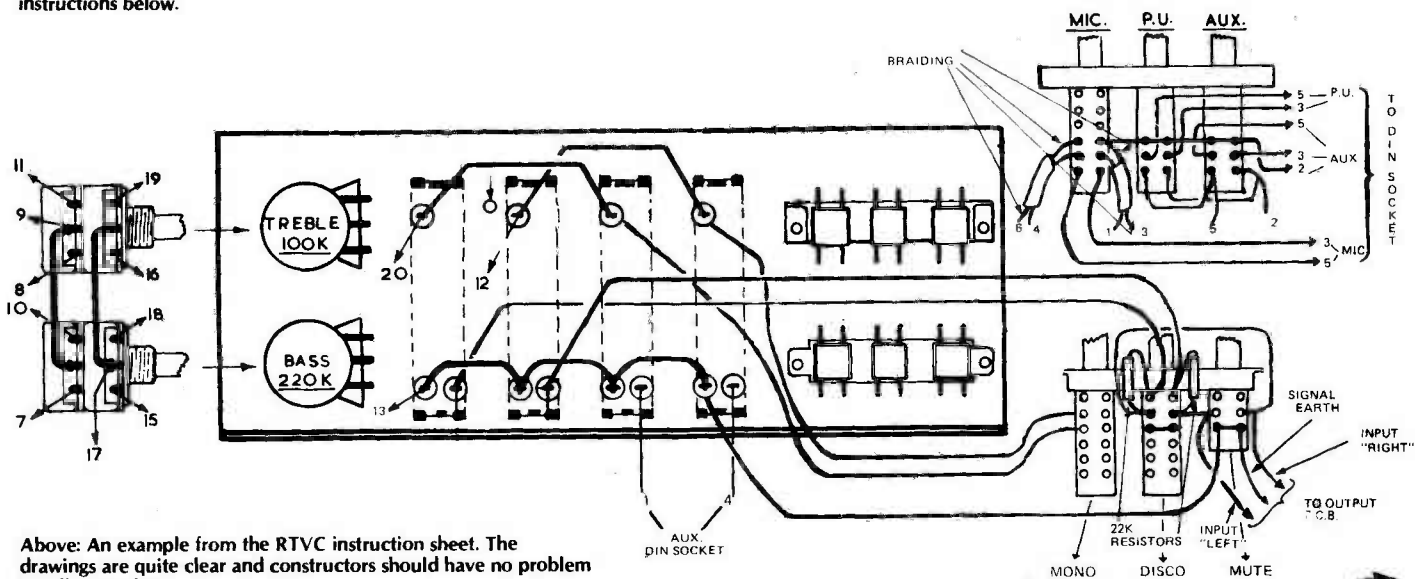Above: Several component changes are required on the preamp module.



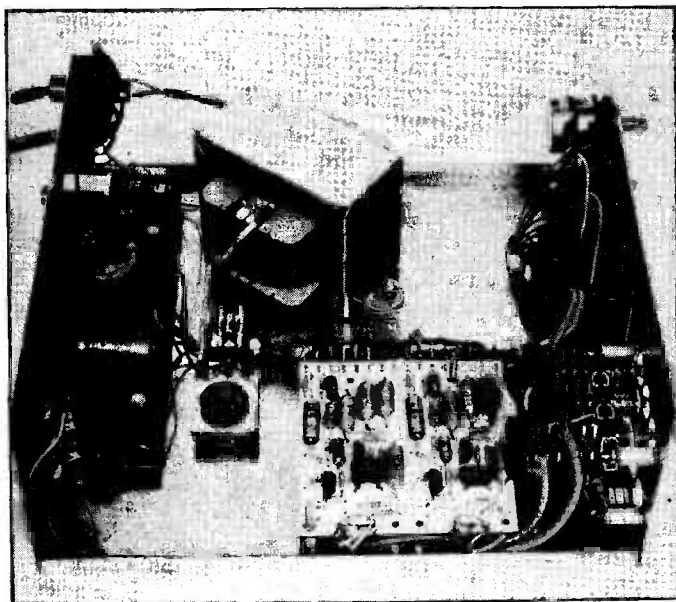Above: An example from the RTVC instruction sheet. The drawings are quite clear and constructors should have no problem in following them.



Everything in place and ready for testing. All the sockets mount on the rear panel — three inputs, DIN loudspeaker sockets and a headphone socket. Inserting the headphones automatically mutes the speakers (provided you got the wiring right!). The power ICs bolt directly to the rear panel too, so that the chassis provides both heatsink and earth return; but make sure you connect the mains earth too.

In Use

The amplifier worked perfectly first time; and even the office audiophile admitted that the kit represented good value for money. Some hum is evident when no signal is present but this is not noticeable when you're actually playing music. Having already built the '12 + 12' kit which this amplifier replaces, I feel that the new version offers a definite improvement in layout, appearance, ease of construction and sound quality. Although the kit took me eight hours to complete, this was partly due to double-checking the errors in the instructions and partly to deciding the best approach to adopt — I'm sure I could build a second one in half the time.

I have contacted RTVC regarding the errors and await their reply, which will be published in Digest next month.

Conclusions

For the price involved this kit represents a good buy (I once built a homebrew power amp with tone controls from discrete components that cost me £20). However, the kit would probably appeal more to the beginner in electronics and so the errors in the instructions and the need to drill the PCB are definite minus points. As RTVC suggest in the instructions, having a friend who is familiar with electronics is a good idea if you should need any help.

PETER GREEN

BUYLINES

10 + 10 Watt Stereo Amplifier Kit £14.95 plus £2.90 postage and packing. RTVC, 323 Edgware Road, London W2. Telephone: 01-723 8432.

ETI

Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately twelve issues and is attractively bound and blocked with the ELECTRONICS TODAY INTERNATIONAL logo.

Price U.K. £3.95 including postage, packing and V.A.T., overseas orders add 30p. Why not place your order now and send the completed coupon with remittance to:-

EASIBIND LTD., 4 UXBRIDGE STREET,
LONDON W8 7SZ. Tel: 01-727 0686

Please allow 3/4 weeks for fulfillment of order.

it's easy with **EASIBIND**

Easibind Ltd., 4 Uxbridge St., London, W8 7SZ.

Nat. Giro No. 5157552.

Order Form

ELECTRONICS TODAY INTERNATIONAL

I enclose p.o./cheque value

for binders

Years required

BLOCK LETTERS PLEASE

Name


Address


.....

.....

Date

Registration No. 307469

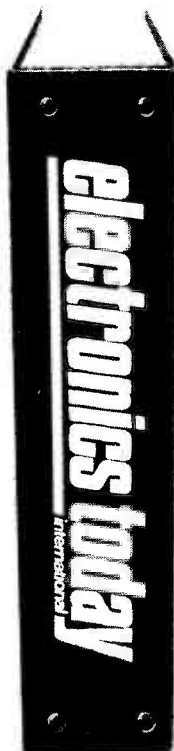

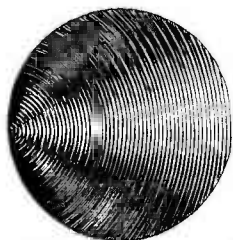


thandar
STOCKIST

B.K. ELECTRONICS

A SOUND CHOICE

thandar
STOCKIST

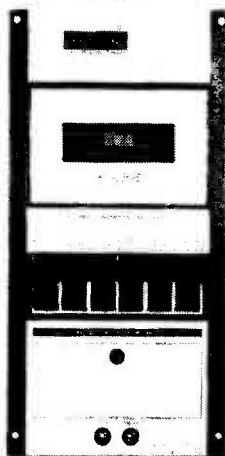★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY




6 piano type keys

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram.

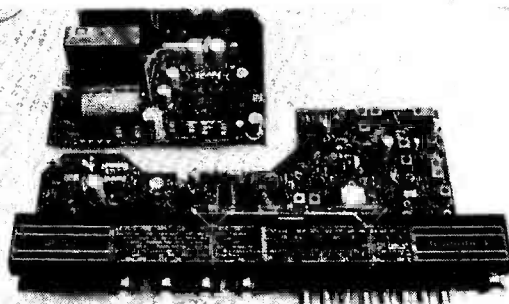Price £25.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.00.



GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3dB.

Tape Sensitivity: Output - typically 150 mV. Input - 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz - 108MHz. Long wave 145kHz - 108kHz. Medium wave. 520kHz - 1620kHz. Short wave. 5.8MHz - 16MHz. **Size:** Tuner - 2 3/4" x 15" x 7 1/2" in approx. Power amplifier - 2" x 7 1/2" x 4 1/2" in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £23.50 plus £2.50 postage and packing.**

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Price:-**

15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5kHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz. magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4kHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohm, 20 oz. magnet, 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6kHz. Sensitivity 92dB. **Price £8.90 each.** £1.25 Packing and Carriage each.

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.45 each.**

Type 'B' 3 1/2in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**

Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**

Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £6.90 each.** Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

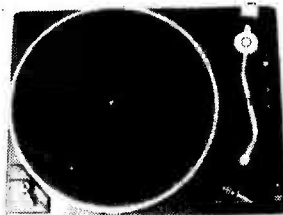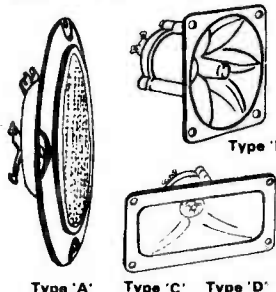12" 80 watt R.M.S. loudspeaker. A superb general purpose twin cone loudspeaker. 50 oz. magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 9kHz. Sensitivity 95dB. **Attractive blue cone with aluminium centre dome.** **Price £16.49 ea x £2.50 P&P.**



JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.


- ★ 'S' shaped tone arm.
- ★ Belt driven.
- ★ Full size 12in platter.
- ★ Precision calibrated counterbalance weight (0-3 grms.)
- ★ Anti-skate (bias) device. Nylon thread weight.
- ★ Damped cueing lever.
- ★ 240V AC operation, (50Hz).
- ★ Cut-out template supplied.
- Size - 12 3/4" x 15 3/4" (approx).
- Price £28.50 plus £2.50 postage and packing.**

FIRE ALARM CENTRAL CONTROL UNIT (S.T.C.)

Ideal for Fire or Burglar Alarm Systems

- ★ Responds to normally open or closed switches (or smoke detectors etc.)
- ★ Complete w/ltb an internal EXIDE lead acid accumulator (dry charged) as a back-up for mains failure. This is trickle charged.
- ★ 6v-2 amp output for Fire/Burglar alarm, etc.
- ★ Re-set button for silencing Fire/Burglar alarm.
- ★ Internal buzzer which sounds if re-set button if pressed until initiating switch is cleared.
- ★ Wall mounting, complete with red case, approx. 11" x 7 1/2" x 4".
- ★ 240v AC operation.
- Price 18.50 + £3 postage and packing.**

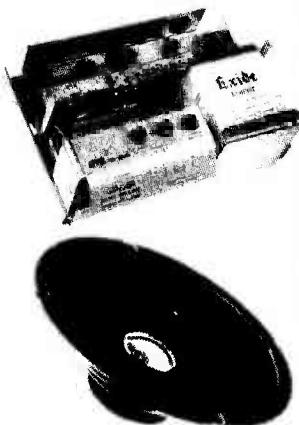LOUDSPEAKER
High quality full range 8in loudspeaker. 10 watts RMS, 8ohm. Rolled surround with aluminium centre dome. **Price £3.75 each plus £1.00 Postage and Packing.**




B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



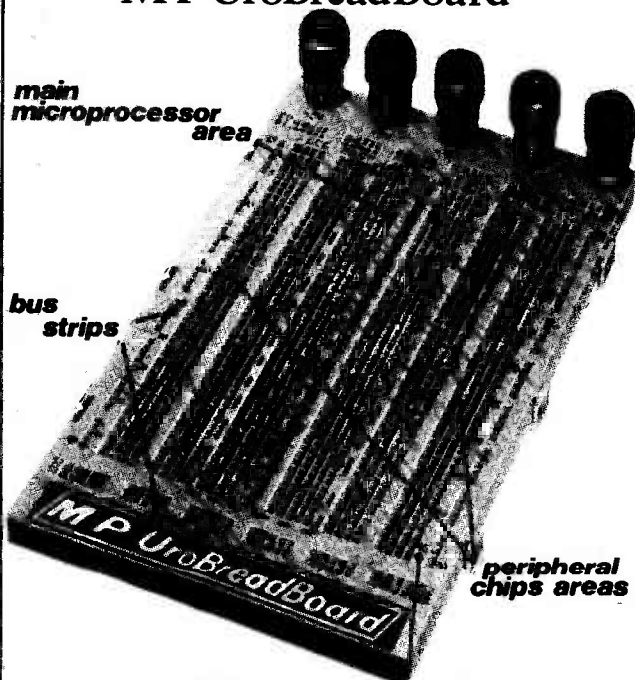If you're into
MICROPROCESSORS
 then they should be into an
MP UroBreadBoard



alpha numeric indexing

- * MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- * Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- * Power Bus Strips on all sides
- * 5 incoming turret Power Terminals
- * Component Support Bracket included
- * Over 1400 contact points
- * Alpha-Numeric column and row indexing
- * Eurocard size (160mm x 100mm)
- * Slots onto all BIMBOARDS
- * Non-Slip rubber backing
- * Ideal for schools and colleges
- * Long life, <10m.ohms, nickel silver contacts

The **PROFESSIONALS** breadboard
 that **BEGINNERS** can start on

BOSS INDUSTRIAL MOULDINGS LTD

2 Herne Hill Rd, London SE24 0AU, England
 Telephone 01-737 2383 Telex 919693
 Cables & Telegrams: LITZEN LONDON SE24

Please send me MPUroBreadBoard(s) @ £18.
 This price includes VAT & PP, is applicable from Mar. 1, '81,
 but please add 15% for Overseas Orders, make cheques/P.O.
 payable to BOSS Industrial Mouldings Ltd and allow 10 days
 for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £.....

Name'
 Company
 Address

 Telephone Number ETI/5/81

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED
 Die pressed case, Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite
 HIGH PERFORMANCE
 ELECTRONIC IGNITION

Electronics Design Associates, Dept. ETI/5
 2 Bath Street, Walsall, WS1 3DE
 Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REDD

I enclose cheque/PO's for

X5 KIT £16.95

£

Cheque No.

ACCESS OR BARCLAY CARD No.

Send SAE if brochure only required.


ELECTRONIC GAMES

COLOUR CARTRIDGE T.V. GAME



SEMI-PROGRAMMABLE T.V. GAME
+ 4 Cartridges + Mains Adaptor
Normal Price £73
NOW REDUCED TO: £39.50
inc. VAT

DATABASE T.V. GAME

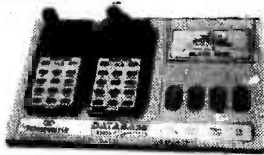

FULLY PROGRAMMABLE CARTRIDGE T.V. GAME
14 Cartridges available
Normal Price £87.86
NOW REDUCED TO: £59
inc. VAT

ATARI T.V. GAME




The most popular T.V. Game on the market with a range of over 40 cartridges including SPACE INVADERS with over 112 games on one cartridge.
£98.50
inc. VAT

SPACE INVADERS



Hand-held Invaders Games available £19.95
+ Invaders Cartridges available to fit ATARI/RADOFIN/ACETRONIC/PHILIPS G7000
+ Cartridges also available for MATTEL/TELENG/ROWTRON/DATABASE/INTERTON

CHESS COMPUTERS

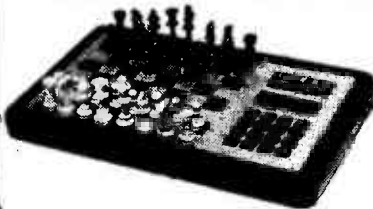

We carry a range of over 15 different Chess computers:
Electronic Chess £29.95
Chess Traveller £49.95
Chess Challenger 7 £79.00
Sensory 8 £119.00
Sensory Voice £259.00
SPECIAL OFFERS:
VOICE CHESS CHALLENGER
Normal Price £245 NOW £135.00
SARGON 2.5/BORIS 2.5
Normal Price £273.70 NOW £199.95
All prices include V.A.T.

TELETEXT



ADD-ON ADAPTOR £199


THE RADOFIN TELETEXT ADD-ON ADAPTOR

Plug the adaptor into the aerial socket of your colour T.V. and receive the CEEFAX and ORACLE television information services.

THIS NEW MODEL INCORPORATES:

- Double height character facility
- True PAL Colour
- Meets latest BBC & IBA broadcast specifications
- Push button channel change
- Unnecessary to remove the unit to watch normal TV programmes
- Gold-plated circuit board for reliability
- New SUPERIMPOSE News Flash facility

SPEAK & SPELL

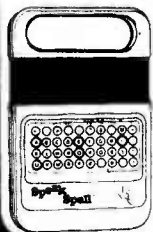

Normal Price £49.95
NOW REDUCED TO:

£39.50 inc. VAT

Teach your child to spell properly with this unique learning aid. Fully automatic features and scoring. Additional word modules available to extend the range of words.

ADDING MACHINE OLYMPIA HHP 1010




Normal Price £57.21
NOW REDUCED TO:

£34 inc. VAT

Uses ordinary paper!
No need to buy expensive thermal paper!
Fast add listing PRINTER/CALCULATOR. 2 lines per second, 10 digit capacity. Uses normal adding machine rolls. Battery or mains operated.
Size 9 1/4" x 4 1/4" x 2 3/4"
(Mains adaptor extra)

24 TUNE ELECTRONIC DOOR BELL

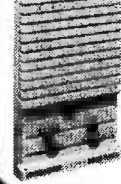

Normal Price £19.70
NOW REDUCED TO:

£12.70 inc. VAT

Plays 24 different tunes with separate speed control and volume control. Select the most appropriate tune for your visitor, with appropriate tunes for different times of the year!

MATTEL T.V. GAME




The most advanced T.V. game in the world 20 cartridges available. Add-on KEYCARD coming **£199.95** inc. VAT
MATEL to a home computer with 18K RAM, fully expandable and programmable in Microsoft Basic. Other accessories will be available later in the year.

THE OLYMPIA — POST OFFICE APPROVED

TELEPHONE ANSWERING MACHINE

WITH REMOTE CALL-IN BLEEPER

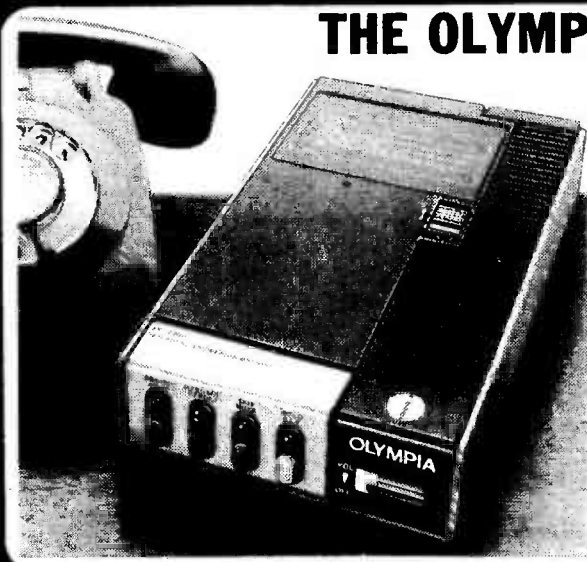


This telephone answering machine is manufactured by Olympia Business Machines, one of the largest Office Equipment manufacturers in the U.K. It is fully POST OFFICE APPROVED and will answer and record messages for 24 hours a day. With your remote call-in bleeper you can receive these messages by telephone wherever you are in the world. The remote call-in bleeper activates the Answer/Record Unit, which will at your command repeat messages, keep or erase them, and is home or office. The machine can also be used for message referral, if you have an urgent appointment, but are expecting an important call, simply record the 'phone number' and location where you can be reached. With optional extra beepers (£13 each) this facility can be extended to colleagues and members of the family. Using a C90 standard cassette you can record as many as 45 messages. The announcement can be up to 16 seconds long and the incoming message up to 30 seconds long.

£135 inc. VAT

The machine is easy to install and comes with full instructions. It is easily wired to your junction box with the spade connectors provided or alternatively a jack plug can be provided to plug into a jack socket. Most important, of course, is the fact that it is fully POST OFFICE APPROVED.

The price of £135 (inc. V.A.T.) includes the machine, an extra-light remote call-in bleeper, the microphone message tape, A/C mains adaptor. The unit is 9 1/4" x 6 1/2" x 7 1/2" and is fully guaranteed for 12 months. The telephone can be placed directly on the unit — no additional desk space is required.

FOR FREE BROCHURES — TEL: 01-301 1111

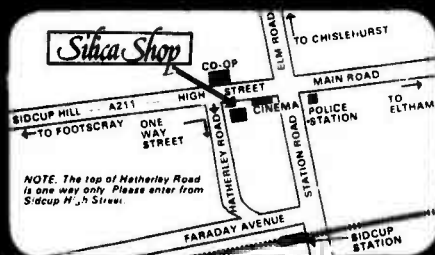

For free illustrated brochures and reviews on our range of electronic games, please telephone 01 301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/BARCLAYCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48hr delivery service available.


- CALLERS WELCOME — Demonstrations daily at our Sidcup shop, open from 9am-6pm, Monday-Saturday (Early Closing Thursday 1pm - Late evening Friday 8pm)
- 2 YEAR GUARANTEE — All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee.
- MONEY BACK UNDERTAKING — If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.
- AFTER SALES SERVICE — Available on all machines out of guarantee.
- CUMULATIVE PRICES — we are never knowingly underbid.
- HELPFUL ADVICE — Available on the suitability of each machine.
- CREDIT FACILITIES — Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
- PART EXCHANGE SCHEME — available on 2nd hand machines.
- CREDIT CARDS WELCOME — Access, Barclaycard, Dinners Club, American Express

SILICA SHOP LIMITED Dept. ET15

1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX
Telephone: 01-301 1111 or 01-309 1111

SILICA SHOP

SYNTHESISER SEQUENCER

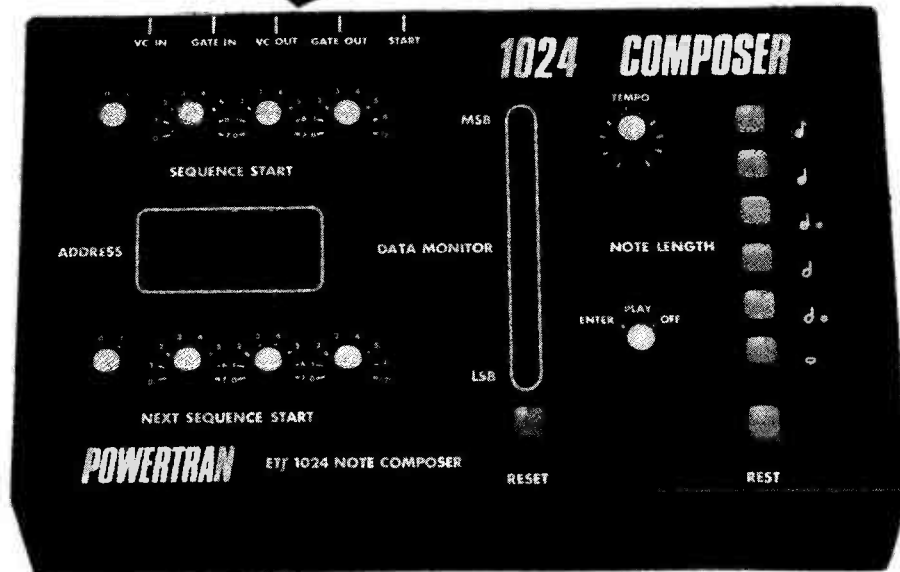

Treat your synth to this sequencer/composer and let it play sequences of up to 1024 notes. Design by Richard Becker of Powertran Electronics.

The 1024 composer is a machine which will repeatedly cause a synthesiser to play a pre-determined series of notes either as short sequences or a large composition of 1024 notes, ie several minutes long. The sequence can be of any number of notes from two to 1024. If the length is less than 1024 then the unused sections of the memory of the composer can be used for alternative sequences as there is full control over the starting and finishing points of the sequence. For example, 64 different 16-note sequences or 128 different eight-note sequences could be stored. The address of the note being played or entered is shown clearly on four seven-segment LED displays whilst the address at the beginning and end of the sequence selected are indicated by the position of the rotary switches which set them up.

The memory stores not only the pitch of the notes but also their length. There is a choice of six lengths ranging from half a beat to four beats. In addition, a rest or series of rests of one beat can be entered.

Socket To Me

The composer is programmed from the synthesiser by plugging into the VOLTAGE CONTROL OUT and GATE OUT sockets, Transcendent 2000 owners needn't feel left out! You can easily add a couple of jack sockets to the rear panel of the 2000 and fit three bits of wire; VC OUT to IC6 pin 6, GATE OUT to IC4 pin 6 and common line to common line on the HI OUT socket. As for any other synths without these sockets, if the handbook mentions 1 V/octave (the standard) you will be able

to find the control voltage at the input of the VCO and the gate voltage at the input of the ADSR. The synth control voltage is converted to a digital code by an integrated A-to-D (analogue to digital) converter. An integrated D-to-A converter does the opposite on playback.

The outputs of the composer plug into the EXT VC IN and EX GATE IN sockets of the synth. Provision is made for the gate voltage to be of either polarity depending on the synth's requirement (the Transcendent 2000 requires a negative gate voltage). A synth usually sounds at its best when the filter is tracking with the VCO. If there is a control input for the VCF put the control voltage into here too. If there is no such socket it will be possible to find a suitable point on the VCF to inject the control voltage. On the Transcendent 2000 take VC IN to Q10 pin 12 via a 43k resistor.

Musical Memories



Now that we are plugged in, one of the note length switches is pressed. Pressing a key now programs in that note's pitch and length. To enter a rest, ie an interval with no note being played, press the rest switch followed by any key as many times as there are beats in the rest period.

It doesn't matter how long you take between entering notes. Go down to the pub in the middle of your composition if you like; it will still play back with perfect timing. What's more it doesn't matter if there's a power cut or anyone pulls out the plug while you're away. Hands up all those of you who have lost a painstakingly entered computer program that way! The com-

poser, though mains powered, has a trickle charged Nickel-Cadmium battery to supply the memory (which uses a pair of CMOS 4K synchronous RAMs) when there's no mains connected. After switch-off the memory will retain the data for months and will change only when reprogrammed. Should you find that you have entered a bum note — no hassle. Just advance the START-OF-SEQUENCE switches to the offending entry, press RESET, enter the correct note/note length combination. Take the address to where you left off, press RESET and carry on.

Construction And Setting Up

The PCB is double-sided so start by linking the two sides with link pins, soldered to both sides, at the points indicated by black dots on the overlay. Now fit everything else except the displays. The tempo potentiometer is soldered to the side of the board which its pins enter. Mica washers are required under the 7915 and the 7815 to prevent shorting to the tracks. To fit the displays at the correct height above the board, stretch some 22 swg wire to stiffen it, cut 46 2" lengths and bend through 90° the last 3 mm of each one. Lay a 10 mm thick spacer bar across IC11-14 and lay the displays onto the spacer. Pass a wire through each hole in the displays and down into the PCB, solder the bent ends to the display, turn over the PCB, trim off the excess wire and solder in place. The photographs should make this clear.

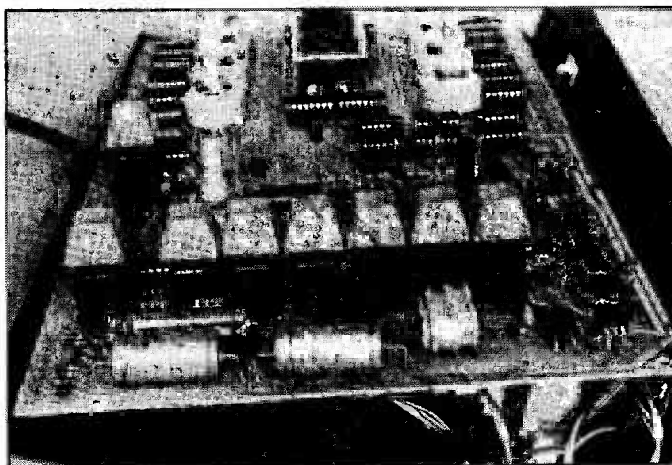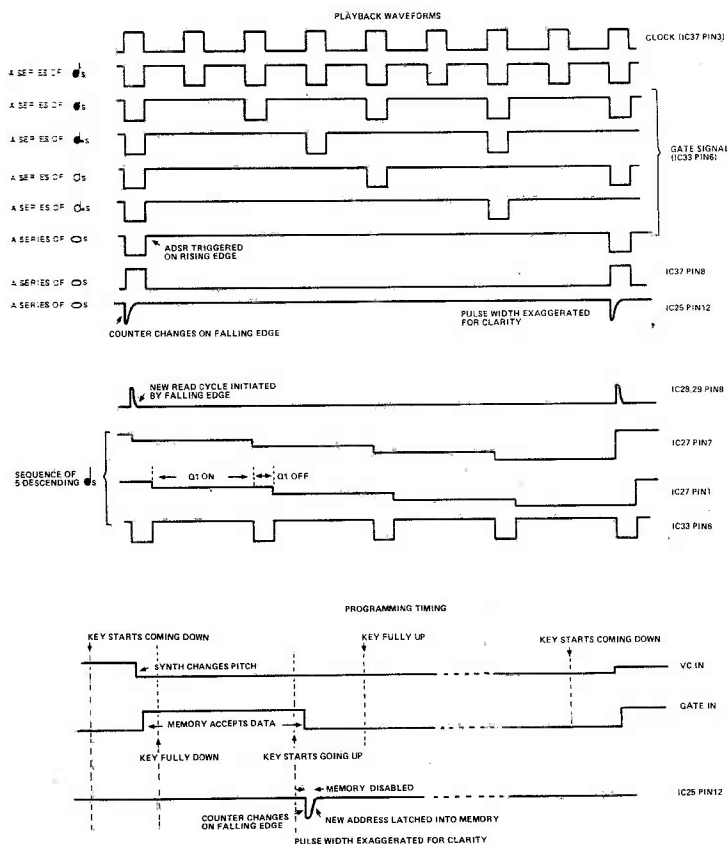

Above and below: All the switches except the start switch mount directly on the PCB. The photograph below also shows the mounting details of the display.


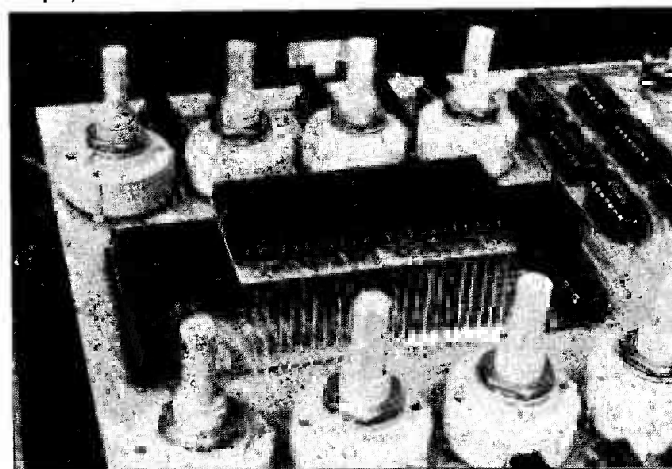


Fig.1 Waveforms at various points in the circuit during playback and programming.

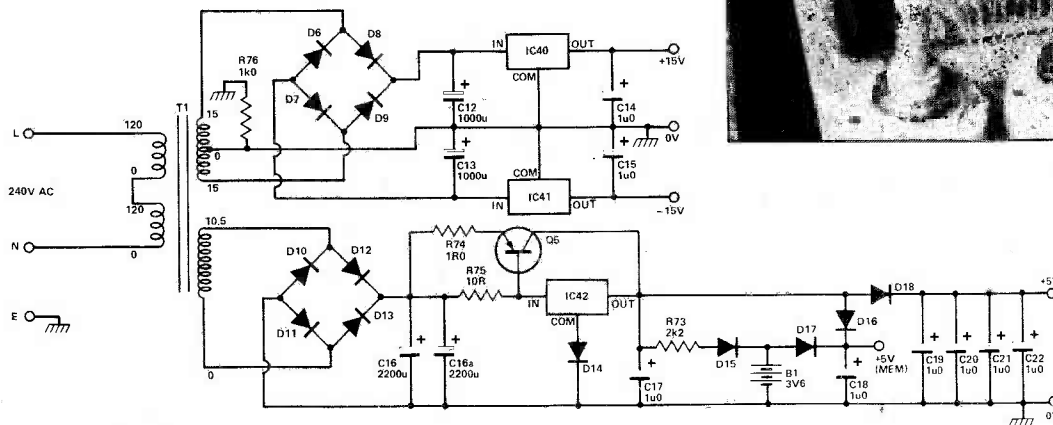

NOTE:
IC40 IS 7815
IC41 IS 7915
IC42 IS 7805
D5 IS TIP30A
D6-14, 18 ARE 1N4002
D15-17 ARE 1N4148

Fig.2 Circuit diagram for the power supply. Note that R76 (not given in the Parts List) solders directly to the mains transformer. See Fig.4.

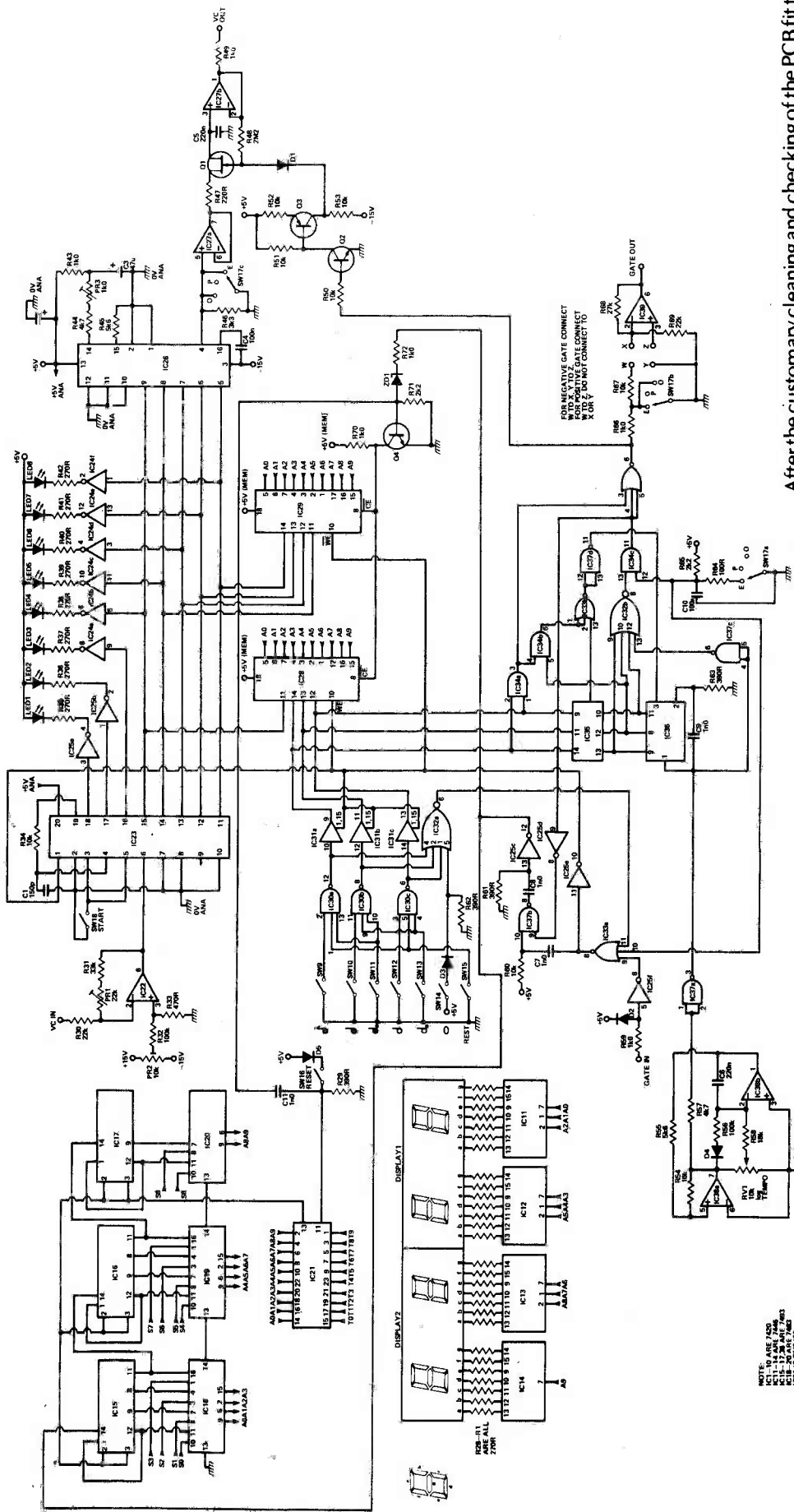


Fig.3 Circuit diagram of the composer. The binary encoding circuitry for the switches is shown below.

BUYLINES

A complete set of parts for this project including fully finished metalwork, nuts, bolts etc will be available from Powertran Electronics for £89.50 + VAT, post free. For delivery by Securicor add £2.50 (VAT inclusive). Powertran also supply separate parts eg. metalwork set, PCB etc — telephone Andover 64455 or write to: Powertran Electronics, Portway Industrial Estate, Andover, Hants, SP10 3NM.

After the customary cleaning and checking of the PCB fit to the cabinet, wire up the base/rear panel, set the presets to midway and plug in. Switch to ENTER, press a NOTE LENGTH switch and the START switch together with any key. This starts the ADC converting and is done at each switch-on. Press the top note of the keyboard together with any NOTE LENGTH switch and adjust the input offset null preset (PR2) until the red LEDs are all off, whilst the green LEDs (indicating the three least significant bits which are not stored) show either binary 3 (011), ie bottom two LEDs on, or binary 4 (100), ie the third one up on. The LEDs may flicker between these states. Next press the key two octaves down and adjust the gain control PR1 so that only the top two of the red LEDs are on whilst the green ones again show binary 3 or 4. This ensures that the ADC is halfway between changing the code given by the five most significant bits.

NOTE: IC1 AND IC2 ARE 74181 AND 74180 RESPECTIVELY. IC3, IC4, IC5, IC999, IC1000.

HOW IT WORKS

The voltage control input (pitch data) is applied via IC22 to the A-to-D converter IC23 which produces an eight-bit binary code equivalent to the pitch voltage. C1 and R34, in conjunction with an internal Schmitt trigger, form the internal clock operating at a few hundred kilohertz. All eight bits are monitored by LEDs, driven by IC24 and IC25a and b, although only the five most significant bits are used. These go on a data bus connecting to the memory and the D-to-A converter IC26, the reference current for which enters pin 14. The quantized current from pin 4 generates a voltage across R46. Q1, C5, IC27b form a sample and hold circuit, controlled by the output gate signal. This permits a change in pitch only at the same time as the gate pulse starts. The output of IC26 changes a clock phase earlier.

IC1-10 encode the addresses set up on SW1-8 to the equivalent 10-bit binary codes. IC15-17 form a binary counter which is reset to all zeros at suitable times by the output of IC21. IC18-20 are binary adders which add the output of the counter to the output of IC1-5 to produce the address code for the memory. Thus when the counter is reset, the memory address is that set up by the START OF SEQUENCE switches SW1-4. The outputs of IC6-10 are compared with the memory address by the 10-bit comparator IC21 — a reset signal is generated when they are the same, so the sequence is finished and goes back to the start. The seven-segment displays are driven by the decoders IC11-14 which are connected to the memory address bus.

When entering data the counter is clocked by the gate pulse applied via IC25f, IC33a, IC37b, IC25c. Assuming the synth to be correctly adjusted with the pitch voltage changing before the gate signal is produced, the pitch voltage changes when a key goes down and the ADC generates the appropriate code. The gate signal then puts the memory into the write mode and enables the tri-state buffer IC31 and the ADC, entering the ADC data and the note lengthrest data from IC30, IC31 into the memory. As the key is released the gate signal ceases, the memory is returned to the read mode and the buffer and ADC are disabled. The end of the gate signal results in a negative pulse from IC25c pin 12. On its negative going edge the counter adds one to the address. The pulse is also applied via Q4 to pin 8, the enable input of the memory, briefly disabling it. As pin 8 returns to 0 V the new address is latched in. The base of Q4 is also connected to the reset circuit so that the latched-in address is updated when the counter is reset.

IC38 is an asymmetric relaxation oscillator producing a 1:2 mark/space ratio pulse at IC37 pin 3, the negative edge of which clocks the divide-by-eight counter IC36. During playback the output of IC36 is compared with the note lengthrest data by four bit comparator IC35. When there is equality IC35 pin 6 goes high and is applied to one of the two reset pins of IC36 via IC33b, IC37d. When the clock returns to high the other reset pin (pin 2) also goes high, resetting the counter. The counter therefore counts as far as the binary code from the memory, stays there for one phase of the clock and resets to zero. The all-zeros state of the counter is detected by IC32b, the output of which clocks the address counter. The clock (inverted) is applied to IC32 pin 13 to restrict its output to a single clock phase when the counter receives no reset ie when the note length is four beats and the memory reads out all zeros. The output of IC32b becomes the gate signal after passing through IC33c, which inhibits the gate when data '1X1' is detected by IC34a ie when there is a rest (101 programmed in). The counter is reset after two clock pulses by the output of IC34b. When there is a mains supply the logic receives 5 V via D18, the memory receives 5 V via D16 and the battery is charged via D15. D14 raises the output of IC42 from 5 V to about 5V6 to compensate for the drops across D16, D18. When there is no mains supply the logic is shut down but the memory still gets 3 V from the battery via D17. As the logic is all down Q4 turns off, disabling the memory so that only microamps are consumed.

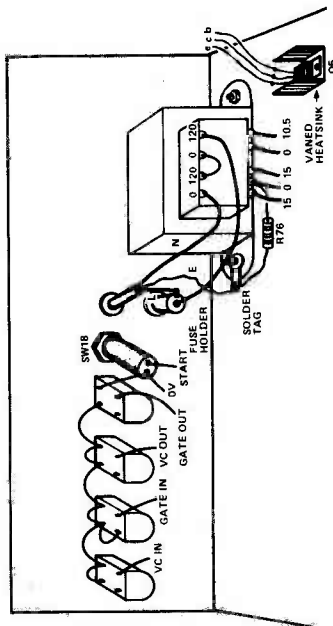
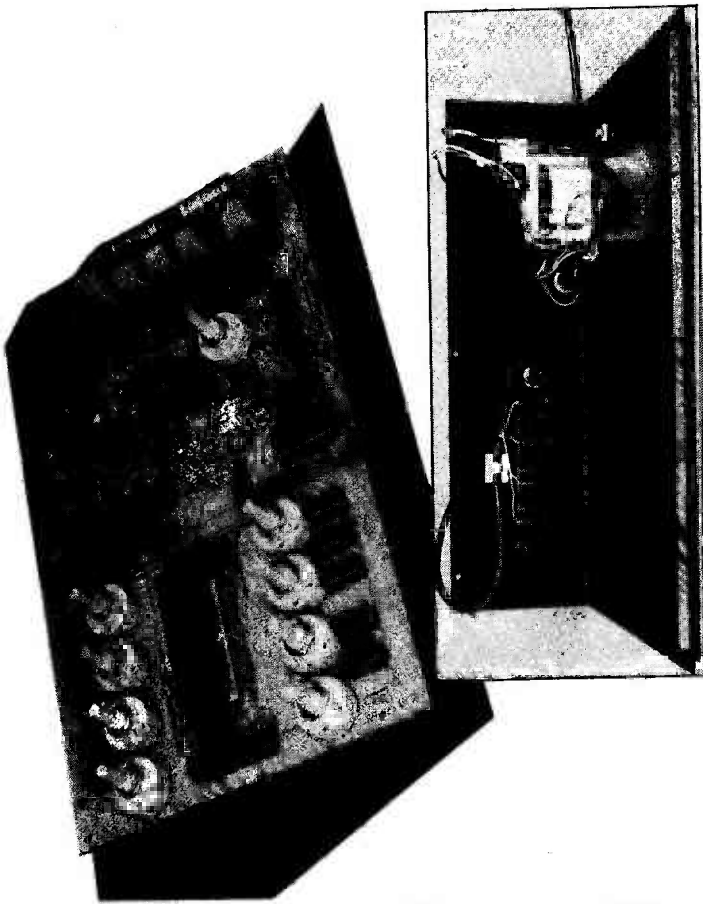
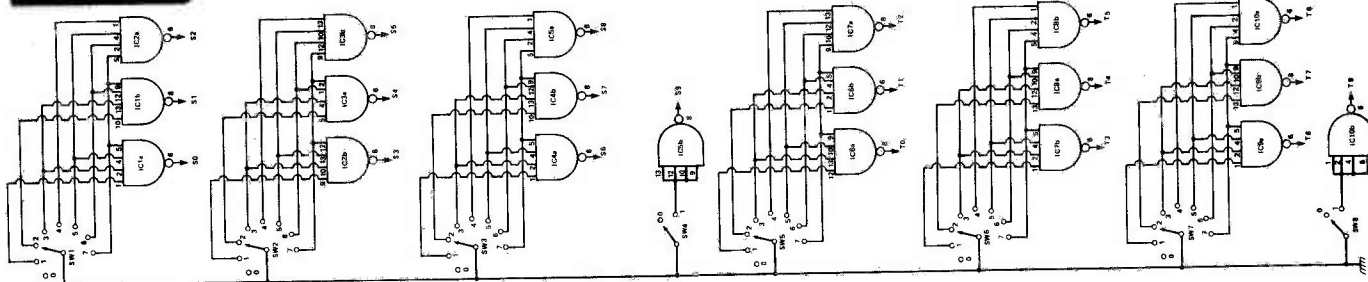


Fig.4 How to wire the off-board components.

Fig.5 (left) The switch encoder circuitry.

To confirm the correct encoding of each note, enter each one down the keyboard, switch to PLAY, press RESET and observe the red LEDs progressively showing a larger binary number.

Set the START OF NEXT SEQUENCE switches to 0003 and the START OF SEQUENCE switches to 0000, press RESET, enter the note two octaves down from the highest three times (any note length). Switch to PLAY with TEMPO halfway advanced and adjust PR3 for 2 V on VC OUT ie set the control voltage to 1 V/octave. Now you can bolt together the cabinet and start composing!


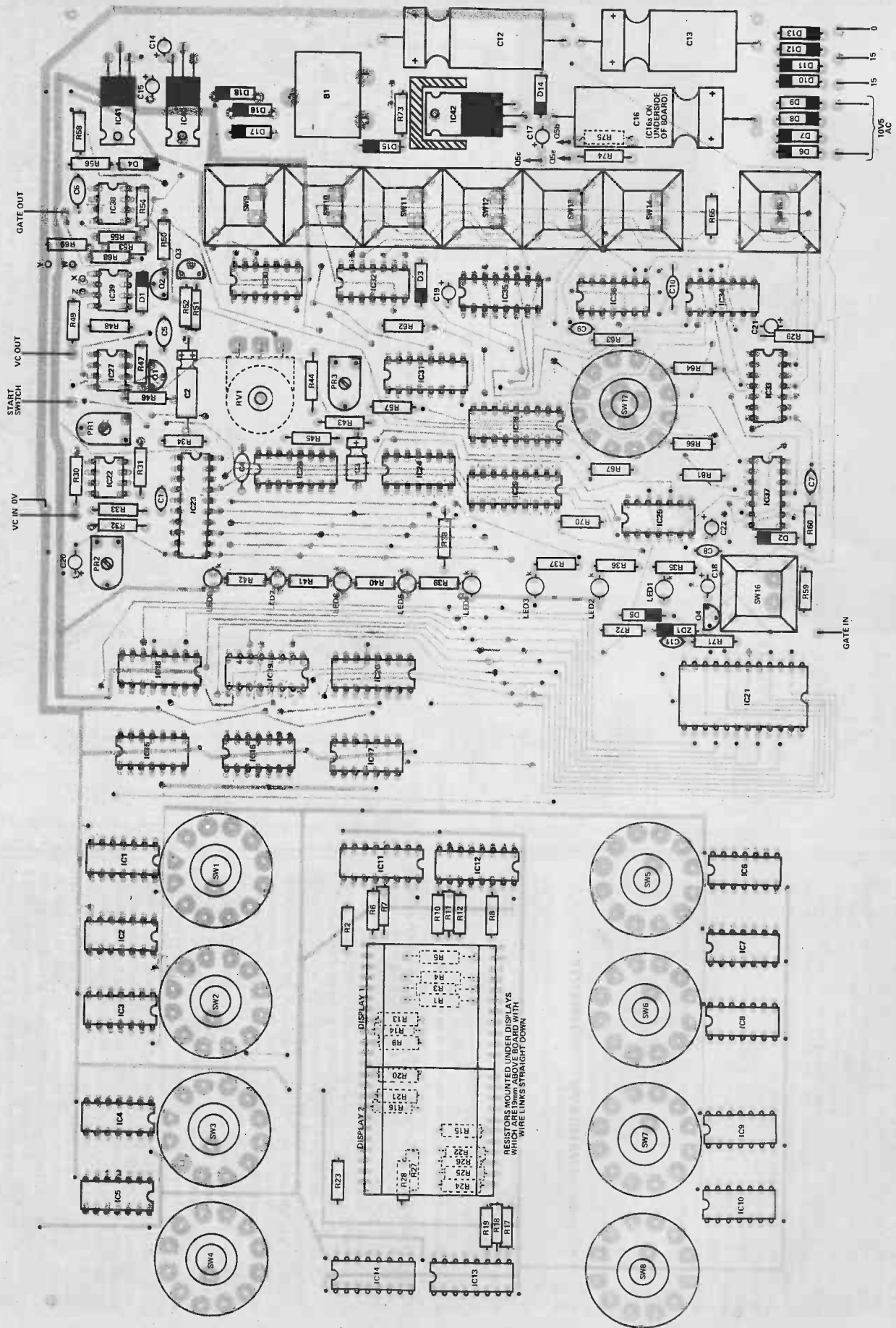



Fig.6 Overlay for the composer. The PCB is double-sided; note that this view is of the component side of the board and shows the copper tracks for that side. C16a is soldered underneath the board using the spare pads adjacent to C16.

PARTS LIST

Resistors (1/4 W 5% carbon film except where stated)	PR2	10k miniature horizontal preset	7427
R1-28, 35-42	PR3	1k0 miniature horizontal preset	7408
R29, 61, 62, 63	Capacitors		7485
R30	C1	150p ceramic	74132
R31	C2	220u 10 V axial electrolytic	1458
R32	C3	47u 10 V axial electrolytic	7815
R33	C4, 10	100n polyester	7915
R34, 50, 51, 52,	C5, 6	220n polycarbonate	7805
54, 60, 67	C7, 8, 9, 11	1n0 ceramic	BF244C
R43	C12, 13	1000u 25 V axial electrolytic	BC182L
R44	C14, 15, 17-22	1u0 tantalum	BC212L
R45	C16, 16a	2200u 25 V axial electrolytic	TIP30A
R46	Semiconductors		1N4148
R47	IC1-10		1N4002
R48	IC11-14		2V7 400 mW
R49, 59, 66, 70, 72,	IC15-17, 36		TIL222
R53	IC18-20		TIL220
R55	IC21		LED48
R56	IC22, 39		DISPLAY 1, 2
R57	IC23		TTL may be either 74 series or 74LS series
R58	IC24		Switches
R64	IC25		SW1-8
R65, 71, 73	IC26		SW9-16
R68	IC27		SW17
R69	IC28, 29		SW18
R74	IC30		Miscellaneous
R75	IC31		IC sockets, 3V6 Ni-Cd PCB-mounting battery, TV5 heatsink (2 off), transformer (secondaries T5-0-15 @ 100 mA, 10V5 @ 1 A), fuse holder, double-sided PCB, jack sockets (4 off), cabinet, spacers etc.
Potentiometers	IC32		
PV1			
PR1			

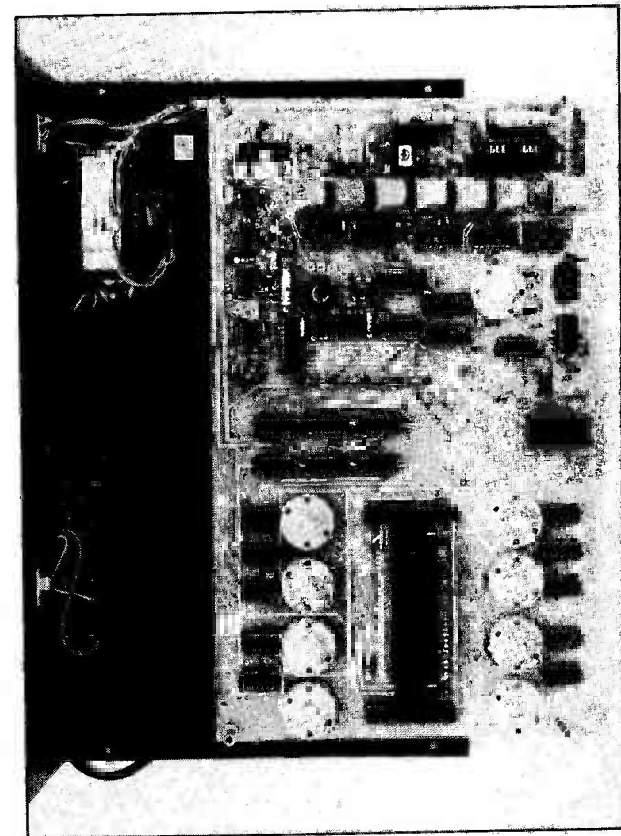

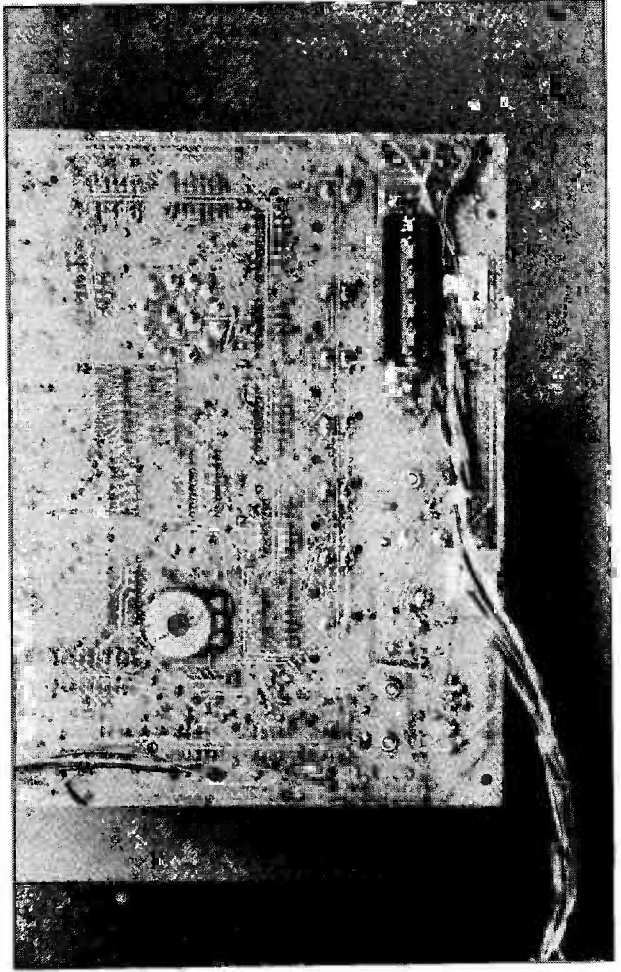The complete PCB, with wiring finished and ready for fixing to the front panel.



Underside of the PCB showing RV1 and C16a in place.



SIMPLY AHEAD
and staying there

The range grows... bigger... better...

New Profile Amplifiers - Two New Series

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connections via five pins on the underside. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.



Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR


(Standard O-P Transistors)

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A. for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

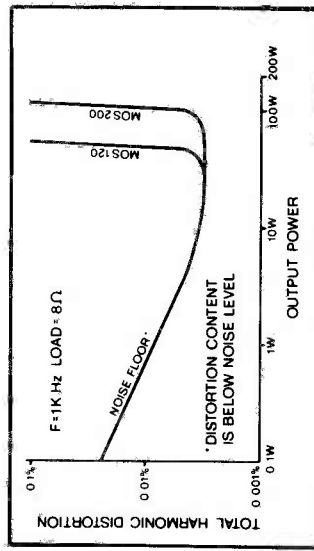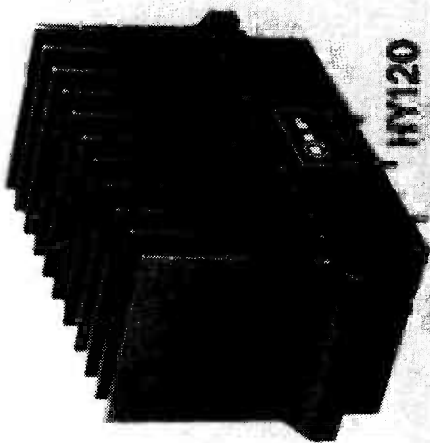


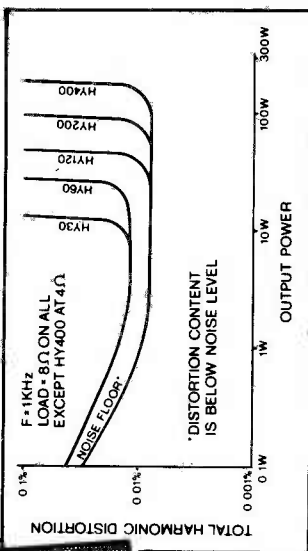Load impedance both models 4Ω-∞ Input sensitivity both models 500mV
Frequency response both models 15Hz-100KHz -3dB



Load impedance all models 4Ω-∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz -3dB

THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages. Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.

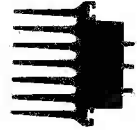

NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity - Mag. PU - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.

- HY6 mono £6.44 + 9p VAT Connectors included
- HY66 stereo £12.19 + £1.83 VAT Connectors included
- B6 Mounting Board for one HY6 78p + 12p VAT
- B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our factory. Thus these I.L.P. power supply units are space-saving in size and their better overall design helps enormously when assembling building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.


- PSU30 ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS £8.10 + £1.22 VAT
- PSU36 for use with 1 or 2 HY30's
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
- PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
- PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER

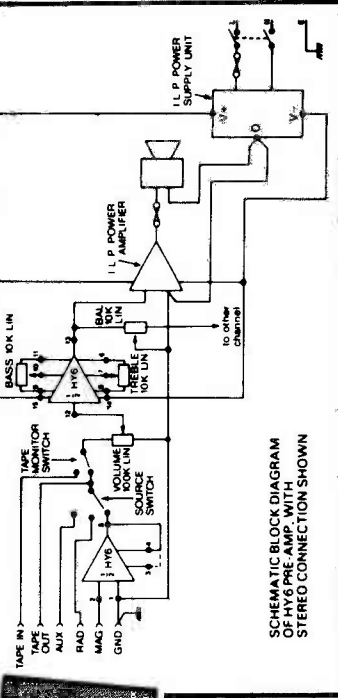Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



SCHEMATIC BLOCK DIAGRAM OF AN I.L.P. STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 V

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply

..... Total purchase price £


I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

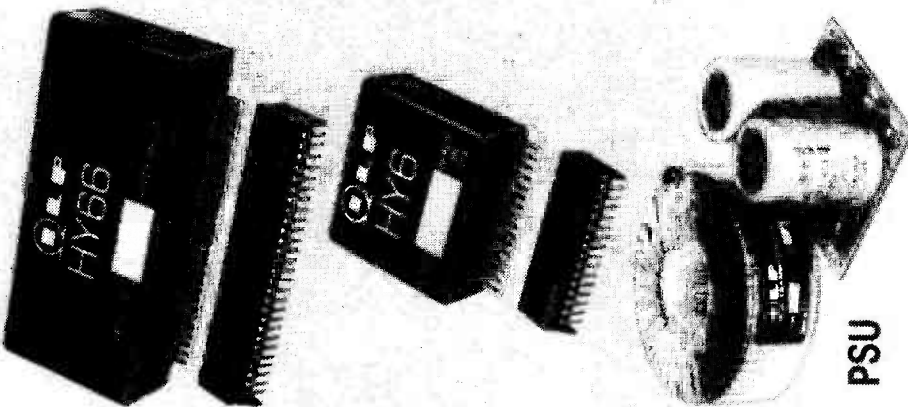

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE



ELECTRONICS LTD.

FREE POST 6 Graham Bell House, Roper Close, Canterbury, Kent. CT2 7EP.
Telephone (0227) 54778 | Technical (0227) 64723 | Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

ALWAYS

A CHANGING RANGE OF OSCILLOSCOPES, COMPUTERS, TERMINAL ETC.

Item No.	1	TEKTRONIX STORAGE OSCILLOSCOPE Type 434. Current Model. As new. 12 inch warranty (No warranty £1,400)	£1,850
2	TEKTRONIX STORAGE OSCILLOSCOPE type 564 with 3A6 & 3B4	£260	
3	HAMEG OSCILLOSCOPE type 412. Dual Trace 20 MHz	£250	
4	TELEQUINT OSCILLOSCOPE type D61A. Dual Trace 10MHz	£200	
5	SCOPEX OSCILLOSCOPE type 4D10. Dual Trace 10MHz	£170	
6	HEWLETT PACKARD OSCILLOSCOPE type 120B. (X-Y)	£120	
7	MARCONI WAVE ANALYSER TF2330. Good condition	£150	
8	AVO UNIVERSAL BRIDGE B150 with adaptor A151	£80	
9	ADVANCE SIGNAL GENERATOR type E2 100KHz-100MHz	£40	
10	B & K AUTO VIBRATOR EXCITER CONTROL type 1018	£50	
11	SOLARTRON Digital Voltmeter type LM1420.2	£20	
12	SOLARTRON PLS GENERATOR type SC65A	£20	
13	ADVANCE V.H.F. Millivoltmeter type VM79 - No probes	£35	
14	ADVANCE A.F. SIGNAL GENERATOR type J2	£25	
15	KINGHT RF Sig Gen KG686 with Sweep Marker Gen KG687. The Pair	£90	
16	ADVANCE Audio Signal Generator HIE 15Hz to 50KHz	£45	
17	DELTA VIDEO MONITOR	£50	
18	LYONS PULSE GENERATOR type PG-2E	£45	
19	COBSON SINE/SQUARE WAVE GENERATOR 20Hz-1MHz	£20	
20	AVO UNIVERSAL BRIDGE type 1	£75	
21	P.S.I. RMS VOLTMETER type A1301	£30	
22	LABGEAR RGB COLOUR MATCH GENERATOR CM 8004-PG	£75	
23	ADVANCE LF OSCILLATOR type SC65A	£20	
24	TAYLOR AM/FM SIGNAL GENERATOR type 62A Mk II	£125	
25	MARCONI UNIVERSAL BRIDGE type TF1313 1/4%	£200	
26	MARCONI WIDE RANGE OSCILLATOR type TF1370 10Hz-10MHz	£90	
27	SOLARTRON TRUE RMS VOLTMETER type VM1484	£75	
28	RANK V.H.F. SIGNAL STRENGTH INDICATOR	£25	
29	RACAL COUNTER ELECTRONIC FREQUENCY 32MHz type 836	£75	
30	WAYNE KERR CAPACITANCE BRIDGE type B541C	£40	
31	WAYNE KERR COMPONENT BRIDGE type B121	£45	
32	HEWLETT PACKARD DC CURRENT SOURCE type 6181B 0-100V; 0-250mA	£175	
33	MARCONI SAUNDERS LEVELLING AMPLIFIER type 6567	£95	
34	TEKTRONIX PRE TRIGGER PULSE GENERATOR type 111	£375	
35	RACAL H.F. SELECTIVE ANALYSER type 9056	£10KHz-	
36	MARCONI STANDARD SIGNAL GENERATOR type TF144H 10KHz-72MHz	£225	
37	SCHLUMBERGER/SOLARTRON AUTOMATIC COUNTER type FB2602	£150	
38	BRANDENBURG PHOTOMULTIPLIER POWER UNIT 0-2500Volts	£90	
39	SCHLUMBERGER/SOLARTRON COMPUTING VOLTMETER type JM1776	£90	
40	HEWLETT PACKARD AC CONVERTOR type 3481A	£90	
41	MURPHREE WAVE ANALYSER K-134-A 30-310Hz	£75	
42	PHILIPS COMPARATOR 278KHz	£50	
43	HEATHKIT CAPACITOR CHECKER IT-28	£25	
44	HEWLETT PACKARD DIGITAL VOLTMETER type 3440A	£90	
45	HEWLETT PACKARD FREQUENCY CONVERTOR type 8728A	£130	
46	RACAL AUTO FREQUENCY CONVERTOR type 903R 500MHz	£25	
47	AIRMEC ELECTRONIC VOLTMETER type 314A	£75	

48 VARIAN RUBIDIUM FREQUENCY STANDARD 100KHz/1MHz/5MHz

48	KEITHLEY INSTRUMENTS REGULATED HIGH VOLTAGE SUPPLY TYPE 241 Accuracy +/- 0.5% or 1mv	£800
50	T. O. ELECTRONIC POKYBORDER type EPR-2T	£250
51	STODDARD AIRCRAFT Radio Interference and Field Intensity Meter type NM-52A 375-1000MHz (2 pieces)	£275
52	TAYLOR VALVE TESTER type 45D	£45
53	RHODE & SCHWARZ UHF TEST RECEIVER BN1623 280-940MHz (4800MHz)	£125
54	R & S SIG DIAPHRAGM 300-2400 MHz BN3562	£95
55	R & S Unbalanced Standard ATTENUATOR BN1804/50	£45
56	R & S VHF-UHF FREQUENCY METER 30-3000MHz BN442	£80
57	R & S DIRECT CAPACITANCE METER BN5201	£75
58	WAYNE KERR UNIVERSAL BRIDGE type B521 (CT375)	£280
59	B & K HETERODYNE VOLTMETER type 2005	£235
60	HEWLETT PACKARD CLIP ON DC MILLIAMPMETER type 428A with probe	£70
61	SOLARTRON DIGITAL VOLTMETER type LM1420.2	£20
62	SOLARTRON DIGITAL VOLTMETER type 1420.2 with Mean AC Unit	£35
63	SOLARTRON DIGITAL VOLTMETER type 1867	£35
64	MARCONI SIGNAL GENERATOR type TF95A3/S (CT402)	£225
65	JARROLD SWEEP GENERATOR 20-112 MHz	£40
66	HEWLETT PACKARD VALVE VOLTMETER type 412A	£35
67	HATFIELD SELECTIVE LEVEL METER type 1001	£90
68	COBSON NOISE LEVEL METER CT464	£18
69	HEATHKIT DECADE RESISTANCE BOX DR1U	£10
70	MARCONI VARIABLE ATTENUATOR type TF1073A/S (CT421)	£15
71	NOCHIAR UNIVERSAL COUNTER TIMER type A1149	£40
72	WAYNE KERR UNIVERSAL BRIDGE type B221	£80
73	WAYNE KERR AF SIGNAL GENERATOR type S121 10Hz-120KHz	£90
74	SIGNAL GENERATOR type CT344 0.1Hz-10MHz	£30
75	CLARE FLASH TESTER type Q103B	£25
76	MARCONI RF ATTENUATOR type TF1073A	£35
77	HEATHKIT VALVE MILLIVOLTMETER AV-3U	£15
78	TELEONIC SWEEPER 450-900MHz	£55
79	COBSON SWEEP OSCILLATOR type CT202	£35
80	WEIR DIGITAL VOLTMETER type 500 Mk 3	£20
81	AIRMEC ALPHEA SIGNAL GENERATOR type 204 1-320MHz	£250
82	HATFIELD TRANSISTORISED SELECTIVE LEVEL METER SFO 7820	£90
83	S.T.C. LEVEL MEASURING SET type 74309B	£30
84	AVO TRANSISTOR ANALYSER type CT446	£30
85	SIEMENS SUPERMET RECEIVER 30Hz-1MHz	£25
86	R & S MICROWAVE POWER METER BN24 1250-3200MHz	£35
87	ADVANCE SIGNAL GENERATOR B48 10KHz-100MHz	£25
88	HEWLETT PACKARD DIGITAL RECORDER type 5050B	£25
89	BRYANS X-Y PLOTTER - No pen	£75
90	ADVANCE X-Y RECORDER type HR100 - No pen	£60
91	MARCONI DOUBLE PULSE GENERATOR type TF1400/S	£30
92	RADREITER WAVE ANALYSER type PFA 203A 30Hz-16KHz	£90
93	R & S RESONANCE FREQUENCY METER BN4312/2 30-300MHz	£70
94	S.T.C. OSCILLATOR type 74308A	£70
95	WAYNE KERR VIDEO OSCILLATOR type 022B 10KHz-10MHz	£30
96	HATFIELD P80PHOMETER Drg 657/167A	£50
97	TEKTRONIX SAMPLING OSCILLOSCOPE type 661 with 4S1 Vamp 5T1A TB.	£275
98	HEWLETT PACKARD MEMORY DISPLAY 5480A with 5486A Control TB and 5486A two channel input	£225
99	E.H.T. Unit 230 Volts 50 or 25VA 7.5KV	£18
100	AVO VALVE CHARACTERISTIC METER	£20

PLEASE CHECK AVAILABILITY BEFORE ORDERING

CREED MODEL 75

Printer with keyboard. Late model
Still the cheapest way to get a printout from your microprocessor. Basic data and connections supplied.

Used, good condition

ONLY £25 each

As new, Ministry boxed **£40 each**

RACAL SA520

Frequency counter. Small compact unit.
£15 each

INFRA RED IMAGE CONVERTER Type 9606 (CV 144)

1 1/4" diameter. Requires single low current 3KV to 6KV supply individually boxed. With data.

£12.50 each

Infra Red Lamps also advertised

FERRET A.T.E.

£650

Phone for details

VARIAN RUBIDIUM STANDARD

Model R20. 5mhz, 1mhz, 0.1mhz

£600

EX-MINISTRY SOLID STATE 400 Hz INVERTOR

28 VDC input, 115V output. Size 7 x 2 1/2 x 1 1/2 in approx. Connection details supplied.
£18 each. P&P £2

TRANSISTOR INVERTOR

115V AC 1.7 Amp Input. Switching is at 20KHz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied.
£1.25 each. P&P £2.

CONVERT THIS UNIT TO A SUPER BATTERY CHARGER

Attractive green ministry quality case with removable top and bottom plates - heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for **£3.50. P&P £2.** Four units £12. Carriage £5.

STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a techo. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p
or 5 for **£5 P&P £1.50.**

STEPPING MOTORS

200 Steps. 20 oz/in. torque, 12/24 volt input 4-wire.
£12 each. P&P £1.50

KEYBOARD PAD

Size 3x2 1/2" high with 12 Alma Read Switches. Blue keys marked in green 0-9 and a star with one blank. **£4 each. P&P £1,** or 5 for **£15 P&P £2.**

MINIATURE KEYBOARD

Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 each.**

CRYSTALS 50p each.
Flat metal case - 19.2KHz; 844.8KHz; B7G - 10MHz

LOUDSPEAKERS. Transistorised hand-held, no leads. Standard internal batteries supplied. Howl Switch £20 ea. P&P £2
INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 1 1/2" x 1 1/2" dia. **£1.50 ea.** 240V 1560 Watts. Size 2 3/4" x 1 1/2" dia., **£3 ea.**
BRIDGE RECTIFIER. 2 Amp 50p ea.
PHOTO DIODE DETECTOR 4" fly leads. 25p ea.
AMPHLEK. 17-way chassis mounted edge connectors 0.1 spacing. **15p ea.**
I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) 80p
FANS. 115V 13 Watts. Size 3/4 x 3/4 x 1 1/2" BRAND NEW. **£4.50 ea.** Second hand **£2.50 ea.**
DELAY LINE. 50 nanosecs. 3 connections - ground-in-out Size 2 x 7/16 x 5/16" New **25p ea.**
MOTOR 12V DC with pulley and integral semiconductor. Speed control. New **£1 ea.**
LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. **15p ea.**
DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New **10p ea.** 100 for **£7.50**

SOME TEKTRONIX 500 RANGE OSCILLOSCOPES

with Single Trace Plug-ins. Working.
From **£100.** Phone for details

DIODES

All new full spec. devices
IN3063 BAX 13. 1544, 1N4148;
1N3470; 1N4151.
100 off **£1.50, 1,000 off £10**

PULSE TRANSFORMER. Sub min. Size 1/2 x 5/16 x 1/4"

Secondary centre tapped. New **20p ea.**
REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus. **£1 each.**
DON'T TAKE CHANCES. Use the proper EHT CABLE, 10p per metre or **£7.50** per 100 metres/drum. P&P £2.
PHOTODIAPHRIC LAMPS. Pearl 230V 500 watt. Screw cap **75p ea.** Box of 12 **£5.50. P&P £1.50.**
RAPID DISCHARGE capacitors 8mf 4Kv £5 each. P&P £2.
MYSTERY IC PACK. Some 40 pin - good mixture - all new devices. 25 Ics for **£1. P&P 50p.**
DECOUPLING CAPACITORS 0.05mf 10V; 0.01mf/d; 0.047mf 250V; 33K, 330pf. All values 100 for **£1.50.**
E.H.T. Capacitor 500pf 8KV 20p each.
10-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10 metres for **£3.**
GEC UHF 4-button tuner. **£1.50 each.**
CENTRAL 115V FANS 4 1/2" x 4" x 1 1/2" **£4.50 ea.**
EX-USED equipment. tested. **40p each.**
CONTRACTORS. Heavy Duty 24V DC 5 make **£1 each.**
GEC UHF/VHF 6-button tuner. **£2 each.**
831A PHOTO MULTIPLIER £2 each. P&P £1.
RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degrees C **£2.50 each.**
SOLID STATE UHF TUNERS 30 ea **£1 each.**
BRAND REX blue wire wraps. 30 metres for **£1. P&P 25p.**
SLIDER CONTROL 500K Log. Single track. Complete with knob. Length 3 1/2". **25p each.**
TRANSFORMERS
AUTO 240V input 115V. 1 Amp output £1.25 each. P&P £1.25.
240V input. Soc. 5V. 1.86A. Size 2 1/2 x 2 x 2". Good quality. **£1.50 ea. P&P £1.**
240V input Soc. 12V. 0.92A. Size 2 1/2 x 2 x 2". Good quality. **£1.50 ea. P&P £1.**
240V input 12V 100MA. Size 80 x 40 x 42mm. 50p each.
240V input. Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm. £1 ea.
115V input. Soc. 5V 250MA. Size 1 1/16" x 1.5 x 1 1/4". 2 for 50p.
115V input. Sec. 10-0-10V1A. Size 2 1/2 x 2 x 2". 2 for 150p.
SEMICONDUCTORS
1N4005 - 5p; 1N4002 - 3p.
At 5p each:
8Y1; 8D148B; BC157; BC158; BC237; BF197; OA90; OA81; BA154; BA243.
At 25p each:
TIP31; TIP41A; 2N5198; 1AF139; 2TX341.
BY127 10p; BF181 20p; BD239 45p; BD241 40p; MA343AT 45p; BD228 50p; BD233 & BD234 Comp Pair 25W - 803p per pr. at 50p each.
REGULATOR TBA625 8to 20V in - 5V out 100MA T05 Con. 50p each BF256C 20p.
TV AMPLIFIER TBA 120 20p each.

Integrated Circuits

7453	5p	74H51	7p	75325	£1
7451	5p	74538	10p	SN15682	4p
7402	12p	74502	12p	MC4028	8p
7476	20p	74154	70p	7417	14p
7495	35p	74C02	18p	7441	40p
74C00	17p	74C04	18p	74C36	50p
74H74	12p	74C74	18p	74C161	24p

MOTOROLA DUAL: in Line 8 pin Opto Coupler **30p each.** Gold plate tester version **50p each.**
EPROMS 2708 £5.50 each.
ELECTROSTATIC VOLTMETER. 7.5KV £5 ea. P&P £1.50.
Other ranges available - please enquire.
TRIMMERS. Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. All at 5p each.
HOKEYWELL humidity controllers **50p each.**
THYRISTOR TIMER. Solid State. 15 sec adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay **50p each.**
MINIATURE PC MOUNT SLIDE SWITCH. 2 pole 2 way 10p each.
4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits. Good brilliancy at 1.5V. 15 connections **£2.50 each.** Some E.H.T. Transformers and Capacitors available. Please enquire.
TELEPHONES 706 style black; grey or blue **£5.50 ea;** 746 style black or grey **£7.50.** Older style black **£2.50 each.** Discoloured grey 706 **£4 ea.** P&P **£1.50** per telephone.
DC SERVO MOTOR 110V 2.5AMP continuous. Double shaft. Brand new. 4 wire. 4 brush **£25 ea.** Plus carriage.
PC Mount POSTS. Wire wound with knob 200 ohm & 10 ohm. 10p ea.
MINI. RELAY 24V. 2 pole c/o. Brand new. **75p each.**
TIME DELAY RELAY 0.1 to 10 secs. 115V AC. DPDT. **£5 each.**
CAPACITORS at 5p each. 0.1uf 400V. Small rec. block PC Mount German class; 3300pf; 220nf/250V; 0.01mf/160V.
INSERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brand new wrapped **75p each** or 10 for **£7.**
CORONAL TRANSFORMERS. Input 0-120-240 Volts. Output 0-12V; 0-12V. 10VA per winding. Encapsulated - identical to R.S. Components at **£9.90.** OUR SPECIAL PRICE **£5 ea.** P&P **£1.50.**
TANTALUM CAPACITORS - All at 10p each - 100 off **£7.50.** 22mf 6V; 39mf 10V; 22mf 35V; 1mf 35V.
MINIATURE SLIDE SWITCHES. Single pole 2 way 10p each. 10 off 90p.
HEAVY DUTY RHEOSTAT. 7.50hm 5.5amp. Diameter 5". Standard 1/4" shaft **£2.50 each. P&P £1.50.**

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or 500 ohm. Tested. **£25 each** or 5 for **£100.**

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1.50 - where P&P not stated please use own discretion - excess refunded.

£5 CARRIAGE ON ALL UNITS. P&P OR CARRIAGE AND VAT AT 15% ON TOTAL MUST BE ADDED TO ALL ORDERS.

CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.

BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTEHEAD LTD

NORWOOD ROAD, READING

TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

SONIC HOLOGRAPHY

Hologram: a three-dimensional image. Sonic: pertaining to sound. Sonic Hologram, therefore, a three-dimensional sound image? Well almost! Ron Harris explains.

Sonic holography refers to a new principle of music reproduction being pioneered by Carver in their C4000 preamplifier. The aim is to more closely approach in the average room, the sound field found in a concert hall, using only the normal stereo pair of loudspeakers.

In operation the circuit's effect is to spread the sound image well beyond the speakers and add a marked 'depth' to the music. Such manipulation of the signal goes against the present trend in British hi-fi to exclude all controls except volume and input select. When examined closely this approach has just the faintest whiff of cowardice about it — rather than try and design a good compensation circuit it is easier to leave it out altogether.

It is also true that some of the best amplifiers around today follow this rationale — the Meridian and the Exposure for example — and are none the worse for doing so. However, all living rooms need equalisation to overcome their imperfections and some help is better than none. The ideal answer is probably a parametric equaliser which can be tuned to cancel the major system/room resonances and hence flatten the overall response closer to that ideal straight line.

Control Lines

The 4000 is the exact opposite of the Meridian. It has controls for EVERYTHING. Tone controls are provided for each channel with variable turn-over frequencies, a most sensible and useful addition. An auto-correlator and an expander are also included with variable threshold for each. Between them they offer the experimenter a phenomenal increase in perceived signal-to-noise ratio — albeit at a small degradation in absolute sound quality.

The main feature is undoubtedly the Hologram Generator with its associated time-delay amps. Holographic reproduction can be obtained from the normal two speakers perfectly well, but for those wishing to enhance the effect still further, the time-delay feature is useful. We will return to this later, firstly let us consider how the basic hologram circuit operates.

Binaural Beginnings


Most readers will have heard, or at least heard of, the binaural recording techniques, where music is captured on tape using a dummy head with microphones positioned in the 'ears'. When replayed on headphones, a remarkably accurate model of the original sound field is set up around the listener, ie it sounds very close to the hall in which the recording was made.

Reproduce a binaural record through loudspeakers, however, and the field is destroyed. Headphones work because they isolate each ear from the other channel completely. The right ear hears only the sound which reached that microphone in the dummy head.

The aim of Carver's Hologram circuitry is to attempt to simulate this isolation in a room using the loudspeakers. It does it by 'cross-feeding' each channel with an anti-phased version of the other. The left speaker thus receives a normal LH signal plus an added-in RH channel 'cancellation' signal.

In order to sound 'correct' to the ear, some compensation is required for the fact that the ears are different distances from the speakers and that the head throws a sound 'shadow', effectively altering the perceived frequency response as the sound passes around the head.

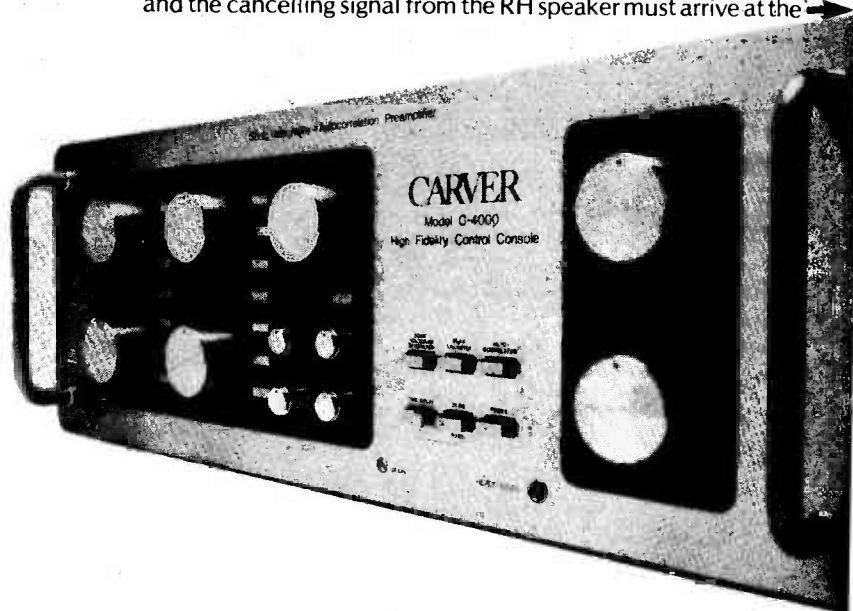To properly isolate the ears, the signal from the LH speaker and the cancelling signal from the RH speaker must arrive at the



Right: The Carver C-4000 Sonic Holography Pre-amplifier. As you can see from the front panel there is no shortage of facilities. The set of six push-button set apart, beneath the logo, control the main circuits — including the Sonic Hologram. It is a nice ergonomic touch to have the Volume Control well separated from the rest as it makes it easier to 'find' in use.

Inputs are provided for two tape decks — with full dubbing — two pickups, a tuner and an 'auxiliary'. Output level may be switch-matched to the particular power-amp in use.

ear simultaneously and correctly equalised. Time delay is thus required and the listening zone will be relatively limited. Excessive movement will mean that the signals do not arrive in sync and little cancellation will occur.

MIT Basics

A Ph.D candidate at MIT in America did some work on determining the amount of time delay needed in compensation and also the exact modifications required to the frequency response. Using a technique similar to binaural recording he took frequency response plots, etc from two tiny microphones placed in his ears.

From this emerged a figure of around 675 mS for the delay, and the complex frequency plot shown in Fig. 3. The closer a filter can be built to approximate this curve, the better will be the isolating effect and hence the sharper the holographic effect.

These plots were taken under anechoic conditions and things become considerably more complex under reflective conditions — the real world. Carver uses a 12 pole filter to shape response below 1 kHz and a second, five pole, filter for higher frequencies. The phasing problems must be horrendous. Time delay is achieved using wide-band FET amplifiers because they produce a better sound quality than IC CCD delay lines.

Amplitude-To-Phase

One additional circuit was required in the final design, to allow for varying methods of 'multi-miking' records. This type of recording does not preserve the original sound field nearly as well as the simple 'crossed pair' techniques and to extract an effective hologram it is necessary to reorganise the amplitude variations in the signal into a particular, very complex, phase relationship. This is fed to the appropriate loudspeakers.

The C-4000 makes use of the fact that stereo positioning is entirely amplitude related, ie if a drum is louder on the left channel than on the right it will appear to emanate from a position closer to that speaker. This enables the preamp to place the sound laterally and the phase information already on the recording is then used to provide a 'depth' relationship.

A two position switch is provided on the preamp which is labelled 'normal' and 'theoretical'. Set to the former it optimises the playback for normal stereo multi-miked recordings and switching to the latter will allow better reproduction of 'natural' recordings ie 'cross-pair' etc.

Practise

That's the theory then, but how does it do in practise? Very well actually. We tested the preamp as a 'normal' piece of hi-fi first of all and it exceeded its specifications comfortably on all counts.

Setting up the holographic generator is a little tricky, but use of the special test record from Carver greatly facilitated things. Once aligned, seating position is critical to around three feet laterally and about seven feet front to back. Outside this area the effect is greatly lessened but still present.

Playing a record and switching in the hologram proved to be an unnerving experience. The sound stage expands enormously and appears totally divorced from the speakers. On a classical piece the effect is simply of being nearer the orchestra with instruments appearing to be playing well outside the speakers!

On rock records, with all their attendant re-mixing, some quite startling things began to happen. The Pink Floyd's 'The Wall' and 'Dark Side' have to be heard to be believed. Live LPs reproduce brilliantly, giving a greatly enhanced 'presence' to the music, much closer to being there!

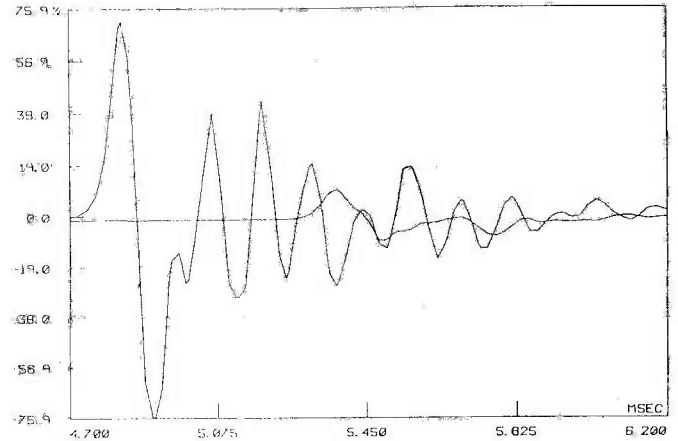


Fig. 1. The time difference between the two ears with a signal source placed at 60° to the left of the listener. The first large rise shows the left ear receiving the pulse, and 675 mS later the right ear hears the same signal, greatly attenuated by the head.

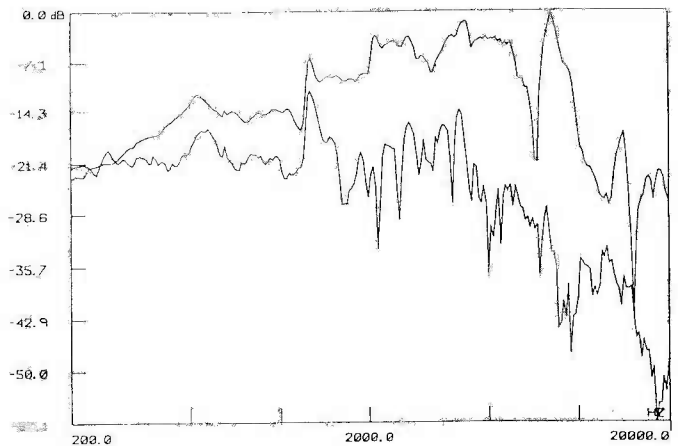


Fig. 2. Frequency response differences between the two ears hearing the same pulse from the same place as in Fig. 1. Below 200 Hz there is little difference as the head is too small to 'shadow' sound below this frequency.


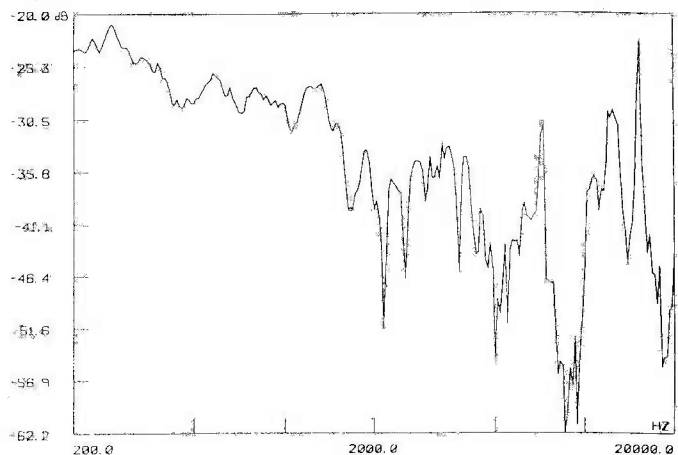


Fig. 3. The difference between the two plots in Fig. 2 drawn against frequency. The various troughs and peaks are introduced by ear lobes, the shape of the head etc.

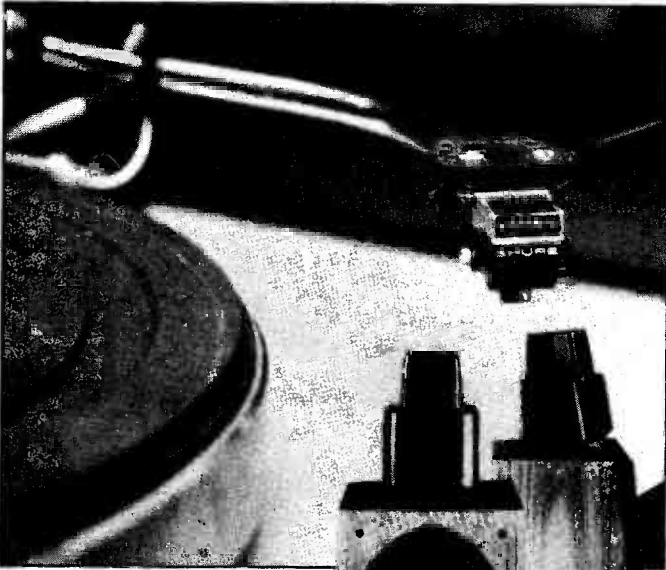

These were the two hi-fi components which produced the most pronounced effect from the C-4000. The Shure V15 IV cartridge and the KEF 105 II loudspeakers. Good results were obtained with all the systems we placed the C-4000 into, but these transducers appeared to work better than others.

Overall the sound is warmer and more accessible and the image is no longer simply hung in between the speakers in a flat two-dimensional manner. Switching back to stereo from holographic reproduction is quite a disappointment in many ways as the depth appears to vanish and the image contracts so much.

Adding Up

The time delay amps included in the preamp (of around 20 W RMS) are to drive additional speakers to the rear of the listener to enhance the effect. Frankly, I didn't feel this was needed at all. Putting in the extra units *did* change things, but two speakers were quite enough!

Experiments also showed that some ancillary equipment works better than others. KEF 105s gave the best results of the speakers tried and the Shure V15 IV cartridge gave consistently better results than any other pickup. It probably maintains better phase relationships between signal components than the rest.

So there it is. A new approach to music reproduction in the home — and one that works. The C-4000 is not cheap at around £600 but in view of the fact that it offers greatly enhanced reproduction of most material it deserves very close consideration.

My thanks to Carver for permission to reproduce the graphs, used herein, from their brochures.

ETI

110 PROJECTS in every book!!

The '110' books have been acclaimed by enthusiasts, students and engineers. Each contains 110 different circuit applications. Use them as project books or as a source book for circuit ideas.

Available NOW!

ETI 5/81

from your local bookshop or in case of difficulty direct from us:

please tick the books you need:

£4.65
tick here

110 CMOS DIGITAL IC PROJECTS
for the Home Constructor
R. M. Marston 0 408 00216 6

£4.65
tick here

110 ELECTRONIC ALARM PROJECTS
for the Home Constructor
R. M. Marston 0 408 00269 7

110 IC TIMER PROJECTS

for the Home Constructor
Jules H. Gilder 0 408 00480 0

£4.65
tick here

110 INTEGRATED CIRCUIT PROJECTS (2nd Edition)

for the Home Constructor
R. M. Marston 0 408 00309 X

£4.65
tick here

£4.65
tick here

110 SEMICONDUCTOR PROJECTS (2nd Edition)

for the Home Constructor
R. M. Marston 0 408 00322 7

£4.65
tick here

110 THYRISTOR PROJECTS

using SCRs and Triacs
R. M. Marston 0 408 0074 5

110 WAVEFORM GENERATOR PROJECTS

for the Home Constructor
R. M. Marston 0 408 00353 7

£4.65
tick here

110 OPERATIONAL AMPLIFIER PROJECTS

for the Home Constructor
R. M. Marston 0 408 00153 4

£4.65
tick here

Order NOW! Cut out this coupon and return it to Patricia Davies at the address below.

Please send me _____ copy/copies as marked above. I enclose a cheque/postal order for £ _____ in total payment:

From _____

Address _____

Please send me your FULL COLOUR Brochure

110 THYRISTOR PROJECTS using SCRs and Triacs

110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30


RAM AND EPROM NEW LOW VAT INCLUSIVE PRICES

2716 5v Rail	£9-50	4116	200 NS 16KX1 DYN.	8 for £19-95
2716 3 Rail	£8-50	2114L-3	300 NS 1KX4 ST.	8 for £22-50
2708 450 NS	£4-50	2102L-3	650 NS 1KX1 ST.	8 for £ 5-50
2708 Ex Equip	£2-25	TMS4030JL	300 NS 4KX1 DYN	8 for £ 9-95

All devices full spec. and guaranteed. Bulk enquiries welcome.

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.


TELETYPE ASR33 I/O TERMINALS

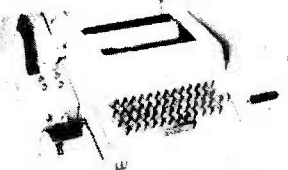

From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT
Sound proof enclosure £25.00 + VAT

ICL TERMPRINTER 300 BAUD TERMINALS

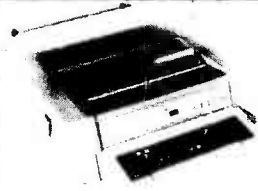


PRICES REDUCED

ONLY £295 + CAR + VAT

Made under licence from the world famous GE Co. The ICL Termpriprinter is a small attractive unit with so many features it is impossible to list them in the space available! Brief spec. as follows; RS232 serial interface, switchable baud rates 110, 150, 300, (30 cps), upper and lower case correspondence type face, standard paper, almost silent running, form feed, electronic tab settings, suited for word processor applications plus many more features. Supplied in good condition and in working order. Limited quantity.

SCOOP PURCHASE 12" VIDEO MONITORS

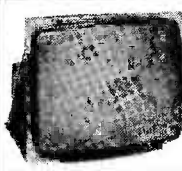

CONNECT DIRECT TO YOUR MICRO

Made by the "BALL MIRATEL" CORPORATION USA the CD12 is a self contained, mains powered chassis professional monitor. All controls are built on a single PCB with exception of the brightness control which can be brought out for external use. Many features such as composite video, quoted bandwidth of 19 Mhz, superb linearity and definition make this a must for any MICRO/CCTV application.
Brand new and boxed only + carriage £7.50 + VAT. **£97.50 + VAT**
Input harness, brightness pot and connector £2.50 + VAT. Dimensions 9"H x 11"D x 11 1/2"W
HURRY WHILE STOCKS LAST


EX STOCK SOFTY EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.
Write or phone for more details.

3K x 8 STATIC RAM CARDS

Complete with circuit only **£24.50 + £1.75 P.P.**
Dimensions 264 x 195mm. 0.1" connector.

EQUIPMENT CASES

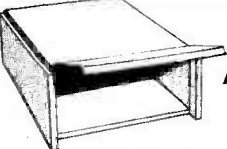

GIVE YOUR M.P.U. A HOME ONLY £9.95 + 1.85 pp

Superb professional fully enclosed, made for the G.P.O. to the highest standard, offered at a fraction of their original cost they feature aluminium sides, hinged removable front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand new may have minor scuff marks/scratches due to bad storage. Dimensions 16"D x 6 1/2"H x 14 3/4"W

OP PRESS - STOP PRESS - STOP PRESS - STEP INTO THE 80's

WITH TOMORROW'S WORLD TECHNOLOGY TODAY The "TANTEL" Post Office approved

PRESTEL-VIEWDATA ADAPTOR

At last this amazing piece of micro technology is available at a price you can afford. Just connect to the aerial socket of any colour or black and white domestic TV receiver and to your Post Office installed jack socket and you are into the exciting world of PRESTEL. Via simple push button use you are able to view a staggering 170,000 pages of up to the minute information on many services and utilities, order goods from companies, even play games!! All this and more without ever leaving your armchair!

ONLY £170 + £1.75 carr + VAT Send £197.50p

Note: When ordering please give the address and telephone number where the Tantal adaptor is to be used, we will arrange all details with the Post Office for installation of the jack socket (normally within 7 days).

MEMOREX/BASF 7 MB HARD DISK DRIVES

Model 630-1B disk drives by Memorex BASF. TTL signals in and out, high speed, IBM 2311 compatible. Sold in good condition but unguaranteed.

£175.00 + VAT BUYERS COLLECT

"THE MULTIVOLT PSU"

The PSU to end all your MPU/LAB requirements, made by "Weir" Electronics at over £200.00. The supply features full regulation, current limit, and overvoltage protection on all 7 outputs, just look at the spec.

+5v @ 12 amps, +5v @ 4.5 amps, +5v @ 4 amps, +30v @ 2 amps, +12v @ 2.5 amps, -12v @ 2.5 amps and -9v @ 1 amp.
A superb unit supplied in two grades, complete with data.
Brand New, Fully Tested **£59.99**
Used and Untested **£39.99**
Carriage and Insurance **£7.50**

NATIONAL MA1012 LED CLOCK MODULE

★ 12 HOUR
★ ALARM
★ 50/60 HZ
The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only Suitable transformer £1.75. **£5.25**

JUST IN SECONDHAND CHASSIS 9" BLUE-BEST MAINS POWERED VIDEO MONITORS

Secondhand chassis 9" Blue-best mains powered video monitors, composite video input with inbuilt 5v 3 amp DC P.S.U. Tested, but unguaranteed

£39.99 + £7.50 carriage Complete with circuit.

MANUFACTURERS ONLY

100,000 EX STOCK Miniature relays continental series by Keyswitch, etc. all contact forms all impedances.

CALL FOR QUOTES

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge rect. etc. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed. 50 + BAG £2.95 100 + BAGS £5.15

WE'VE BOUGHT ANOTHER SHIPMENT! SAVE OVER £1300!! DZM 180 CPS HIGH SPEED MATRIX PRINTERS

This must be one of our greatest bulk deals, this fabulous printer is listed at over £1800 and judging by the construction we are not surprised. Made under license from the LOGABAX Co. the DMZ180 is an exceptionally sturdy high speed 180 cps matrix printer, capable of printing up to 132 characters per line on standard "Fan Fold" sprocket fed paper. A precision 7 x 7 matrix head using ruby bearings, gives a clear concise type font. Many other features include internal buffer for high throughput, standard ink ribbon, software controllable form and tab functions, standard "CENTRONICS" ASCII parallel interface etc. etc.
Optional extras Floor Stand £30.00 + VAT, Paper Stand £18.00 + VAT



NOW ONLY £499 + Carr + VAT

RCA FULLY CASED ASCII CODED KEYBOARDS



Strait from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5v rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. **£43.95**
VP611 Same as VP601 with numeric pad. **£54.95**
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. **£60.95**
VP616 Same as VP606, with numeric pad, Post, Packing and Insurance. **£72.50**
£1.95
ORDER NOW OR SEND FOR DETAILS.

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex-equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages. 110 V.A.C. £5.05 + pp 90p OR 240v A.C. £8.15 + pp 90p DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2"

ELECTRONIC COMPONENTS & EQUIPMENT 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's., P.C.B.'s., Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME!" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kds £ 4.75 + pp £1.25 5kds £ 6.75 + pp £1.80
10kds £11.75 + pp £2.25 20kds £19.99 + pp £4.75

ELECTRONICS

Dept. E.T.I. 64-66 Melfort Rd., Thornton Heath, Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800
MAIL ORDER INFORMATION
Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bona Fida account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply.
Supplied complete with circuit at only £10.95 + £1.75pp. Believed working but untested, unguaranteed.

Hobby Electronics

BRISTOL EXHIBITION CENTRE

'81

Hobby Electronics

BRISTOL EXHIBITION CENTRE

'81

Hobby Electronics

BRISTOL EXHIBITION CENTRE

'81

COMPUTERS • AUDIO • RADIO • MUSIC • LOGIC • COMPONENTS • CB
HOBBY ELECTRONICS GOES WEST

London has more than its fair share of electronics shows, but we know that electronics enthusiasts are by no means limited to the capital. For that reason the first annual Hobby Electronics Show is to be held in Bristol — centre of the South-West.

What's to see there?

- major electronics component suppliers
- special exhibition offers
- Wales & West schools' electronic project competition (*has your school submitted an entry yet? Available from Hobby Electronics 81)

TICKETS — at the door — **ADULT** : £1.00. **CHILD, STUDENT, OAP** : 50p.

GAMES KIT • TEST GEAR • MAGAZINES • SPECIAL OFFERS • BOOKS

OPEN DAYS :

Friday May 29th : 10am — 7pm • Saturday May 30th : 10am — 6pm • Sunday May 31st : 10am — 4pm

Hobby Electronics

BRISTOL EXHIBITION CENTRE

ETI MAY 1981

Why queue? Order your tickets now from:

Send to: Advance Tickets, Midmage Ltd, 145 Charing Cross Rd, London WC2H 0EE

Please send tickets @ 50p (Student/Child/OAP) tickets @ £1.00

I enclose P.O./Cheque for £.....

GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 40p post

THE SPECTACULAR 1981 GREENWELD

Component Catalogue

£1 BARGAIN PACKS
Each pack £1; any 25 packs £22

Bigger and better than ever!!!

- * 60p discount vouchers
- * First Class reply paid envelope
- * Free Bargain List
- * Priority Order Form
- * VAT inclusive prices
- * Quantity prices for bulk buyers
- * Free Data Sheet

SEND 75p FOR YOUR COPY NOW!!

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST, VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors. 5% 10 of each value 22p to 1,000pF. Total 210. **£4.80.**
K002 Extended range 22p to 0.1µF. 330 values. **£7.86.**

K003 Polyester capacitors. 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ. 110 altogether for **£5.60.**

K004 Mylar capacitors. min 100V type. 10 each all values from 1,000pF to 10,000pF. Total 130 for **£4.70.**

K007 Electrolytic capacitors 25V working small physical size. 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.89.**
K008 Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for **£8.35.**

K021 Miniature carbon film 5% resistors. CR25 series. 10 of each value from 10R to 1M. CR12 series. Total 810 resistors. **£5.85.**
K022 Extended range. Total 850 resistors from 1R to 10M. **£8.20.**

K041 Zener diodes 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V. E24 series. Total 280 for **£16.95.**

NEW 1000 10W resistors — 10 each red & yellow 3mm x 5mm, with clips. Total 60 LEDs for **£8.95**

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia x 20mm **86p.**
Z402 Miniature type buzzer. 6, 9 or 12V. only 22x15x16mm. Very neat **86p.**
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only **£1.**

A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied **£1.60.**

BARGAIN LIST 13

10-page A4 list with 800 different items, many unusual, all at cut-price — switches, relays, pots, Rs, Cs, connectors, hardware, semi-conductors, motors, displays, packs, panels, motors, etc. And it's FREE!!! — just send 9x4 stamped SAE.

REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: Output voltage 0-28V
Output current 20mA-2A
Source Impedance 0R1
Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only **£7.75**

1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, **£8.50** per box; 4 boxes **£30**; 10 boxes **£78.**

DISC CERAMICS

0.22µF 12V 9mm dia. Ideal for decoupling. 100 for **£2.75**; 1000 **£20.**
0.05µF 12V 15mm dia. 100 **£1.50**; 1000 **£12.**
Pack of disc ceramics, assorted values and voltages — 200 for **£1.**

TRANSFORMERS

Mains primary, 50V 20A sec. **£20.** Mains pri. 110V 15A sec **£30**; 20A **£40.**

SLIDER POT SCOP!!!

Made by Piher, types PL40CP & PL60C. Sully prices for superb goods!
PL40CP — 69x16x9mm, 40mm slide length, 220R, 2k2 or 10k in kit. Prices (any mix): 1-24 **26p**; 25-99 **17p**; 100+ **14p.**
PL60C — 84x10x7mm, 60mm slide length 5k, 10k, 100k. Prices 1-24 **26p**; 25-99 **22p**; 100+ **17p.**

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only **£7.75.** Suitable transformer and pots **£6.** Send SAE for fuller details.

CALC CHIPS 60p!!!

New full spec, supplied with data. Type MK50321 — full function inc. memory. Only **60p.**

K101 16 BC239B transistors
K102 15 BC149A transistors
K103 10 BC546B transistors
K104 18 BC182B transistors
K105 50 1N4148 diodes
K106 18 BC184L transistors
K107 18 BC213L transistors
K108 8 2N5060 thyristors. 30V 0.8A TO92 case.

K109 15 BC114 transistors
K110 4 80131 transistors
K111 4 80132 transistors
K112 12 3A 100V rects. wire ended
K113 30 DA002 rects 150V 0.5A
K114 15 XK6116 (BF241) transistors
K115 18 SP1218 (2N3702) transistors
K116 10 MPS101 NPN 140V TO92
K117 10 BF450 PNP TF IF amp transistor
K118 16 ME4101 NPN 60V AF low noise
K119 12 2N5401 NPN 160V TO92
K121 20 7N5 400mW zeners
K122 10 VR525 5.25V 2.2W
K123 10 56V 1W zener
K124 50 .02µF disc ceramic

K125 200 1k 5% 1/4W carbon film resistors
K126 100 300pF 63V polystyrene preformed caps
K127 25 47µF 25V axial lead caps
K128 25 15µF 40V do
K129 8 AA113 diodes
K130 25 470R V 0.1W presets
K131 10 VA1008 thermistor dip kits
K133 20 3 way 5A term blocks
K134 50 unmarked untested OC71 type transistors

K135 30 4.7µF 10V radial elec
K136 4 AC187A transistors
K137 5 18µF 100V non-polarized caps
K138 30 1/4" coil former with slug
K139 40 .025µF 50V mylar caps
K140 30 .05 do
K141 40 0.01µF 400V axial caps (C296)
K142 25 wire ended nois sid size. 30V
K143 200 squares mica insulation 25mm sq.
K144 30 IR5 3W wirewound resistors
K145 10 1500µF 1.6V caps — radial PC mntg.
K146 25 330µF 4V axial caps
K147 3 150V F 350V caps — radial PC mntg
K148 30 transistor former type X228
K149 12 Ferris rod type X036
K150 10 switches type W430
K151 12 0.125" red LEDs
K152 10 0.2" red LEDs

K153 30 T05 bean sinks, same as G104
K154 15 5 pin 180° pin socket, dip kit
K155 100 metres thin flex (10x2m lengths)
K156 15 1/4" chassis mntg luseholder
K157 12 16 pin QIL-QIL IC sockets
K158 6 SPCD centre off white rocker switches

K159 20 0.3W presets 500k V with knurled knob
K161 20 0.3W presets 2k5 V
K162 20 0.3W presets 2M5 V with knurled knob
K163 400 15R 1/4W 5% preformed vert mntg resistors
K164 50 22pF 2% silver mica caps
K165 20 Submin read switch, body 20mm long
K166 100 3300pF 630V polyester PC mntg caps

K168 50 AA144 diode preformed as above
K169 30 8V2 400mW zener as K167
K171 25 11V do
K173 12 1.5µF 25V tant bead caps
K174 12 0.47µF 25V tant bead caps
K175 24 150R 0.1W vert presets
K177 24 470R 0.1W horiz presets
K178 24 470R 0.1W vert presets
K179 24 2k 0.1W horiz presets
K180 24 2k 0.1W vert presets
K181 24 2k2 0.1W horiz presets
K185 200 1R 1/4W CF preformed Rs for horiz mntg, 15mm centres

K187 18 PE5030 NPN SI TO92 transistors. Vce 35V, Hfe 75
K188 18 FS44 PNP SI TO92 transistors. Vce 20V, Hfe 300
K189 30 1N649 600V 0.4A diodes, preformed for H mntg
K190 16 BZY85 8V2 250mW zener diodes
K191 8 BY300/800 Top Hat switching diode 600V 6A
K192 25 RGP108 100V 1A switching diode

COMPONENT PANELS

Z525 Contains 11 8000Ω 60V 2N5061 SCRs, 11 6V8 zeners, 11 1N4004 diodes plus Rs, Cs, etc. Only **£1.**

Z529 74 Series ICs — Gates and complex logic, 20 asst ICs on panels **£1**; 100 ICs **£6.**
Z527 2x6V reed relays. 6x25030 or 25230. 6x400V rects, plus Rs. Only **60p.**


TTL, LINEAR, OPTO

All new full spec — Fairchild/SGS
TTL: 5400, 5401, 5402, 5403, 5404, 5405, 5410, 5421, 5430, 5450, 5451, 5453, 5460. — All 12p ea. 5470, 5472, 5474, 5475, 5476, 5480, 5488, 5490, 54107, 54121, 54122 — all 20p ea. 5482, 54126 — 40p ea. Others (74S, H) on B/L 12 (SAE plate).
LINEAR: 9665 or 9666, 7 x 50V Darlington in 16 Dtl **60p**; 75452 or 4 dual pench driver **70p**; XK1444 7 CMOS P-channel buffers, 15V 16 Dtl **24p.**

OPTO: Isolators, FCD831 **60p**; TTL115/118 **80p**; FPE100/106 Infra red LED **£2.50**; FND847 7 seg 0.8" CA £2; FND850 CA **£2.** (Data on request for linear & opto devices.)

BULK BUYERS LIST — Big bargains for quantity buyers. Resistors from **£3.80/k**, caps **£7/k**. Send SAE for list.

OHIO SCIENTIFIC COMPUTERS

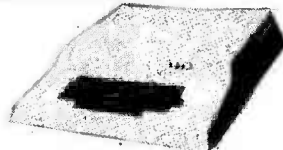

The special offer of the century (only Swanley could do it!) — For just **£158** we will supply Superboard 3 with a free power supply and modulator kit and our free guard band kit (a brilliant breakthrough in itself for this kit extends the display to 32x32, gives 1200 and 300 baud tape speeds, increases the computing speed by 50% and converts the display to 50Hz for flicker free viewing). Guard band kit is also supplied separately for **£10**. 4K extra ram **£16.95**. Case **£27**. Cassette recorder **£17**. Cegmon improved monitor rom **£29.50**. Assembler/Editor tape **£26**. Word processor program **£10**. Display expansion kit, 30 lines x 54 characters for Superboard 2 (not 3) **£20**. Chess memory expansion offer: Buy a 610 expansion board with 8K ram on board and space for another 16K for **£158** and get a free 5V 4A power kit and any extra ram you want for **£3/K**. Buy a minifloppy disc drive + case + power supply + DOS for **£275** and we will do the extra ram for **£2/K** (max 16K). Wemon Improved monitor rom **£19.95**. New Series 2 Challenger C1P: cheapo 4K version **£202**. Ohio 8K version (illustrated) **£259**.

SINCLAIR PRODUCTS*

Sinclair products only are all post free. SC110 Oscilloscope **£139**. Adaptor **£4**. Rechargeable batteries **£7.95**, X1 probe **£8.00**, X10 probe **£8.85**. Carry case **£9.90**. PFM200 **£34.50**. Adaptor **£4**. Case **£1.73**. connector kit **£11.27**. PDM35 **£32.95**. adaptor **£4**, case **£1.73**. DM235 **£56.50**. DM350 **£78.50**. DM450 **£107.95**. adaptor **£4**, case **£8.80**. rechargeable batts **£7.95**. Microvision TV **£89**, adaptor **£6.88**.

BATTERY ELIMINATORS* +
3-way type 6/7/2/9V **£3.50**. 100ma radio types with press-studs **9v** **£4.95**, 9+9v **£5.25**. Car converter 12v input, output 3/4 1/2 6/7 1/2 9v **800ma** **£3.04**.

BATTERY ELIMINATOR KITS* +
100ma radio types with press-studs **9v** **£1.79**, 9+9v **£2.50**. Stabilized 8-way types 3/4 1/2 6/7 1/2 9v/12/15/18v 100ma **£3.12**, 1 Amp **£6.30**. Stabilized power kits 2-18v 100ma **£3.12**, 1-30v 1A **£6.50**, 1-30v 2A **£16.30**. TTL and computer supplies 5V stabilized 1/2A **£3**, 3A **£14**. 6A **£20**. 12v car converters 6/7 1/2 9v 1A **£1.62**.

TV GAMES* +
AY-3-8500 + kit **£12.98**. AY-3-8550 + kit **£9.28**.

PRINTED CIRCUIT MATERIALS* +
PC etching kit, economy **£2.42**, standard **£5.76**. 40 sq in pcb 50p. 1lb FeCl2 **£2.20**. Etch resist pens: economy 50p, dalo 90p. Drill bits 1/32" or 1mm 35p. Etching dish 92p. Laminate cutter **£1.30**.

BI-PAK AUDIO MODULES* +
AL30A **£4.53**. PA12 **£3.31**. PS12 **£1.75**. T5381 **£2.90**. S450 **£27.90**. AL80 **£5.62**. PA100 **£19.24**. SPM80 **£5.26**. BMT80 **£6.62**. Stereo 30 **£24.14**. AL80 **£8.56**.

COMPONENTS* +
1N4148 1.5p. 1N4002 3.7p. NE555 8 dil 28p. 741 8 dil 26p. BC182. BC184. BC212. BC214. BC547. BC548 8.1p. Resistors 5% 1/4W E12 10R to 10M 1.0p. 0.8p for 50+ of one value. Polyester capacitors 160v .015, .088mf 2.9p, .047, .1mf 4.4p, .01mf 3.3p, .022, .033mf 3.7p, .15, .22, .33mf 5.4p, .47mf 8.0p. Polystyrene capacitors E12 63v 10 to 1000pF 4p, 1n2 to 10n 5p. Ceramic capacitors 50v **£6** 22pF to 47n 2.5p. Electrolytic capacitors 50v .5, 1, 2mf 6p, 25v .5, 1mf 6p, 16v 22, 33mf 6p, 47mf 5p, 100mf 7p, 330, 470mf 9p, 1000mf 11p. Zeners 400mw E24 2v7 to 33v 7p. Preset pots audio sockets 0.1W horiz or vert 100 to 2M2 6p. IC sockets 8 dil 8.7p, 14 dil 10.1p, 16 dil 12p.

PRINTERS



Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard 2: OKI Microline 80 (illustrated) **£259**. Base 2 800MST **£299**. Seikoshi GP80 **£225**. Epson MX80 tractor **£299**. Epson MX90 tractor + friction **£399**. Epson MX70 **£278**. Epson TX80 **£296**.
MEMORY CHIPS
2114 450ns **£2.15**. 4116 200ns **£2.83**. 4027 **£1.30**. All low current.

SWANLEY ELECTRONICS

Dept ETI, 32 Goldsea Rd, Swanley, Kent, BR8 8E2

Postage **£3.50** on computers, **£4.50** on printers and **45p** on other orders. Lists 27p post free. Please add VAT to all prices except those sections marked with a * which already include it at the old 15% rate. Overseas and credit orders welcome. ZX80 part exchange possible.

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years. Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages. Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK — THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators — Digital Meters etc.

Please send your FREE brochure without obligation to:

Name: _____
Address: _____

I am interested in —
PRACTICAL ELECTRONICS.....
COMPUTER TECHNOLOGY.....
OTHER SUBJECTS.....
(Please state your interest)


BLOCK CAPS PLEASE

ETI/5/817

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

INFRA RED REMOTE-CONTROL

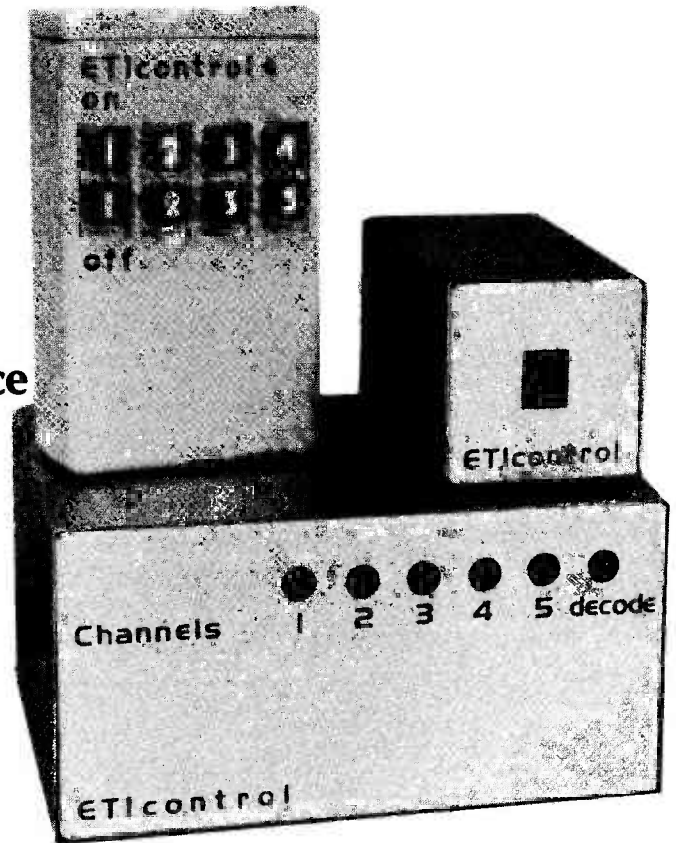Specifically designed to remote-control three mains switches and two lamp dimmers in a single room, this infra-red system can be used to activate virtually any electrical appliance from the comfort of the armchair or bed. Pure luxury at a modest price. Design by Ray Marston. Development by Plamen Pazov.



This sophisticated five-channel infra-red remote control system comprises a small hand-held transmitter and a combined receiver/decoder unit that provides five independent channels of decoded outputs (logic 0 or logic 1). Three of the control channels are of the latching type and are each controlled by a pair of push-buttons (one ON, one OFF) on the transmitter: an ON instruction produces a logic 1 output from the appropriate channel of the decoder, while an OFF instruction produces a logic 0 output.

The remaining two control channels are of the non-latching type and are each controlled by a single push-button in the transmitter: the decoder produces a logic 1 output when a non-latching transmitter button is pressed or a logic 0 output when the button is released. The transmitter thus uses a total of eight push-buttons to control the total of five remote-control channels. The system has a typical remote-control range (from transmitter to receiver) of about 10 m.

The system is specifically designed to control up to three mains power switches and two lamp dimmers in a single room. With this in mind, the remote-controlled power switch and the remote-controlled touch dimmer projects described elsewhere in this issue of ETI, and the noiseless power switch project of the March '81 issue, have been specifically designed to interface with the outputs of the decoder unit of this five-channel remote-control system. The power switches are designed to be controlled by the latching channels, and the dimmers by the non-latching channels.

Thus, you can use the system to turn on lamps, TVs, hi-fi systems, or any other appliances that draw mains currents below 5 A, by using it in conjunction with this month's remote-controlled power switch project; or to control electric heaters or other appliances that draw mains currents up to 15 A by using it in conjunction with the noiseless power switch from the March issue; plus two touch controlled lamp dimmers, all from the comfort of an armchair or bed.

In practice, of course, you can use the single hand-held transmitter to control up to five appliances in every room of the

house if you so wish. All you need to do is fit a duplicate receiver/decoder unit, etc., in all required rooms. Thus, you can use the transmitter to control dimmers, hi-fi and TV when you are in the lounge, and use the same transmitter to control a lamp, radio and electric heater when you are lying in bed. Nice.

Construction: The Transmitter



The transmitter unit is specifically designed to fit in a small Verobox (see Buylines). All components, including the eight push-button switches, are mounted on a single PCB, with the switches mounted directly on the copper side of the PCB and all other components mounted on the 'plain' side. A good deal of care is required in the construction.

Start the construction by etching the PCB and cutting it to size, noting its unusual shape. Now assemble all components other than the push-button switches, LED1 and IC1 on the plain side of the PCB and solder them in place, noting the following points;

(i) All but three of the resistors are mounted vertically on the PCB; (ii) An 18-pin DIL socket is soldered to the PCB to accommodate IC1; (iii) The two IR diodes are mounted vertically on the PCB but are then bent at right angles to pass through holes cut in the case front panel. Slide switch SW1 is soldered directly to Veropins on the PCB and is angled so that its control knob passes through a slot in the front panel. Capacitor C1 has a 10V rating and needs to be as small as possible. ➔

Fig.1 (Right) Circuit diagram for the infra-red transmitter.

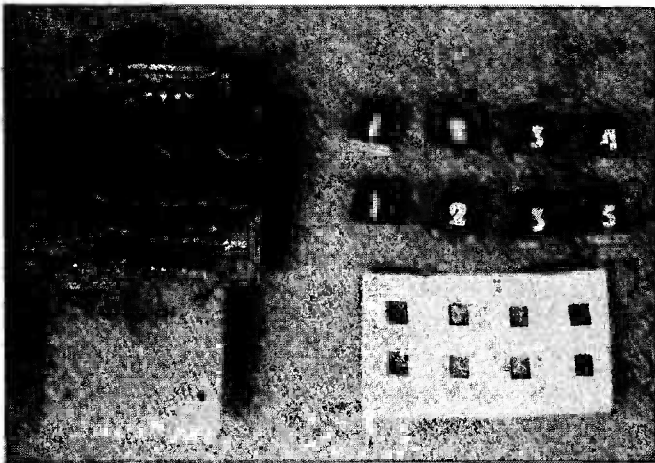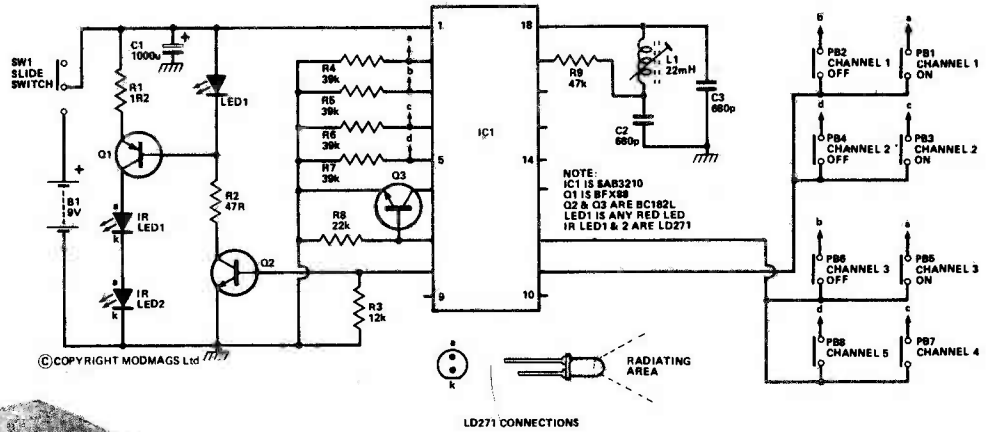Below: The completed transmitter. The two infra-red LEDs and the on/off switch are mounted through the front panel; the 'transmit' LED is positioned on the top of the case with the push-buttons so that it can be seen during operation. Note that channels 1 to 3 have two buttons each (on and off). Channels 4 and 5 are non-latching and only require one button.



This photograph shows the copper side of the assembled PCB, with the ingredients of the 'mylar sandwich'. The plastic fits over the switches and the caps hold it in place.

HOW IT WORKS

TRANSMITTER

The heart of the transmitter is IC1, an LSI PMOS chip. This chip receives instructions via an eight-row (pins 9-16) by four-column (pins 2-5) matrix that can be activated by up to 32 push-button switches. Only eight switches are used in our application. The circuit is clocked at about 60 kHz by the R9-L1-C2-C3 oscillator when the IC is active.

When the transmitter is in the quiescent state the IC is disconnected from the battery by turn-on transistor Q3 and the complete circuit (including the clock oscillator) is de-energised. Under this condition the entire circuit draws a total leakage current of only a few microamps from the supply battery. When any of the key switches are pressed, negative potential is applied to one of the 'row' pins via one of the resistors R4-7; pin 7 goes high and turns Q3 on, thus energising the IC and its clock oscillator.

Whenever the IC is energised by a press-button operation a keyboard scanner comes into operation, detects the code of the actuated switch and converts this information into a clock-related serial output code that appears on pin 8 and is unique to that particular switch. This serial code signal is fed to the infra-red transmitter LEDs via Q2 and Q1.

The transmitter serial code consists of a start bit, followed by six information bits, which are read out in biphasic code at half the clock frequency. This seven-bit serial code signal has a total frame time of about 11 ms and is repeated at a time-base rate of about 130 ms throughout the duration of a key press. When the press-button is released a seven-bit 'end of signal' code frame is transmitted and the transmitter then automatically deactivates again when Q3 turns off.

The serial output code from pin 8 is amplified by Q2 and is used to pulse constant-current generator Q1 on and off via R2 and LED1. Q1 feeds current pulses of several hundred milliamps to the two series-connected infra-red transmitter LEDs, this high current being supplied by storage capacitor C1. Although the peak IR LED currents are very high (thus ensuring a good operating range), the mean currents (averaged over one time-base period) amount to only 5 mA or so.

Thus, considering that the transmitter will typically only be required to operate for about half-a-second per instruction, it can be seen that roughly 100,000 instructions can be transmitted from a single PP3 battery during its life. Put another way, a single PP3 is capable of transmitting 250 instructions every day for about one year.

BUYLINES

The SAB3210 and SAB3271 are available from Electrovalue and Watford Electronics — Watford can also supply the LD271 and SFH205. The push-button switches and switch caps are available from Ambit International, as is the variable inductor L1. The cases used for the preamp and decoder unit are obtainable from West Hyde Developments (order as Samos 006 and 001 respectively).

PROJECT : IR Remote Control

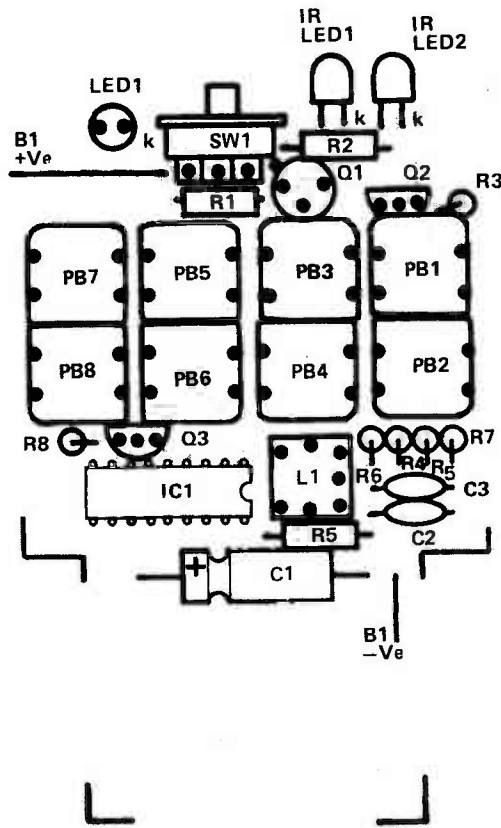


Fig.2 Component overlay for the infra-red transmitter; the board is a peculiar shape so that it will fit the case specified. Most of the resistors are mounted vertically to save space. The overlay is drawn with the component side uppermost — PCB1-8 and LED1 are actually soldered on the copper side, as shown in the photographs.

PARTS LIST

TRANSMITTER

Resistors (All 1/4 W, 5%)

R1	1R2
R2	47R
R3	12k
R4,5,6,7	39k
R8	22k
R9	47k

Capacitors

C1	1000u 10 V axial electrolytic
C2,3	680p polystyrene

Semiconductors

IC1	SAB3210
Q1	BFX88
Q2,3	BC182L
LED1	any red LED
IR LED1,2	LD271

Miscellaneous

SW1	miniature slide switch
PB1-8	KHC10901 (push-to-make non-locking)
L1	87BN132HM (22 mH variable inductor)
Verocase (code 202-21303), caps for switches (KT5 — 8 off)	

Now turn the PCB over and solder the eight push-button switches (and LED1) to the copper side. A great deal of care is required here and a miniature soldering iron is needed. Proceed as follows. First, remove the snap-on caps of the switches and straighten the four switch mounting legs, using a pair of pliers. Note that small pips are moulded into the underside of the switches, to fix their height slightly above the surface of the PCB: do not remove these pips. Now press one switch into position from the PCB copper side and solder its four legs to the PCB. Repeat the process, soldering one switch at a time, until all eight switches are in place. You'll find this a distinctly fiddly process.


When all eight switches are in place, take a strip of white mylar film (available from your local art shop), place it over the bank of switches, cut holes in the strip so that the eight push-button operating shafts pass freely through the mylar, and then fit the switch caps back in place and check that the switches operate freely. The mylar film simply enhances the appearance of the finished transmitter unit.

This completes the construction of the electronics side of the transmitter and it can now be given a simple functional test. First, set the adjustable core of L1 to mid position, fit IC1 into place, connect a 9 V (PP3) battery, and turn SW1 on. Now press the push-button switches one at a time and check in each case that LED1 flashes intermittently for the press duration. If all is well, you can fit the unit into its case, as follows.

First, offer the PCB assembly up to the top half of the case (the battery holder is in the lower half), align it with the two small front mounting holes and carefully mark out the positions of the eight push-button switches on the case, so that four broad accommodating slots can be cut in the case to accept the switches as shown in the photographs. Cut the slots and re-check the fit.

Now similarly line up the PCB assembly so that holes/slots can be cut in the metal front panel to accept LED1, the two IR diodes, and the control knob of SW1. Once the holes are cut, complete the connections to the PP3 battery in the holder in the lower half of the case and screw the whole assembly together. The transmitter construction is then complete.

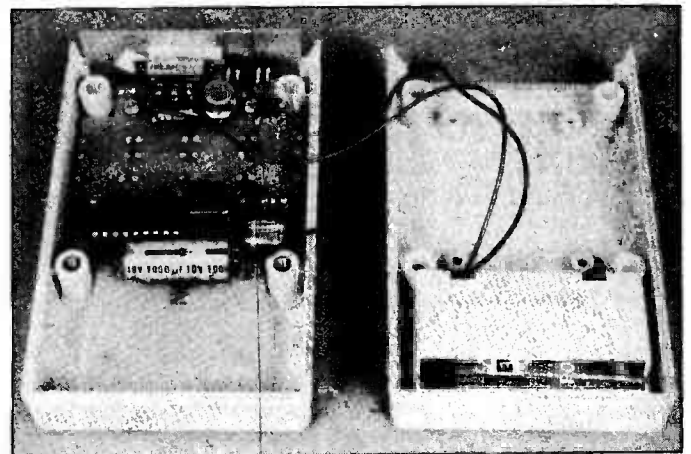Note that the transmitter cannot be given a final test until the receiver/decoder construction is complete. When using the unit, however, note that the only function of SW1 is that of ensuring that the transmitter will not be activated accidentally when carried in the pocket, etc: in normal use SW1 can be left permanently on, since the unit consumes virtually zero quiescent current.



The transmitter PCB mounted in its case. You can see how the infra-red LEDs are bent at right-angles, and the slide switch soldered to Vero pins, so that they face forward through the front panel.


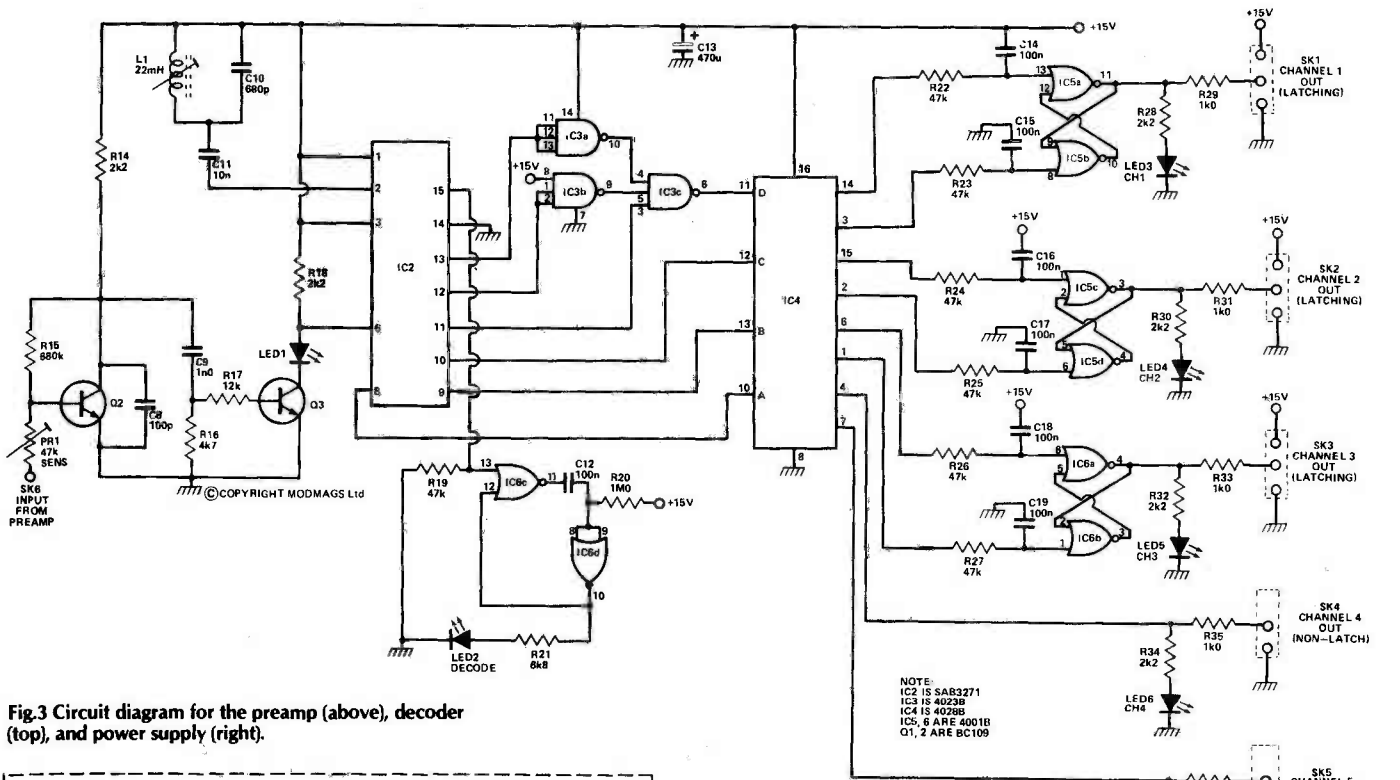
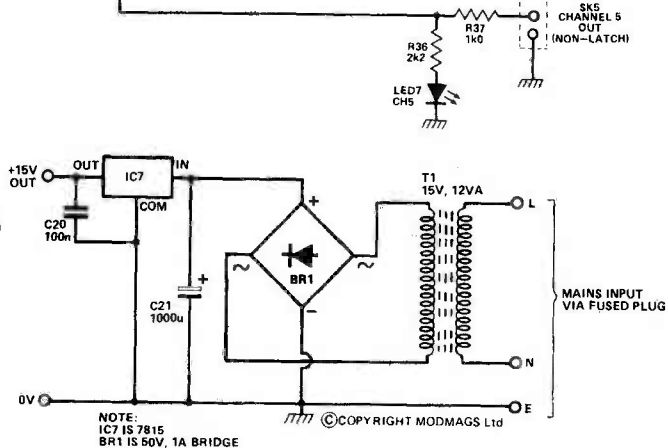


Fig.3 Circuit diagram for the preamp (above), decoder (top), and power supply (right).

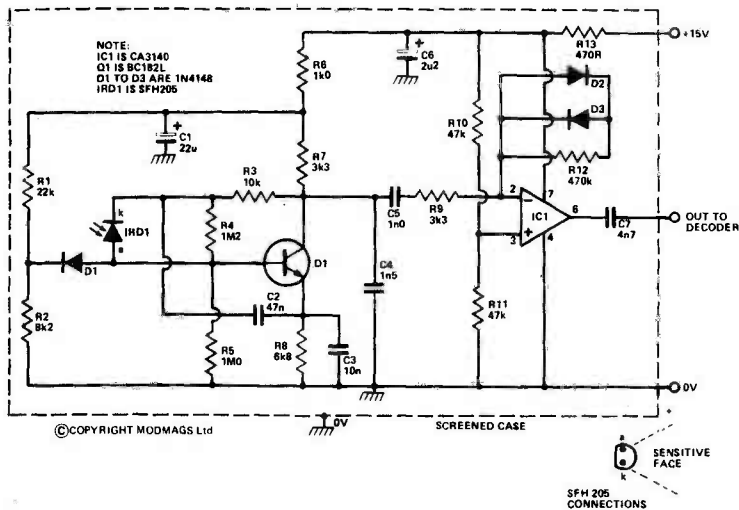


Construction: The Receiver/Decoder

The receiver/decoder is built as two units, with the IR preamp housed in one small screened case and the main decoder circuit and power supply housed in a separate, larger, box: the two units are interconnected by a length of three-core cable. In use, the preamp is placed in a clearly visible position in the room and the main unit is hidden out of sight.

Start the construction by building the IR preamplifier, assembling the components as shown by the overlay. Take care to ensure that infra-red detector IRD1 is connected with the correct polarity. When construction is complete, mount the PCB in a steel or tin case, after first cutting a hole in the case front for IRD1, and ground the case to the 0 V supply line. Finally, fit a DIN socket in the rear of the case, to facilitate connections to the main decoder/power supply unit, and complete the interwiring.

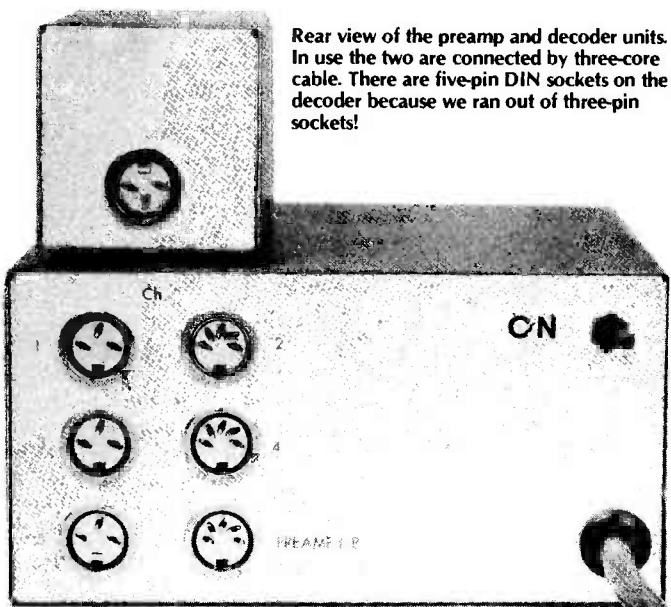Rear view of the preamp and decoder units. In use the two are connected by three-core cable. There are five-pin DIN sockets on the decoder because we ran out of three-pin sockets!



HOW IT WORKS

THE RECEIVER/DECODER

The receiver/decoder unit detects the infra-red signals from the remote-control transmitter, amplifies them to a useful level, decodes the information that the signals carry, and then uses this information to implement a switching action on one or other of the latching or non-latching outputs of the decoder. These outputs can then be used to activate external power switches and lamp dimmers, etc. The receiver/decoder unit comprises three main sections, an infra-red receiver/preamplifier, the main receiver/decoder unit, and the power supply.

The transmitter IR signals have a basic frequency of about 30 kHz (half the transmitter clock frequency): they are detected by IRD1 in the receiver preamp and are amplified first by Q1 and then by IC1. A problem in designing IR preamplifiers is that the circuit not only has to provide high gain for long range operation but must also not saturate when the transmitter is placed only a few inches from the receiver.

With the latter point in mind, R1-R2-D1 and C2 are used to prevent the bias point of Q1 shifting under heavy drive conditions. D2 and D3 clip the level of the final IC1 output signal, to prevent overdriving of following stages. The values of C2-C3-C4-C5 and C7 are chosen to make the preamplifier reasonably frequency selective, thereby ensuring a good low-noise figure. The preamplifier unit must be mounted in an electrically screened case.

The output of the preamp is further amplified by the Q2-Q3 stages of the decoder circuit and are then passed on to pin 6 of IC2. Preset PR1 enables the effective sensitivity of the circuit to be varied over a wide range and LED1 is used as a sensitivity indicator when initially setting up the circuit.

IC2, which uses L1 and C10-C11 as clock elements, inspects the incoming pin 6 signal, checks it for compatibility with its own clock frequency and with certain logic parameters, and if all is well converts the seven-bit biphasic serial input signal into an equivalent six-bit parallel code, which appears on pins 8 to 13. Simultaneously, each time that a correct code conversion is made, a brief positive pulse appears on pin 15, and this pulse is used to trigger monostable IC6c-IC6d and thereby drive LED2 on to give a visual indication of the decoding action of the circuit; this LED indication is of value when initially adjusting L1 to set up the system.


The six-bit parallel output code signals of IC2 are fed to IC3 and IC4, which decode eight of the possible six-bit combinations (corresponding to the eight possible codes generated by the eight push-buttons in the infra-red transmitter) and these decoded signals are made available on pins 14, 3, 15, 2, 6, 1, 4 and 7 of IC4. Each of these outputs is normally low, but can be driven high by closing the appropriate button on the IR transmitter.

The pin 4 and pin 7 outputs of IC4 are made available, via 1k Ω limiting resistors, at output sockets SK4 and SK5 respectively of the decoder unit, and act as non-latching remote control output channels. The 14/3, 15/2 and 6/1 outputs, on the other hand, are each used to control a simple set-reset bistable which has its output taken to one of the SK1-3 sockets, each of which acts as a latching remote control channel output. Note that the inputs to the bistables are damped by simple R-C networks, to eliminate transient activation. Also note that all output channels are provided with LED indicators, to give a visual indication of the channel state.


The complete receiver/decoder unit is powered from 15 V DC supply, derived from the mains via T1-BR1 and IC7. This supply is also made available at channel output sockets SK1 to SK3 and can be used to power auxiliary circuitry, such as the remote-controlled power switch described elsewhere in this issue of ETI.

Proceed now with the construction of the main decoder/power supply unit, noting that some care is needed in the construction of the PCB. Start the PCB assembly by fitting the four wire links and the Veropins and then systematically fit the remaining components in place, working through the assembly from the left (PSU components) to the right. Fit the regulator (IC7) with a small heatsink, sufficient to dissipate roughly 3 W.


When the assembly is complete, fit the PCB assembly into a suitable case, together with mains transformer T1, six DIN sockets (one input, five output) and the six indicating LEDs, and complete the interwiring. Finally, complete the mains connections and check that the 15 V regulator circuit is working correctly, with outputs available at sockets SK1 to SK3. If all is well the system is ready for setting up.

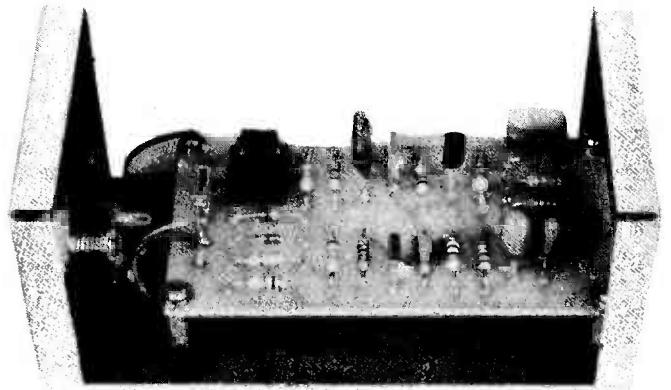

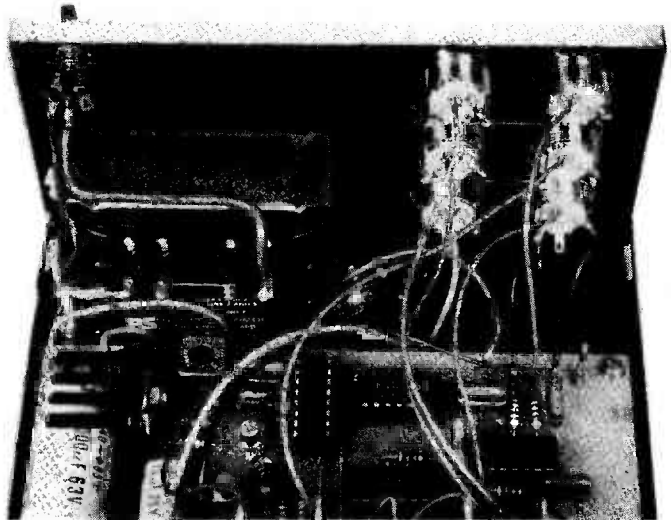Inside the preamplifier case; power and signals pass via the DIN socket on the left. The infra-red detector diode is fitted at the far right of the PCB and requires a cut-out in the side of the case.



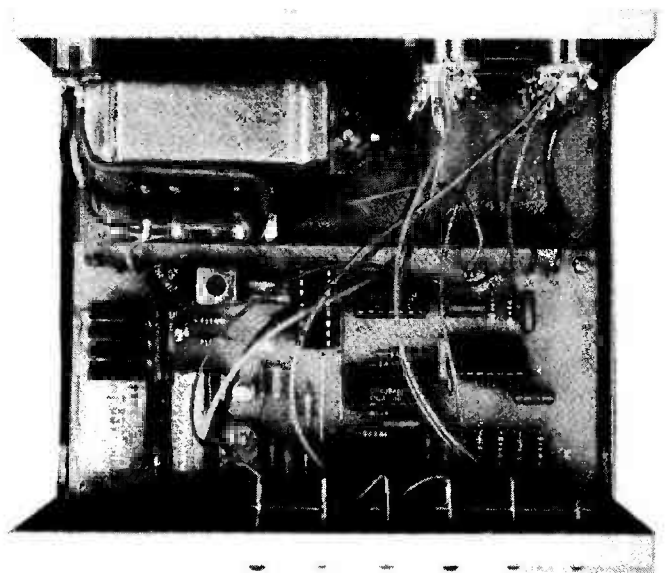Close-up of the wiring for the sockets on the decoder unit. One of these is for the input from the preamp — the other five distribute the decoded signals to the equipment under control.



General view of the decoder/power supply unit showing the internal layout. The common ground connection for the LEDs is made by soldering a length of tinned copper wire to the cathodes.

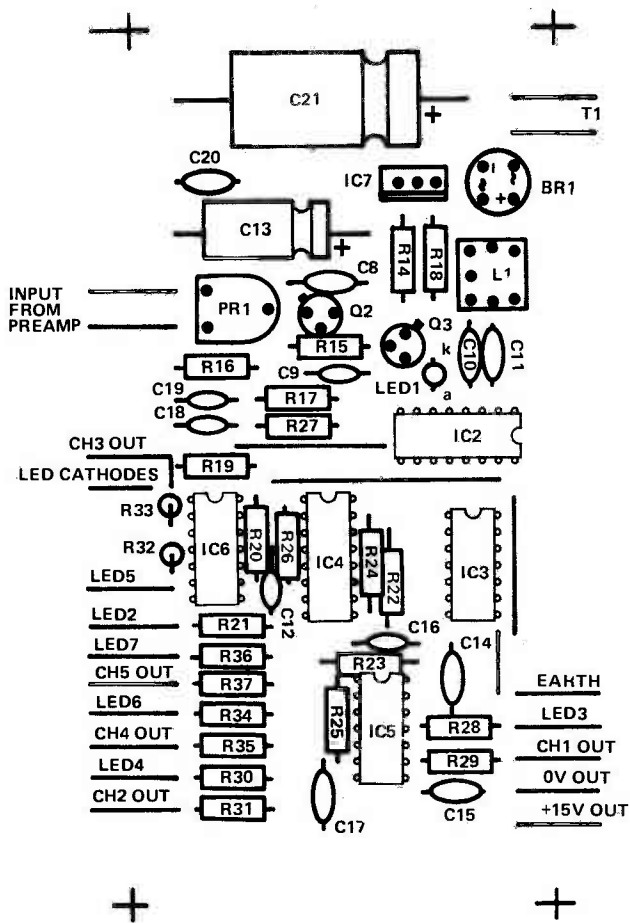


Fig.4 Component overlay for the decoder PCB. Note that LED1 is for setting up only and is soldered to the PCB.

Setting Up The System

To initially set up the five-channel remote control system, proceed as follows. First, interconnect the preamp and the main decoder/power supply unit. Switch the units on and adjust preset PR1 so that LED1 (mounted on the PCB) just glows faintly and then turn PR1 back so that the LED just turns off. Now operate the transmitter by pressing one of its buttons and see if LED2 illuminates, indicating that a decoding action is taking place. Adjust the core of L1 (in the decoder) to find the extreme positions at which decoding ceases and then finally set the core halfway between these points. If you can't get the circuit to work, use a scope to check that a code signal is being received from the output of the preamp; if not, you've probably fitted the transmitter LEDs or the preamp detector diode the wrong way round.

When all is well, check (by means of the indicating LEDs) that you can turn all five control channels on and off by using the appropriate press buttons on the transmitter. Finally, check that the system has a control range up to about 10 m, slightly adjusting the PR1 setting if necessary. The setting up procedure is then complete and the system is ready for use.

Using The System

To use the system with the touch dimmer, simply take the outputs of the SK4 and/or SK5 non-latching channels to the + and - inputs of the dimmer unit. To use the system with this month's power switch project, use the latching outputs of sockets SK1, SK2 or SK3 to feed instructions and power to the switch units.

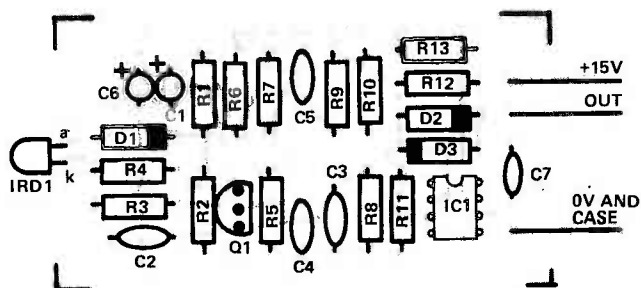


Fig.5 Overlay for the preamplifier. The leads of IRD1 have to be bent so that the sensitive face points forward.

PARTS LIST

IR PREAMP/DECODER/POWER SUPPLY

Resistors (All 1/4 W, 5%)

R1	22k
R2	8k2
R3	10k
R4	1M2
R5,20	1M0
R6,29,31,33,35,37	1k0
R7,9	3k3
R8,21	6k8
R10,11,19,22,23,24,25,26,27	47k
R12	470k
R13	470R
R14,18,28,30,32,34,36	2k2
R15	680k
R16	4k7
R17	12k

Potentiometers

PR1	47k miniature horizontal preset
-----	---------------------------------

Capacitors

C1	22u 25 V tantalum
C2	47n polyester (C280)
C3,11	10n polyester (C280)
C4	1n5 polycarbonate
C5,9	1n0 polycarbonate
C6	2u2 35 V tantalum
C7	4n7 polycarbonate
C8	100p polystyrene
C10	680p polystyrene
C12,14,15,16,17,18,19,20	100n polyester (C280)
C13	470u 25 V axial electrolytic
C21	1000u 63 V axial electrolytic

Semiconductors

IC1	CA3140
IC2	SAB3271
IC3	4023B
IC4	4028B
IC5,6	4001B
IC7	7815
Q1	BC182L
Q2,3	BC109
BR1	50 V, 1 A bridge rectifier
D1-3	1N4148
IRD1	SFH205
LED1-7	0.2" red LED

Miscellaneous

L1	87BN132HM (22 mH variable inductor)
SK1-6	three-pin DIN sockets
Transformer (15 V, 12 VA), 3/8" grommet, cases (see Buylines).	

Finally, to use the system to control the noiseless power switch project of the March '81 issue, use one of the latching outputs of the decoder to feed control information only (NOT power) to the noiseless switch.

ETI

THREE FOR FREE FROM GSC



EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B


EXP 325 £1.60 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



EXP 350 £3.15 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs Has 270 contact points including two 20 point bus-bars.



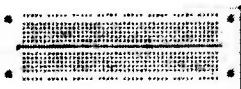EXP 300 £5.75 The most widely bought bread-board in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics



EXP 600 £8.30 Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.



EXP 650 £3.60 Has .6" centre spacing so is perfect for MICROPROCESSOR applications.



EXP 4B £2.30 Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

THE GSC 24 HOUR SERVICE TELEPHONE (0799) 21682
With your Access, American Express, Barclaycard number and your order will be in the post immediately
GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Ltd, Dept. 9TT
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21662
Telex: 817477

Available from selected stockists ELECTRONICS BY NUMBERS

No. 10 SOIL MOISTURE TESTER

No more wilting houseplants with this soil moisture test. Just place the probes into the soil and it will light up to tell you whether the soil is "too wet" or "too dry". You don't even need green fingers.


No. 11 DIGITAL ROULETTE

The suspense and excitement of the casino in your own home. Just press the button, the circle of lights go round and there is the sound of the roulette wheel as well, both gradually slowing down to reveal the winning number.

No. 12 EGG TIMER

How do you like your eggs done, hard or soft, just set the timer and it will sound when the egg is done to your liking. Long battery life because it switches itself off automatically. So get cracking now!

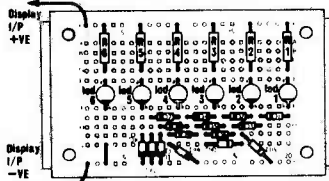Want to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph;



You will need: One EXP 300 or EXP 350 breadboard 15 silicon diodes

6 resistors 6 Light Emitting Diodes


Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components, connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

For full detailed instructions and layouts of Projects 10, 11 and 12, simply take the coupon to your nearest GSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you have missed projects, 1, 2 and 3, or 4, 5 and 6, or 7, 8 and 9, please tick the appropriate box in the coupon.


PROTO-BOARDS

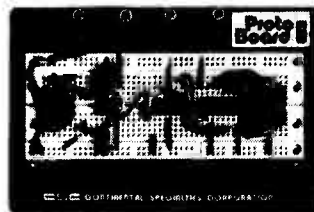The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT £9.20

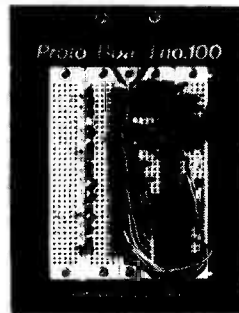

PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80

IT'S EASY WITH G.S.C.

TO RECEIVE YOUR FREE COPY OF PROJECTS 7, 8 and 9

Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

For immediate action

The GSC 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately.

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN DIP	UNIT PRICE INC. P&P @ 15% VAT	Qty req.
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.40	
EXP 300	550	6	£ 7.70	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus-Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	

PROTO-BOARDS	CONTACTS	IC CAPACITY 14 PIN DIP	UNIT PRICE INC. P&P @ 15% VAT	Qty req.
PB6	630	6	£11.73	
PB100	760	10	£14.72	

GSC (UK) Ltd., Dept. 9TT, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682. Telex: 817477.

NAME

ADDRESS

.....

.....

I enclose cheque/P.O. for £.....

Debit my Barclaycard, Access,

American Express card No.

..... Expiry date

If you missed project No's

1 to 9 tick box.

For Free catalogue tick box

Rapid Electronics

Pack No.		Pack No.			
A10	10 PP3 battery leads	50p	F331	1 BD139 transistor	45p
A72	10 3.5mm jack plugs	80p	F421	1 MJ2955 transistor	110p
A73	10 3.5mm jack sockets	80p	F43	5 78L05 regulators	180p
A74A	5 Standard jack plugs	80p	F46A	1 7805 regulator	70p
A75A	5 Strd. jack sockets	90p	F47A	1 7812 regulator	70p
A84A	5 5 pin 180 DIN plugs	90p	F49A	1 7905 regulator	75p
A85A	5 5 pin 180 DIN sockets	55p	F53	1 LM317T variable reg.	200p
C21	5 Min. slide switches	75p	F54	LM323K 3A 5V reg.	500p
C28	5 Push to make switches	70p	H11	20 1N4002 diodes	75p
C29*	5 Push to break switches	90p	H30	2 W005 bridge rectifiers	45p
C50	20 8 pin DIL sockets	170p	H60	100 1N4148 diodes	180p
C51	20 14 pin DIL sockets	200p	H73	2 C106D thyristors	90p
C52	20 16 pin DIL sockets	220p	J5	10 0.2in red LEDs	100p
E10	Resistor kit, 650 resistors 1/4W	480p	J25	10 0.2in green LEDs	150p
-	10 ea value 4.7 to 1M		J45	10 0.2in yellow LEDs	150p
-	5K-1M log in lin	35p	J70	20 0.2in LED clips	60p
-	Slide potentiometers, 60mm		J7	10 0.125in red LEDs	100p
-	travel, 5K-500K log or lin	65p	J27	10 0.125in green LEDs	150p
E26	10 100K min. presets	70p	J47	10 0.125in yellow LEDs	150p
E31	10 1u 63V electrolytics	50p	J72	20 0.125in LED clips	60p
E33	10 4u7 63V radial elec.	50p	J75	1 FND500 CC display	100p
E34	10 10u 25V radial elec.	50p	K5	5 741 op amps.	90p
E37	10 100u 25V radial elec.	75p	K20	5 CA3140 op amps.	225p
E44	10 1u 35V bead tans.	100p	K30	5 LM301A op amps.	140p
E50	10 0.01 C280 polyester	50p	K40	1 LM324 op amps.	50p
E54	10 0.01 C280 polyester	50p	K50	1 LM380 2W amp.	70p
E10	10 BC107 transistors	90p	K75	1 LM3914 LED bar graph	320p
F11	10 BC108 transistors	90p	K85	5 NE555 timers	110p
F12	10 BC109 transistors	90p	K90	1 NE556 timer	50p
F17	10 BC214L transistors	90p	K100	5 TL081 op amps.	175p
F27A	5 2N3819 transistors	100p	L8	5 4011 CMOS	130p
F311	1 BD131 transistor	45p	L9	1 4013 CMOS	40p
F312	1 BD132 transistor	45p	L11	1 4017 CMOS	75p
			L22	1 4049 CMOS	45p

All prices include VAT. Please add 50p postage and packing. Send s.a.e. for our complete catalogue.

Rapid Electronics Limited

Hillcroft House, Station Road, Fynsford, Kent



MECHANISM WITH ALARM



Assemble it in an evening!
MECHANISM & CASE
Inc. assembly instructions

DIGITAL 24 HOUR CLOCK

● SILENT RUNNING
● LARGE ILLUMINATED NUMERALS

£5.00

THREE FOR £13.50

£6.99

MECHANISMS 10 FOR £39. 100 FOR £300

● AC MAINS
● SIZE 6 3/4 x 2 3/8 x 2 3/4

Your receipt is a 2-year guarantee

HALF PRICE OFFER

HENRY'S Radio

HENRY'S RADIO
404 EDGWARE ROAD,
LONDON W2 1ED 01-723 1008

EXPORT ENQUIRIES INVITED

DELIVERY FROM STOCK

PARNDON ELECTRONICS LTD.

Dept. No. 22, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
 Special stock pack, 60 values, 10 off each **£5.50**

DIODES: IN4148 3p each. Min order quantity - 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems
 4 Way **86p** each. 6 Way **£1.00** each. 8 Way **£1.20** each

DIL SOCKETS: High quality, low profile sockets.
 8 pin - **10p**. 14 pin - **13p**. 16 pin - **15p**. 18 pin - **19p**. 20 pin - **25p**.
 22 pin - **29p**. 24 pin - **35p**. 28 pin - **39p**. 40 pin - **57p**.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
 MIN. ORDER - UK. £1.00. OVERSEAS £5. CASH WITH ORDER PLEASE

MUSICAL MICRO 24 TUNE DOOR BELL

BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied.

Plays 24 well-known tunes including:

- Star Spangled Banner,
- William Tell Overture,
- Greensleeves, Rule Britannia,
- Colonel Bogey, Oh come all ye faithful,
- plus many other popular tunes.

ONLY £11.95
+ 75p p&D
UK ONLY

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE. PLEASE ALLOW 7-21 DAYS FOR DELIVERY.

Please send me TO CHROMATRONICS, RIVER WAY, HARLOW, ESSEX Telephone (0279) 418611 ET1.5.81

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____ or debit my ACCESS/BARCLAYCARD account no _____


Signature _____

CHROMATRONICS

The SENSATIONAL CROFTON Offer

9" metal cased monitors at the lowest price ever - **£55.77 incl. VAT and carriage extra.**

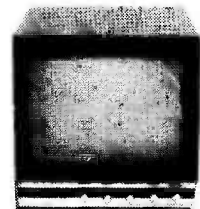P4 phosphor standard. P31 and P39 available at an extra **£11.50** total.





Sony colour camera type 2010P only **£335.00** total including VAT and P & P. 12v operation IV composite video out.

Shugart Floppy Disk Drives

SA400	£146.05
SA450	£280.31
SA800	£337.52

Prices include VAT

Ask for Crofton Mail Order Catalogue. All major credit cards accepted.

All items subject to availability. The above prices include VAT. Carriage will be charged at cost.

Phone or write to
CROFTON ELECTRONICS LIMITED
 35 Grosvenor Road, Twickenham, Middx TW1 4AD.
 Tel: 01-891 1923/1513

electronics today international BOOK SERVICE

How to order; Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires **£4.25**
 Beginners Guide to Transistors Reddihough **£4.25**
 Beginners Guide to Integrated Circuits Sinclair **£4.25**
 Understanding Electronic Circuits Sinclair **£5.10**
 Understanding Electronic Components Sinclair **£5.10**
 Beginners Guide to Radio King **£4.25**
 Beginners Guide to Audio Sinclair **£4.25**
 Understanding Electronics, Waring **£4.90**

COOKBOOKS

TV Typewriters Cookbook **£7.75**
 CMOS Cookbook **£8.20**
 Active Filters **£11.30**
 IC Timer Cookbook **£7.65**
 IC Op-Amp Cookbook **£10.00**
 Video Cookbook **£8.50**
 TTL Cookbook **£7.55**
 The Basic Cook **£4.00**
 IC Converter Cookbook **£9.50**
 Master IC Cookbook Hallmark **£7.45**

APPLICATIONS

Fire and Theft Security Systems B. Weis **£2.15**
 How To Build Electronic Kits Chapel **£3.25**
 110 Electronic Alarm Projects R.M. Marston **£4.95**
 110 Semiconductor Projects for the Home Constructor R. M. Marston **£4.95**
 110 Integrated Circuit Projects for the Home Constructor R. M. Marston **£4.95**
 110 Thyristor Projects Using SCRs R. M. Marston **£4.95**
 110 Wave Form Generator Projects R. M. Marston **£4.95**

COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book **£10.00**
 Beginners Guide to Computers and Microprocessors with Projects C. Adams **£6.05**
 BASIC Computer Games Ahl **£6.05**
 BASIC for Home Computers A self-teaching guide B. Albrecht **£6.60**
 Illustrating BASIC D. Alcock **£4.25**
 Troubleshooting to Microprocessors and Digital Logic Goodman **£5.90**
 Z-80 Microcomputer Handbook W. Barden **£7.75**
 How to Program Microcomputers W. Barden **£7.25**
 Introduction to Microcomputers and Microprocessors A. Barna **£9.50**
 Microprocessors in Instruments and Control R. J. Bibbero **£13.10**
 Basic BASIC J. S. Coan **£7.40**
 Advanced BASIC J. S. Coan **£6.40**
 Getting Acquainted with Microprocessors L. Frenzel **£7.25**
 Beginners Guide to Microprocessors C. M. Gilmore **£4.90**
 1001 Things to do with Your Personal Computer Sawusch **£6.00**
 Beginning BASIC R. E. Gosling **£4.75**
 Microprocessor Programming for Computer Hobbyists N. Graham **£7.15**
 Miniprocessors from Calculators to Computers Heiserman **£5.35**
 Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn **£17.40**
 BASIC Programming J. G. Kemeny **£8.20**
 Microprocessor Systems Design E. Klingman **£17.65**
 Intro to Microprocessors Leventhal **£11.00**
 Microprocessor — Technology, Architecture & Applications D. R. McGlynn **£11.30**
 Interactive Computing with BASIC Monro **£4.35**
 BASIC with Style P. Nagin **£4.50**
 Software Design for Microcomputers Ogdin **£8.65**
 Microcomputer Design Ogdin **£7.45**
 Microcomputer Base Design Peatman **£6.10**
 Hands on BASIC with a PET Peckham **£10.50**
 Complete Microcomputer Systems Handbook **£8.75**
 6800 Software Gourmet Guide and Cookbook Scelbi **£9.20**
 8080 Software Gourmet Guide and Cookbook **£9.20**
 The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony **£8.35**
 8080/8085 Software Design Titus **£7.60**
 57 Practical Programs & Games in BASIC Tractor **£6.65**
 How to Design, Build and Program Your own Working Computer System **£7.10**
 Your Own Computer Waite **£2.25**
 Microprocessor/Microprogramming Handbook Ward **£6.20**

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly **£7.25**
 Practical Digital Design Using ICs J. Greenfield **£16.00**
 Designing With TTL Integrated Circuits Texas Instruments **£9.80**
 How To Use IC Circuit Logic Elements J. Streater **£4.85**
 110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston **£4.95**
 Understanding CMOS Integrated Circuits R. Melen **£4.60**
 MOS Digital ICs G. Flynn **£5.25**

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair **£4.00**
 Working with the Oscilloscope A. Saunders **£4.60**
 Servicing with the Oscilloscope A. King **£7.50**
 Radio Television and Audio Test Instruments King **£8.30**

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) **£8.45**
 110 Operational Amplifier Projects for the Home Constructor R. M. Marston **£4.95**
 Designing With Operational Amplifiers Burr Brown **£19.65**
 Operational Amplifiers Design and Applications G. Tobery (Burr Brown) **£7.80**

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carison **£7.65**
 Digital Signal Processing Theory & Applications L. R. Rabiner **£24.40**
 Electronic Communication Systems G. Kennedy **£8.75**
 Frequency Synthesis, Theory & Design Mannassewitsch **£25.00**
 Principles of Communication Systems H. Taub **£8.40**

THEORY

Introduction to Digital Filtering Bogner **£10.60**
 Transistor Circuit Design Texas Instruments **£10.00**
 Foundations of Wireless Electronics M. G. Scroggie **£6.10**
 Electronic Circuit Design Handbook 4th Edition **£16.75**
 Master Guide to Electronic Circuits Adams **£9.25**

REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner **£38.00**
 Electronic Components M. A. Colwell **£3.40**
 Electronic Diagrams M. A. Colwell **£3.40**
 International Transistor Selector T. D. Towers New update **£10.70**
 International FET Selector T. D. Towers New update **£4.60**
 International Op-Amp Linear IC Selector Towers **£8.00**
 International Microprocessor Selector (NEW) Towers **£16.00**
 Radio, TV and Audio Technical Reference Amos **£37.00**

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair **£4.00**
 Integrated Electronics J. Milman **£6.20**
 Practical Solid State DC Supplies T. D. Towers **£6.50**
 Practical Triac/SCR Projects for the Experimenter R. Fox **£2.35**
 Printed Circuit Assembly Hughes & Colwell **£3.40**


Fallen behind recent advances?
 Just starting out?

Need a decent reference book?

ETI Book Service provides an easy way of getting your hands on the right title.

DIGITAL THERMOMETER

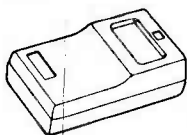This is one of our range of PROJECT KITS. It includes all the parts required to complete the project, including the case. Calibration is very simple and an accuracy of up to 1% can be obtained. The instrument covers the range -50°C to $+150^{\circ}\text{C}$. Read-out is on an LCD display. Power requirement is a 9V Battery. An ideal instrument for home or laboratory. Full instructions included.



PROJECT KIT 800104 £26.50

MUSICAL BOX

This 'electronic musical box' can be used in a variety of applications. These include toys, video games and doorbells. It can be programmed to play no less than 27 tunes. The circuit is based on the AY-3-1350 which offers a considerable improvement over similar devices. The output can be switched from 'piano' to 'organ' like quality. The project includes all the components, case, loudspeaker and full instructions. An easy project for the beginner. An additional amplifier is available if required.

PROJECT KIT 80502K £25-95 (Musical Box)
PROJECT KIT 80543K £3-95 (Stamp Amplifier)

The High COM system of noise reduction, developed by TELEFUNKEN, offers considerable advantages over existing systems. The Compressor/Expander circuits are designed around a specially designed IC, the U401B. The unit is designed for use with cassette and reel-to-reel tape systems to give professional quality, low noise recordings.

TECHNICAL SPECIFICATIONS:

Frequency Range 20-18Hz (+0, -3dB)
Signal/Noise ratio 80dB (DIN input)
85dB (Socket input)
Input Sensitivity DIN 0.6mV/6k ohm
Output Sensitivity DIN 130mV/79k ohm

Distortion less than 0.2%
Noise reduction at 100Hz : 15dB
at 3kHz : 20dB
at 15kHz : 25dB

FULL SPECIFICATION AVAILABLE

The project packs include all the electronic components, self adhesive front panel, prebuilt and tested HIGH COM modules and PCBs. The meter circuit uses an LED bar display and is essential for the operation of the unit.

HIGH COM (81117-1) £49-55
Meter/Display (9860 + 9817) £15.40
HIGH COM Power Supply (8117-2) £14.50
Case for project POA

DISCO PROJECTS

MINIMIXER

This mixer is easy to assemble, most parts are mounted on the single PCB. It incorporates two stereo disc inputs, two microphone inputs and a stereo tape input. Slider controls for level controls, rotary pots for tone controls. Distortion is approx 0.1%, frequency response 20Hz to 25kHz (3dB)

Project Pack 81068 £37-50 Case £7-50

DISCO LIGHTS

This ceiling lights project controls a matrix of 25 x 100W lamps. A pre-programmed IC switches them in 22 different sequences of patterns. Patterns can be repeated if required. Triac controlled outputs. Lamps not supplied. Mains operation.

Project Pack 81012 £53-95

SWINGING POSTER

A specially printed poster comes to life when the red and green lamps powered by this circuit are switched on. A random sequence makes the disco girl appear to dance. Poster included. Lamps not provided (100W)

Project Pack £17-70

HOW TO ORDER

Send a cheque or postal order to DORAM ELECTRONICS LTD or write or ring with your ACCESS account number. All our prices include VAT at 15%. Overseas customers please deduct 15%. Please add 40p to the cost of all UK orders for postage and packing. An answering service is available to take your orders outside our normal office hours. We are a MAIL ORDER business.

SUMMER ISSUE OF OUR CATALOGUE AVAILABLE - Send 14p stamp for your copy.

PROJECT PACKS include PCB, Components and data, Cases etc extra.



PROJECT PACKS

Pools Predictor (79053) LED Display	£ 8-15
Ioniser (9823) Negative ion generator	£10-50
Talk Funny (80052) Ring Modulator	£10-00
Photo Process Timer (81101)	£18-20
Cackling Egg Timer (9985) It clucks!	£ 7-20
Sound Effects Unit (81112) Guns, trains etc	£ 8-30
Elektornado (9874) 100W power Amp	£19-50
Top-preamp (80023) Hifi preamp	£34-40
Guitar Preamp (77020)	£ 6-50
Analogue Reverb (9973) 100mS delay	£27-70
Elektor Vocoder (80068) 10 channels	£162-50
2½ Digit DVM (81105)	£23-35
AM Receiver (81111) Easy to build	£10-25
Touch switch (81008) 12 positions	£10-00
200W Disco Power Amp (81082)	£20-85
Swinging Poster (81073) Moving picture	£17-20
STAMP (80543) Mini amplifier	£ 3-75
Steam Train Sound (80019) sound effects	£ 6-50
Pest Pester (80130) Insect repellent	£ 2-35
Stereo Disc Preamp (80532)	£ 5-20
Programmable Car Wiper delay (80086)	£15-85
Active Car Aerial (80018) AM/FM amplifier	£13-85
Aerial Booster (80022)	£ 5-65
Full list in our new catalogue.	

DORAM

ELECTRONICS LTD

Fitzroy House, Market Place,
Swaffham, Norfolk PE37 7QH

Tel: (0760) 21627

ASTROLOGUE

When it finally gets off the ground, the Space Shuttle may have a solar power system. Ian Graham reports on the latest developments



Despite last minute hitches in the Space Shuttle's first-flight preparations, plans for future flights are well advanced. To help provide power for Space Shuttle flights, Lockheed Missiles & Space Company is building a huge solar array wing for NASA. The wing, which folds up like an accordion, will be used on an early mission to prove that Solar Electric Propulsion (SEP) arrays can generate the enormous power required.

The amount of fuel that can be carried on-board the Shuttle

limits its time in orbit to seven days. The SEP array offers a means of extending the vehicle's orbital period.

The experimental wing is 105 ft long and 13½ ft wide. In space it is unfolded from the cargo bay, and on its first flight it will be unfolded and retracted several times to study its behaviour in space.


Materially Speaking

The wing is not a rigid structure, but is made from a lightweight, flexible plastic (called kapton) and contains wrap-around-contact cells welded directly to the array blanket. This printed circuit approach has been adopted to eliminate heavy adhesives and allow greater flexibility during handling.

The structure represents an advance in solar power generation. It can produce 66 W per kilogram compared with 20 W per kilogram in present systems. Up to 75 W per kilogram is feasible using the same structural concepts.

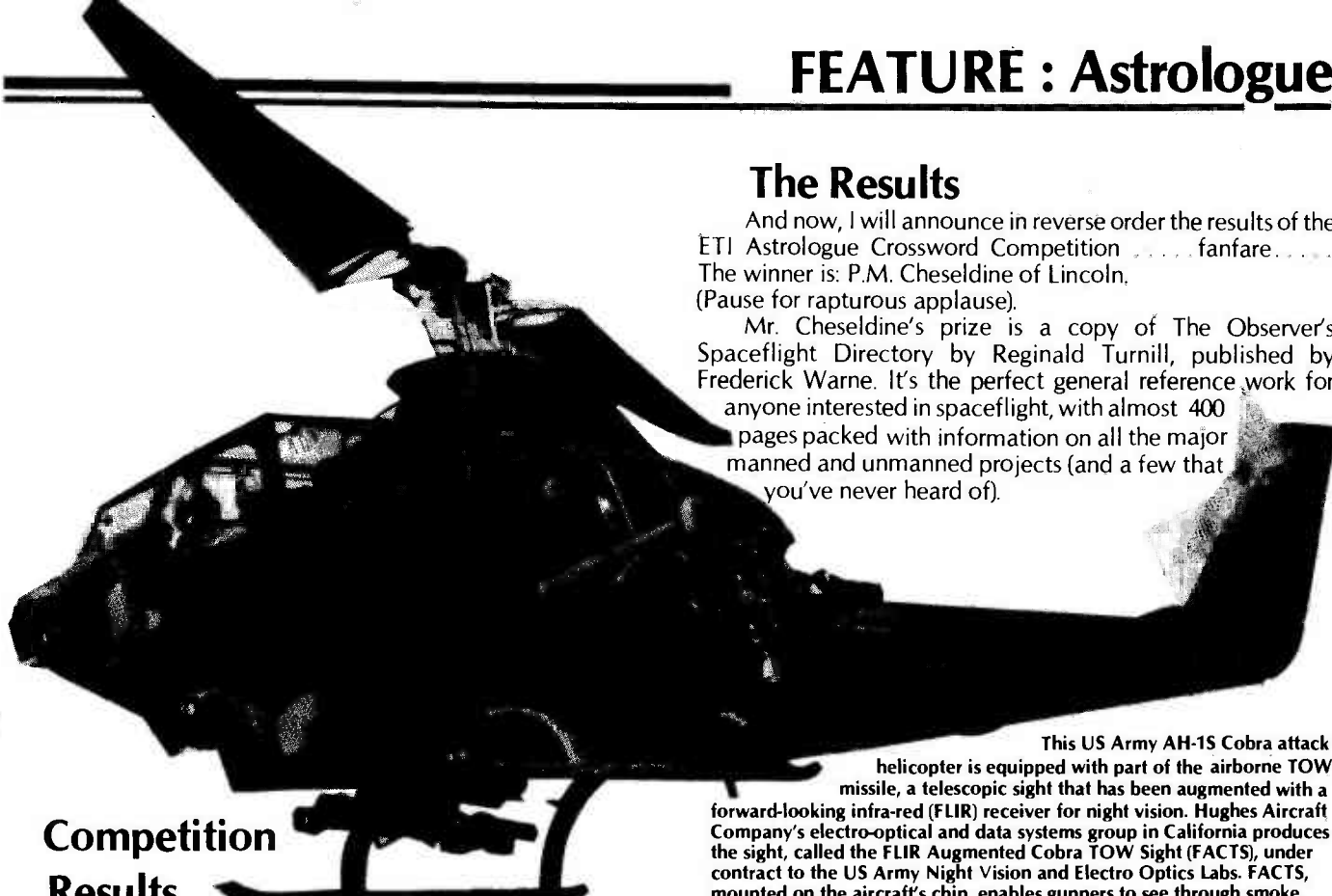Lockheed originally produced this design for use with a space propulsion system incorporating ion engines to power Earth-orbital and planetary missions. The potential fuel economy of ion propulsion is 10 times that of any conventional propulsion system.






Competition Results

January 31st marked the end of the Astrologue Crossword Competition, set in the January issue. Check your answers against the correct solutions shown here. Most of the millions of entries received (a slight exaggeration) were correct. Some found their way to Astrologue from as far away as South Africa and India. However, the business of totting up the numerical value of the solutions sorted out the men from the boys.

If you gave each square of the grid a value and did the arithmetic, you should have arrived at 1522. If you wrote down all the solutions and added up the value of each, you should have had 2169 on the bottom line (as some letters appeared in both across and down positions and were counted twice). Some enterprising readers came up with their own computer programs to take the pain out of the arithmetic. My thanks to Henry Budgett of Computing Today for his assistance in bringing the magic of the silicon chip to bear on the Astrologue Crossword.

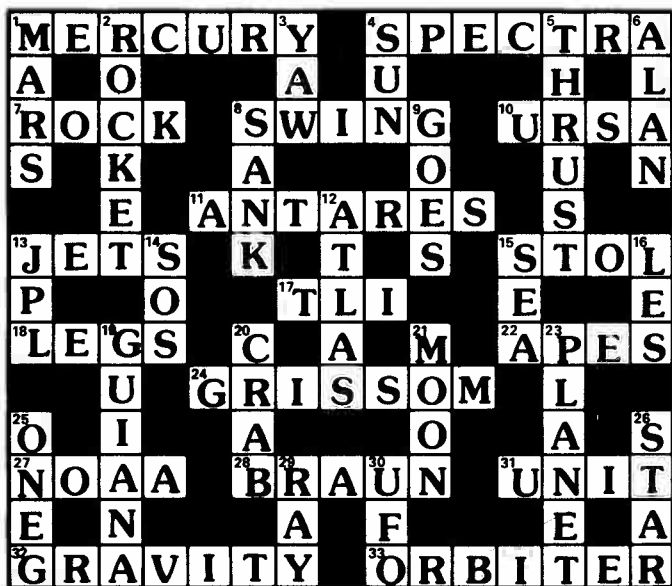

The Results

And now, I will announce in reverse order the results of the ETI Astrologue Crossword Competition . . . fanfare . . . The winner is: P.M. Cheseldine of Lincoln. (Pause for rapturous applause).

Mr. Cheseldine's prize is a copy of The Observer's Spaceflight Directory by Reginald Turnill, published by Frederick Warne. It's the perfect general reference work for anyone interested in spaceflight, with almost 400 pages packed with information on all the major manned and unmanned projects (and a few that you've never heard of).

This US Army AH-1S Cobra attack helicopter is equipped with part of the airborne TOW missile, a telescopic sight that has been augmented with a forward-looking infra-red (FLIR) receiver for night vision. Hughes Aircraft Company's electro-optical and data systems group in California produces the sight, called the FLIR Augmented Cobra TOW Sight (FACTS), under contract to the US Army Night Vision and Electro Optics Labs. FACTS, mounted on the aircraft's chin, enables gunners to see through smoke, haze or darkness to accurately fire TOW missiles, rockets and cannon. It makes the helicopter gunship a round-the-clock combat machine.

SHORTS

Representatives of 17 European governments met in Paris in January to discuss plans for an Operational Meteosat System. It was felt that such a system would be of substantial benefit to Europe and would also be a valuable contribution to the global observation programme of the World Meteorological Organisation. Meteosat 1, launched in November 1977, still collects weather information from land, marine and airborne observation platforms.

British Aerospace Dynamics Group's Bristol Division has just taken delivery of a fourth Ferranti Argus 700 computer system, valued at £93,000. This latest addition to British Aerospace's 700 family will be used in the development of real-time software for military applications.

Galileo, NASA's Jupiter probe (featured in ETI March '81 Astrologue), will be fitted with a European engine. Messerschmitt-Bolkow-Blohn are to build the engine, which will consist of one main thrust chamber and 10 small attitude control thrusters.

The Space Shuttle launch has been put back to some time in April, because of a fault found in the thermal insulation of the External Tank. When the tank was fuelled, some of the insulation separated from the contracting tank. Martin-Marietta engineers will have to make repairs in situ.

One of Jimmy Carter's last acts before packing up his knick-knacks was to propose a 1982 NASA budget of \$6.72 billion, more than a 20% increase over this year's budget. The Space Shuttle gains by the increase — its funding goes up from £1.94 billion to £2.23 billion.



Apollo I. Its sound quality is as outstanding as its looks. (And makes the price sound ridiculous.)

Three waveband radio and cassette recorder (battery/mains).

BIG SET QUALITY

Big set sound quality from a portable radio/cassette recorder?

That's the remarkable achievement of the Apollo I. It really does have the rich tonal quality you'd only expect in an expensive home unit. On radio or cassette, reproduction is crystal clear even at full volume and over the whole of the tone range. The band change switch gives you the choice of FM, Medium or long wave and a big tuning control provides you with sensitive station tuning, helped by very clear and legible dial markings.

BIG FUNCTION RANGE

Remarkable, too, is the Apollo I's range of functions. In addition to the three band radio and cassette playing capability, it lets you record direct from the radio, record through the built-in condenser microphone, record through an external microphone (not included), and play yourself to sleep with taped music that switches off automatically.

Only
£19.95

plus £2.95 p & p

EXTRA 'EXTRAS'

Apollo I has many features you'd hardly expect if it was twice the price. For example: automatic volume control on the built-in microphone, ear-phone monitoring of recordings, battery or mains operation, provision for remote control, etc.

SENSATIONAL VALUE

Most remarkable thing about Apollo I, though, has to be its price. Any multi-function set would be extremely good value for this kind of money. But the Apollo, with so many 'extras' and such superb quality reproduction, is an absolute bargain. Guaranteed for 12 months.

- Exceptional sound quality
- Battery/mains operation
- Sensitive tuning
- Push button recorder
- Built-in microphone
- Tone control
- Auto recording level control
- Auto stop
- Sleep function switch
- Earphone
- Sockets for external microphone and remote control.

DATA

Output 2W (max). Power consumption 8W. Speaker 4in. 4ohm. Dimensions 11½in x 8in x 3¼in (approx). Weight 5lb.

☎ Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention.

MITRAD 68-70 High Street, Kettering, Northants. NN16 8SY. Tel. (0536) 522024

To Mitrad, 68-70 High Street, Kettering, Northants.

Please send me Apollo I radio/cassette recorder at £19.95 plus £2.95 p & p (£22.90)

Total value of my order £ _____

I enclose cheque/PO made payable to Mitrad. Or debit my

Access/Barclaycard No. _____



Signature _____

Name _____

Address _____

(BLOCK LETTERS PLEASE)

Allow up to 28 days for delivery. Full refund if not completely satisfied. Registered in England No 2554356 Code 003/ET



Self Instruction Courses from Cambridge Learning


They're faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction — you know that you are learning and without mindless drudgery. With a good self-instruction course you become the world's best teacher.

MICROCOMPUTERS ARE COMING— RIDE THE WAVE! LEARN TO PROGRAM!

MILLIONS OF JOBS ARE THREATENED, BUT MILLIONS MORE WILL BE CREATED

LEARN BASIC

The language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flow-charting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest, and computer games.

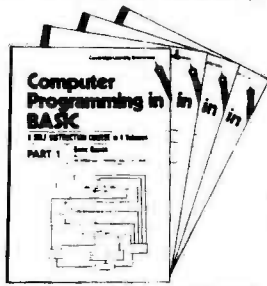

COMPUTER PROGRAMMING IN BASIC (CPB) 4 Vols. £10.00

Book 1 Computers and what they do well: READ, DATA, PRINT, powers, brackets, variable names; LET, errors, coding simple programs.
Book 2 High- and low-level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.
Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
Book 4 Advanced BASIC; subroutines; string variables; files, complex programming; examples; glossary.

THE BASIC HANDBOOK (BHB) £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL (ANS) £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here, as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.


THE ALGORITHM WRITER'S GUIDE (AWG) £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

JOIN THE DIGITAL REVOLUTION!

DESIGN OF DIGITAL SYSTEMS (DDS) 6 Vols. £13.50

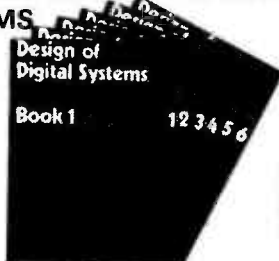Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers.




BOOK 1 Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems. **BOOK 2** OR and AND functions; multiple-input gates; truth tables. *De Morgan's Laws*; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic. **BOOK 3** Half, full, serial, and parallel adders; subtraction; processors and ALU's; multiplication and division. **BOOK 4** Flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters. *ROMS and RAMS*. **BOOK 5** Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address de-coding. **BOOK 6** CPU; memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems.

Digital calculators and watches came in during the 1970's. Soon you will see digital cash cards, telephones, car instruments, and TV messages from your friends.

DIGITAL COMPUTER LOGIC AND ELECTRONICS (DCL) 4 Vols. £7.50

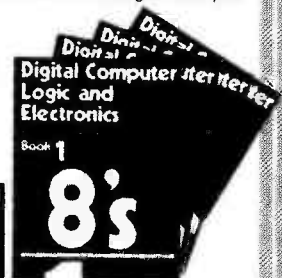A course covering the material in *italics* on the left, but at a slower pace. (4 vols)



GUARANTEE — No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition within 28 days. Our free booklist is sent with each order.

CAMBRIDGE LEARNING LTD. (Registered in England No. 1328762)

Unit 12, Rivermill Site, FREEPOST, St. Ives, HUNTINGDON, Cambs PE17 4BR - Phone 0480 67446

Order Form

To: Cambridge Learning Ltd., Unit 12, Rivermill Site, Freeport, St. Ives, Huntingdon, Cambs, PE17 4BR

PLEASE SEND: Quantity

CPB (£10.00)
BHB (£11.50)
ANS (£5.90)
AWG (£4.00)
DDS (£13.50)
DCL (£7.50)

THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL: Europe, North Africa, Middle East, add 1/3 to price of books. Japan, Australia, New Zealand, Pacific Islands add 1/2. Elsewhere add 1/2.

U.K. Delivery: up to 28 days (or send 50p per course for 1st class post)

Name

Address

FOUR WAYS TO PAY

- 1) A U.K. cheque or a U.K. postal order (Not Eire)
- 2) A bank draft in sterling on a London bank (available at any major bank)
- 3) Please charge my Access, American Express, Barclaycard, Diners, Visa, Mastercharge, Trustcard.

Card No


Expiry Date

Signed

Or phone us with these credit card details on 0480 67446 (24 hour ansafone service)

DIGITAL CLOCK

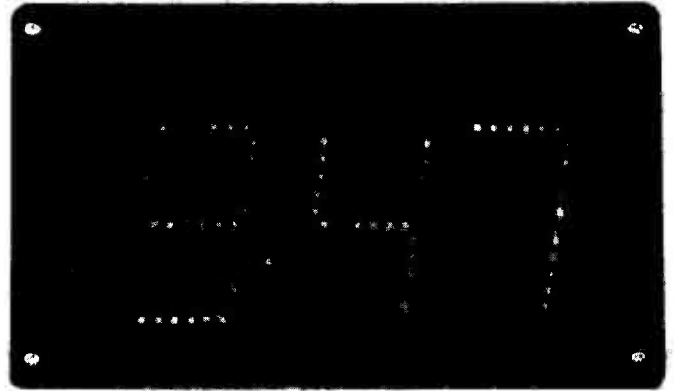Here's the ideal thing for the kitchen, workshop, garage or shed — in fact, anywhere you need a digital clock that just can't be missed! Design by Barry Wilkinson.



Isn't it what you've always wanted — a digital clock with a decent sized display? Seeing the time at a glance is convenient in many situations and that's precisely what this clock has been designed for. The display features three seven-segment digits for the 'minutes units', 'minutes tens' and 'hours units' plus a single column '1' for the hours tens' displays. Each segment in the individual display is made up of a string of LEDs connected in series. Each vertical segment contains five individual LEDs, while each horizontal segment contains six. Overall height of the display is around 60 mm.

We used rectangular LEDs as they provided by far the best looking display compared to the more familiar round LEDs. A 'flashing colon' between the hours and minutes digits is provided to reassure you that the clock is going! However, as a binary divider clocking from the mains is used to drive the clock, a 1 S output is unfortunately not available and so the next best output was chosen. This proved to be a division of 32 and thus, from 50 Hz, a pulse is obtained every 1.56 S — this is used to flash the colon.

Design

There are a number of interesting aspects to the design of this digital clock. For a start, conventional CMOS binary dividers have been used in preference to one of the special clock divider chips. The latter are very handy, no doubt about that, but they are incapable of driving a large sized display like the one used here. The voltage drop across each segment of the multi-LED display varies depending on the type and colour of LED used. Whilst we have used red LEDs, which have a voltage drop of around 1V6 each, green or yellow LEDs may be used and these have around a 2V1 drop each; some of the new 'high efficiency' LEDs also exhibit a 2V1 drop. This means that for a horizontal segment in our display, the maximum voltage drop may be as high as 12V6 (six LEDs times 2V1). The clock chips available cannot readily cope with this but CMOS decoders can be arranged to do what we want.

You will notice from the circuit that the LED segments are driven by 4511 CMOS decoders which provide up to 25 mA per segment, with the actual current being determined by current limiting resistors. The current per segment in our circuit is limited to around 20 mA. However, the maximum voltage across CMOS is limited to 15 V and a supply of around 18 V was necessary to allow for the drop across the display segment plus the drop across the limiting resistor and the 1V5 lost in the 4511 output circuit. To overcome this difficulty, we stabilised the negative supply rail for the CMOS to 12 V and the negative side of all the display segments is taken to the *unregulated* negative

supply. The zener action of the LEDs (ie, there is no current flow below about 1V4 per LED) ensures that the outputs of the 4511 are never 'pulled' below their negative supply rail.

Construction

We found it necessary to use a double-sided printed circuit board for this project to avoid a large, cumbersome board which we feel sure you'd agree would be rather unattractive.

The board used in our prototype did not use plated-through holes as it is not really necessary. However, there are many fine tracks on the board and we recommend you use a soldering iron with a small tip. When soldering tracks on the top side of the board where a component lead connects to a corresponding track on the underside of the board, always ensure that you heat the joint sufficiently to get a good flow of solder and avoid a dry joint.


To commence assembly, first check that the three mounting holes around the board perimeter and the two holes for the time setting push button switches are the correct diameter. It's awfully hard to drill the board after the other components are mounted.

Commence assembly by soldering in all the resistors, capacitors and diodes and the two transistors. You could leave C1, which mounts on the rear side of the board, until all the other components are assembled if you wish. Take care with the orientation of the diodes, paying particular attention to the component overlay. Note that different value current-limiting resistors are required, according to the type (and thus the voltage drop) of LEDs chosen. Refer to Table 1 for the appropriate values.


Resistor	1V6 LEDs	2V1 LEDs
R7, 10, 13, 14, 17	180R	150R
R20, 23, 26, 29	180R	150R
R8, 9, 11, 12, 15, 16	270R	180R
R18, 19, 24, 25, 27, 28	270R	180R
R30, 31	270R	180R

Table 1. Value of current limiting resistors for the LEDs.

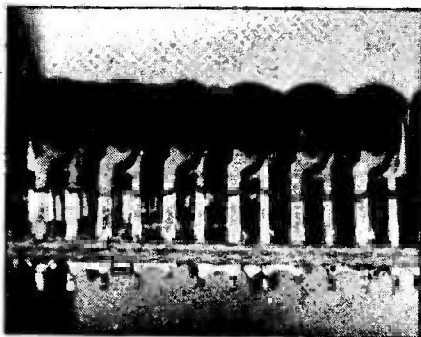As CMOS ICs are used, take care when inserting them that you handle the devices with due care. Carefully remove them from their packaging, taking care not to handle the pins — pick them up with your thumb and forefinger grasping the ends of the package, not the pins. Make sure you have them correctly.



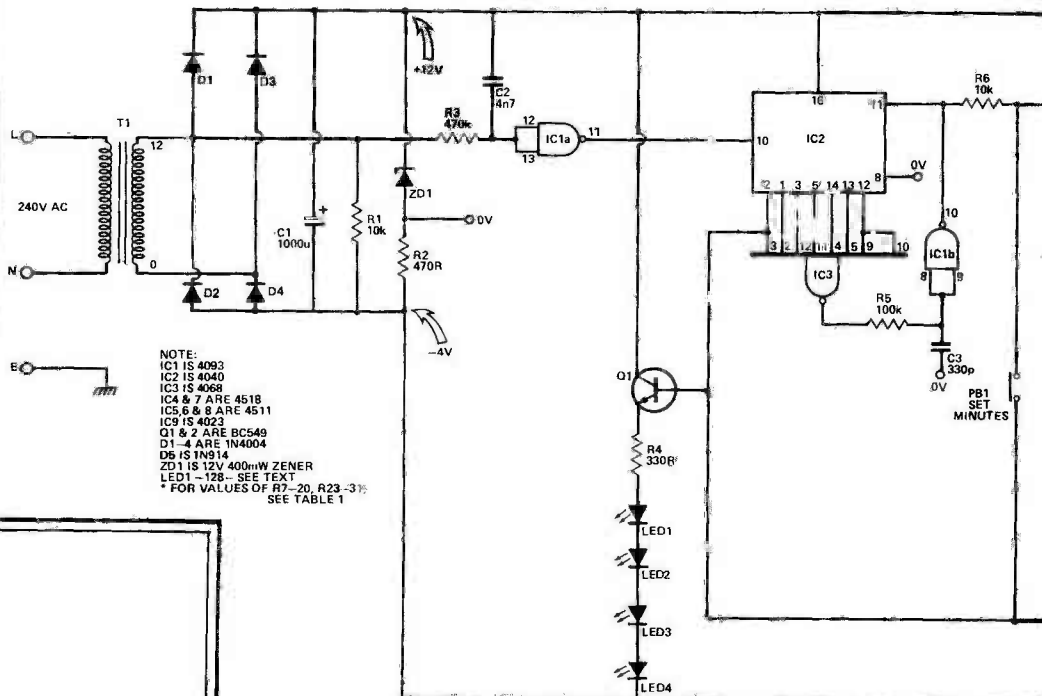Above: The LEDs are mounted by butting the 'shoulders' on the leads against the PCB.
Fig.1 (Right) Circuit diagram of the Digital Clock.



NOTE:
IC1 IS 4093
IC2 IS 4040
IC3 IS 4023
IC4 & 7 ARE 4518
IC5, 6 & 8 ARE 4511
IC9 IS 4023
Q1 & 2 ARE BC549
D1-4 ARE 1N4004
D5 IS 1N914
ZD1 IS 12V 400mW ZENER
LED1-128- SEE TEXT
* FOR VALUES OF R7-20, R23-31 SEE TABLE 1

PARTS LIST

Resistors (all 1/4 W, 5%)

R1,6,21,22	10k
R2	470R
R3	470k
R4	330R
R5,32	100k
R7-20	see Table 1
R23-31	see Table 1

Capacitors

C1	1000u 25 V electrolytic, PCB-mounting
C2	4n7 polyester
C3,4	330p ceramic

Semiconductors

IC1	4093B
IC2	4040B
IC3	4068B
IC4,7	4518B
IC5,6,8	4511B
IC9	4023B
Q1,2	BC549
D1-4	1N4004
D5	1N914
ZD1	12 V, 400 mW
LED1-128	rectangular LEDs (see text)


Miscellaneous


PB1,2	push-button switches, non-latching
Transformer (12 V @ 1 A), sheet of plastic, case etc.	

The power supply is simply a transformer with a 12 V secondary, whose output is full wave rectified by D1-4 and filtered by C1. The IC supply is stabilised by ZD1 to 12 V DC. The AC voltage is also coupled to the input of IC1a by R3 to provide a 50 Hz clock frequency. R3 protects IC1a against input damage as the AC voltage exceeds the supply rail of the ICs. C2 acts as a filter to prevent false counting, and IC1 has Schmitt trigger inputs which also help to prevent false triggering. The output of IC1a is a clean 50 Hz square wave.

To derive the 'minutes' output the mains frequency must be divided by 3000: this is done by IC2, a 12-stage binary counter. The total division ratio of this IC is 1:4096, so the outputs of the 4th, 5th, 6th, 8th, 9th, 10th and 12th stages are decoded (when all are high), taking the output of IC3 low on the count of 3000 (binary 101110111000). After a short delay (about 30 uS) due to R5/C3, the output of IC1b goes high, resetting IC2. This immediately causes the output of IC3 to return high

Fig.2 The overlay as seen from the component side. Note that this is a double-sided board.

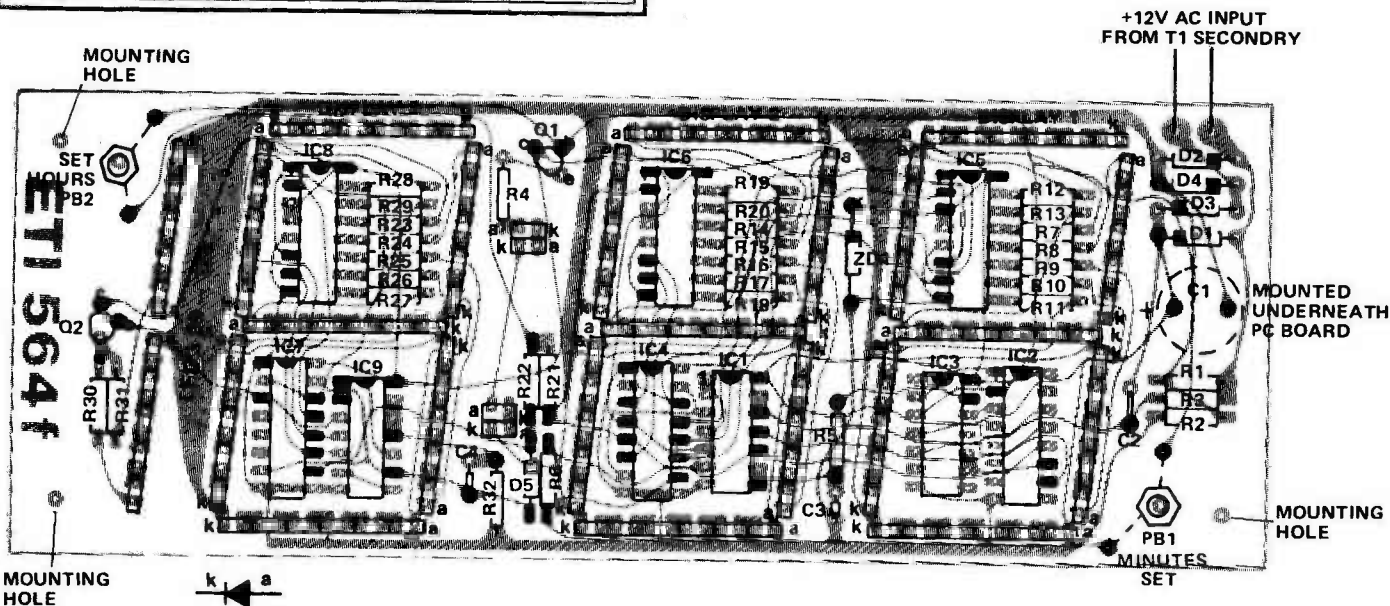

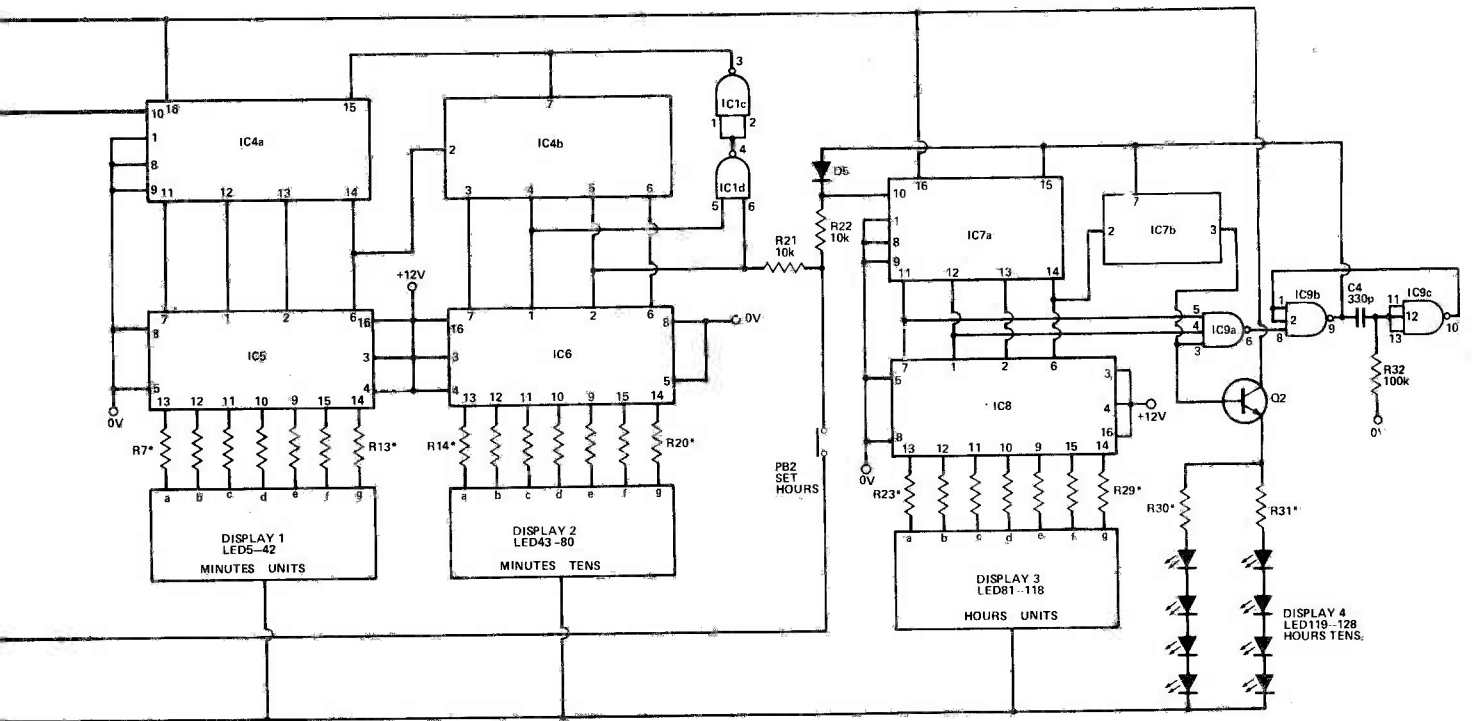

HOW IT WORKS


but, again due to R5/C3, the output of IC1b will remain high for about 20 μ s, ensuring correct resetting and the clocking of the minutes counter.

One of the outputs of IC2 (pin 2) is used to drive the colon and to provide the clock pulses for the 'fast set' modes. Using a binary divider means that a 1 Hz pulse is not available, so we chose the 1.56 S output (50/32).

The output of IC1b (a 20 μ s pulse once per minute) is used to clock IC4a, one half of a dual decade counter. The outputs of IC4a are decoded by IC5, which drives the 'minutes units' display. The 'divided-by-10' output of IC4a clocks IC4b, whose outputs are decoded by IC6 to display the 'tens of minutes'. As time has yet to be decimised (!), IC4b is set to divide by six. This is done by IC1d which detects when the 2nd and 3rd outputs are high (binary 0110) and provides the reset pulse via IC1c.

The third output of IC4 is used to clock the hours counter, IC7. This, like IC4, is a dual decade counter with the first half being decoded by IC8 and the second being clocked by the output of the first. As only a simple '1' is needed for the tens of hours (12 hour clock) no decoder is necessary, only a buffering transistor. IC9a detects when IC7 reaches decimal 13 (0001 0011 binary) and triggers a monostable formed by IC9b and IC9c. This is used to reset IC7 to zero hours but as there is no zero hour in the 12 hour system we need to reset to a '1'. This is done by D5, which pulls pin 10 of IC7 high for the duration of the reset pulse and allows it to fall back again a few microseconds after the end of reset pulse, (the delay being due to stray capacitance). This causes IC7 to clock on to '1'.

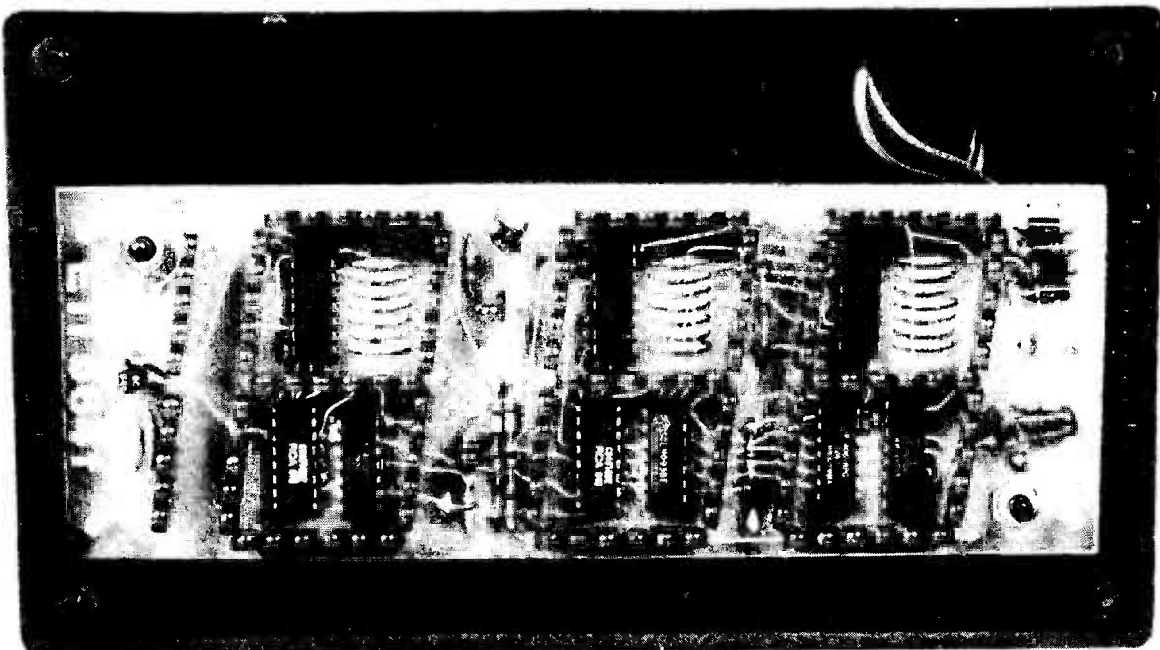Fast setting is done simply by injecting the 1.56 S pulse directly into the minutes or hours counters, using the push buttons.



oriented before inserting them in the board. Also ensure that you put each IC in its correct place and on the correct side of the board too! Sockets cannot be used for the ICs as many of the pins are soldered on both sides of the board.

LED Astray

The rectangular LEDs specified measure 2.5 mm wide by 5 mm long. If you elect to use conventional round LEDs, the miniature 3-4 mm diameter types should be used. Many of the larger sized round LEDs will not fit this PCB as they have a shoulder around the base of the unit that measures 6 mm in diameter, preventing the close packing possible with the other types.

The LEDs we used have a shoulder or 'step' in their leads a few millimetres from the base. We pushed the LEDs down onto the PCB until this shoulder stopped them going any further. The outside lead of each segment array was soldered and then each group checked for alignment before soldering the other leads. Once you have the LEDs mounted and soldered in place, the two push button switches may be mounted.

At this stage, if you are satisfied everything has been mounted correctly, the board may be tested — *but give it another thorough check first!* In particular, look for solder 'bridges' between IC pins or across closely-spaced tracks as well as possible dry joints.

Simply apply 12 V AC to the two pins marked on the board overlay and see that the clock operates as it should. Try the 'hours set' and 'minutes set' buttons to see that they have the required effect. If all is not well, switch off and re-check the component placement and orientation, check for dry joints, etc.

Now the clock may be finally assembled. An earth lug should be mounted under one of the transformer mounting bolts and the mains cable earth soldered to it. The PCB should be mounted behind a sheet of red plastic (if you're using red LEDs) to improve the contrast of the display and hide the other components. It will be necessary to drill two small holes in the plastic opposite the time-set buttons — a match can then be inserted to depress the buttons. If you prefer, you can mount the switches off-board and fit them in a convenient position on the case. Make sure the case has adequate ventilation, as the clock dissipates some 10 W. Once the clock is complete, all that remains is to plug in and set the time.

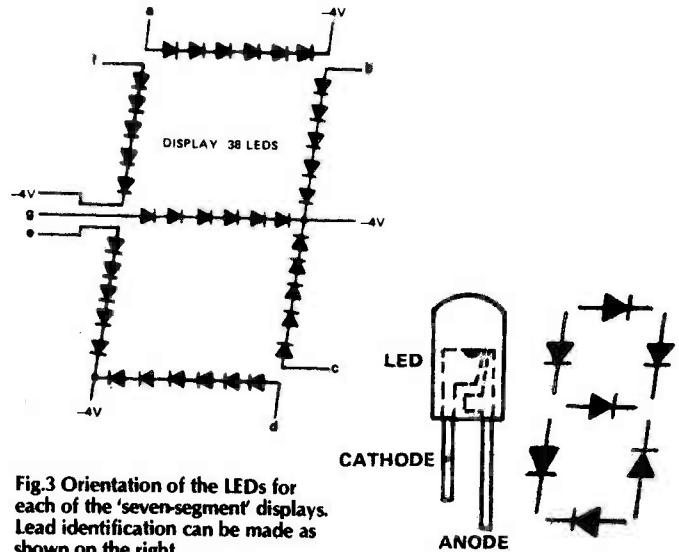


Fig.3 Orientation of the LEDs for each of the 'seven-segment' displays. Lead identification can be made as shown on the right.

CIRCUIT DIAGRAMS/OVERLAYS/ FLOWCHARTS!

Do you require professionally drawn Circuit diagrams, Overlays, Flowcharts etc. drawn from your own designs? MM Design & Print offer a quick, accurate and cheap Technical Illustration and lettering service to readers of ETI. We illustrate anything from a single chip amplifier to a colour television circuit design, with finished artwork supplied to your specification. For further details please ring Paul Edwards, on 01-437 1002/7 extension 29, or write to the address below.



Part of the Modmags Group,

145 Charing Cross Road,
WC2H 0EE


Setting the time

1. Switch on.
2. Press the minutes button until the minutes display is correct. To prevent multiple pulsing due to contact bounce, the button should be pressed and released when the colon is off.
3. Set the hours in a similar manner to the minutes. If the minutes display is less than 40, again operate the button when the colon is off. If the minutes display is 40 or more, operate the button when the colon is on.
4. An easy way to set the clock to the exact time is to first set it some 20 - 30 S fast by the push buttons, then compare it to a known time standard (you might use a radio time signal for this). Turn off the power for the exact time difference and the clock will cease counting. The large filter capacitor will hold its charge long enough to store the last time, for up to a few minutes, until power is returned. When the time signal equals the clock display, turn the power back on.

BUYLINES

There should be no problem obtaining any of the components for this project as nothing is out of the ordinary. Although you can expect to pay nearly £30 for the LEDs alone, it should be borne in mind that the nearest commercial equivalent to this clock costs over £100.

CREATE ONE YOURSELF

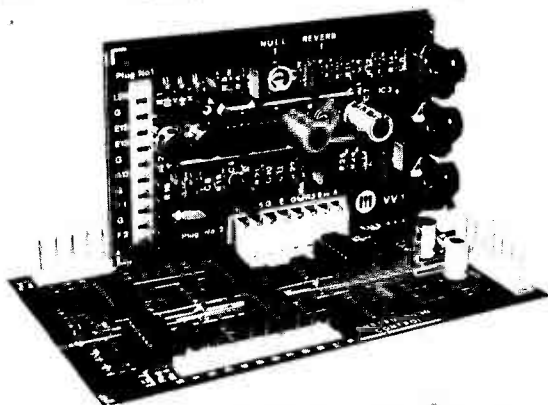

ILLUSTRATED HERE — PART OF THE ELECTRONIC "INSIDES" OF A WERSI



PRESETS — STRINGS — WALKING BASS PATTERNS — CO
 TROMB
 CARDS — TROMB
 REVERB — PL
 FL
 TROMB
 BASS PATTERNS — STEELBAND
 CHIMES — HARMONIC BASS PATTERNS — STEELBAND
 PATTERNS — CONTRA BASSION — BASS PATTERNS
 TRUMPET — PERCUSSION — BASS PATTERNS
 RECORD PLAYBACK — BASS PATTERNS
 BASS TUBA — HARMONIC BASS PATTERNS
 CONTRABASS — FREE RUN WITH ORGAN — BASS PATTERNS
 ORCHESTRA — BRASS PATTERNS — BASS PATTERNS
 STEELBAND — BASS PATTERNS — BASS PATTERNS
 STEREO SOUND — HARMONIC BASS PATTERNS
 SOUND COMPOSERS — BASS PATTERNS
 COMPUTER — BASS PATTERNS — BASS PATTERNS
 BASS PATTERNS — BASS PATTERNS — BASS PATTERNS
 STOP SOUND — BASS PATTERNS — BASS PATTERNS
 CHIMES — HARMONIC BASS PATTERNS — BASS PATTERNS
 HARMONIC BASS PATTERNS — BASS PATTERNS
 MULTITIMBRE — BASS PATTERNS — BASS PATTERNS
 WALKING BASS PATTERNS — BASS PATTERNS
 GLISSANDO — BASS PATTERNS — BASS PATTERNS
 REVERB — BASS PATTERNS — BASS PATTERNS
 TREMOLO — BASS PATTERNS — BASS PATTERNS
 PRESETS — BASS PATTERNS — BASS PATTERNS

Aura and WERSI Show You How

Create one of Wersi's electronic organs by building it yourself from an easy to build kit. Create a perfect match in decor by picking a spinet or console in contemporary or traditional styling. Create your own personalized instrument by picking just those features that fit your playing style.

Create your own custom electronic organ by having WERSI build it for you. Create the keyboard instrument that exactly fits your needs in styling and features. Create a lifetime investment with WERSI's unique updating system which allows you to ADD new features in the future.

Want to know more about WERSI AURA SOUNDS are the first company to successfully market WERSI Organs and kits in the U.K. Our technical telephone support service is second to none. There's a friendly welcome and free demonstration at our three showrooms. Fill in the coupon and enclose a cheque/P.O. for £1.00 payable to AURA SOUNDS

LTD. FOR IMMEDIATE ACTION TELEPHONE 01-668 9733 24 HOUR ANSWERING SERVICE. QUOTING ACCESS/BARCLAYCARD NUMBER.

AURA SOUNDS LTD.
14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.
Tel: 01-882 9733

17 Upper Charter Arcade, Barnsley, Yorkshire.
Tel: (0226) 5248

Please send me the full colour WERSI Catalogue. I enclose cheque/P.O. for £1.

NAME _____

ADDRESS _____

Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.

AND AURA SOUNDS — THE WINNING COMBINATION

Greenbank

Greenbank Electronics
(Dept T5E) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel: 051 645 3391)



TERMS, VAT, C.W.O. Cheques or payable to Greenbank Electronics and crossed.
Add VAT at 15% except where stated otherwise. Post etc: UK 40p
(+5p VAT = 45p) per order. Export: NO VAT add 40p (Eira), £1 (Europe) and
£3.50 elsewhere. Access, Barclaycard, Visa, (telephone orders accepted).
(Polys, materials, post dep'ts, etc can telephone their orders for immediate
despatch on account.)



UV 141, UV ERASER



Two easy to use units designed for both the professional and amateur
UV-germy user

Features

- Can erase up to 14 proms.
- Special short wave ultraviolet 70p
- Erase time variable between 5 and 50 minutes in 5 minute steps (preventing
over exposure which may shorten prom life)
- Sliding tray carries proms on conductive foam
- Safety interlock switch prevents the timing circuit from operating and
switching on the tube with the tray open.
- "Main On" and "Tube On" indicators
- Smart textured case
- Complete instructions supplied

Supplied complete with mains plug and flex

Model UV 141: Price £77.70

Also available without flex as

Model UV 140: Price £61.20

TEX MICROSYSTEMS "EPROMPT" UV ERASER



A low cost alternative to the above erasers (UV 140/141) claimed by the
manufacturer to erase up to 32 chips in 15-30 mins. This is the cheapest eraser
we have seen. The unit has no timer, power switch or safety interlock switch. The
user places up to 32 chips into loose conducting foam in the erasure tray (16
along the base, 8 on each side). The chips are held in place by the UV tube which
sits in the tray. (Unlike the UV 140/141, no special precautions have been taken to
prevent the seepage of UV light, but the manufacturers state that "incident
light from this device is quite safe at distances above 12 inches")

(Dimensions - 325 x 64 x 38mm)

EPROMPT ERASER Price £33

EUROCARD COMPUTER BOARDS

*Custom 801 Modular Z80 Based System, Details in preparation, free on request.

"BIG BOARD" Z80 COMPUTER KIT

We hope this item will be in stock by the time this advert reaches you. But please
check to see before sending any money! Features: 64K Dynamic RAM, Floppy
Disk Controller, 80 x 24 Char. Video output £395. CP/M Disk Operating System
to suit. £95.

MODULAR COMPUTER SYSTEM CARDS

A range of 'International' (114 x 203mm) size cards which may be purchased
individually as desired, or to build up a complete system. Further details available
on request. All boards are epoxy glass with gold plated edge plug.

VDU A. B. G (set of 3)	£27.20
SC/MPP-3 SC/MPP CPU	£9.40
MPA-7 Buffer/SC/MPP CPU	£9.40
MZB-3 Z80-CPU	£9.40
MXA-1 2K of 2102	£9.40
MXA-3 8K of 2114	£9.40
MXD-2 16K of 4116	£9.40
PRM-2 4K of 5204	£9.40
PRM-8 8K of 2708	£9.40
SRM-14 8K of 2516 + 6K of 2114	£9.40
SD-2 RS-232 (net)	£9.40
TPA-2 Tape Interface	£9.40
IP-2 Input Port	£9.40
OCR-6 Keyboard Input	£9.40
OP-3 Output Port	£9.40
PP-2 PROM Programmer	£9.40
PSU-A4 Power Supply	£9.40
PSU-B 5V Power Supply	£5.50
PSU-C 25V Power Supply	£5.50
13 slot backboard, can be used with most of the above boards, 13" x 4 1/2"	£11.80
ISBUS-1.1	

FLOPPY DISK CONTROLLER BOARD

This is used in conjunction with 'Kemtron' Z80 boards
to interface to twin single density 5 1/4" floppy disks. It
is not available as a bare board, but only built and tested.
Regrettably Kemtron do not supply circuit diagram.

To run CP/M on the system a serial interface (e.g. SIO
board) to some sort of VDU or terminal is required, and
48K of RAM (e.g. three MKX-2 boards). The MZB 3
board has facilities for power on/jump and a boot
prom to load the CP/M operating system from the disk
boot PROM (2708).

CP/M 801 "B" floppy disk £39.00

8" FLOPPY DISK DRIVES

DRE Model 7100 £380.00

T.V. MONITOR P.C.B. for OEM users

This is an assembled P.C.B. size 130 x 100mm, which you add to your
own 12" 1/4" black and white C.R.T. (100 degree, 20mm dot neck) to
obtain a T.V. monitor at modest cost. (Regrettably we cannot supply
the C.R.T. at present.)

Proved controls, contrast, brightness, etc. are included, and the only
inputs needed are 15 Volts - 10% AC at 1.5 Amps and 1 Volt peak
composite video input.

Supplied with circuit diagram £33.50

DOT MATRIX PRINTER

This is about the same price as for example the Necom Imp,
but has many features only previously found in models costing
hundreds of pounds more.

Standard interfaces (incl. 'astrix') RS-232, 20mA, IDE, ABR.
Centronics I/O, 15 bond rates to 9600, 100 characters per
second, 64, 72, 80, 96, 120 or 132 characters per line, rear,
bottom or front paper loading, friction or tractor feed, can
accept user defined characters, can also print graphics under
program control. Has 'soft-touch' facility. Supplied with mains
cable and full operator's manual.

Price £325.00

EUROCARD 19" CARD FRAME

Kit of 2 end plates + angles, 2 front and 2 rear Me bars, 4
corner location strips

Accessories

Card guides (each of 10) £1.53

Connector mounting strips (pair) £3.27

Case covers x4 £19.80

(or fit into separate 3U 19" 0-type case) £33.58

DNR 41612 Eurocard Connectors

64 way Plug rows a+c (84/98) £2.22

54 way Socket rows a+c (84/98) £3.39

54 way Plug rows a+b (84/54) £4.71

64 way Socket rows a+b (84/64) £4.24

CMOS

These cut prices for Amateur Users and Export. Note: industrial users - quantity
prices available. Mostly Motorola, RCA

4000 18p	4042 80p	4095 £1.97	4410 £8.55	4531 £1.45
4001 25p	4043 90p	4096 £1.97	4411 £10.72	4532 £1.30
4002 25p	4044 90p	4097 £3.98	4412P £14.93	4534 £3.60
4006 95p	4045 £2.63	4098 £1.92	4415P £3.24	4536 £3.80
4007 18p	4046 £1.10	4099 £2.00	4427 £5.66	4537 £26.10
4008 40p	4047 17.1p	4100 £1.92	4433 £12.30	4538 £1.20
4009 40p	4048 17.1p	4101 £1.92	4435P £5.40	4539 97p
4010 50p	4049 45p	4102 £3.67	4450 £3.81	4541 £1.19
4011 25p	4050 49p	4103 £3.67	4451 £3.81	4543 £1.80
4012 18p	4051 80p	4104 £1.85	4461 £3.93	4549 £4.38
4013 50p	4052 90p	4105 £1.85	4462 £4.41	4552 £14.85
4014 84p	4053 90p	4106 92p	4468P £4.28	4553 £4.50
4015 84p	4054 £2.18	4107 £1.28	4490P £3.14	4554 £1.38
4016 45p	4055 £2.55	4108 £7.54	4500 £6.95	4555 70p
4017 80p	4056 £2.55	4109 £1.28	4501 29p	4556 72p
4018 85p	4059 £3.23	4110 £3.00	4502 £1.28	4557 £3.86
4019 45p	4060 £2.10	4111 £1.77	4503 70p	4558 £1.25
4020 95p	4062 £18.00	4112 £1.54	4505 £5.71	4559 £4.38
4021 £1.10	4063 £1.90	4113 £1.54	4506 50p	4560 £2.50
4022 £1.00	4066 35p	4114 £1.54	4507 35p	4561 81p
4023 27p	4067 £7.21	4115 £1.54	4508 £2.90	4562 £3.80
4024 84p	4068 27p	4116 £1.54	4509 £1.19	4563 £1.25
4025 27p	4069 80p	4117 £3.03	4511 £1.00	4564 £2.38
4026 £3.25	4070 30p	4118 £1.90	4512 80p	4569 £2.50
4027 50p	4071 25p	4119 £2.41	4514 £2.65	4572 40p
4028 90p	4072 25p	4120 £2.41	4515 £3.00	4580 £4.72
4029 90p	4073 25p	4121 £3.27	4516 £1.10	4582 £6.67
4030 84p	4074 25p	4122 £4.48	4517 £4.48	4584 £1.14
4031 £4.31	4075 25p	4123 £2.31	4518 £1.00	4583 50p
4032 £1.31	4076 £1.07	4124 90p	4519 80p	4584 90p
4033 £2.63	4078 25p	4125 90p	4520 £1.00	4585 £1.27
4034 £2.00	4081 27p	4126 90p	4521 £2.50	4587 £2.44
4035 £1.10	4082 27p	4127 90p	4522 £1.11	4588 £2.98
4037 £1.00	4085 £1.35	4128 90p	4523 £1.00	4589 £3.05
4038 £1.20	4086 £1.35	4129 £1.15	4527 £1.50	4700 £1.75
4039 £2.70	4088 £2.91	4134 £1.16	4528 £1.28	
4040 £1.00	4093 80p	4408 £9.37	4529 £1.30	
4041 £1.59	4094 £2.50	4409 £9.37	4530 70p	

74C

74C00 25p	74C10 57p	74C103 £1.15	74C104 57p	74C327 £3.01
74C02 25p	74C13 57p	74C104 £1.80	74C105 57p	74C328 £5.01
74C04 25p	74C15 57p	74C106 £1.80	74C106 57p	74C329 £17.90
74C08 25p	74C17 57p	74C107 90p	74C107 57p	74C330 57p
74C10 25p	74C19 57p	74C108 90p	74C108 57p	80C06 85p
74C12 25p	74C21 57p	74C109 £1.15	74C109 £1.40	80C08 92p
74C14 25p	74C23 57p	74C110 £1.15	74C111 £7.30	80C09 85p
74C20 25p	74C25 57p	74C111 £1.15	74C112 £7.30	80C10 85p
74C28 25p	74C27 57p	74C112 £1.15	74C113 £1.40	80C12 85p
74C30 25p	74C29 57p	74C113 £1.15	74C114 £1.40	80C13 85p
74C32 25p	74C31 57p	74C114 £1.15	74C115 £1.40	80C14 85p
74C34 25p	74C33 57p	74C115 £1.15	74C116 £1.40	80C15 85p
74C36 25p	74C35 57p	74C116 £1.15	74C117 £1.40	80C16 85p
74C38 25p	74C37 57p	74C117 £1.15	74C118 £1.40	80C17 85p
74C40 25p	74C39 57p	74C118 £1.15	74C119 £1.40	80C18 85p
		74C119 £1.15	74C120 £1.40	
		74C120 £1.15	74C121 £1.40	
		74C121 £1.15	74C122 £1.40	
		74C122 £1.15	74C123 £1.40	
		74C123 £1.15	74C124 £1.40	
		74C124 £1.15	74C125 £1.40	

74LS


74LS00 14p	74LS153 35p	74LS154 90p	74LS244 £1.70	74LS374 £1.95
74LS01 14p	74LS155 76p	74LS154 £1.70	74LS245 £3.50	74LS375 £1.60
74LS02 16p	74LS156 48p	74LS155 £1.70	74LS247 £1.90	74LS377 £2.12
74LS03 16p	74LS157 40p	74LS156 90p	74LS248 £1.90	74LS378 £1.94
74LS04 16p	74LS158 40p	74LS157 76p	74LS249 £1.90	74LS379 £1.94
74LS05 20p	74LS159 40p	74LS158 96p	74LS251 £1.42	74LS384 85p
74LS06 22p	74LS160 £1.15	74LS159 96p	74LS253 £1.34	74LS386 85p
74LS09 22p	74LS161 90p	74LS160 £1.28	74LS255 £1.10	74L390 92.30
74LS10 20p	74LS162 90p	74LS161 90p	74LS258 £1.40	74LS393 £2.30
74LS11 22p	74LS163 60p	74LS162 £1.38	74LS259 £1.00	74LS396 £2.18
74LS12 23p	74LS164 60p	74LS163 £1.38	74LS261 £4.50	74LS398 £1.82
74LS13 38p	74LS165 55p	74LS164 £1.14	74LS266 52p	74LS398 £2.76
74LS14 38p	74LS166 55p	74LS165 75p	74LS273 £2.44	74LS399 £2.38
74LS15 38p	74LS167 55p	74LS166 £2.26	74LS275 £2.50	74LS445 £1.50
74LS16 38p	74LS168 55p	74LS167 £2.26	74LS279 £1.62	74LS447 £1.44
74LS17 38p	74LS169 55p	74LS168 £2.26	74LS281 £1.62	74LS490 £1.00
74LS18 38p	74LS170 55p	74LS169 £2.26	74LS283 £1.62	74LS522 £1.32
74LS19 38p	74LS171 55p	74LS170 £2.26	74LS285 £1.62	74LS528 £2.76
74LS20 38p	74LS172 55p	74LS171 £2.26	74LS289 £1.28	74LS569 £1.82
74LS21 22p	74LS173 55p	74LS172 £2.26	74LS293 £1.28	74LS670 £2.48
74LS22 22p	74LS174 55p	74LS173 £2.26	74LS295 £1.85	
74LS23 22p	74LS175 55p	74LS174 £2.26	74LS298 £1.68	
74LS24 22p	74LS176 55p	74LS175 £2.26	74LS324 £2.40	
74LS25 22p	74LS177 55p	74LS176 £2.26	74LS325 £2.90	
74LS26 44p	74LS178 55p	74LS177 £2.26	74LS326 £2.94	
74LS27 28p	74LS179 55p	74LS178 £2.26	74LS327 £2.86	
74LS28 28p	74LS180 55p	74LS179 £2.26	74LS347 £1.48	
74LS29 28p	74LS181 55p	74LS180 £2.26	74LS348 £1.86	
74LS30 22p	74LS182 55p	74LS181 £2.26	74LS349 £1.86	
74LS31 22p	74LS183 55p	74LS182 £2.26	74LS352 £2.28	
74LS32 27p	74LS184 55p	74LS183 £2.26	74LS353 £2.28	
74LS33 39p	74LS185 55p	74LS184 £2.26	74LS365 65p	
74LS37 39p	74LS186 55p	74LS185 £2.26	74LS366 65p	
74LS38 39p	74LS187 55p	74LS186 £2.26	74LS367 65p	
74LS39 39p	74LS188 55p	74LS187 £2.26	74LS368 66p	
74LS40 39p	74LS189 55p	74LS188 £2.26	74LS373 £1.86	
		74LS189 £2.26		
		74LS190 £2.26		
		74LS191 £2.26		
		74LS192 £2.26		
		74LS193 £2.26		
	</			

ELECTRONICS

DIGEST

Vol. 1 No. 4
ON SALE
NOW

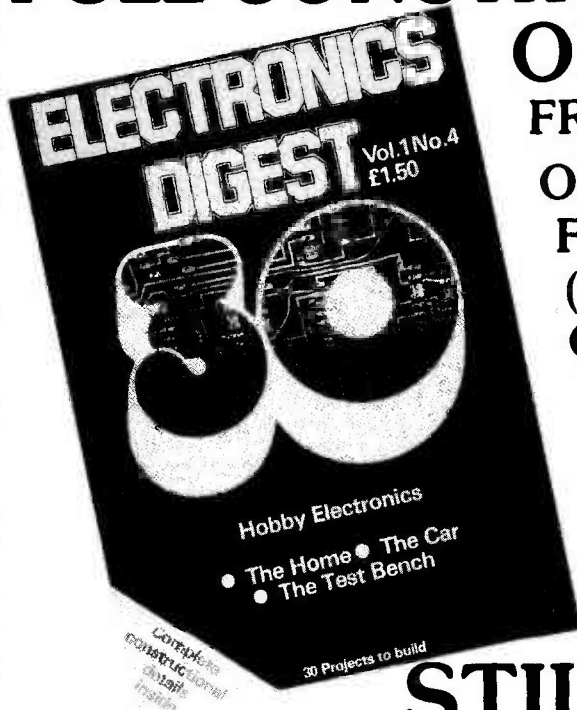**FULL CONSTRUCTIONAL DETAILS
OF TOP PROJECTS
FROM HOBBY ELECTRONICS**



ONLY £1.50

FROM YOUR NEWSAGENT

(THAT'S ONLY 5p PER PROJECT!!)

OR £1.75 ALL INCLUSIVE

FROM:

SPECIALS,

MODMAGS LTD,

**145, CHARING CROSS ROAD,
LONDON WC2H 0EE.**

STILL ONLY £1.50

Vol. 2

No. 1

ON

SALE

MAY 15th

We boldly venture into split infinitives and Volume 2 of Electronics Digest with featured articles on home and office security, the burglary business AND a FREE photography magazine with constructional projects.

Build your own variable delay flash trigger — we show you how to use it. We also feature designs for the 3 major security system types — infra-red, ultrasonic and switch sensor. Which is best, what are the advantages and disadvantages? Read the Electronics Digest Security Special to find out.

MICROBASICS

This month Microbasics returns to the hardware. Henry Budgett takes a look at the 6500 family in general, and the 6502 in particular.

The hardware side of Microbasics is returning briefly this month for a close look at just one chip, the 6502 CPU. Although this device has hogged the limelight owing to its starring roles in such machines as the PET, Apple, Microtan and ATOM it is far more than just a one-off. Part of a complete family of devices, the 6500 series, it represents the public face of the design architecture. Why look at it in detail? Well, in the near future you are going to see one of its brethren in a major new role, but more of that in a month or two.

Family Characteristics

Figure 1 and Table 1 give the details of the whole range; there is a new device promised but I don't have details yet. Although I'm going to concentrate on the 6502, most of the information is directly relevant to the others in the family.

Physically it is supplied as a standard 40 pin DIP which needs a single 5 V supply and a clock generator. Internally the device operates on a two phase clock but this is generated from

Features	R6503, R6513	R6504, R6514	R6505, R6515	R6506	R6507
Addressing Capability	4096 Bytes (AB00-AB11)	8192 Bytes (AB00-AB12)	4096 Bytes (AB00-AB11)	8192 Bytes (AB00-AB11)	8192 Bytes (AB00-AB12)
Interrupt Request Capability	IRQ, NMI	IRQ	IRQ	IRQ	—
"Ready" Signal	—	—	RDY	—	RDY
*Timing Signals Required	Single Phase TTL Level ϕ 0 (IN) or Crystal or RC	Single Phase TTL Level ϕ 0 (IN) or Crystal or RC	Single Phase TTL Level ϕ 0 (IN) or Crystal or RC	Single Phase TTL Level ϕ 0 (IN) or Crystal or RC	Single Phase TTL Level ϕ 0 (IN) or Crystal or RC
Other Control Signals	RES, R/W	RES, R/W	RES, RW	ϕ 1 (OUT), RES, RW	RES, RW

*6513, 6514 and 6515 are slave microprocessors requiring external ϕ 1 and ϕ 2 clock inputs

Table 1. Details of each of the CPUs.

a single input which should be crystal controlled. The CPU actually sends the second clock phase back out again for synchronisation purposes and this appears on pin 39.

The size of the internal data bus and its associated registers is eight bits — hence the term 'eight bit micro'. These registers and the rest of the internal workings are shown in Fig. 2. It should

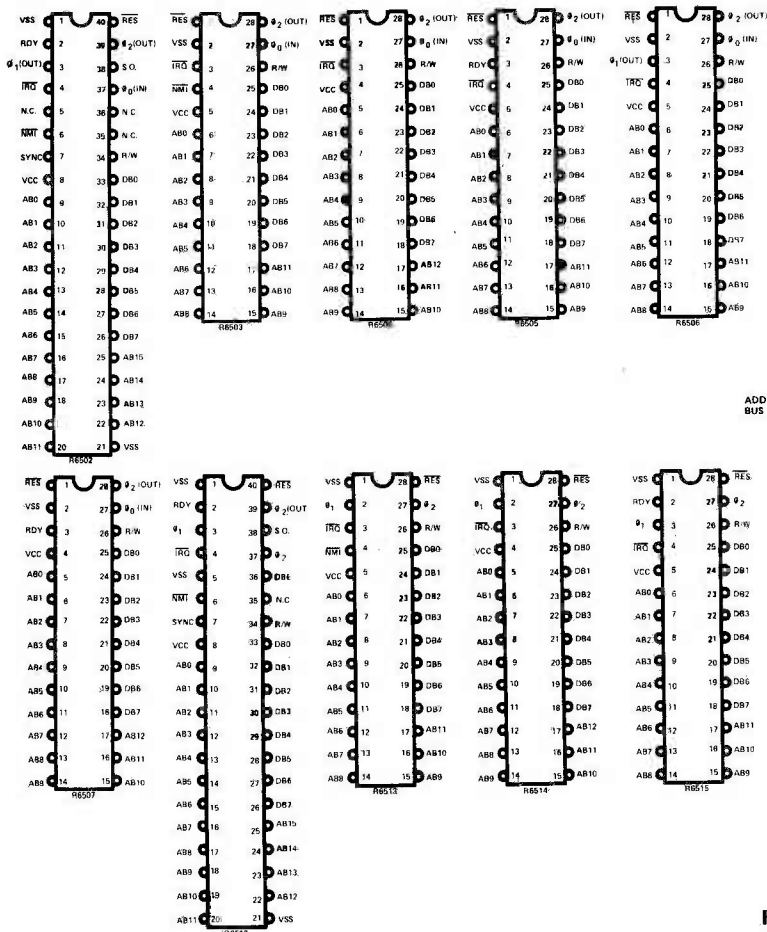


Fig.1 Pin designations for all the CPUs in the 6500 family.

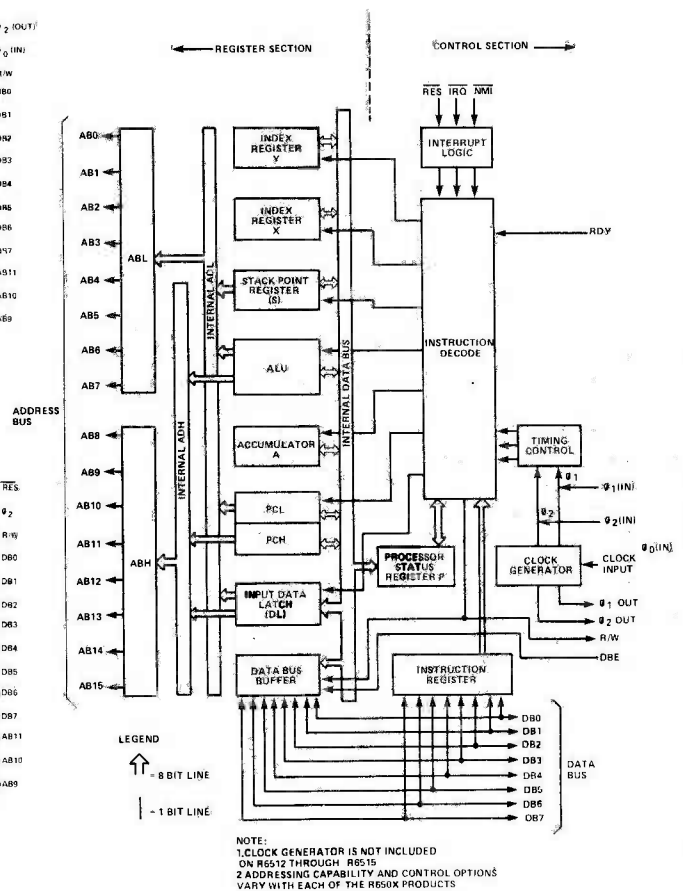


Fig.2 Block diagram of a 6500-series CPU. The registers are all eight bits wide except the program counter; this consists of a high and low byte (PCH and PCL).

be noted that this block diagram is for the generalised 6500 device and not the 6502 specifically but the differences are slight. Although the data bus is only eight bits wide the address bus is a full 16 bits across which gives access to 65,536 possible memory locations. Some of the other members of the family, notably those with only 28 pins, have a more limited addressing capability. Table 1 has the details.

Pin By Pin

In order to take a close look at the functioning of the device I'll go through it pin by pin. Where to start? Being logical (?) let's begin with the data bus. This occupies eight pins, 26 to 33 (DB7 to DB0) and is a true tri-state, bi-directional highway. What's actually on it at any given instant is controlled by the pins R/W (34) and RDY (2). The functions of these will be explained later.

The address bus is found on pins 9 to 25 (AB0 to AB15). This is a unidirectional bus, you can't 'read' an address. The addressing capabilities of these 16 lines are shown in Fig. 3, obviously those 6500 series devices with fewer address lines can only access a part of this range. An address is set onto the lines during the $\emptyset 1$ clock pulse and is stated as being 'valid', jargon for being stable and OK, some 300 nS after $\emptyset 1$ goes high (given a 1 MHz clock). The address remains stable on the bus until the next $\emptyset 1$ clock pulse.

BINARY ADDRESS								DECIMAL NUMBER	HEXADECIMAL Address Code		ADDRESSABLE MEMORY FIELD (65536 Bytes)								
High-Order				Low-Order					Page Number	Byte Number									
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0				
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	00	00	00
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	00	01	01
0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	255	00	FF	FF
0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	256	01	00	00
1	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1	65279	FE	FF	FF
1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0	65280	FF	00	00
1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	1	65281	FF	01	01
1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	65535	FF	FF	FF

Fig.3 The addressing range of the 6500-series. Only part of this range can be covered by some of the CPUs.

Of Reading And Writing

The R/W pin (34) controls the direction in which information travels on the data bus. The line is normally high (READ mode), unless the processor wishes to send something to memory or the outside world (WRITE mode) in which case it is forced low. All transitions (changes of state) occur during the $\emptyset 1$ period which allows data to be transferred during the $\emptyset 2$ clock period. The second major control line for the buses is the Ready (RDY) line found on pin 2. This is normally high but when pulled low, during $\emptyset 1$, it effectively shuts the CPU down — provided the current operation is not a WRITE. This allows slow memory devices such as EPROMs to be catered for and, more importantly, operations such as DMA, Direct Memory Access, to occur.

Interruptions

The 6502 supports two types of interrupt, Non Maskable and 'normal'. The Non Maskable Interrupt (NMI) is a control input found on pin 6 and this should normally be held high. The processor must break off from whatever process it is currently performing (it performs essential 'housekeeping' first) when this line goes low. Being an edge triggered control the line can stay low indefinitely without causing further interrupts, to issue another it must first be taken high and then low again. When an NMI occurs the current status of the program counter and the status word are saved on the stack and the program counter is then loaded with the interrupt vector, in the case of the 6502 this

is FFFA and FFFB. The contents of this memory pair contain a further address which is the start of the interrupt service routine.

The case of the other interrupt is rather more complicated in that it can be turned off if you want by manipulating a bit in the status register. The physical manifestation (classy eh?) of this control is a pin labelled IRQ (4) which is normally held high. When pulled low by a peripheral device it signals an interrupt to the processor. If the interrupts are enabled then a similar action to that of the NMI is performed. It should be noted that the IRQ line is not edge triggered so as long as the line is low the CPU will try to service interrupts.

The ultimate interrupt to any CPU is the RESET (\overline{RES}) signal which is found on pin 40. During power-up this line should be held low until conditions have stabilised and then taken high. In practice a simple RC combination will suffice. When the line goes high it causes the processor to fetch a new 'vector' from a specific address, this loads the program counter to a known starting point in the user program. In this way the machine powers up with all the functions set correctly; the line should also be fed out to all the support chips to ensure that they too turn on correctly.

Alone in the 6500 series the 6502 possesses a control line called SYNC which is found on pin 7. This is used to identify the specific cycle taking place within the CPU, (it approximates to the M1 signal in the 8080). The line goes high during $\emptyset 1$ of an OP-CODE FETCH and is used to tell the outside world to mind its own business for a while. If the RDY control is taken low during the same $\emptyset 1$ cycle as the SYNC goes high it stops the processor in its current state. This allows single instructions to be executed if handled correctly.

There is one further control line called SO which appears on pin 38. It is not used — except with a specialised I/O port — so you can ignore it.

Registered Design

So much for the outside, what goes on inside that hunk of black plastic? The block diagram of Fig. 2 shows the registers; the only ones of interest from our point of view are the stack pointer, the program counter and the status word. Although the address range of the 6502 requires a full 16 bit bus the stack pointer only contains eight bits. These eight bits act as the lower half of an address, the top half being set at 01 Hex. The 6502 stack is an area of memory that resides in Page 1 (hence the 01 Hex top half), which is used by the CPU and the user programs as a temporary storage area.

A Program Counter consists of a 16 bit register which contains the address of the next instruction to be executed, or rather it contains the address of the next memory location which will be accessed.

The status word is important to both the hardware and software engineer. Eight bits wide, it contains seven flags which indicate the current status of sections of the hardware within the CPU. Bit 0 indicates the carry status; it gets set if the result of a calculation in the Accumulator exceeds 255, and is effectively a ninth bit in the Accumulator. Bits 1, 3, 6 and 7 are concerned with the programming aspects of the device and Bit 5 is not used. This leaves Bit 2 which is the Interrupt Disable flag that I mentioned earlier, and Bit 4 which indicates that a BREAK instruction has been found.

Programming The Beast

As this is mainly a hardware orientated article I'm not going to say anything about the actual programming of the 6502; only that ETI has a major new project planned which involves the 6500 series and will answer all your questions. I can't go into any greater detail at present, but in a month or two all will be revealed.

ETI

computing today

MAY 1981

ISSN 0142-7210

65p

LIVING IN BABEL?


With the ever increasing family of computer languages to contend with we decided to start taking a look at some of the most important ones for the micro user. Just what they do and why one does it better than another are the sort of questions we'll be trying to answer over the next few issues. We start with COMAL, the newest recruit onto the micro scene.

BINDING IT TOGETHER

Many computers seem to lack sufficient documentation and, unfortunately, the ZX80 is no exception. A veritable library seems to have sprung up around it and we take a look at some of the best, and worst, on offer.

CONQUERING EVEREST FOR FUN

Computer games often take real-life events and mimic them in miniature. This example is more than just a game, it's a complete simulation of an attempt to climb Everest, down to the last oxygen cylinder and footsore Sherpa. Can you plan far enough ahead to cope with sudden changes in the weather or will you risk all in a quick dash for the summit? It calls for strong nerves and a clear mind but will fit into just 8K of RAM, how's that for good planning?

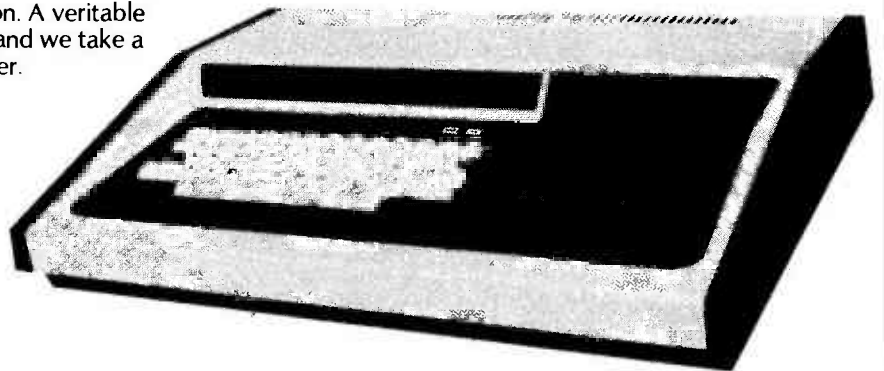

GETTING OUT AND ABOUT

So you want more I/O than your computer is provided with? Well, you might actually have more than you thought in the first place. We show you how to increase the power of your PIO in easy practical steps. Any computer with a parallel port qualifies for this improvement.

A LITTLE BIT OF MAGIC

Following in the footsteps of the successful TRS-80 came the Video Genie system. Now, however, it may well have taken a step or two ahead of its American cousin by going all multicoloured. We sent in our expert to have a look and his report on this low-cost colour graphics machine makes very interesting reading for anyone thinking of taking the Eastern path to computerisation.

THE
ZX80
POCKET BOOK

Learning
BASIC with your
Sinclair
ZX80

Robin Norman

Sinclair
ZX80

ON SALE AT YOUR
NEWSAGENT
FRIDAY
10th
APRIL

MONTH • COMPUTING TODAY • NEXT

COMPUTING TODAY • NEXT

new books from sams and prentice-hall

sams books

Andrew C. Staugaard, Jr.
 **6801, 68701 and
6803 Microcomputer
Programming and
Interfacing**

£9.05 pb 352 pages 672-21726-0

Jonathan A. Titus, Christopher A.
Titus and David G. Larsen
 8085A Cookbook

Describing how to design a
microcomputer using the 8085A
microprocessor, this book explains
in detail basic concepts such as
organization and timing.

£9.05 pb 352 pages 672-21697-3

Walter G. Jung
 **IC Op-Amp
Cookbook
2nd Edition**

Many significant state-of-the-art
advances are discussed in this new
edition, such as JFET and MOSFET
units in both single and multiple
formats.

£9.70 pb 480 pages 672-21695-7

Don Lancaster
 **Son of Cheap
Video**

This sequel to the popular **Cheap
Video Cookbook** explains how to get
alphanumerics and graphics video
out of a microcomputer and onto an
ordinary TV set.

£5.80 pb 224 pages 672-21723-6

prentice-hall books

Lance A. Leventhal
 **Microcomputer
Experimentation with
the Motorola
MEK6800D2**

A complete laboratory manual, this
book stresses practical applications
of microprocessors in such fields as
communications, test equipment and
industrial process control.

£11.00 pb 368 pages 13-580761-1

James W. Coffron
 **Practical
Hardware Details for
the 8080, 8085, Z80
and 6800 Micro-
processor Systems**

£14.25 hb 352 pages 13-691089-0

James Coffron
 **Practical
Troubleshooting
Techniques for
Microprocessor
Systems**

£12.95 hb 256 pages 13-694273-3



**Prentice-Hall
International**

Prices are correct at the time of going to press
but may be subject to change. **ET15**

book orders

These books can be ordered from your bookseller or in case of
difficulty from Department 30, Prentice-Hall International,
66 Wood Lane End, Hemel Hempstead, Hertfordshire, HP2 4RG, England.
Please mark the number of books you wish to order in the boxes beside each
title and return the advertisement to the address above with your payment.

Name _____
Address _____

I enclose a cheque/P.O. for £ _____

Please add 55p per book for postage and packing. Payment should be made
out to **International Book Distributors**. Please allow 28 days for delivery

AUDIO VIDEO SERVICES

18 Galworthy Ave.,
Romford RM8 4PX
Tel: (01) 599 8680

7400	TTL	74107	35p	4017	70p	LS13	40p	2112	300p
7402	11p	74109	46p	4023	20p	LS14	56p	2114	280p
7403	12p	74121	34p	4024	60p	LS20	20p	4116	300p
7404	14p	74123	50p	4027	40p	LS26	26p	2708	45p
7407	30p	74141	50p	4029	95p	LS30	20p	2718	75p
7410	18p	74151	65p	4040	85p	LS42	70p		
7413	30p	74153	70p	4046	100p	LS47	78p	DL704	100p
7414	40p	74157	75p	4048	35p	LS51	25p	DL707	100p
7416	30p	74180	75p	4050	35p	LS54	25p	DL747	150p
7420	15p	74161	75p	4051	70p	LS73	50p	DL750	150p
7426	40p	74164	90p	4052	70p	LS74	27p	TIL209	12p
7430	16p	74174	80p	4053	70p	LS80	40p	TIL211	15p
7441	70p	74175	80p	4055	125p	LS82	70p	TIL220	14p
7442	70p	74390	185p	4060	110p	LS93	60p	TIL228	15p
7447	48p	74393	185p	4081	27p	LS107	45p		
7551	18p			4082	27p	LS109	70p	REGULATORS	
7454	18p			4511	95p	LS123	75p	TO-220	
7473	28p	4001	15p	4518	90p	LS125	50p	7805	55p
7474	28p	4002	15p	4520	90p	LS126	50p	7812	80p
7486	30p	4006	65p	4543	150p	LS151	55p	7815	80p
7489	30p	4011	18p	4555	70p	LS153	55p	7905	80p
7492	35p	4012	20p			LS157	65p	7912	80p
7493	30p	4013	45p			LS160	90p	7915	80p
		4016	35p			LS161	95p		
						LS164	95p	DIL SOCKETS	
						LS174	100p	8 pin	8p
						LS17	100p	14 pin	10p
						LS221	110p	16 pin	12p
						2102	120p	18 pin	18p
								20 pin	20p
								24 pin	24p
								28 pin	28p
								40 pin	40p

MAIL ORDER ONLY. C.W.O. Add 35p P&P 15% VAT
Many more items in stock. Send SAE for full price list.

A career in product marketing?

YOUR KNOWLEDGE OF ELECTRONIC COMPONENTS COULD BE THE KEY TO A SECURE AND FINANCIALLY REWARDING CAREER IN ELECTRONIC COMPONENT DISTRIBUTION. PREFERRED AGE BETWEEN 20-26 YEARS.

We are the U.K.'s largest semiconductor distributor and we are looking for people with an interest and/or knowledge of up-to-date electronic components to become Product Marketing Engineers at our head office, here in Slough -

The job develops commercial skills and offers prospects for very rapid advancement for people who are prepared to work hard and are ambitious.

We offer an attractive starting salary plus salary reviews twice-yearly plus a company car to the successful candidates.

Call or write to: **Julian Barnard or John Evans**
Macro-Marketing Ltd, Burnham Lane
Slough, Berks SL1 6LN
Burnham (06286) 61266

IONISER KIT

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels like fresh ocean air, pure crisp and wonderfully refreshing.

All parts P.C.B. and full instructions £10. A suitable case including front panel, neon switch, etc. Available at £8 extra

H.E. KITS

Car Booster ZD50 £18; Multi Option Siren ZD36 £10.50; Car Equaliser ZD52 £13.30; Envelope Generator ZD20 £11.79; R/C Speed Controller ZD3 £9.60; White Noise Effects Unit ZD18 £16.85; Track Cleaner ZD12 £7.75; Drill Speed Controller ZD21 £7.

All Hobby Kits supplied cases except ZD3. All kits contain components as specified plus Texas I.C. sockets where required. Also connecting wire. Special introductory offer to E.T.I. readers, a pack of nuts, bolts, washers, self-cutting, self-tapping screws supplied with each kit.

SPECIAL OFFERS

Texas I.T.T. 1N4148, 100 for £1.50.	
Fairchild FLV ISO Red 2 LEDs 10 for £1; 100 for £7.50.	
Mullard Computer Electrolytics S/T 21,000 U.F. 40V	£3.50
Daly Electrolytic Capacitors 2000µF, 100V	£1.50
I.T.T. BCY 72 Transistors leads pre-formed	10 for 50p
Varicap Tuners ELC1042	£6.00
Varicap Tuner ELC1043	£6.00
Philips Scope Tube 5" CV2191/DG-13-2	£10.00
Thorn-Sylvania Scope Tube 5" SE5J	£17.50 (Callers only)
Toshiba 12" TV Tube 310GAB4	£12.50 (Callers only)

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra orders. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of Kits.

T. POWELL

306 ST. PAUL'S ROAD
HIGHBURY CORNER
LONDON, N.1
TELEPHONE: 01-226 1489

Our new address
(from March 18th)
44 WALLACE ROAD
LONDON, N.1.

(Callers by appointment)

Access/Visa accepted Hours: Mon. to Fri. 9-5.30. Sat. 9-4.30

Dept. ET18, Unit 9/10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165, 01-278 7369. Telex: 8953084 Maclin G.

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of P&P and VAT - please refer to "Ordering Information" before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.

NEW, LOW, LOW PRICES ON MEMORIES

Compare our prices before you buy elsewhere! All devices are brand new, factory prime, full spec. and fully guaranteed!

All prices exclude P&P and VAT. Please refer to Ordering Information before ordering.

DON'T DELAY - BUY TODAY - SUCH LOW PRICES DON'T LAST FOREVER!!

STATIC RAMS	1-24	25-99	100+
2114L 200 NS	1.75	1.60	1.45
Lower Power			

DYNAMIC RAMS	1-24	25-99	100+
4116 150NS	2.50	2.25	1.95
4116 Ceramic Package			

Goldplated 200 NS	1.50	1.30	1.20
HM4864 64K (65Kx1)			
Single 5V 200 NS	14.95	10.95	9.95

CMS RAMS	1-24	25-99	100+
TC5514P 4K(1K x 4)			
or equivalent			

450NS	3.95	3.50	2.95
HM6116 16K (2K x 8)			

150 NS	15.95	14.95	13.95
EPROMS	1-24	25-99	100+
2708 450 NS	2.95	2.75	2.50
2716 5V 450 NS	3.25	2.95	2.75
2532 5V 450 NS	10.95	9.95	8.95

Ordering information. Unless otherwise stated for orders under £50 add 50p p.p. Add 15% VAT to total (no VAT on books). All devices are brand new, factory prime and full spec and subject to prior sales and availability. Prices subject to change without notice. Minimum telephone order using ACCESS, is £10. If ordering by post with ACCESS, include name, address and card no. written clearly. Please allow 4/6 weeks delivery on books.



NEW SENSATIONAL LOW PRICE ON 64K DYNAMIC RAMS ONLY £9.95

Minimum order (10 pcs (Total price £115 inc. P&P 50p & VAT) (for quantity 1-9, £14.95 + P&P + VAT) Ex-STOCK WHILE SUPPLY LASTS! From HITACHI, HM4864-3 (65K x 1) 200NS, Single +5V Supply, 16 pin. Complete with data sheet and cross reference list.

NOW LONDON-BASED FOR EVEN FASTER SERVICE!

See new address above

KEYBOARD ENCODER	TL490	175p
AY52876	XR2206	325p
	XR2207	375p

VOLTAGE REGULATORS	7805 7812	50p
	7905 7912	80p
	78HOSSC	575p
	78HGKC	625p

EPROMS	2708 450 NS	350p
	2716 5V 450 NS	475p
	2732 12K 450 NS	£14.95
	2732 Intel type	295p

NEW!	450 NS	£14.95
	256NS16K x 8	
	512NS16K x 8	
	512NS16K x 8	
	9900P	

UARTS	AY 5101A	325p
	AY 5101B	398p
	IM4012	325p

CPU'S	MC 1468	625p
	6801	750p
	6802	750p
	6809	645p
	6809	925p
	6809A	£19
	6809A	£25p
	6809A	£10.95
	Z80	700p
	Z80A	900p
	Z8001	£125
	Z8002	£95
	Z8003	£24.95

DIP SWITCHES	4pole	99p
	6pole	115p
	8pole	140p
	10pole	175p

LINEAR IC'S	AY 31350	795p
	AY 38910	825p
	709	30p
	723	33p
	741	18p
	ICL7106	575p
	ICL7107	695p
	ICL8338	295p
	ICM7216A	1875p
	ICM7216B	1675p
	ICM7555	80p
	LM301AM	30p
	LM311	50p
	LM318	75p
	LM324	45p
	LM339	45p
	LM380	65p
	LM1496	65p
	LM1871	550p
	LM1872	550p
	LM3900	50p
	LM3914	225p
	LM3915	225p
	LM13600	125p
	NE555	18p
	NE556	50p
	DL704	85p
	DL707	85p
	MSV164	225p

BIPOLAR RAMS	27L500	995p
	9341-DC	1125p

INTERFACE LINEAR	MC1488	90p
	MC1489	90p
	DM8123	125p

CMOS RAMS	5101 1K (256 x 4) 450 NS	350p
	4315 4K (4K x 1) 450 NS	995p
	TC5514P4K (1K x 4) 450 NS	495p
	HM6116 15K (2K x 8)	
	150 NS 24-pin NEW!	£19.95
	HM6116 16K (2K x 8)	89.95
	150 NS 24-pin NEW!	£19.95

FLOPPY DISK CONTROLLERS	FD 1771 B-01 SID Inverted Bus	£19.95
	FD 1791 B-01 D Inverted Bus	£32.95

NEW SUPER MUSIC MACHINE KIT!

AT LAST - an affordable kit that can be PROGRAMMED TO PLAY ANY SONG OR GROUP OF SONGS! Instead of a nightmare of numerous ICs and expensive Bipolar ROMs the SUPER MUSIC MACHINE uses a SPECIAL MASK PROGRAMMED COMPUTER CHIP one CMOS gate and the most popular erasable EPROM, the 2708/2716 series. BASIC KIT includes drilled plated and screened PCB board and ALL components except the EPROM and 12V transformer. The basic kit will play short renditions of 25 tunes through its 7 WATT AMPLIFIER SECTION. Add an optional ROM and any tune program will be played. If you have the equipment to program 2708 EPROMs, we supply full information on programming your own music!

- FEATURES**
- Basic kit contains 25 short tunes in the main IC.
 - Will address external ROM for up to 1,000 MORE NOTES per ROM (ROM is not included).
 - Optional on 12V AC or 12V DC at 500mA. (Using unit on 12V DC and with optional ROM requires 9V bias battery not included).
 - 7 watts of audio power will drive 8 or 16 ohm speakers or horn speakers (not included).
 - DIP switches not included.
 - NEXT TUNE provision steps sequentially through all tunes.
 - Tune address can be wire jumper selected or board is designed to take DIP switches.
 - PITCH VOLUME and TEMPO are all adjustable.
 - SPECIAL CHIME SEQUENCES can be activated regardless of tune address to provide for multiple doorbell applications.
 - All tunes consist of electronic musical notes played one at a time. There are no chords or harmony sound to the music.
 - STEP-BY-STEP ASSEMBLY INSTRUCTION provided.
 - Large number of PREPROGRAMMED ROMs with program and classical tunes readily available. Send SAE for list and prices.

ONLY £16.75 for basic kit (plus p&p 60p).

SE 01 Sound Effects Kit

The SE 01 is a complete kit that contains all the parts to build a programmable effects generator. Designed around the new Texas Instruments SN 76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SFL Oscillator, VCO Noise, One Shot and Envelope Controls A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/2" x 3" PCB Board features a prototype area for using added circuitry. Easily programmed to duplicate Explosion, Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mV amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included). COMPLETE KIT ONLY £14.99 P&P 67p VAT.

BOOKS BY HOWARD W. SAM'S INC. SALE!

(Please order books by reference number and title. Please add 75p P&P per book. No VAT)

REF.	TITLE	NORMAL PRICE	SALE PRICE
21168	Active Filter Cookbook	£10.95	£7.75
21440	Aviation Electronics	£6.75	£5.75
21558	Audio IC Op Amp Application	£5.95	£4.75
21586	Basic Programming Primer	£6.50	£4.75
21554	Boolean Algebra for Computer Logic	£4.50	£3.75
21447	The 8080A Bugbook Microcomputer		
	Interfacing & Programming	£5.04	£3.75
21465	Building and Installing Electronics Intrusion Alarms	£3.95	£2.75
21524	The Cheap Video Cookbook	£4.50	£3.75
21398	CMOS Cookbook	£7.75	£6.75
21652	Computer Dictionary 3rd Ed	£8.95	£7.75
21693	Computers & Programming Guides for Scientists & Engineers	£11.95	£8.75
21697	8085A Cookbook	£7.50	£5.75
21539	Design of Active Filters with Experiments	£5.95	£4.75
21536	DEBUG An 8080 Interpretive Debugger	£3.75	£2.75
21537	Design of Op Amp Circuits with Experiments	£5.95	£4.75
21686	Design of CMOS Circuits with Experiments	£5.95	£3.75
21550	Introductory Experiments in Digital Electronics & 8080A Microcomputer Programming & Interfacing Book 1	£9.95	£7.75
21551	Introductory Experiments in Digital Electronics & 8080A Microcomputer Programming & Interfacing Book 2	£9.95	£7.75
21351	How to Buy and Use Minicomputers and Microcomputers	£7.50	£5.75
21684	How to Program 8080 & Interface 6800	£10.50	£7.75
21459	How to Program Microcomputers	£6.75	£4.75
21127	How to Read Schematic Diagrams	£4.25	£3.75
21613	How to Use Integrated Circuits Logic Elements	£4.50	£3.75
21527	IC Converter Cookbook	£10.50	£8.75

6809 S-100 SINGLE BOARD COMPUTER

- Meets IEEE S-100 Standard!
- Selectable BAUD Rates!
- Manual includes: 11 x 7 Schematic, Parts List, User Notes, Software Listings and MORE
- 4K, 8K, 16K ROM!
- 2K RAM!
- ACIA, PIA, 8080 Simulated I/O! Bareboard only £49! (plus £1 p&p).
- CPU (6809) £19.00! ADSOM, Monitor (2716) £25! COMPLETE BOARD ASSEMBLED AND TESTED ONLY £250! (plus £2 p&p)

UNIVERSAL SCR

C106D 400V/5A Sale 30p

THE NEW GI COMPUTER SOUND CHIP

The amazing AY-3-8910 is a fantastically powerful sound and music generator, perfect for use with any 8-bit micro processor. Contains 3 tone channels, noise generator, 3 channels of amplitude controls, 16 bit envelope period control, 2 parallel I/O, 3D/A converters plus much more. All in 40 pin DIP Super easy to interface to the S 100 or other Busses. ONLY £8.50 + VAT, including FREE reprint of BYTE 79 article! Also add £2.25 for 60 page data manual. *For the next launch, our crossover will not direct a 150 piece orchestra but rather a trio of microcomputers controlling a bank of AY-3-8910s. BYTE July 79.

NEW EXCITING ENTERTAINING SOFTWARE FOR THE APPLE II AND APPLE II PLUS! ASTEROIDS IN SPACE!!

If you liked Invaders you'll love ASTEROIDS IN SPACE by Bruce Wallace! Your spaceship is travelling in the middle of a shower of asteroids. Blast the asteroids with lasers, but beware - BIG ASTEROIDS FRAGMENT INTO SMALL ASTEROIDS! The apple game paddles allow you to rotate your spaceship, fire its laser gun and give it thrust to propel it through endless space. From time to time, you will encounter an alien spaceship whose mission is to DESTROY YOU, so you'd better destroy it first! High resolution graphics and sound effects add to the arcade like excitement this program generates. RUNS ON ANY APPLE II WITH AT LEAST 32K AND ONE DISK DRIVE! ON DISKETTE ONLY £14.95

DTL	830	55p	74LS112	75p	4042	73p
	935	65p	74LS123	63p	4043	86p
	937	55p	74LS125	50p	4044	88p
	944	65p	74LS126	50p	4045	160p
	946	55p	74LS132	79p	4047	99p
	947	55p	74LS138	63p	4048	56p
	962	55p	74LS139	75p	4049	38p
	9099	90p	74LS148	170p	4050	40p

7400

7400	11p	74LS151	75p	4051	69p
7401	12p	74LS153	75p	4052	75p
7402	12p	74LS155	65p	4053	73p
7403	13p	74LS157	74p	4054	111p
7404	17p	74LS160	115p	4055	121p
7409	18p	74LS161	78p	4056	121p
7410	18p	74LS163	90p	4059	560p
7412	18p	74LS164	90p	4060	112p
7413	18p	74LS165	150p	4063	112p
7414	18p	74LS166	190p	4066	56p
7415	28p	74LS173	100p	4067	422p
7420	16p	74LS174	99p	4068	19p
7430	18p	74LS175	99p	4069	19p
7432	25p	74LS181	280p	4070	25p
7440	16p	74LS190	110p	4071	25p
7442	68p	74LS195	87p	4072	25p
7448	75p	74LS196	100p	4075	20p
7473	32p	74LS221	110p	4076	88p
7474	32p	74LS240	210p	4077	23p
7475	40p	74LS241	200p	4078	29p
7476	40p	74LS242	225p	4081	23p
7490	35p	74LS244	175p	4082	25p
7492	50p	74LS247	220p	4085	86p
7493	50p	74LS249	120p	4086	68p
7496	45p	74LS251	120p	4089	130p
7491	35p	74LS252	110p	4093	68p
74123	45p	74LS259	110p	4094	225p
74154	90p	74LS271	175p	4095	99p
74157	55p	74LS291	95p	4096	325p
74122	45p	74LS292	120p	4098	110p
74125	50p	74LS293	110p	4099	180p
74195	100p	74LS312	170p	4501	25p
74196	100p	74LS314	170p	4502	112p
74283	140p	74LS315	140p	4503	68p
74290	120p	74LS393	135p	4507	52p
74365	90p	74LS496	140p	4508	285p
74395	90p	74LS497	260p	4510	76p

74LS

CMOS	74LS00	12p	4001	19p
	74LS01	12p	4002	19p
	74LS02	13p	4003	19p
	74LS03	13p	4006	75p
	74LS04	13p	4007	19p
	74LS08	20p	4008	80p


SPOT DESIGNS

Guitar Treble Booster

This simple treble booster circuit can be used to give a more brilliant sound to an electric guitar and could possibly be of use with other instruments. Q1 is connected as a straightforward common emitter amplifier with R3 as the collector load, R4 as the emitter bias resistor and R1 plus R2 to provide base biasing. Although the voltage gain provided by a common emitter stage is normally quite high, this is not the case here, since the emitter bias resistor is not bypassed by a capacitor. As R3 and R4 have the same value, the voltage gain of the circuit is approximately unity.

In fact there is an emitter bypass capacitor (C3), but this has a low value and is in series with R5 and RV2. With RV2 at maximum resistance the effect of C3 on the response of the unit is minimal and for practical purposes the degree of treble boost applied is of no significance. If RV2 is adjusted for lower resistance, C3 has more effect and begins to produce a significant amount of treble boost. The boost is only produced at higher frequencies incidentally, due to the low value of C3 and its consequent high impedance ineffectiveness at low frequencies. With RV2 at minimum resistance the response starts to rise at about 800 Hz and reaches a maximum degree of boost of about 26 dB at frequencies of around 10 kHz or more. R5 limits the degree of high frequency boost and this is necessary in the interest of low noise and good stability.

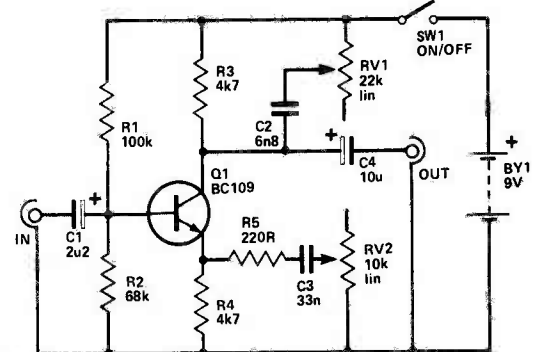The full degree of boost at the highest audio frequencies may give a sound that is too harsh for some tastes and so RV1 and C2 have



(C) COPYRIGHT MODMAGS Ltd

been included in the circuit. With RV1 at maximum resistance these do not have any significant effect on the unit, but at lower resistance settings the high frequency response becomes flattened off and towards minimum resistance the response turns over at frequencies above about 8 kHz. RV1 and RV2, therefore, give considerable control over the treble boost and enable the response to be tailored to suit individual tastes.

Simple MW Radio

This simple medium wave broadcast receiver has an output power of up to about 150 mW RMS for an internal high impedance loudspeaker and is based on two ICs. The familiar ZN414 is used to provide the RF amplifier, detector and AGC functions, while a ULN2283B device is used as the audio power amplifier.


The circuitry around IC1 is quite straightforward with D1, D2 and R1 being used as a shunt stabiliser, which gives the required operating voltage of 1V2 to 1V3 for IC1. CV1 is the tuning control and L1 is the tuned winding of the ferrite aerial. The ZN414 has a high input impedance which renders the low impedance coupling winding on the ferrite aerial unnecessary. This can either be ignored or it can be carefully removed from the aerial, if preferred.

RF filtering at the output of IC1 is provided by C3, R3 and C4. Effective RF filtering is essential as a small amount of RF leakage into the

input of audio amplifier IC2 would almost certainly be sufficient to cause severe instability in the circuit as a whole. RV1 is the volume control and is also used to bias the input of IC2. C5 decouples the supply to the input stages of IC2 and helps to prevent low frequency instability due to feedback through the supply lines. C6 couples the output of IC2 to the loudspeaker.

IC1 provides an audio output signal of 25-30 mV RMS on reasonably strong signals. The voltage gain of IC2 is set at a nominal figure of 43 dB (about 140 times) by an internal negative feedback circuit and this is, therefore, well matched to the signal level provided by IC1.

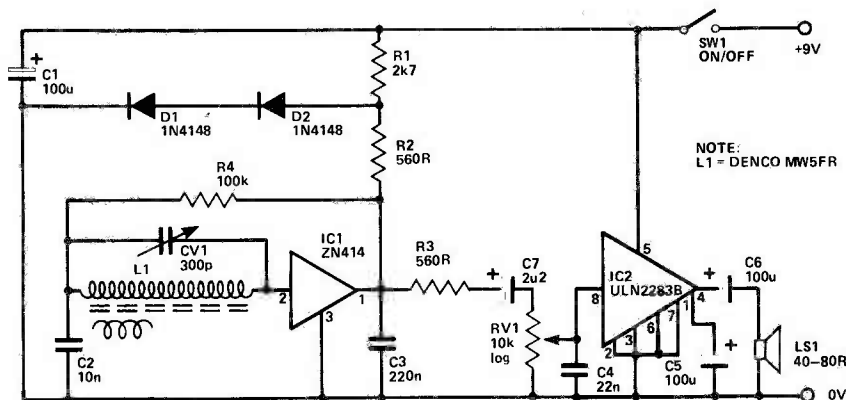The quiescent current consumption of the circuit is typically about 15 mA, but as IC2 has a class AB output stage, the current consumption rises somewhat (to a maximum average level of about 25 mA) at higher volume settings. The ULN2283B device used in the IC2 position is available from Ambit International.



(C) COPYRIGHT MODMAGS Ltd

CLEF ELECTRONIC MUSIC

MASTER RHYTHM

As published in Practical Electronics



KIT. - £79. BUILT - £114

- FULLY PROGRAMMABLE TWENTY-FOUR PATTERNS
- EIGHT PARALLEL TRACKS
- TWELVE INSTRUMENTS
- SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

PIANOS

SPECIALISTS SINCE 1972 STAGE & DOMESTIC TYPES



The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique. Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufacture.



SIX OCTAVES £207
7½ OCTAVES £232

STRINGS £169

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch plus two-phase Chorus.

ROTOR-CHORUS £89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" p.c.b. Mains P.S.U. included.

KEYBOARDS

Square Front with two hole actuator—easily cut.

49 NOTE—£25; 73 NOTE—£39
88 NOTE—£47

OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates — in Australia please contact JAYCAR in Sydney


ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)
44A BRAMHALL LANE SOUTH, BRAMHALL,
STOCKPORT, CHESHIRE SK7 1AH. 061-439 3297

RADIATION DETECTORS

BE PREPARED WITH THIS DETECTOR

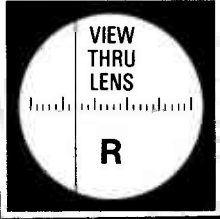Recommended for General use.
CIVIL DEFENCE ● FIRE SERVICES ● MEDICAL



THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS.

UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.

PRECISION INSTRUMENT. METAL CASE, WEIGHT 2oz.

CONTAINS 3 LENSES. RUGGED CONSTRUCTION.

MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.

Be prepared, buy whilst available.

HENRY'S

Standard model 0-5 or 0-50R ONLY

£6.95 inc. VAT
Post & Packing 60p



404 EDGWARE ROAD, LONDON W2 1ED



A NEW ADVENTURE IN COOKING! COMPONENTS AND CHIPS FROM

Fast Service — Low Prices — Great Menu **ELECTRONICS**


COMPUTER GRADE HIGH RIPPLE CAPS				TTL ICs				Type N LS S				XTALS			D RANGE CONNECTORS			TRANSISTORS						
MF	Volts	Dim mm	Price pp	Type	N	LS	S	74107	32p	-	-	Frequency	Case	Price	Ways	Plug	Block	2N667	22p	AD162	40p	BC251A	15p	
1500*	100	80-35	70p	7400	10p	15p	25p	74109	30p	-	-	19.20KHz	HC6U	300p	9	103p	125p	2N669	35p	BC108	10p	BC252	16p	
2200	40	50-25	150p	7401	12p	-	-	74112	-	-	90p	38.40KHz	HC6U	400p	15	117p	201p	2N706A	25p	BC109	10p	BC321	13p	
3300	25	50-25	150p	7402	12p	15p	14p	74114	-	-	45p	100.00KHz	HC6U	300p	25	172p	258p	2N1136A	25p	BC147	7p	BC337	13p	
3300*	63	115-35	80p	7403	16p	-	-	74116	195p	-	-	110.00KHz	HC7C	400p	37	235p	414p	2N2646	45p	BC148	7p	BC338	14p	
3300*	150	100-65	180p	7404	14p	15p	-	74117	75p	-	-	1.00MHz	HC6U	320p	50	290p	546p	2N2904	23p	BC149	7p	BC348	15p	
4700	75	115-35	190p	7405	18p	-	-	74121	28p	-	-	2.00MHz	HC6U	280p	2N2906	23p	BC157	8p	BC254	12p	BC347	12p		
11000	25	88-50	180p	7406	32p	-	-	74122	41p	-	-	4.00MHz	HC6U	280p	2N2926	7p	BC159	10p	BC548	8p	BC548	8p		
15000	16	80-35	180p	7407	32p	-	-	74123	45p	-	-	5.00MHz	HC18	280p	2N3053	25p	BC167	10p	BC549	9p	BC549	9p		
15000	40	115-35	190p	7408	32p	-	-	74125	53p	-	-	6.00MHz	HC18	280p	2N3055H	60p	BC170	10p	BC733A	120p	BC733A	120p		
22000	16	80-50	220p	7409	22p	-	-	74128	72p	-	-	10.00MHz	HC18	280p	2N3440	60p	BC170A	11p	BC742C	80p	BC742C	80p		
22000	25	115-35	250p	7410	15p	19p	-	74132	68p	-	-	11.20MHz	HC18	280p	1103	-	50p	2N3526	7p	BC172	10p	BC750	28p	
29000	25	105-70	270p	7411	15p	38p	-	74133	-	-	25p	10.25MHz	HC18	280p	2101-4	-	410p	2N3528	7p	BC173	10p	BC751	28p	
34000	50	145-75	350p	7412	20p	-	-	74137	180p	-	-	11.20MHz	HC18	280p	*2114L-3	300NS	35p	2N3559	60p	BC174	10p	BC752	28p	
64000	40	115-75	590p	7413	30p	-	-	74140	103p	-	-	20.00MHz	HC18	280p	4006-4	-	95p	2N3703	8p	BC171A	11p	BC752	28p	
68000	16	115-60	575p	7414	50p	-	-	74150	98p	-	-	DL XTAL OSC @ 600KHz	HC18	280p	4027	37NS	350p	2N3704	8p	BC172A	10p	BC753	28p	
138.000	10	145-75	600p	7415	27p	-	-	74151	60p	-	100p	5000 XTALS EX-STOCK	HC18	280p	*4116	20NS	200p	2N3771	150p	BC172B	10p	BC754	28p	
180.000	30	220-75	750p	7417	20p	18p	-	74153	85p	-	-	PHONE YOUR FREQUENCY	HC18	280p	5101L	450NS	495p	2N3906	15p	BC172C	10p	BC755	28p	
				7423	30p	-	-	74154	98p	-	-				TMS3114SH REG	140p		2N4304	20p	BC172	10p	BC756	28p	
				7427	34p	-	-	74155	60p	-	-				*4116	8 for	1995p	2N4351	50p	BC173C	10p	BC757	28p	
				7428	35p	-	-	74157	60p	-	65p						2N4352	50p	BC174B	10p	BC758	28p		
				7430	17p	20p	-	74161	90p	-	-						2N5447	10p	BC182L	10p	BC759	28p		
				7432	28p	30p	-	74163	80p	-	-						2N5449	12p	BC207B	15p	BC760	28p		
				7437	35p	-	-	74164	120p	-	110p						2N5493	55p	BC212L	8p	BC761	28p		
				7438	30p	35p	-	74166	120p	-	-						2N6385	125p	BC213A	8p	BC762	28p		
				7439	30p	-	-	74170	235p	-	-						AC179	16p	BC250A	12p	BC763	28p		
				7440	17p	19p	-	74172	445p	-	-						AD161	40p	BC251	14p	BC764	28p		
				7441	65p	-	-	74173	110p	-	-													
				7442	55p	-	-	74174	85p	-	-													
				7445	120p	-	-	74175	80p	-	100p													
				7447	45p	-	-	74180	85p	-	-													
				7450	17p	-	-	74181	150p	-	-													
				7451	-	22p	-	74182	-	-	90p													
				7454	17p	23p	-	74190	85p	-	-													
				7470	39p	-	-	74191	85p	-	-													
				7472	28p	-	-	74193	85p	-	95p													
				7473	34p	-	-	74194	85p	-	-													
				7474	28p	32p	36p	74197	75p	-	-													
				7475	28p	-	-	74198	140p	-	-													
				7476	39p	-	-	74241	150p	-	95p													
				7485	90p	-	-	74266	-	-	-													
				7486	34p	35p	-	74273	265p	-	-													
				7489	200p	-	-	74279	80p	-	-													
				7490	28p	-	-	74283	155p	-	-													
				7492	50p	-	-	74284	400p	-	-													
				7493	28p	-	-	74285	400p	-	-													
				7495	65p	-	-	74298	180p	-	-													
				7496	80p	-	-	74366	95p	-	-													
				7497	175p	-	-	74387	90p	-	-													
				74100	110p	-	-	74390	-	-	140p													
				74104	130p	-	-	74393	195p	-	-													

DISPLAY ELECTRONICS 64-66 Melfort Road Thornton Heath, Croydon, Surrey CR4 7RN Telephone Orders: 01-689 7702/01-689 6800

Please add 50p Post and Packing All Prices Include VAT

Bona Fide Account Orders Minimum £10.00 Warehouse Open 10-5.30 Mon-Sat 1,000's of Other Items

REMOTE- CONTROLLED TOUCH

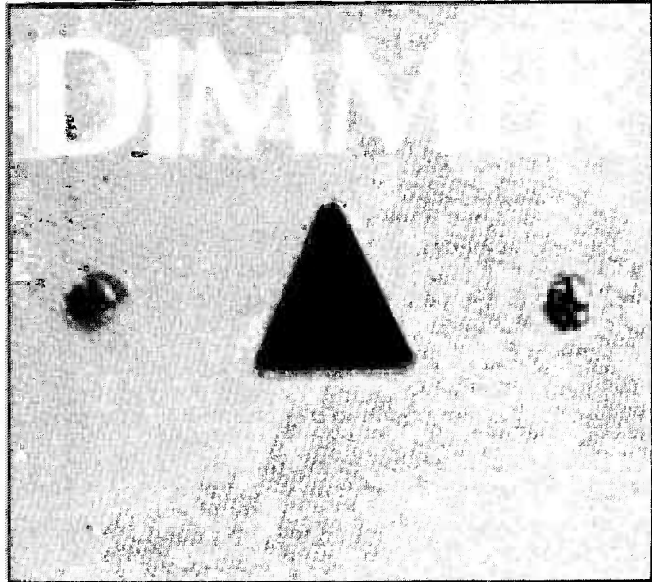

This smart lamp dimmer can be controlled directly by the built-in touch pad or remotely with the five-channel transmitter unit described elsewhere in this issue. Design by Ray Marston. Development by Plamen Pazov.

This sophisticated little touch dimmer is an updated version of the programmable touch dimmer described in the April '80 issue of ETI, in that this new unit can be controlled either directly by a touch pad fitted to the unit or remotely with a press button on the transmitter of the five channel remote control system described elsewhere in this issue; the new dimmer can thus be remote-controlled from the comfort of an armchair, etc. The 'five channel' system can, in fact, independently control two of these dimmer units. Each dimmer can power any lamp load up to 300 W.

The dimmer is 'smart' in that it has built-in logic and sensing networks that enable the unit to be turned on or off or dimmed up or down by using a single touch pad or remote-control button. If the pad (or switch) is simply touched for a brief period (60 to 400 mS) the lamp merely changes state, ie, from off to on, or vice versa, depending on the previous state.

A longer touch (greater than 400 mS) causes the lamp brilliance to cycle slowly from dim to bright or vice versa for the duration of the touch, taking about 7 S to span the full brilliance range: when the touch is removed the prevailing brilliance level is latched into memory and maintained indefinitely. At switch-off (a brief touch) the prevailing brightness level remains in store and is automatically resumed again at switch-on (another brief touch). In the case of dimming, control starts from the stored value.

Remote Control

The dimmer can be controlled locally by the touch pad or remotely using the infra-red remote controller. In either case, the dimmer works in the OR mode, so that alternate operation is directly available. The remote control system has a maximum range (from transmitter to receiver) of about 10 m; the remote control facility can be implemented by a pair or wires taken to the dimmer from one of the decoder outputs of the remote control system. These wires pass only a few milliamps from a 12 V

source and can easily be concealed in a slot made in the wall plaster. The wires connect to an opto-isolator built into the dimmer unit and this isolator ensure that the wires have several kilovolts of mains isolation, thereby ensuring a very high safety factor.

Construction

Our prototype is designed to fit into a standard plaster-depth lighting switch box. Before starting construction, check the project's suitability to your existing wiring by making an accurate cardboard cut-out of the PCB and checking that it will fit comfortably into your existing lighting switch box. If not, you'll need to fit a new (modern) box. If all is well you can proceed with the construction.

Construction calls for a certain amount of care. Note that the S556B IC is a special-purpose touch dimmer device manufactured by Siemens and must not be confused with the similarly numbered NE566N VCO IC. On our prototype we've mounted the S566B and the 6 pin opto-isolator IC in a single 16 pin DIL socket. Triac SCR1 is fitted with a small heatsink, made from a piece of scrap aluminium; ensure that this heatsink will not foul the lighting switch box when the dimmer unit is fitted in to place. Note that two Veropins are fitted to the PCB to provide the remote-control connections. Connections to the mains live terminal and the lamp load are made via a two-way screw terminal strip mounted on the PCB.

Blank Checks

When construction is complete, connect the unit to the mains via a lamp load in accordance with the circuit diagram and the overlay and give the unit a functional check, using the touch pad point at the centre of the PCB. Check that the unit dims and turns on and off as already described. Also check that it does not cause excessive interference on your radio set; if ex- ➔

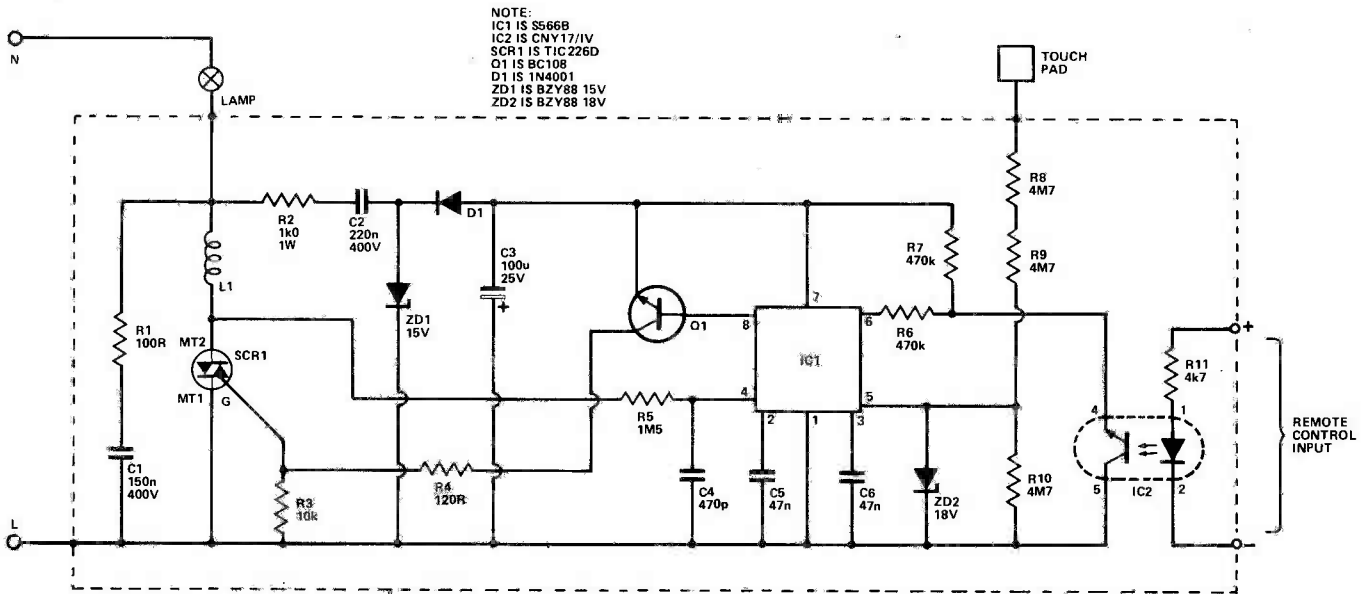


Fig.1 Circuit diagram.

HOW IT WORKS

The 'intelligent' action of the circuit is carried out in special-purpose PMOS integrated circuit IC1. This chip receives instructions from a touch-pad or a touch 'switch'. It processes the input touch-duration information and then sends (or does not send) appropriate gate drive pulses to triac SCR1 via pin 8 and current-boosting transistor Q1.

If IC1 decides that the lamp should be switched on it sends one 30 μ s, 100 mA gate pulse to the triac in each mains half cycle (every 10 mS), at some phase-delayed time after the start (zero-crossing point) of each half cycle. The magnitude of the phase delay determines the brilliance of the lamp. If the triac is triggered shortly after the start of each half cycle (short delay) the lamp burns brightly; if it is triggered near the end of each half cycle (long delay) the lamp burns dimly. The maximum and minimum phase delays are limited to 150° and 30° respectively, enabling the lamp power to be varied from roughly 3% to 97% of maximum by the triac.

Although IC1 and Q1 generate relatively high peak drive power (1 W2), their mean power dissipation is very low (about 12 mW). This power is derived from the mains via R2-C2-ZD1-D1 and C3 and is delivered to IC1 and Q1 as a smooth 14 V DC from reservoir capacitor

C3. This method of operation is only made possible by the fact that the triac is not gated on until at least 30° after the start of each half cycle, thereby enabling C3 to attain and maintain a virtually full 14 V charge throughout each half cycle. The IC logic operation is synchronised to the zero-crossing points of the mains signal by the R5-C4 network.

Touch information can be fed to either pin 5 or pin 6 of IC1. The pin 5 input is intended for genuine touch contact use and works on the high-impedance hum-pickup principle. The touch pad is effectively connected to the mains live terminal via high-value resistors R8-R9-R10, which limit the touch pad current to safe and minimal levels. ZD2 limits the pin 5 hum signal amplitudes to safe values.

The pin 6 input is intended for use with push-button switches connected between the mains live terminal and the junction of R6-R7. In our circuit the built-in transistor of opto-isolator IC2 is used in place of a conventional push-button and can be activated by one of the non-latching decoder outputs of our five-channel remote control-system.

The dimmer can be used with lamp loads up to 300 W, this limitation being imposed by the heat dissipation of triac SCR1. L1, R1 and C1 are RFI-suppression components.

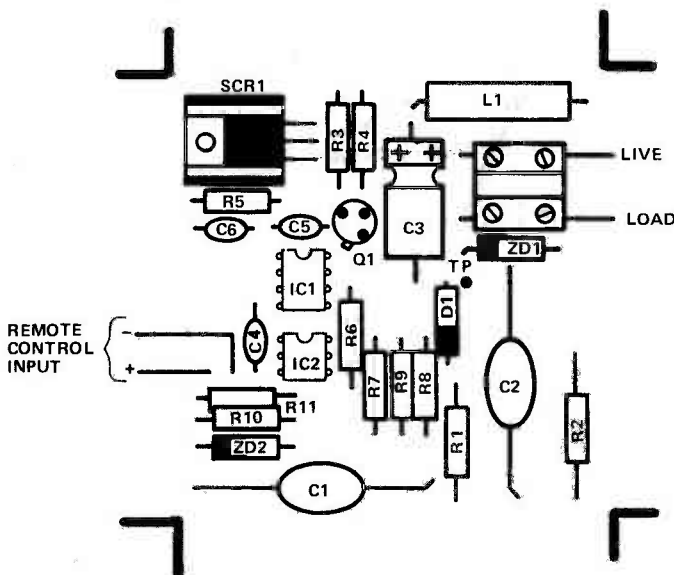


Fig.2 Component overlay for the touch dimmer.

PARTS LIST

Resistors (all 1/4 W 5% unless otherwise stated)

R1	100R
R2	1k0 1 W
R3	10k
R4	120R
R5	1M5
R6,7	470k
R8,9,10	4M7

Capacitors

C1	150n 400 V polyester
C2	220n 400 V polyester
C3	100u 25 V axial electrolytic
C4	470p ceramic
C5,6	470n polyester


Semiconductors

IC1	S566B
IC2	CNY17/IV
SCR1	TIC226D
Q1	BC108
D1	1N4001
ZD1	BZY88 15V zener
ZD2	BZY88 18 V zener

Miscellaneous

L1	3 A suppressor choke (ref. TV3C)
MK blanking plate, touch plate, 2-way terminal block.	

PROJECT : Touch Dimmer

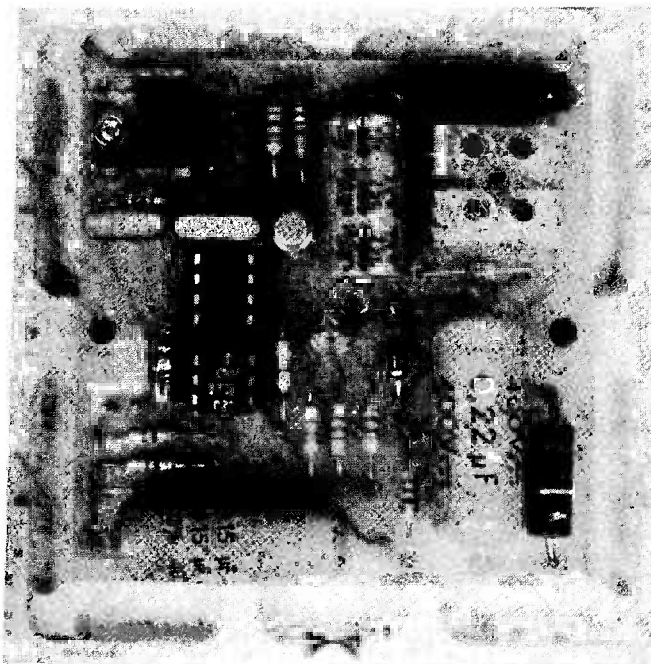

Component-side view of the PCB. Note the small heatsink on the triac and the small size of the high-voltage capacitors. The PCB is secured by the central fixing bolt.

cessive interference is experienced, try reducing the value of R1 to 47R. To check the remote control facility, use a push button switch to connect a 9-12 V DC supply to the terminals, observing the polarity shown.

When you are satisfied that the unit is operating correctly you can fit the PCB and the touch pad (see Buylines) to a standard blanking plate (available from your local electrical shop) as shown in the photos. The plate is provided with a central 'knock-out' hole. Open the hole, push the touch pad through the plate hole and the central hole in the PCB and bolt the two units firmly together, using a pair of nuts and washers (one on either side of the PCB) fitted to the screwed thread of the touch pad; a certain amount of fiddling may be necessary to ensure a firm fitting. Check that the holes on either side of the PCB line up with the securing holes in the blanking plate.

When you finally fit the completed unit into its switch box take care to ensure that no shorts occur. To play really safe, you can cover the inside of the box and the SCR1 heatsink with insulation tape at vulnerable points. You can bury the remote-control wires in a groove made in the plaster, taking the connections to the dimmer through one of several knock-out holes provided in the switch box. The other end of the wires goes to one of the non-latching outputs of the remote-control decoder.

BUYLINES

This project uses a few hard-to-get parts. Electrovalue can supply IC1, IC2 and the choke. Watford can supply IC1, SCR1 and the anodised touch plate. All other components should be readily available, but ensure that the capacitors are reasonably small types.

ETI

Join the Professionals...

Crimson modular audio amplifiers feature: ★ Low values of transient and steady-state distortions ★ Envelope distortion (below 500 Hz) less than 0.05% ★ on-board electronic protection ★ P.C.B. pin and edge connector termination ★ Full range of complimentary components, i.e. P.S.U.'s, heatsinks etc. available from Crimson.

The Crimson range of amplifier modules are built to very high standards and have earned an enviable reputation in every field to which they have been applied. The boards come ready built and tested (guaranteed for two years) and can be used to advantage where high quality signal amplification is required. The power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge mode. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are catered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is basically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also on-board is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and gives the required boost for low output moving coil type cartridges. External components required are potentiometers for volume and balance, switches for phono cartridges. External components required are potentiometers for volume and balance, switches for phono cartridges and a regulated ±15V D.C. power source (REG1). Complimenting this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

Numerous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Power amplifier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review, August 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietary flight cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in Wireless World October/November 1980. Further details of how to use the modules are contained in the Users / Application Manual available at £0.50.

SPECIFICATIONS


Type	D/P8ohms*	D/P4ohms*	PSU	H/Sinks	Slew	S/N	Sensitivity	T.H.D. (typ)	FR	Size
CE 608	38		CP51	50mm	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz (3dB)	80 x 120 x 25
CE1004	44	70	CP53	100mm	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz (3dB)	80 x 120 x 25
CE1008	66		CP53	100mm	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz (3dB)	80 x 120 x 25
CE1704	85	121	CP56	150mm FM1	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz (3dB)	80 x 120 x 25
CE1708	125		CP56	150mm FM1	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz (3dB)	80 x 120 x 25
CP3000		250	CP56	FM2	30V/μs	110dB	775mV	0.0035%	1.5Hz 50kHz (3dB)	161 x 102 x 35
CPR1(S)	Output	775mV	REG1		3V/μs	90dB	2.8mV/RMS	0.008%	20Hz 20kHz	128 x 80 x 35
MC1(S)	Output	2mV	REG1		66dB	80dB/150	0.008%	20Hz 20kHz	128 x 80 x 35	
XO2, XO3	Output	775 2500mV	REG1		9V/μs	90dB	2775mV	0.01%	X over points	150 x 40 x 20

*Power output is quoted WRMS and is given for two modules run off the same power supply. Higher powers are obtainable if using one module per P.S.U. or if using a stabilised P.S.U.

PRICES - HELD FROM MAY - TO APRIL '81

Power Amplifier Modules	Power Supply Modules	Heatsinks	Pre Amplifier Modules	Active Crossovers	Hardware
CE 608 £21.00	CP51 (8VA) £19.50	50mm £1.30	CPR1 £34.00	XO2 £19.00	Pre Amp £38.00
CE1004 £24.50	CP53 (150VA) £23.50	100mm £2.40	CPR1S £44.50	XO3 £28.35	Power Amp £38.00
CE1008 £27.50	CP56 (250VA) £30.00	150mm £3.50	MC1 £26.00	MU1 £7.50	Thermal Cutsouts £1.90
CE1704 £35.00	REG1 £9.30	FM1 £36.00	MC1S £37.00		
CE1708 £35.00	TR6 £12.50	FM2 £42.00			

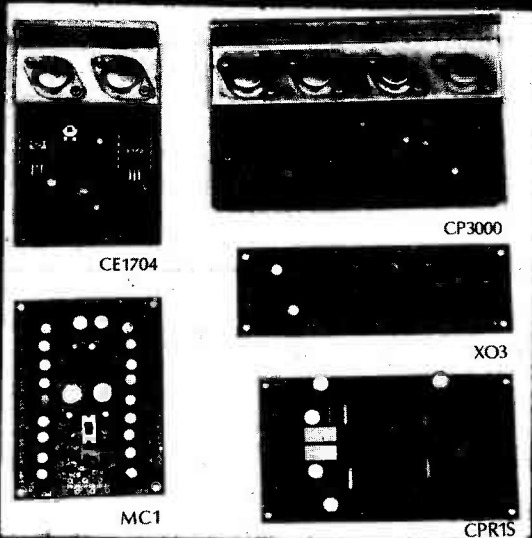Barclaycard
VISA
Master Charge
Newcom Access



Crimson Elektrik

9 CLAYMILL ROAD, LEICESTER LE4 7JJ, ENGLAND. Tel. 0533 761920. Telex 34694 Chamco G CRIMLEK

PLEASE SEND ME MORE DETAILS OF ALL CRIMSON ELEKTRIK AMPLIFIERS
Name _____
Address _____
ETI 5.81

CHROMASONIC electronics


48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD — 100 yards from Archway Station & 9 Bus Routes
 TELEPHONE: 01-263 9493/01-263 9495

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS

PETS & SYSTEMS

8N 8K RAM — £399
 16N 16K RAM — £499
 32N 32K RAM £599
 CASSETTE DECK — £55

343K Twin Floppy Disk
£695

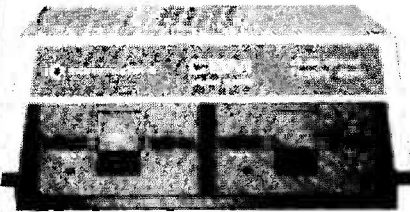


COMPLETE 32K SYSTEM £1789


NEW 32K with 80 col Screen
 Twin Disk Drive 950K **£825**
£895

All with new keyboard
 and green screen

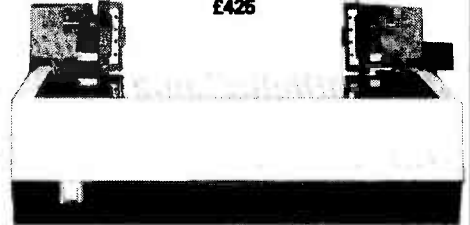FRICION FEED PRINTER
£375
Tractor Feed Printer
£425



NEW SHOP

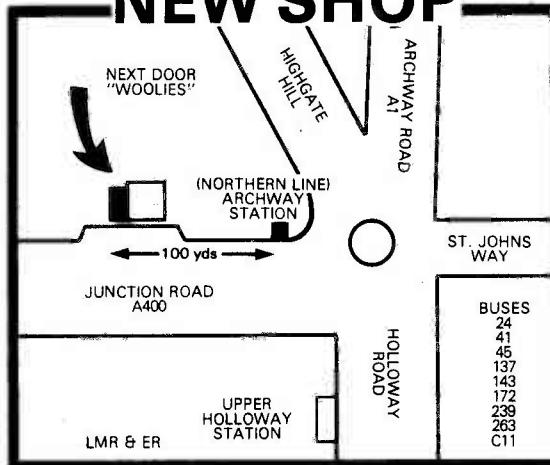

MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£79.95**
- ★ 16K kit **£106.95**
- ★ Printed Circuit Board **£29.95**
- ★ 40 pin-40 pin header plug **£8.50**

VIDEO GENIE

VIDEO GENIE based on TRS80



Utilises Z80, 12k level II Basic, Integral Cassette Deck, UHF O/P

16k RAM,
 all TRS80 features
£289

CASES

Available for UK101, Superboard, Nascom. Appx. DIM 17" x 15" 435 x 384 mm

PRICE £24.50
 Post & Packing £1.50

UK101 P.P.I

Built & tested. Interfaces TX80 Printer direct. Can be programmed to operate relays, motors, various other peripherals "CENTRONICS COMPATABLE"
 Plugs into IC socket. LED binary display fully documented. **£29.95**

UK101

£179 IN KIT FORM
£229 READY BUILT & TESTED
£255 COMPLETE IN CASE


4K Expansion (8x2114) NOW ONLY £14.00

- No extras required
- ★ Free sampler tape
 - ★ Full Qwerty keyboard
 - ★ 8K basic
 - ★ Ram expandable to 8K on board (4K inc)

★ Kansas City tape interface
 ★ **NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL £22.00**



PRINTERS

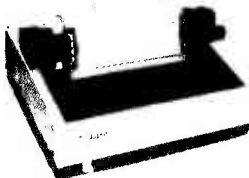


EPSON MX 80 £359
EPSON TX80 £295

Dot-matrix printer with Pet graphics interface: Centronics parallel and serial: Pet and Apple compatible.



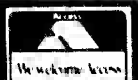Please add VAT 15% to all prices. Postage on computers, printers and cassette deck charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome, credit facilities arranged.



CHROMASONIC electronics

**NEW SHOP & SHOWROOM
NOW OPEN**

Telephone: 01-263 9493/01-263 9495

UK101 SOUND

Sound Generator and combined parallel in out port kit, containing P.C.B., AY-3-8910, 6820 PIA. Fully documented and demo tape. **£29.95.**
AY-3-8910 £8.50.

UK101 SOFTWARE

	£
Space Invaders	6.50
Real Time Clock	3.00
Chequers	3.00
Orhello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10xC12 Blank Tapes	4.00

MEMORY

D.RAMS	£ p
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	3.95

S.RAMS	
2102A	1.30
2102A2	1.69
2112A	2.75
2114/4045	2.75
4035	1.07
4044-5257	6.93
6810	3.50

BULK PURCHASE	
8x2114	14.00
8x4116	18.00
16x2114	26.00

Colour Board available at long last. Please write or phone for details. £84.95.

EPROMs

2708	4.25
2716 (5v)	6.95
2532	29.95

SUPPORT CHIPS

Z80 CTC	5.95
Z80A CTC	6.95
Z80 P10	5.95
Z80A P10	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
9224	2.75
8228	
8251	4.95
8253	9.75
8255	4.50
TMS9901	13.16
TMS9902	11.18
TMS9904 (74LS362)	8.40

ROM

2513 (UC)	5.95
-----------	------

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	1.50
8T97	1.50
8T98	1.50

I.C. SOCKETS

	D.I.L.	W/W
8 pin	.09	.25
14 pin	.11	.35
16 pin	.12	.42
18 pin	.16	.50
20 pin	.20	.62
22 pin	.22	.65
24 pin	.24	.70
28 pin	.30	.80
36 pin	—	.99
40 pin	.40	1.10

BAUD RATE GENS


MC14411	8.75
MM5307	8.75

C.P.U.

Z80 2.5Meg	7.95
Z80A 4Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

**SEND S.A.E. FOR COMPLETE PRICE LIST
OR PHONE 01-263 9493**

THE NEW AND UNIQUE VEROBLOC

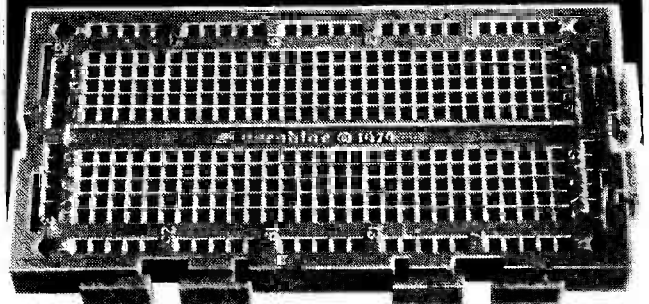


ADDS TO YOUR CAPABILITY

Already used in industry, this solderless breadboard is now available to the hobbyist. Unique because of its universal interlocking facility meaning you no longer need lots of different boards.

Send now for the unique Verobloc.

Order code 200-21092G. £4.16p inclusive.

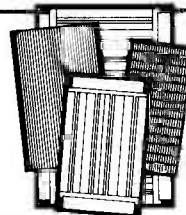

**AND VERO HAVE
ADDED TO THEIR
TRADITIONAL RANGE
OF HIGH QUALITY
BOARDS,
ALSO EX-STOCK.**

No.	Order Code	Description	Size (mm)	Price
1)	10-2845B	Microboard	160 x 100	5.66
2)	10-2846H	Microboard	160 x 233.4	12.41
3)	200-21084E	V-Q Board	147.83 x 73.66	1.65
4)	09-2196L	Veroboard	160 x 100	1.63

Carriage & VAT included.

Vero Electronics Limited, Retail Dept., Industrial Estate,
Chandler's Ford, Hampshire SO5 3ZR. Tel (04215) 62829

State quantity and order codes required _____

Name _____

Address _____

I enclose Cheque/PO for £ _____ or debit my Barclay Card/


Access No _____

Exp. date _____

vero

AUDIOPHILE

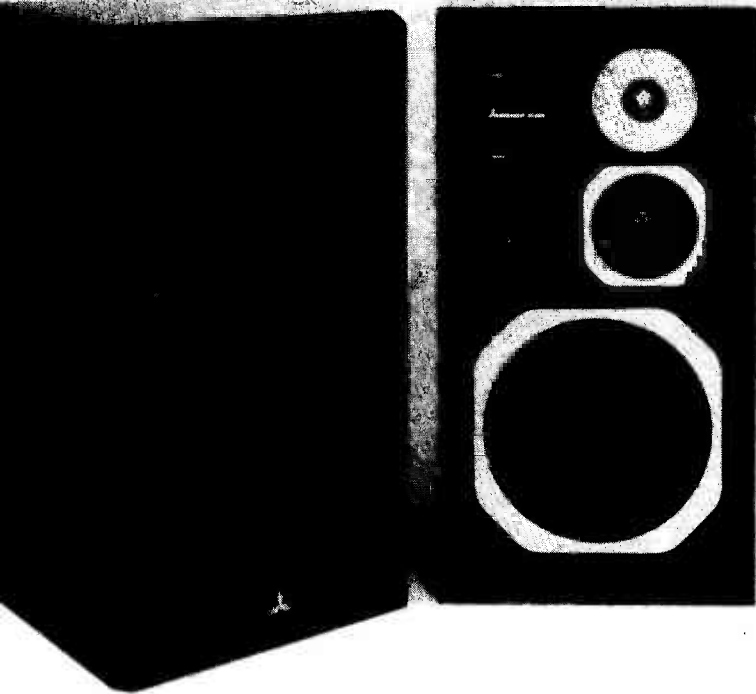This month Ron Harris reviews a new eastern loudspeaker design and a pair of pickups whose coils are mobile, whose price is low and whose output is high!



We begin this month with a review of the Mitsubishi DS-32B, a £250 speaker from the land of the rising yen. Loudspeakers remain the one significant area of hi-fi which the Oriental production machine has — so far — failed to dominate.

Only the Yamaha NS1000 and the Sony G1 have achieved any sort of acclaim in England's green and pleasant land, despite recent spending to engineer a "European Sound". The DS-32B is the Mitsubishi attempt to redress that balance.

It is a three-unit bass reflex design, claimed to handle 120 W of amplifier power and constructed to a very high standard indeed. The enclosures are supplied in stereo pairs (offset drive unit) with level controls fitted to the cone mid-range unit and the titanium tweeters.

Magnetic Personality

Mitsubishi make great play of the magnets used on their units, claiming to have developed a new ferro-nickel alloy for the woofer. Basically, what it actually comes down to is that strong magnets with high field strength and a 'long' gap have been employed to ensure linearity on high cone excursions.

The level controls are positioned on the front panel behind the grille and offer three positions of adjustment to the user. First reactions of the suspicious British will undoubtedly be to turn down the treble control.

The second will be to put it back again.

These units show none of their earlier Eastern brethren's tendency to cut through anything in their path with a sword-edged treble. If anything, Mitsubishi have over-compensated a little.

At approx 24 x 12 x 13 inches these speakers are not going to dominate the average living room, but they should be used on stands for best results — about 10-12 inches clear of the carpet will put the tweeter nicely at ear level and free the bass response remarkably. Connection is simple, as the speaker uses those 'push-clamp' terminals, which bite into the lead once released. Not as useful as screw terminals, but a universe ahead of the dreaded DIN.

Tested Responses

The DS-32B should not prove a difficult load to drive, as the impedance did not fall below 4R at any point in the frequency spectrum. Second order filters are used in the crossover networks, giving a 12 dB/oct roll-off, centred on frequencies of 800 Hz and 5 kHz. The unit changover was smooth, with no attendant irregularities in the frequency response of the speaker as a whole.

The titanium tweeter gave a particularly fine account of itself, exhibiting a smooth and extended performance with excellent dispersion — the offset arrangement means that 'lobes' are created in the dispersion pattern of a stereo pair, thus creating a better field around a central listening position.

For listening tests the DS-32Bs were set up — on stands — next to my reference speakers, the KEF 105 II. Obviously no attempt at direct comparison can be made, but it is important when auditioning, loudspeakers in particular, to have a standard available for comparison.

Ear Lies The Rub

Overall the DS-32B gave a very creditable performance. The balance tends to be a little 'warm' and the mid-range is slightly recessed in the 1 kHz-3 kHz region. Whilst this does take any hint of an 'edge' off the sound it lends a slightly unreal smoothness to the sound. I found I was turning up the mid-range unit to restore the balance. For the size of cabinet the bass response is very good, with nice definition of the instruments. The cut-off is sharp at the bottom end and this would tend to enhance the clarity of an enclosure of this size, so this is no bad thing overall.

At the top of the spectrum, that metal tweeter is well integrated into the system and has a generally good performance. It can sometimes add a little uncertainty to high energy, high frequency material, but only sometimes and only to a degree which is very acceptable at its price.

Concluding Tones

Judged against the asking price, I feel the DS-32B is an excellent speaker. Its value for money rating *has* to be high, when you consider the quality of the finish and high degree of engineering present in the units.

The sound quality is competitive indeed and deserves a chance to compare itself against better known enclosures from this side of the channel. I can recommend the DS-32B and would suggest that anyone in the £200-£300 speaker market makes the effort to hear them before committing his money.

Moving Onto Coils

Moving coil cartridges have only recently descended into the mainstream of hi-fi. With that emergence has come an increase in the number of units which do not require a step-up device, thus reducing the cost.

The best known of these was probably the Ultimo 10X — 'was' because the model has now been replaced (by Dynavector) by the Mark 2. And this, by the sheerest of contrived coincidences is one of two high-output cartridges under test this month. The other is the Mayware MC3L, a fine-line stylus design from the 'Formula 4' people.

The output of these units is similar at around 2-3 mV, sufficient to drive most preamps and higher than many moving magnet designs. You can pick up the rest of the technical details from Table One. As the two cartridges are priced at approximately £65 and £55 respectively they are well within the financial reaches of 'mid-fi' buyers and offer an interesting alternative to other moving magnet cartridges in this price range.

The Ultimo End?

The 10X2 is an increased output version of its predecessor, but unusually in these days and ways, no price increase accompanies the model change. Indeed under the Dynavector exchange system, if you trade in your old unit it will generate a hefty discount on the price of a new 10X2. Therefore you could say the price has actually *fallen* for a change.

The cartridge is a low compliance design, at around 15 cu, and will this transmit more energy back into the arm than units such as the 900IGC and 600LAC which are possessed of more units in their compliances.

This means that the arm used will have to have a fairly high mass, to bring the combined resonant frequency to an acceptable frequency — above warps but below audibility — say between 10 Hz and 15 Hz. To test the 10X2 I used an AT 1010 and an integrated turntable with mid-mass arm. In addition an SME Series III was used with its mass suitably raised to match the Dynavector.


Because the SME is such a low mass design, it is possible to *add* mass to its effective value, in order to use low compliance pick-ups. Any readers out there who wish to know more details of this can write to SME for information sheet No. 24. Tell them ETI sent you!

Good Public Image

The 10X2 is startling to see in the end of *any* arm, having retained that transparent red plastic case, with a long cantilever and rigid mounting bracket. The disc clearance is substantial to say the least, and arm height should be carefully adjusted.



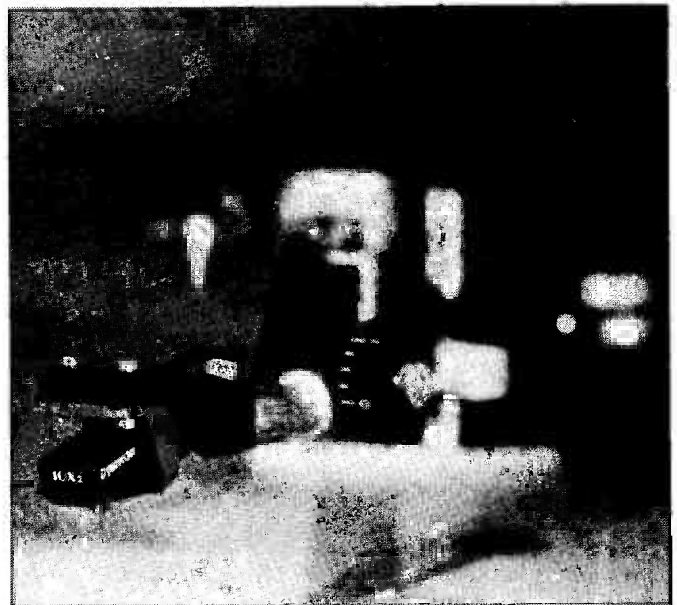The 10X2 in close up. Note the massive fixing bracket and the "see-through" casing. Bright red too.




Fitted to an arm, on this the Dynavector, the 10X2 looks a little less imposing. It never looks anything less than striking, though!

The sound is a distinct improvement on the already high standard of its earlier version. The balance is well struck between bass extension and detail in the low registers, and the imaging is nothing short of excellent. Treble quality is sweet and extended with very good detail rendition.

At the price the Dynavector offers very good value for money indeed, having most of the virtues of the more expensive moving coils and lacking their vice of price (!?) If I have any criticism at all of the 10X2 it is in that the low mid-range can sound a little constricted with some material, such as massed voices. It is a minor aberration.

A sound design then, well recommended, and with the advantages of (i) not needing a step-up device and (ii) a good trade-in deal on your old Ultimo if you're upgrading. ➔


TABLE ONE

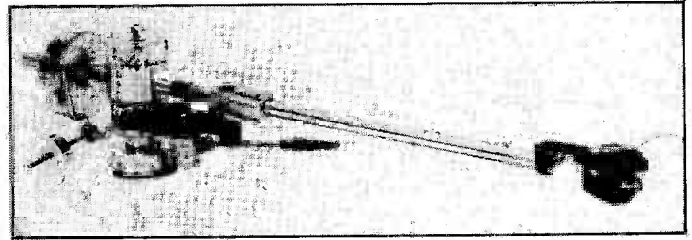


Above: the faithful Formula 4 pickup arm in which the cartridges were tried during listening tests. It is well suited to low compliance designs such as these, and gave good results.

	MAYWARE MC3L	DYNAVECTOR DV10X2
Compliance (vertical-horizontal) (cm/dyne)	8×10^{-6}	15×10^{-6}
Output level (1 kHz/5 cm sec)	2.6 mV	2.4 mV
Stylus type	line contact	elliptical
Separation (5 kHz)	22 dB	24 dB
Freq response (20 Hz-20 kHz)	± 2 dB (see graph)	± 2 dB (see graph)
Optimum tracking weight	2 g	1.6 g
Weight	7 g	9.6 g
Typical price	£53	£68 (less with exchange)

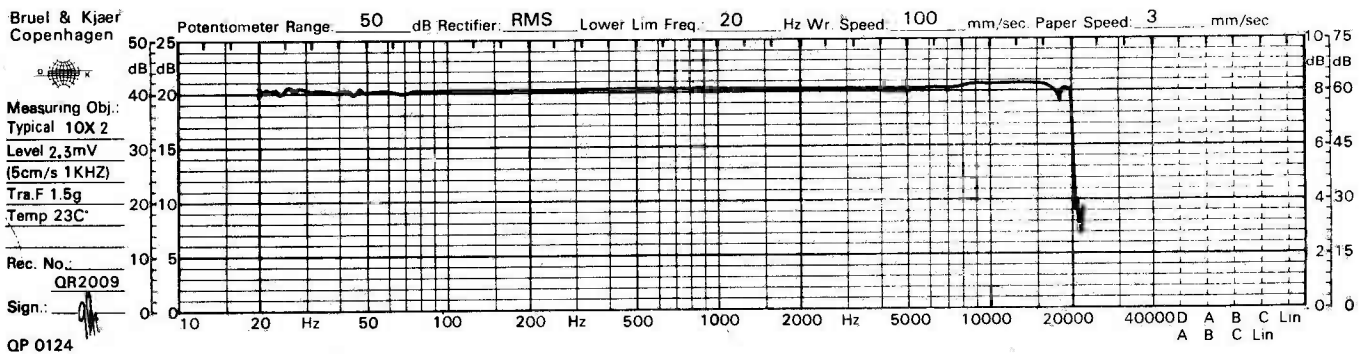Left: the lab test results for the MC3L and the 10X2 set out for comparison.



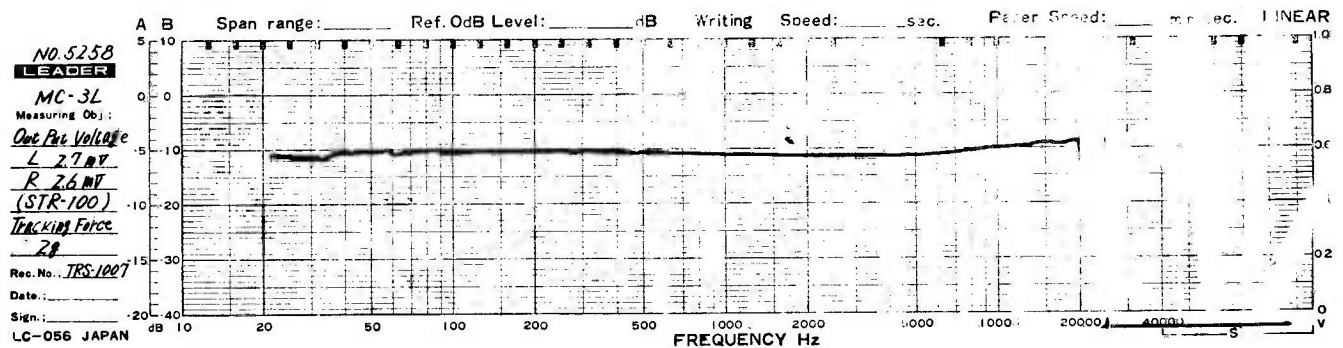Above: the frequency response of the new Dynavektor 10X2 pickup. Not a lot to comment on is there?




Above: measured frequency response of the Mayware MC3L moving coil cartridge.

Mayware Mayhap

The MC3L is the latest from Mayware, best known for their excellent Formula 4 pickup arm — now in its Mark 3 incarnation. Their previous pickup, the MC-2C, is a low device of high quality and so the DC3L is their next step in cartridge design.

Visually it is the opposite of the flamboyant Dynavektor, being simple and black in appearance. The cartridge body is very sensibly shaped with a good large surface area to the top, which aids fixing to the arm. This means that the pickup as a whole will be better integrated, as it will inevitably be more rigid than it would with a smaller contact area between headshell and cartridge.

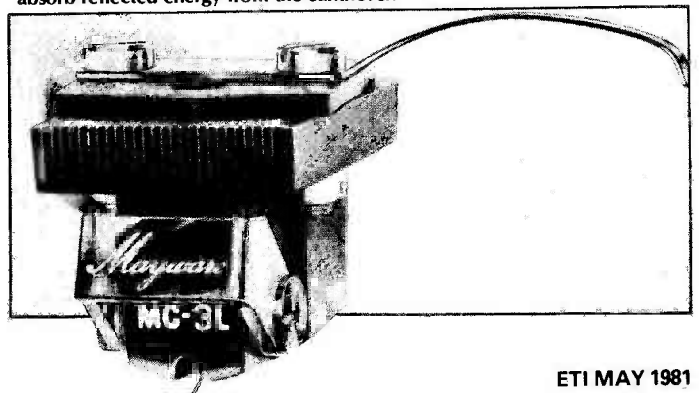Mayware's new high-output moving coil cartridge. The body is designed to absorb reflected energy from the cantilever.



The compliance of this unit is very low indeed at 8 cu, a figure which I feel will limit the arm it can be employed with. For the purposes of review I managed to beg, steal and borrow a Formula 4 (an earlier model) and fitted the unit into it. Listening tests were mainly conducted with this assembly, although for interest and devilment I did fit the MC3L into my SME III, with maximum damping and highly modified effective mass to tune the resonance.

Testing Benches

On test the MC3L acquitted itself well, the frequency response in particular impressing with its high linearity and well maintained separation. Output measured at 2.6 mV per channel.

There was nothing at all to cause the slightest worry here, so I was able to move on happily to playing some music, expecting something pleasant in the light of the test results.

... And Ears

I was not disappointed. Initial impressions, later reinforced by continued use, were of a wealth of detail with fair bass extension and 'smooth-as-silk' treble. Mid-range is firm and weighty with good control of vocals — not always a strength of moving coil units. Overall the balance is full and rich with good imaging and better than average tracking ability. My only real quibble is with that lower-than-low compliance. It does limit the versatility of the MC3L considerably, which is a shame as it has the virtue to delight a wide audience.

Common Ground

These two cartridges have a lot in common, in that neither requires a step-up device, both are low compliance, both are sensibly priced and have that rendition of detail which makes moving coils such an attractive proposition. Few moving magnets (G900 IGC?) can equal them in this respect.

Each has its good and not-so-good points. The 10X2 handled bass energy a little better than the MC3L, but the Mayware leaves it for dead on vocal material where there is a deal of energy in the mid-range; opera in particular. Both sound very good indeed on most rock music and which is 'best' is really up to the purchaser. I shall refrain from choosing between the two — I liked them both!

Reference Point

The cartridge I used as a reference in the comparison was the Ortofon MC30 with the T30 transformer. It is priced right at the top-end of the market and makes an interesting counterpoint to this month's models. I was intending to run the review in this month's Audiophile, but I just haven't the space to do it justice — so I'm holding onto the verbiage until next month. With all the tales of wonders unveiled by such exotic groove followers as the Linn Asak and the Koetsu filling the printed page these days, the Ortofon appears to have been overlooked. This is unjust indeed.

ETI

ELECTRONICS POCKET BOOK

Fourth Edition by E. A. Parr

Chips with everything! — Semiconductor technology has progressed at a startling rate and microprocessor chips have caused an information revolution that will be as significant as the Industrial Revolution proved to be. This fourth edition of *Electronics Pocket Book* is completely new and covers the latest developments in areas such as optoelectronics and microprocessors as well as the basic principles.

The book gives a non-mathematical presentation of the many topics in electronics and is designed to provide the designer, student or enthusiast with a readily accessible source of information.

186 x 120mm 360 pages **£5.60**
0 408 00481 9 Illustrated Paperback

Companion Books

by R. G. Hibberd

Transistor Pocket Book
A comprehensive guide to the principles, characteristics and uses of the various types of transistors, practical circuits being given for the major transistor applications. Related devices, conductor diodes, thyristors, etc. are also covered.

186 x 120mm 312 pages
0 408 00254 9
Illustrated Paperback

£5.60

Integrated Circuit Pocket Book
The book covers both unipolar and bipolar i.c.s. and their applications in linear and digital circuits. It is intended primarily for technicians, students and all who are concerned with integrated circuits and their applications.

186 x 120mm 282 pages
0 408 00255 7

Illustrated Paperback

£5.60

Available from your local Bookseller or in case of difficulty from the Publisher.



ORDER NOW

Cut out this coupon and return it to Patricia Davies Marketing Manager at the address below

Please send me

- Electronics Pocket Book - 4th Edition (Parr) 0 408 00481 9 £5.60 Paperback
- Transistor Pocket Book (Hibberd) 0 408 00254 9 £5.60 Paperback
- Integrated Circuit Pocket Book (Hibberd) 0 408 00255 7 £5.60 Paperback

I enclose a cheque/PO for £_____ in total payment


From _____

Address _____

(ETI 5/81)

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

£395
incl.VAT& P&P

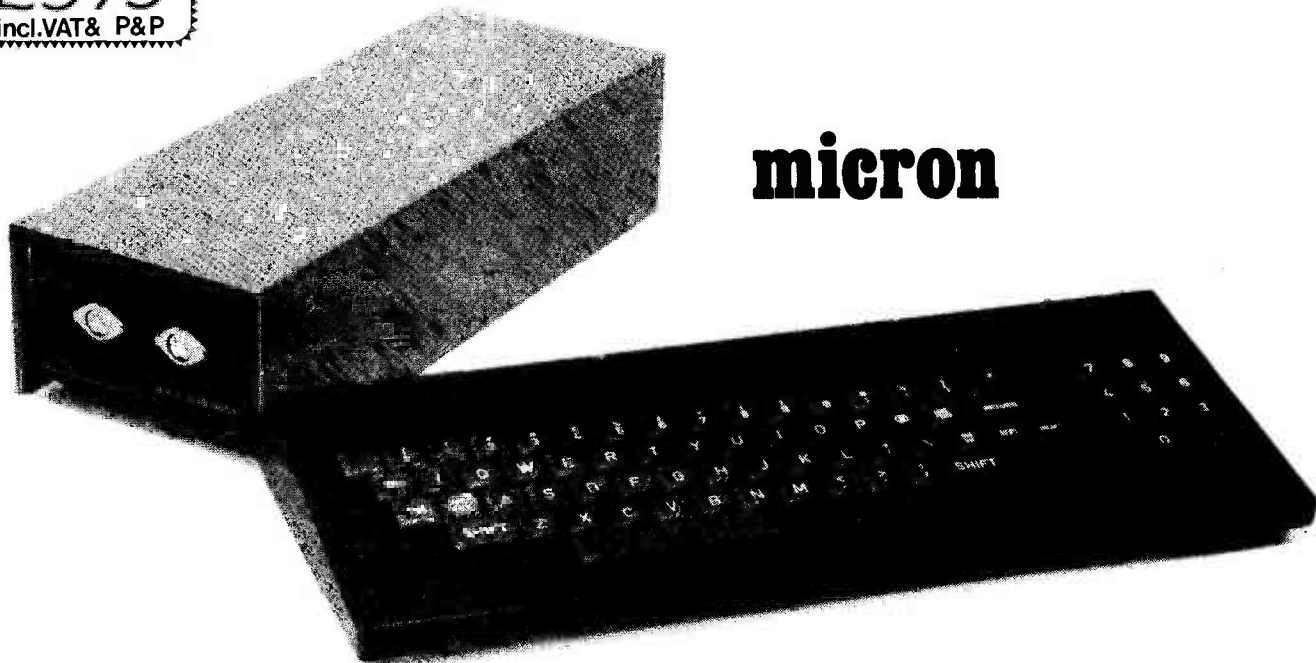

micron

'MICRON' may sound small - but we all know that it's much larger than an atom!

The un-beatable features of Microtan 65 and Tanex have been brought together to give you **Micron**, a ready built and tested computer of outstanding value. Fully supported by comprehensive documentation, **Micron** represents an ideal starting point in personal computing. We've taken a full O.E.M. licence for Microsoft Basic, which means that you'll have the support of the most popular Basic available, (as used on PET, APPLE, TANDY etc.). If you want to expand **Micron** there's no problem, just move into the system rack and choose from the range of Microtan modules. Read the information, study what the magazines have to say about us and compare what we have to offer with other systems, then we feel sure that you'll be convinced that we've produced an excellent product.

- FULLY BUILT, TESTED AND CASED.
- 6502 BASED MICROCOMPUTER.
- VDU ALPHA NUMERIC DISPLAY.
- 8K RAM.
- 32 PARALLEL I/O LINES.
- 2 TTL SERIAL I/O LINES.
- 1 SERIAL I/O PORT WITH RS232/20mA LOOP, AND 16 PROGRAMMABLE BAUD RATES.
- 300 / 2400 BAUD FILENAMED CASS. INTERFACE.
- DATA BUS BUFFERING.
- MEMORY MAPPING CONTROL.
- 71 KEY ASCII KEYBOARD, INCLUDING NUMERIC KEYPAD.
- POWER SUPPLY INCLUDED.


SOFTWARE

- 10K EXTENDED MICROSOFT BASIC.
- ALL THE USUAL BASIC COMMANDS.
- INTEGER AND REAL NUMBERS.
- INTEGER AND REAL ARRAYS.
- INTRINSIC FUNCTIONS: ABS, INT, RND, SGN, SIN, SQR, TAB, USR, ATN, COS, EXP, LOG, TAN.
- USER DEFINED FUNCTIONS.
- READ AND DATA STATEMENTS.
- DUMP AND LOAD PROGRAMS.
- PROGRAM EDITING COMMAND.
- STRING FUNCTION FOR TEXT I/O.
- BASIC CAN CALL MACHINE CODE SUBROUTINE.
- USER MACHINE CODE INTERRUPT HANDLER INTERFACES WITH BASIC.
- XBUG.
- DATA CASSETTE FILE HANDLING IN BASIC

TANGERINE
COMPUTER SYSTEMS LIMITED

Forehill Works
Forehill Ely Cambs England Tel:(0353)3633

microtan 65

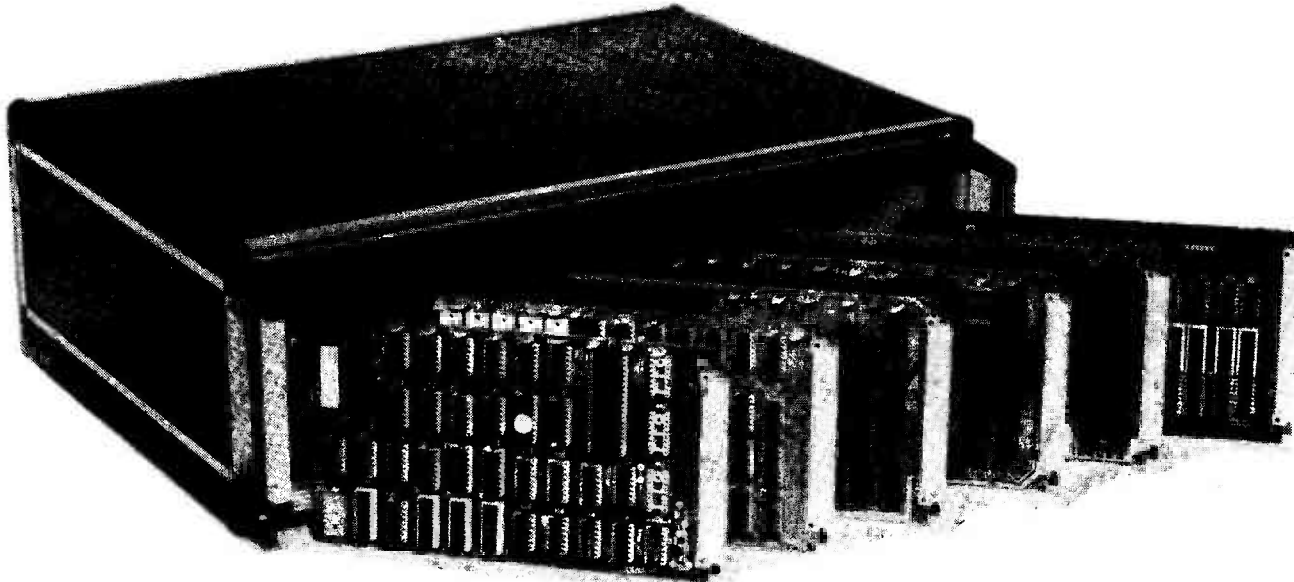

The **Microtan** system is rapidly becoming accepted as the ultimate approach to personal computing. Start with **Microtan 65**, a 6502 based single board computer, and expand to a powerful system in simple and in-expensive stages. The **Microtan** system is a concept and not an afterthought, this means expansion is easy and very efficient! Unlike many other systems, you'll find it difficult to outgrow **Microtan**, and you won't be wasting your money on a product that will only last you a few months! When you are ready to expand, **Tanex** is waiting. The features offered by **Tanex** are tremendous, and you can start into them for just £49.45! Cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, memory mapping and a further 1K of RAM are standard. From thereon expansion is simple, just plug in extra integrated circuits to get yourself 8K of RAM, a further 16 I/O lines and two more counter timers a serial I/O line with RS232/20mA loop and full modem control, XBUG - a firmware package containing cassette file handling routines, plus a line-by-line assembler (translator) and dis-assembler, PLUS 10K EXTENDED MICROSOFT BASIC, a suped-up version of the Basic as used by major manufacturers such as Apple, Tandy and Nascom, NO OTHER LOW COST MICROCOMPUTER OFFERS YOU THIS SUPERB PACKAGE. O.K. so you want more memory, try **Tanram** for size! Upto 40K bytes on one board starting for as little as £50.60. RAM freaks will be pleased to hear that our system mother board offers page memory logic which will support 277K Bytes, satisfied? To house these beautiful modules you can choose between our mini-rack (as used on **Micron**), which accepts **Microtan** and **Tanex**, or our system rack pictured above. The system rack will support 12 modules. What are these extra modules? Well for starters there's a couple of I/O modules, parallel and serial offering upto 128 I/O lines organised as 16 8 bit ports and 8 serial I/O ports respectively. Shortly we'll be introducing high definition (256x256) colour graphics, A to D and D to A modules, IEEE 488 Bus interface, a PROM programmer, disc controller and **TANDOS** - a 6502 CPM system. So there's plenty to keep you busy. Send for more details, and find out how you can get started for just £79.35!

ALL PRICES QUOTED INCLUDE V.A.T.

AIM 65, KIM 1, SIM 1 USERS- READ ON!

We have produced a T.V. interface module which simply connects to the expansion socket of your computer and produces a display of 16 rows by 40 characters! Of even more interest will be our Buffer module, which allows you to expand into our system rack, giving you access to the full range of **Microtan** modules.

Please underline the information required.

AIM T.V. INTERFACE. MICROTAN SYSTEM.

NAME: _____

ADDRESS: _____

PLEASE ENCLOSE 12p STAMP. THANK YOU. _____

REMOTE-CONTROLLED POWER SWITCH

Designed to interface with the five-channel remote control system, this 5 A mains switch can be activated directly or with the remote control transmitter. Design by Ray Marston. Development by Plamen Pazov.

This project is a 5 A mains switch that is specifically designed to interface with the five-channel remote control system described elsewhere in this issue of ETI. When the interface is complete, the switch can be activated either directly by a built-in toggle switch or with a pair of control buttons on the infra-red transmitter. The switch can be remote-controlled at ranges up to 10 m and can be used to activate lamps, TVs and hi-fi systems, etc, from the comfort of an armchair. Three such switches can be controlled by the remote control system.

The power switch is designed to fit into standard surface mounting mains sockets: a single switch can be fitted in a standard socket or two switches can be fitted in a double socket. A feature of the design is that the actual control input to the switch is made via an opto-coupler, which provides several kilovolts of mains isolation; an input current of only a few milliamps from a 9 V or greater supply is required to activate the switch in the remote mode. The switch is thus quite versatile and can, with a little ingenuity, be activated automatically by suitable sensor networks, such as those published in last month's ETI.


Construction

When building this project it must be noted that the PCB is designed to be used with a specific miniature type of relay (see Buylines) and that the board is fairly cramped, with all resistors and diodes mounted vertically on the PCB. The relay has two sets of contacts, which are wired in parallel; external connections to the relay are made using a vertically-mounted two-way terminal strip. All other connections are made using Veropins.

When constructing the unit, build up the PCB as shown, fitting the relay last of all, and fit the unit in one corner of the surface mounting box after first completing the interwiring to SW1, SK1 and SK2 (the mains output socket) in accordance with the circuit diagram.

Now fit the top plate/socket into place, complete the mains connections, connect SK1 to one of the latching outputs of the five-channel decoder and give the unit a functional test. Check that the switch can be turned on and off directly with SW1, and that it can be controlled remotely (using the five-channel transmitter) when SW1 is set to the remote position.

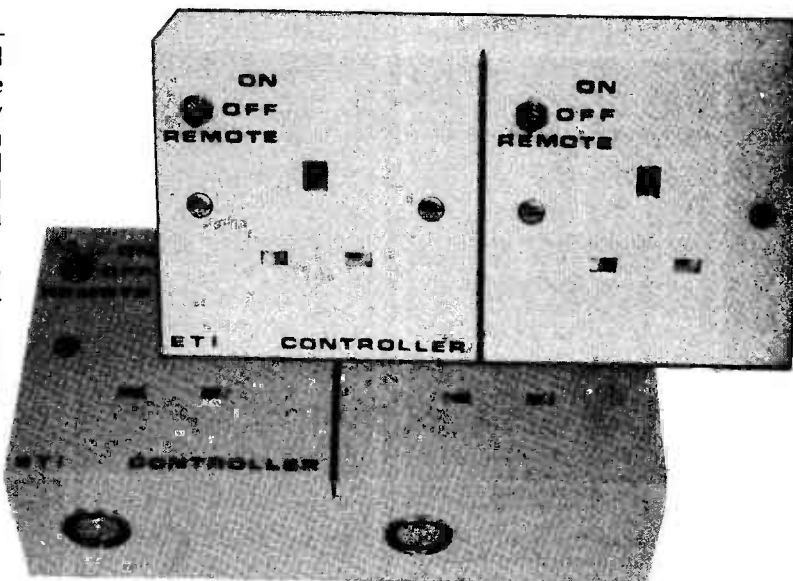Note that SW1 should be fitted to the actual socket plate of the power switch and that socket SK1 (a DIN socket) should be fitted to the lower face of the surface mounting box.



To make a dual power switch unit, simply fit two identical units into a double surface mounting box, but use two single sockets.

HOW IT WORKS

Circuit operation is so simple that it is virtually self-evident. Q1 is used as a relay driver and the relay contacts are used to make or break the live mains connections to output socket SK2. Q1 can be activated either directly by SW1 or remotely via opto-coupler IC1 and one of the latching outputs of the decoder of the five-channel remote control system. The decoder also provides the relay-driving circuit with a 15 V DC supply.

When SW1 is set to the on position, Q1 and the relay are driven on via R2, and parallel-connected contacts RLA/1 and RLA/2 feed mains power to the load through SK2. When SW1 is set to the off position, no drive is fed to Q1 base, so Q1 and the relay are off and no power is fed to the load.

When SW1 is set to the remote position, opto-coupler IC1 is used to control the base drive to Q1. Q1 and the relay turn on when the control input (B) is fed with a logic 1 or high signal, or off when fed with a logic 0 or low signal: these signals are available from the output of the five-channel decoder and can be set with the remote control transmitter.

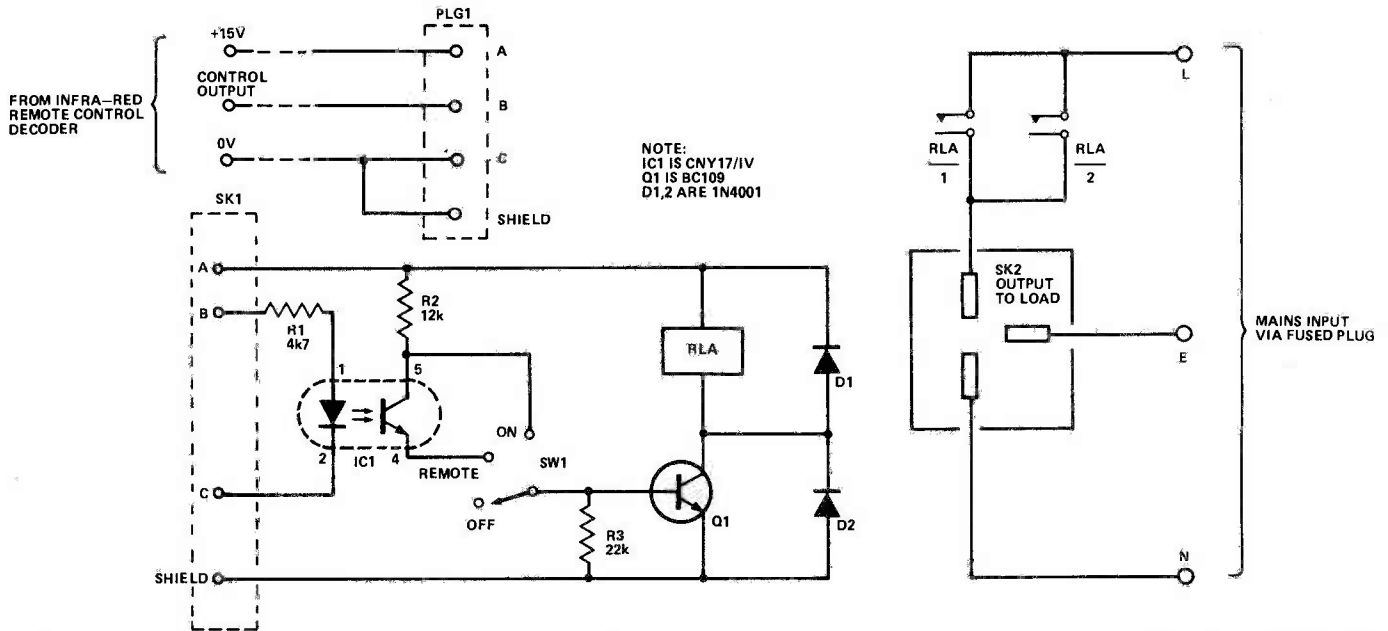


Fig.1 Circuit diagram.

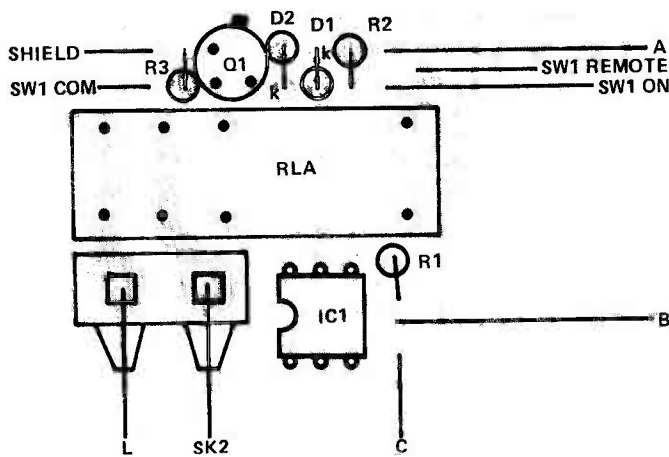


Fig.2 Component overlay. The terminal block is secured by tightening the lower pair of screws onto wires soldered to the PCB.

PARTS LIST

Resistors (all 1/4 W, 5%)

R1	4k7
R2	12k
R3	22k

Semiconductors

IC1	CNY17/IV
Q1	BC109
D1,2	1N4001

Miscellaneous

SW1	three-way toggle switch
SK1	three-pin DIN socket
SK2	surface-mounting mains socket
PLG1	three-pin DIN plug
RLA	12 V, coil > 120R, PCB-mounting, 5 A mains-rated contacts

BUYLINES

The relay is a miniature type for PCB-mounting and is available from Watford Electronics, ref. RL6. The CNY17/IV opto-coupler is available from Electrovalve.



Two internal views of the power switch, showing the interwiring. The mounting box is MK reference number 2025.



3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC **£32.70**



A high performance sound to light system which automatically switches to a chaser when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1.000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed

STEREO DISCO MIXER/PREAMP

LBPA3 **£33.70**

M - Magnetic
C - Ceramic



Magnetic or ceramic deck versions - please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/tones controls/mic mixer/tones/mic. auto fade over decks and P.F.L. The unit can be used with either LB100/150/250

Full set of pots — **£8.63**

3 CHANNEL SOUND/LIGHT

LB31000SL **£22.70**



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

LBPA2 **£17.20**

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots £2.74.

LBPA1 **£19.50**

A stereo hi-fi preamp and tone stage for mag. guitars, etc. Can be used with any LB amps. Set of pots £3.27.

2/4/8 CHANNEL CHASER

LB81000LC **£28.00**



An all logic chaser system for use with up to 8 channels at 1.000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

3-WAY ACTIVE CROSSOVER


LBAC01 **£17.90**



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01 (1 or 2).

4 CHANNEL SEQUENCER

LB41000LS **£19.20**



A 4 channel sequence generator for banks of lamps up to 1.000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

POWER AMPLIFIERS

Tough dealing power amps for use in sound systems. Open/circuit protection and fused. Heavy gauge heat sinks and rugged output devices fail operate down to 4 ohms!

25W R.M.S.	110W R.M.S.	160W R.M.S.	270W R.M.S.
20Hz to 60K 0.07% THD 960B S/N LB25	5Hz to 25K 0.1% THD 1100B S/N LB100	5Hz to 25K 0.1% THD 1100B S/N LB150	5Hz to 25K 0.1% THD 1100B S/N LB250

£11.20 £19.70 £29.20 £43.50

Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

1 AND 3 CHANNEL DIMMERS

LB31000LD **£16.20**



Single channel version LB11000LD **£7.20**

Power dimmer units for theatre/stage applications up to 1.000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders — LB31000LD (no pots) **£15.00** Sliders 75p each

POWER AMP POWER SUPPLIES

LB25PS	LB100PS	LB150PS	LB250PS
£11.20 P/P £1.20	£16.20 P/P £1.40	£19.00 P/P £1.40	£26.50 P/P £1.70

FOR GUITAR, P.A. AND DISCO

PIEZO HORNS **£5.75**

P/P 50p

ROPE LIGHTS/DRIVER

LB41000LC-S **£24.20**



4 COLOUR ROPES
(6 metre) **£36.50**
(8 metre) **£45.40**

ROPE LIGHTS **£45.40**

A four channel chaser up to 1.000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control

CELESTION LOUDSPEAKERS

(All standard cone 8 ohms)

G10-50	G12-65	G10-100	G15-100
(10 inch 50W)	(12 inch 65W)	(12 inch 100W)	(15 inch 100W)

£14.70 £20.70 £26.45 £36.45

P/P £1.70 P/P £1.70 P/P £1.70 P/P £2

NEW - MINI MODULES - NEW

Ingenuously designed mini pre-amplifier building blocks for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.

LBMM1 Pre-amp for mics, guitars etc.
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5
LBMM3 Bass boost/cut for either LBMM1/2/3/4/5
LBMM4 Mid boost/cut for either LBMM1/2/3/4/5
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5
LBPSU1 ± 15V regulated for up to 12 modules
LBPSU ± 15V regulated for up to 50 modules

MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £8.70; MMS £5.70; PSU1 £7.20; RPSU £14.50.

Mini Module Discount: Any types between 10 and 24 (quantity) — 20% 25+ — 30%.

L & B
ELECTRONIC MODULES
PROFESSIONAL ENGINEERING BY PROFESSIONALS
45 Wortley Road, West Croydon, Surrey
CR0 3EB. Tel. 01-689 4138

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.

All prices shown are V.A.T. inclusive. Please include 50p post/packing except where individually stated. To mail order, send cheque/P.O./registered cash or Access number. C.O.D. service £1 extra. For our catalogue/specifications send 50p.

Please note: This company has no connection with LB Electronics of Hillingdon.

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safeloc

Minimum & Sub Miniature				50 VOLT (Pri: 220-240V) Sec 0.19-25.33-40-50V				
Volts	Milli-amps	Ref. No.	Price £	P&P	Amps	Ref. No.	Price £	P&P
3-0.3	200	238	2.60	.70	0.5	102	3.60	.90
0.6, 0.6	1A 1A	212	3.00	.75	1.0	103	4.60	1.05
9-0.9	100	13	2.30	.70	2.0	104	7.30	1.20
0.9, 0.9	330 330	235	2.15	.70	3.0	105	8.60	1.20
0.8-9, 0.8-9	500 500	207	2.75	.75	4.0	106	10.85	1.30
0.8-9, 0.8-9	1A 1A	208	3.85	.75	6.0	107	15.10	1.50
0.15, 0.15	200 200	236	2.15	.70	8.0	118	20.20	1.70
0.20, 0.20	300 300	214	2.75	.90	10.0	119	24.10	2.20
20-12-0 12-20	700(DC)	221	3.50	.90	60 VOLT (Pri: 220-240V) Sec 0.24-30.40-48-60			
0.15-20, 0.15-20	1A 1A	206	4.60	1.05	Amps	Ref. No.	Price £	P&P
0.15-27, 0.15-27	500 500	203	4.05	.85	0.5	124	3.85	.90
0.15-27, 0.15-27	1A 1A	204	6.10	1.05	1.0	126	5.60	1.05

12 AND/OR 24 VOLT

Pri: 220-240 Volts

12v	Amps	Ref. No.	Price £	P&P
0.5	0.25	111	2.30	.75
1.0	0.5	213	2.75	.90
2	1	71	3.25	.90
4	2	70	4.05	.85
6	3	70	5.60	.95
8	4	108	7.40	1.20
10	5	72	8.25	1.20
12	6	116	8.85	1.20
16	8	17	10.85	1.30
20	10	115	13.85	1.50
30	15	187	16.85	1.50
60	30	226	33.35	1.80

30 VOLT (Pri: 220-240V)

Sec 0.12-15-20-24-30V

Amps	Ref. No.	Price £	P&P
0.5	112	2.85	.90
1.0	79	3.60	.90
2.0	3	5.60	1.05
3.0	20	6.30	1.20
4.0	21	6.60	1.20
5.0	51	9.60	1.20
6.0	117	11.10	1.20
8.0	88	14.35	1.50
10.0	89	16.60	1.50

AUTO TRANSFORMERS

Input/Output Tapped 0-115-210-240V

VA (Watts)	Ref. No.	Price £	P&P
20	113	2.65	.90
75	64	4.10	.90
150	4	5.60	1.05

Input/Output Tapped

0-115-210-220-240V

VA (Watts)	Ref. No.	Price £	P&P
300	53	10.10	1.20
500	67	10.85	1.50
1000	84	18.60	1.60

Also 1500/2000/3000VA

MAINS ISOLATING (Centre Tapped & Screened)

Pri: 120/240V Sec: 120/240V

VA (Watts)	Ref. No.	Price £	P&P
60	149	6.60	1.05
100	150	7.60	1.30
200	151	11.10	1.30
250	152	13.30	1.50
350	153	16.30	1.60
1000	156	37.10	3.20

Please add VAT at 15%
Barclaycard and Access facilities available
Trade and Education Welcome

BAYDIS 7a William Street
Herne Bay, Kent
Herne Bay GA586

BUILD YOUR OWN METAL DETECTOR

VLF/TR VCO/TR IB/TR BFO ...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately; write or phone for price. Export welcome; write for quote.



Shadow VLF/TR

Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nail bottle caps even aluminum foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.

The head is thermally and capacitively shielded.
4 modes: deepseeking VLF plus 3 TR discriminating ranges.
Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI.
Complete kit now only £87.87 inc. VAT & post!

Shadow TR/1B

Individual parts: Search head **£21.33** PCB-£6.80 Case £5.33 Adjustable shaft assy. **£5.10** LM393-£1.12. Manual (gives more info than ETI article — and extra function) **£1.12**. All inc. VAT & post! (Other parts also available separately)

Shadow TR/1B (illustrated)

A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. **Complete kit £33.60 inc. VAT and Post.**

Shadow TR/VCO

An advanced version of the TR/1B. Use as a sensitive 1B machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. **Kit price £38.87 inc. VAT and Post.**

Matching stereo headphones for all Shadow models £6.85 inc. VAT and Post.

Shel Kit

Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions **£14.45 inc. VAT and Post.**

ALTEK

(ETI), 1 Green Lane
Walton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please.
Phone (093 22) 44110 anytime!

HIGH POWER MODULE KITS

125 WATT MODEL **£10.50** plus £1.15 p&p (Illustrated)

200 WATT MODEL **£14.95** plus £1.15 p&p


SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response measured at 100 watts 25Hz-20KHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1%
 Dimensions 205 x 90 and 190 x 36 mm
 The P.E. power amp kit is a module for high power applications—disc units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the

aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES

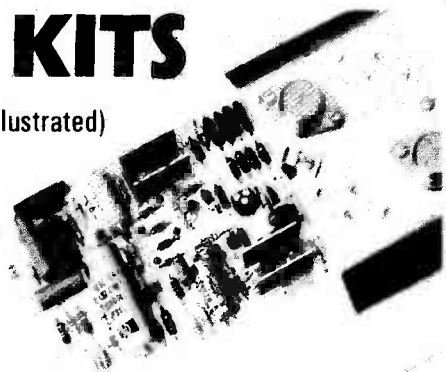Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p
 Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p
 Suitable Mains Power Supply Unit for 125W model **£7.50** plus £3.15 p&p
 Suitable Twin Transformer Power Supply for 200W model **£13.95** plus £4.00 p&p



MULLARD LP1183 STEREO PREAMP

FREE! Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.

PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)



2 WAVE BAND MW LW
 * Easy to build * 5 push button tuning
 * Modern styling design * All new unused components
 * 6 watt output * Ready etched & punched P.C.B.
 * Incorporates suppression circuits * Now with tape input socket


All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia.
 The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

£10.50

Complete with instructions.

CONSTRUCTORS PACK 7A

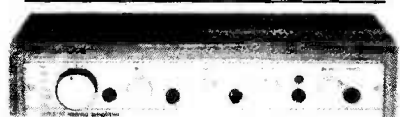Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete **£1.95** per pack, p&p £1.15



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED


Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx

READY TO PLAY **£32.90** plus £3.80 p&p

HI FI STEREO AMPLIFIER MODULES



- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. £1.95 plus 70p p&p
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. £4.95 plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit £3.95 plus £1.15 p&p
- Matching power supply kit with transformer. £3.00 plus £1.96 p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. £1.70 plus 80p p&p
- Complete with application notes.

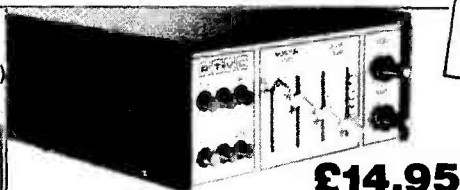

£14.95 plus £2.90 p&p

10+10 WATT STEREO AMPLIFIER KIT


- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier module.
- Attractive black vinyl finish cabinet. Size 9" x 8 1/2" x 3 1/2" approx
- Converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit.

SPECIFICATIONS

Suitable for 4 to 8 ohms speakers
 Frequency response 40Hz — 20KHz
 P.U. 150mV Aux. 200mV Mic. 1.5mV
 Input Sensitivity Bass ± 12db @ 60Hz
 Treble ± 12db @ 10KHz
 Tone controls -1% typically @ 4 watts
 Distortion 220-250 volts 50Hz
 Mains supply

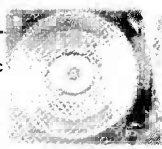BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus £3.15 p&p when purchased with amplifier. Available separately **£10.50** plus £3.16 p&p.



8" SPEAKER KIT 2 8" approx. twin cone domestic use speakers. £4.75 per stereo pair plus £1.70 p&p when purchased with amplifier. Available separately **£6.75** plus £1.70 p&p.


STEREO MAGNETIC PRE-AMP CONVERSION KIT

All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p



323 EDGWARE ROAD, LONDON W2
 21E HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
 All items subject to availability. Price correct at 6/3/81 and subject to change without notice.
 For further information send for instructions 20p plus stamped addressed envelope.
 NOTE: Goods despatched to mainland and N. Ireland only.
 Persons under 16 years not served without parent's authorisation.
 RTVC LTD. reserve the right to alter, update or improve their products without notice.

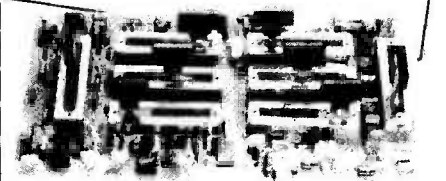

STEREO DISCO PREAMPLIFIER

matching above modules, suitable for twin deck mixing with P.F.L. output and Mic/Tape input. Ready built, ready to play with circuit diagram and application notes to suit our power module kits. **£21.95** plus £1.72 p&p

100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls. Size approx 14" x 4" x 10 1/4". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **£76.00** plus £4.60 p&p




50 WATT MONO DISCO AMPLIFIER

Size approx 13 1/2" x 5 1/2" x 6 1/2". 50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches independent bass and treble controls and master volume. **£30.60** plus £3.68 p&p



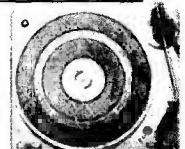BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use. **£12.25** OUR PRICE plus £3.16 p&p Size approx 13" x 11"



PHILLIPS RECORD PLAYER DECK GC037

Size approx 15 1/2" x 12 1/2"
 Hi Fi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimize acoustic feedback. Complete with GP401 stereo magnetic cartridge—LIMITED STOCK. UNBEATABLE OFFER AT **£27.50** complete plus £3.16 p&p



TECH TIPS

555 VCO

J. Harrold, Bristol.

This circuit uses the 555 timer and a few external components to produce a simple low cost VCO, (not just pulse position modulation), and unlike other "cheap" VCOs does not require a MOSFET op-amp costing £1 or more to buffer the output up to a useful level.


The 555 is basically connected in its astable mode, but instead of wiring the top of the timing chain R1, R2, C1 to V_{CC} it is connected to the input voltage V_{IN}. The mark/space ratio is set by R1, R2 in the usual way for the 555 and if R2 ≫ R1, it is unity. It should be remembered that pin 7 is grounded during part of the oscillation so R1 affects the current drawn from the input. The output (pin 3) of 555 can source or sink currents of up to 200 mA and so can drive TTL, CMOS or a high impedance loudspeaker directly. The frequency of oscillation f, in Hertz, is

$$f \sim \frac{1}{C1(R1 + 2R2) \ln \left[\frac{V_{IN} - V_{CC}/3}{V_{IN} - 2V_{CC}/3} \right]}$$

From this it can be seen that oscillation begins as V_{IN} rises above two-thirds V_{CC}, so for maximum frequency sweep V_{CC} should be as low as possible, ie 5 V. If R2 ≫ R1 so that R1 + 2R2 ~ 2R2 then the frequency range depends on the time constant C1.R2 and with the component values shown the output varies fairly linearly from 2 kHz to 15 kHz as V_{IN} varies from 4 V to 12 V.

If the conditions R2 ≫ R1, V_{CC} = 5 V and V_{IN} > 4 V are satisfied, then
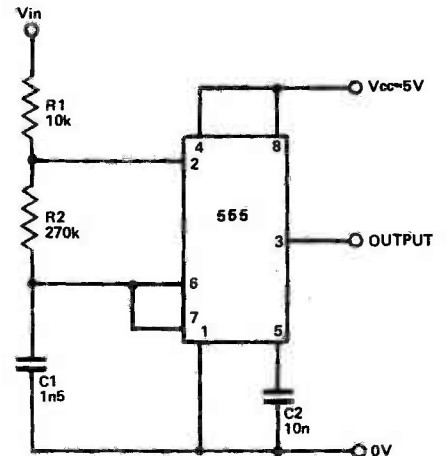
$$f \sim \frac{1}{C1R2} (V_{IN} \times 0.6 - 1.6)$$



If linearity is unimportant, the lower frequency limit can be substantially reduced (f = 0 when V_{IN} < 3/4 V_{CC}).

Capacitor C1 must be a low leakage type. The VCO output can also be modulated by applying a suitable signal to the control voltage (pin 5) of the 555.

Computer-controlled Synthesizer Keyboard

P. McChesney, Wirral.

The technique described here produces an accurate analogue voltage from a synthesizer keyboard by processing digital data and converting it to an analogue voltage, replacing the well-known method that uses resistor ladders. It is primarily aimed at people who already possess a microcomputer and who are building a synthesizer, either of their own design, or using published circuits such as those which have appeared in ETI. Although the technique described might at first sight appear both more elaborate and expensive than the resistor ladder method, it possesses three major advantages — firstly, the number of discrete components is small and although they need not be of high precision, only minimal setting-up is required

to give high stability performance: secondly, software can be written to obtain a sequencer and also to produce special effects: thirdly, no substantial changes are required to make it polyphonic.

Figure 1 shows a diagram of the monophonic design. The keyboard uses a diode matrix such that when one key is pressed, a binary code is produced on the six-bit data bus. This code is linear (for example, if the fourteenth key is pressed, then binary 14 is produced) and of negative logic. It is therefore inverted either by using inverters as shown, or by writing software to perform the same task. The code then goes to the microcomputer (which, in the case of the author, is 6800-based but could have been any microcomputer) which continually checks the data received. If the code is zero, then the computer goes back and checks the code again and continues to do this until a code other than zero is received. Once this happens, the

computer searches a look-up table and outputs a corresponding eight-bit code which is passed to a D-to-A converter. The data in the look-up table follows a log-law and so the analogue output of the DAC likewise follows the log-law. This means that the VCO is linear, thereby making it both simpler and more accurate.

The strobe is optional and serves to prevent stray codes being generated if two keys are pressed simultaneously. Figure 2 shows the arrangement of resistors (tolerance not important) in the strobe. Each switch shown is the spare pole on the keyboard contact. Point X is at V_{CC} when no key is pressed, at 0.5 V_{CC} when one key is pressed and at 0.33 V_{CC} when two keys are pressed, etc. A window discriminator is used to distinguish the case when only one key is pressed (monophonic operation). The output of the discriminator is adjusted to match the TTL levels required by the microcomputer input and the program is

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

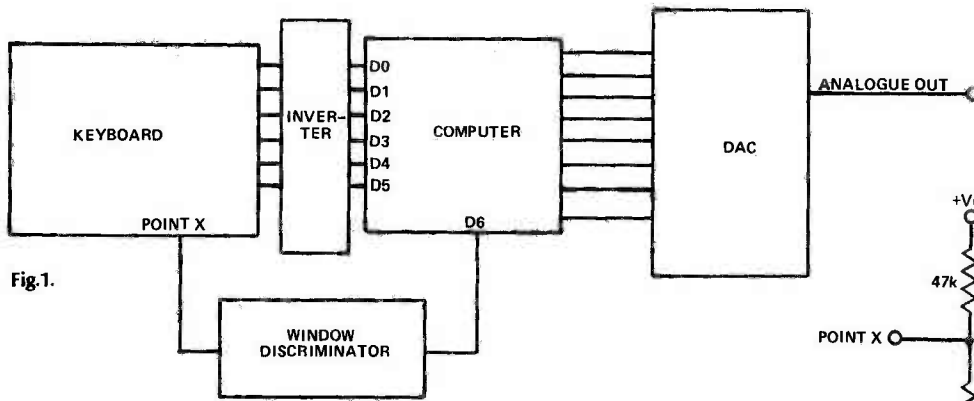


Fig. 1.

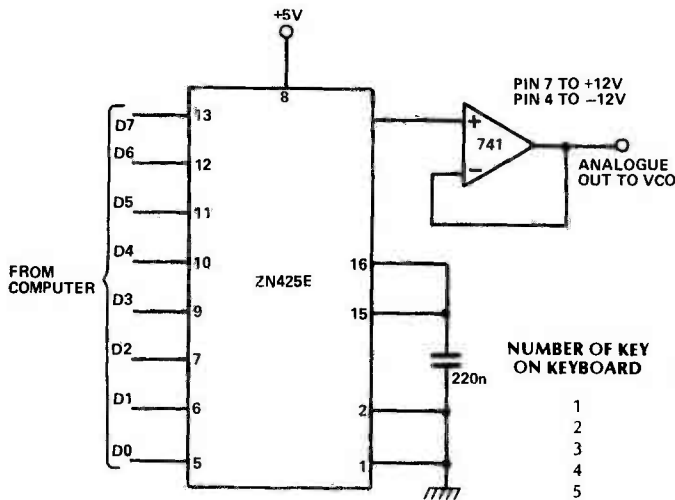


Fig. 2.

TABLE 1

NUMBER OF KEY ON KEYBOARD	SIX-BIT KEY CODE	EIGHT-BIT OUTPUT CODE
1	000001	00010001
2	000010	00010010
3	000011	00010011
4	000100	00010100
5	000101	00010101
6	000110	00010110
7	000111	00011000
8	001000	00011001
9	001001	00011011
10	001010	00011101
11	001011	00011110
12	001100	00100000
13	001101	00100010
14	001110	00100100
15	001111	00100110
16	010000	00101000
17	010001	00101011
18	010010	00101101
19	010011	00110000
20	010100	00110011
21	010101	00110110
22	010110	00111001
23	010111	00111100
24	011000	01000000
25	011001	01000100
26	011010	01001000
27	011011	01001100
28	011100	01010001
29	011101	01010101
30	011110	01011011
31	011111	01100000
32	100000	01100110
33	100001	01101100
34	100010	01110010
35	100011	01111001
36	100100	10000000
37	100101	10001000
38	100110	10010000
39	100111	10011000
40	101000	10100001
41	101001	10101011
42	101010	10110101
43	101011	11000000
44	101100	11001011
45	101101	11010111
46	101110	11100100
47	101111	11110010

TABLE 2

NUMBER OF KEY ON KEYBOARD	SIX-BIT KEY CODE	12-BIT OUTPUT CODE
1	000001	000100001111
2	000010	000100011111
3	000011	000100100001
4	000100	000101000011
5	000101	000101010110
6	000110	000101101010
7	000111	000110000000
8	001000	000110010110
9	001001	000110101111
10	001010	000111001000
11	001011	000111100011
12	001100	001000000000
13	001101	001000011110
14	001110	001000111111
15	001111	001001100001
16	010000	001010000101
17	010001	001010101011
18	010010	001011010100
19	010011	001011111111
20	010100	001100101101
21	010101	001101011101
22	010110	001110010000
23	010111	001111000111
24	011000	010000000000
25	011001	010000111101
26	011010	010001111101
27	011011	010010000101
28	011100	010100001010
29	011101	010101010111
30	011110	010110101000
31	011111	010111111110
32	100000	011001011001
33	100001	011010111010
34	100010	011100100001
35	100011	011110001101
36	100100	100000000000
37	100101	100001111010
38	100110	100011111011
39	100111	100110000011
40	101000	101000010100
41	101001	101010101110
42	101010	101101010000
43	101011	101111111101
44	101100	110010110011
45	101101	110101110100
46	101110	111001000001
47	101111	111100011010

written such that the code from the keyboard is ignored when the discriminator shows that more than one key has been pressed.

The look-up table of the micro-computer already referred to is given in Table 1. The first column gives the number of the key on the four-octave keyboard, the second column shows the binary number (positive logic) produced by the keys, whilst the third column shows the corresponding output number. Depending on the aural sensitivity of the listener, it is possible that at the bottom of the scale, one or two notes might sound slightly off-key due to inaccuracies of about 1.7%. To be undetectable, the note error should ideally be $\pm 0.5\%$ but this is only obtainable using the 12-bit code given in Table 2. Unfortunately, outputting a 12-bit code would require the use of latches on the micro-computer output (which is normally eight bits wide), and also a 12-bit D-to-A converter which could be obtained by using two eight-bit DACs, scaling the output of one by 256 to give the correct weighting and then adding the two outputs together. However, for most applications the eight-bit code given in Table 1 is quite sufficient and has the advantage of requiring only one DAC.

Active Audio Filter


E. Vaughan, High Wycombe

The main drawback of passive IF filters is their insertion loss when using inductors, necessitating the use of a two or three stage high-gain preamp to compensate for this loss. With an active audio filter the insertion loss can be low, non-existent or even provide gain. In this FET filter there is virtually no insertion loss. When this filter is incorporated in a receiver and switched in, there is an apparent improvement in the signal-to-noise ratio and readability of signals. High and low frequency heterodynes and audio chatter outside the filter pass-band are quite noticeably attenuated, making listening much more pleasant.


Waterproofing Problems

J.E. Fox, Birmingham.

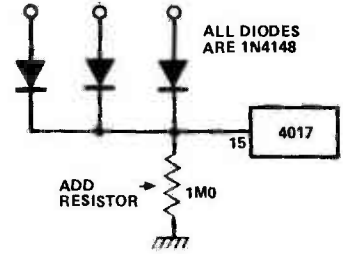Here is a problem I encountered recently which may be of some interest to your readers. I was using 1N4148 diodes as a three-input OR gate to reset a 4017 decade counter. On trying to waterproof the circuit, it failed to count. This was eventually tracked down to a build-up of charge on the reset pin (pin 15). Insertion of a 1MΩ resistor to ground completely solved the problem. Obviously the



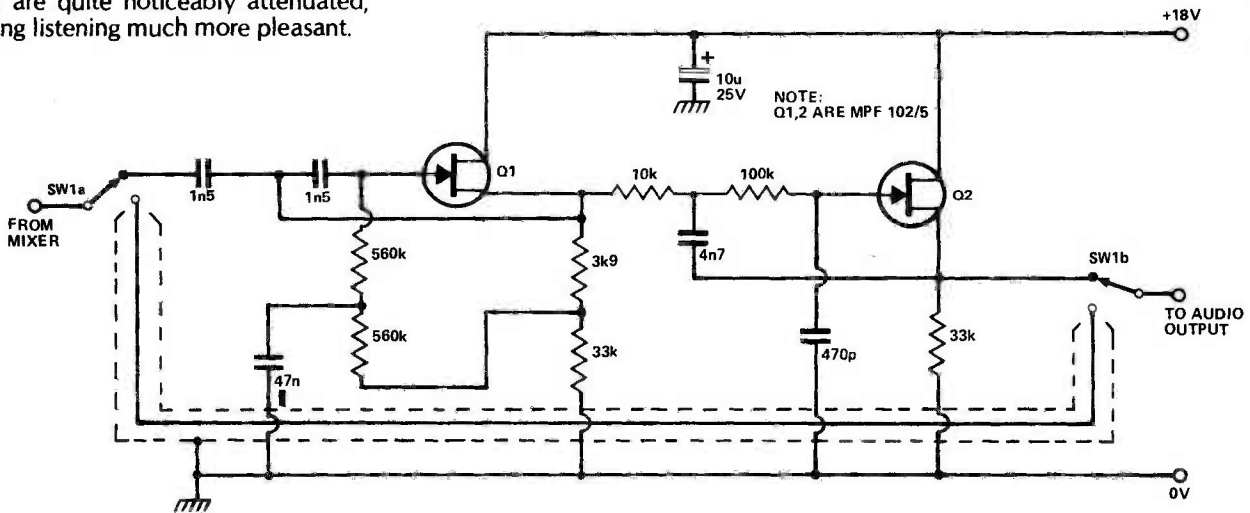waterproofing eliminated any leakage from the reset pin which would occur on a normal PCB.



Power Supply Metering

R.A. Fairs, Twickenham.

When constructing power supplies it is often desirable to include a voltmeter and ammeter in the actual unit. For cost purposes one meter may be made to read the two functions independently using a suitable switch. The first circuit depicts a simple way of achieving this using a single pole switch.

The paralleling resistor (R_p) (which gives the original meter a greater current capability) is left in the circuit unswitched; since it has a very low value, there will be very little voltage dropped across it. For example, a 6 R meter having 10 mA FSD will have $R_p = 0.06 R$ when converted to read 1 A.

$$R_p = R_m / I$$

where I = original current reading of meter for FSD

I = required current reading of meter for FSD



R_m = Resistance of meter

The series resistor to convert the meter to a voltmeter is switched, its value is given by:

$$R_s = \frac{V_{IN} - I R_m}{I}$$

To find the resistance of the meter (R_m) set up the second circuit, and proceed as follows:

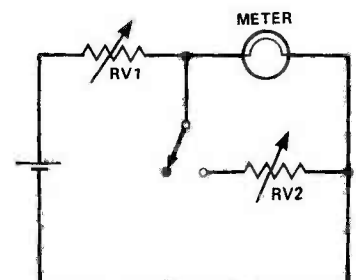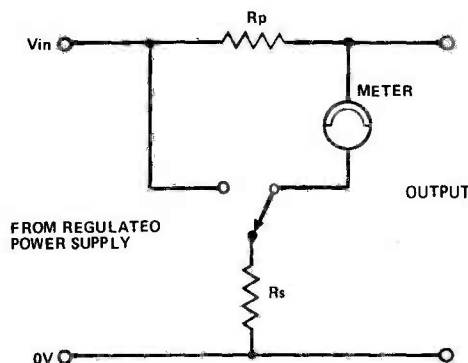- 1) Adjust RV1 for meter FSD.
- 2) Parallel RV2 with the meter via a switch, adjust RV2 so that the meter now reads 1/2 FSD.
- 3) Measure RV2: this is the resistance of the meter.



NOTE: RV1 IS HIGH VALUE RHEOSTAT
RV2 IS LOW VALUE RHEOSTAT

THESE SPACE INVADERS WILL ALARM YOU — the price won't!

**The space invaders are back.
This time right on your wrist!**

CA-90 specification

Time: Hours, minutes, seconds, am/pm, day and date. One-touch changeover between 12/24-hour formats.

Calendar: Automatic; day, date, month and year, preprogrammed until the year 2002.

Calculator: 8 digits (7 digits for negatives). Four basic calculations, with constants for +, -, x, ÷.

Alarm: 24-hour reminder alarm, with "alarm on" symbol.

Hourly time signal: Every hour, on the hour. The signal, with display symbol, can be switched on or off.

Stopwatch: Professional 1/100 second stopwatch measuring net, lap and first and second place times.

Dual time: An alternative time (second time zone) can be memorised. Hours and minutes; 12 or 24 hour format.

Tone control: Pitch can be varied in 10 steps.

Game: Additive digital invader speed game.

Dimensions: 46.0 x 36.0 x 10.55mm (thickness). Resin case/strap. Mineral glass.

The Game

The keyboard is effectively divided in half. Any or all of the left-hand buttons (1, 2, 4, 5, 7, 8) become AIM and any or all of the right-hand buttons become FIRE.

The random digital invaders attack from the bottom right and move across the display. Every time you tap AIM your missile number, displayed top right, progresses by 1. When your missile number coincides with an invader, tap FIRE and that spaceship will disappear, adding to your score. Since this is a speed game, the earlier you destroy an invader, the higher it will score. The game is over if 3 of the 16 spaceships in an encounter penetrate your defences.

There are 2 stages, each stage having 9 encounters. In stage 1 the game speeds up with each encounter and in stage 2 the invaders attack from a closer position. After stage 2 the game reverts back to the beginning of stage 1, but the score, which is added and displayed after each encounter, is carried forward.

Depending very much on your skill, one game can last for as much as an hour or more. The highest score so far will be retained in a non-volatile memory (this will be erased if the stopwatch function is utilised).

CASIO'S MOST AMAZING WATCH EVER

CA-90

All this for

ONLY £24.95

(RRP £27.95)

- Watch
- Calculator
- Alarm
- Hourly chimes
- Stopwatch
- Dual time
- Digital space invader game



Game display

A CLASSIC IN ITS TIME

You don't have to be a highbrow to appreciate the beauty of this clock. Battery powered, it is ideal for office, lounge, kitchen, bedroom, caravan or boat. Compact and lightweight, it can be used as a travel alarm clock or car clock.

MA-1 Alarm Clock



**ONLY
£9.95**

(RRP £11.95)

Large blue LCD display of full digital time. Symphonic alarm or buzzer, with snooze facility, hourly time signal. Integral loudspeaker and amplifier with 3 position volume control. A large top button gives night-time illumination and switches the alarm off. Alarm function: "Symphonie Nr. 40 G Moll" (W. A. Mozart K.550) for about 30 seconds or buzzer for 60 seconds. Three AA size batteries last approx. 15 months. Quartz accuracy. Dimensions: 43mm x 115mm x 76mm (1 3/4 x 4 1/2 x 3 inches).

ILLUSTRATED CATALOGUE

Send 20p (postage) for details of CASIOTONE keyboards, CASIO watches and calculators and selected SEIKO watches. PRICE includes VAT, P&P. Send your cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:

CASIO'S BEST SELLING WATCHES



AA81

M1200

W150B

LCD ANALOGUE/DIGITAL ALARM CHRONOGRAPH with countdown alarm. AA-81 chrome, s/s bracelet £29.95. AA-81G. Gold plated £49.95. AA-82. All s/s £39.95. 12 MELODY ALARM CHRONOGRAPHS with countdown alarm. M-12 resin case/strap £24.95. M1200 all stainless steel £29.95. 100 METRE WATER RESISTANT Alarm chronographs with countdown alarm. W100. Resin case/strap £19.95. W150C Stainless steel case/resin strap £25.95. W150B Stainless steel case/bracelet £32.50.

* PRICES

We will beat any lower advertised price by 5% providing we still make a profit! Just send details and your remittance for the lower amount. Prices include VAT and P&P.

To: TEMPUS (Dept. ETI), 164-167 East Road
Cambridge CB1 1DB

Please send me

Remittance enclosed £

Access or Barclaycard No.

Name

Address

Post Code

TEMPUS

Dept. ETI, FREEPOST
164-167 East Road
Cambridge CB1 1DB
Tel. 0223 312866

Happy Memories

4116 200ns	£1.95	2114 200ns	£2.95
2114 450ns	£2.20	2716 5 volt	£4.95
2708 450ns	£3.95		

MEMOREX SOFT-SECTORED MINI-DISCS for PET, TRS-80, etc. Supplied in **Free Library Case** £19.95 per 10

Low Profile I.C. Sockets by Texas
Pins 8 14 16 18 20 22 24 28 40
Pence 10 11 12 16 17 20 21 28 37

Memory Upgrade Kits for Apple, 2020, TRS-80, etc. **from £18** please phone

Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened.

ALL PRICES INCLUDE V.A.T. POSTAGE FREE ON ORDERS OVER £15, OTHERWISE ADD 30p

Access and Barclaycard Welcome

HAPPY MEMORIES
Dept. ETI
Gladestry, Kington
Herefordshire HR5 3NY
Telephone (054422) 618

LATEST ADDITION TO OUR RANGE OF AUDIO SIGNAL GENERATORS

MODEL AO 150
Very low distortion unit with frequency meter.

£53 (+ UK VAT). P&P £2.50

Earlier models still available (from £23). Send SAE for full lists plus Function Generator, Millivoltmeter, Distortion Analyser, R.F. Signal Generator, etc.

TELERADIO

325 FORE STREET, LONDON N9 0PE
01-807 3719 Closed Thursdays



THE ATOM MAGIC BOOK

£5.50

A wealth of games and other programs plus much useful software and hardware information. Programs include a noisy and fast moving version of Breakout, and one which can store speech.

THE ZX80 MAGIC BOOK

£4.75

Games programs (including Othello, Hexpaw and Moon Lander), and sections on How It Works, Using USB, Converting Programs Written In Other BASICs, and hardware notes including circuits for static and dynamic RAM and I/O extensions.

MAKING THE MOST OF YOUR ZX80

£5.95

Tim Hartnell's superb book on writing programs for the ZX80. With many examples.

1K ZX80 MOVING DISPLAY GAMES PROGRAMS!!!

No flicker, no fuss. S.a.e. for details of cassettes available.

ASCII CODED KEYBOARD

£35 inc. P&P and VAT

Brand new, assembled and tested. 60 keys in stepped rows. Auto repeat function. S.a.e. for data.

TIMEDATA LTD.

57 Swallowdale, Basildon, Essex

TTL CMOS 74LS LEADS LB ELECTRONICS LINEAR RAMS EPROMS SURPLUS TELEPHONE UXBIDGE 55399

SUPERSALE '81
All full spec. 2114 (450ns) £1.85, 8 of £1.65 each. P&P 35p. 2708 £2 p&p 35p. TEXAS INSTRUMENTS 2716 single rail, full spec. £5.
NEW FREEDOM PHONE
The completely portable telephone with intercom and bleep paging facility. Range 200 yards £125 + VAT p&p £3. Leaflet available on request (not PO/HO certified).
MK 1002P (dual 128 bit Shift Reg) 35p.
UA710DC 14 dil 22p, 6 for £1, p&p 30p. (All Full Spec)
2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 35p.
MM5240 AA/J Character Generator £3.50 + data. p/p 35p.
LEAR SIEGLER dot matrix print-head. 7 needle. £19.50 p/p 50p.
ZETTLER low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.5 amps a.c. contacts. 85p p/p 35p.
D TYPE CONNECTORS
9 Way: sockets (solder) 55p.
15 Way: wirewrap plugs only 75p.
50 Way: skt (wirewrap) £1.85.
50 Way: skt £1.45, p&p 25p.
25 Way Male to Female with covers plus minimum 1 metre of cable (12 way) £4 each p/p 35p.
25 Way plug (soldercaill), 25 Way socket £1.50 each.
COVERS
37 Way: 90p (plastic), p&p 35p.
9 Way (metal) 60p, 15 Way (metal) 95p, 25 Way (plastic) 85p, 37 Way reduced from 90p to 80p. 50 Way (plastic) 90p.
DISPLAYS
HP 5082/7414 4 digit DIL display full spec £1.50 each, p&p 35p. Large quantities P.O.A.
LED 3 Digit DIL 55p, p&p 35p.
HP5082/7650 4" cc, left and right decimal point, high brightness (unmarked), only 50p, 12 for £5, p&p 35p.

SUPERSAVER 1
Ribbon Cable Headers 16 DIL Jermyn, gold-plated, with cover 45p, p&p 25p.
Ansley Header plugs. PCB mounting. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing type) p/p 35p.
Ansley I/O Header plugs. 1in 26 Way 65p, 26 Way (right-angled) 85p. 40 Way £1 p/p 35p.
SUPERSAVER 2
Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.
SUPERSAVER 3
PRICE SMASH FND500 .5in. LED displays, full spec 50p each, p&p 35p, large quantities P.O.A.
SUPERSAVER 5
Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.
SUPERSAVER 6
EAO KEY SWITCH oblong fascia, 25mm x 18mm (approx. 18mm hole), fixing supplied, brand new with 2 keys. £2.95 p&p 35p.
SUPERSAVER 7
SN74116 Dual 4 Bit latch 75p, p&p 35p.
SN74118 Arithmetic Logic Unit, 80p, p&p 35p.
SN74194 4 Bit Reg 50p p&p 35p.
SN74198 8 Bit Shift Register, 75p p&p 35p.
SUPERSAVER 8
ITT 4cx 2505 brand new full spec £7.50 each p&p 35p.
SUPERSAVER 9
5 digit 7 segment DIL LED .11" displays 5 for £1.50 p/p 35p.
SUPERSAVER 10
9-way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, 35p, p&p 35p.
SUPERSAVER 11
74LS266 50p. 74LS245 £2.40. 74LS240 £1. 74S260 35p. P&P on all above 35p.

SUPERSAVER 12
TMS 3128NC Static shift register, £1.50, p&p 35p.
SUPERSAVER 14
Recording Designs Ltd digital cassette deck. 50-100 Baud RS232 240V input. A professional superb deck. £48, p&p £2.
SUPERSAVER 15
5K 3/4" multitrack trim pots, PCB mounting, per box of 14 £2.50, p&p 35p.
SUPERSAVER 16
OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1, p&p 35p.
Just arrived. ICL Termini-printer terminal with keyboard. Switchable rates. 4 only. £125 + VAT.
LEDS (Full spec.)
TIL209, red 10p. 0.2in, red 12p. 0.2in, green 28p. 0.2in, yellow 28p. RL54 red Axial lead. 15p. P&P on all above 35p.
VERNITRON Ceramic filters type FM4 10 yMHz 45p, p&p 35p.
TRANSISTORS, BD236 40p, BC183L 10p, BF195 10p, TBA 810S, with data, 85p, 4-way DIL switches, 75p, MC1303 Dual Stereo preamp with data, £1.25, 7in. Nylon cable ties 100 for £1.50. All p&p 35p.
TMS 4030, 4096 x 1 dynamic RAM 200 ns removed from PCBs. £1 each. 16 for £15, p&p 35p.
GPO LINE MATCHING TRANSFORMER. With 12V reed relay etc. removed from equipment. £1 + 40p p&p.
CAPACITOR SCOOP. 1.600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 + 35p p&p.
DON'T KILL YOUR EPROMS. Augat 24 Way low profile socket. Solid gold pins. A superb socket. Leave your eproms in them for programming or usage to prevent breaking off pins. Only 40p each, p&p 35p.

GIVEAWAY
18 pin low profile dill socket 13p EACH or 8 for £1 p&p 35p
Just arrived. ITT 2082 Data Modem. Brand new and boxed, with manual. 600/1200 Baud. Data Modem to CC ITT. V24/RS232C. Channel centre frequencies 1300 and 1700Hz (600 Baud) or 1300 and 2100Hz (1200 Baud). Synchronous or asynchronous operation over 2 or 4 wire, switch or dedicated lines, built in self and lines test functions. Some of the best equipment we have ever obtained. £115 each, p&p £3 (fraction of original cost).
IC HOLDERS (Low-profile)
8 DIL 12p 14 DIL 15p
16 DIL 17p 18 DIL 20p
22 DIL 28p 24 DIL 35p
28 DIL 45p All p&p 35p
WE STOCK a vast range of TTL, CMOS, some 74LS. MINIATURE TOGGLES, etc.
PSUs. We have a large stock of power supplies at very realistic prices (callers).
RELAYS
Banor resettable double pole changeover 12V £1. Both p&p 35p.
JUST ARRIVED - PCB 008 OSCILLATOR Containing 1 NPN transistor, 1 resistor, 1 transformer and PP3 battery connector. 30mm x 20mm (approx). 15p each. 9 for £1, p/p 35p. PCB 009 1 x CD4069, 1 x CD4011, 5 transistors, 7 capacitors, 12 resistors, 1 diode, 45mm x 55 mm (approx). 25p each, p/p 35p.
CENTRONICS 101A Dot Matrix printer. Fully overhauled. 185 char/sec. £250 inc. VAT. Carriage at cost. A GIVEAWAY BUY - ONLY 2 LEFT.
PL259 PLUGS. (State large or small cable entry) 88p.
PL259 SOCKET CHASSIS MOUNT. 50p p&p 30p.

The instruction set for the 10660 CPU can be found in MICROPROCESSOR/MICRO-COMPUTERS by BRANKO SOUCEK - Publishers WILEY INTERNATIONAL SCIENCE.
ICL POWER SUPPLY (exchange units) 240V AC input. Output +24V at 2 amps DC, -24V at 2 amps DC (adjustable to 12V) +5V at 4 amps DC -100V DC and 6.3V AC. £10.50.
Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.
FOR THE PROFESSIONAL USER. CP Clare Keyboard switches with buttons (blank) 65p each p&p 35p.
BURROUGHS keyboard, 96 key station. On-board crystal and TTL. Brand new and boxed. 500mm x 190mm. At the time of advert no data. No keytops at all. Clare pander. Reed switches. Bargain £12 each, p&p £1.50.
PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.
SURPLUS STOCKS PURCHASED FOR CASH
LB ELECTRONICS
11 HERCIES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND
All enquiries s.a.e. please
Telephone answering machine service out of business hours.
New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.
ALL PRICES INCLUSIVE OF VAT UXBIDGE 55399
All components full spec.

